

ELECTRONIC SYSTEMS

Luca Colombo | Politecnico di Milano | a. a. 2022/2023

DISCLAIMER

These notes cover the arguments of the course 'Electronic Systems' held by Professor F. Zappa at Politecnico di Milano during the academic year 2022-2023.

Since they have been authored by a student, errors and imprecisions can be present.

These notes don't aim at being a substitute for the lectures of Professor Zappa, but a simple useful tool for any student (life at PoliMi is already hard as it is, cooperating is nothing but the bare minimum).

Please remember that for a complete understanding of the subject there is no better way than directly attending the course (DIY), which is an approach that I personally suggest to anyone. Indeed, the course is really enjoyable and the professor very clear and helpful.

In any case, if you found these notes particularly helpful and want to buy me a coffee for the effort, you're more than welcome: <https://paypal.me/LucaColombox>

lucacolombo29@gmail.com

BASICS ON ELECTRONICS

RESISTORS



Typical resistors' values spans from 0.1 Ohm up to few MOhms (eventually also Giga-Ohm). Then all components have their own tolerance, because every manufacturing mechanism has its tolerances. Cost of course changes a lot with tolerances.

Moreover, we have also power dissipation; we have also to specify the **power rating** of a resistor. The power rating is the power the resistor is going to dissipate under operation. It is obtained with $V \cdot I$, that if $V = 5V$ and $I = 1mA$ is e.g. 5W (**NB**: the equation $P = V^2/R = R \cdot I^2$ can be used only if the component is a resistor).

I have to specify the power rating because if I use the same resistor in a different circuit with different voltages or currents, the power dissipation is different. If the amount of power to be dissipated is too high, the resistor could break → in principle I would need a resistor with a higher power dissipation but with the same resistor value. Usually, the power value expected must be overrated by the resistor by a factor 3/2 (150%).

MILANO 1893

  - Values:** 0.1Ω ÷ 4.7MΩ
- Tolerances:** 10% ÷ 1%
- Power ratings:** 1/8, 1/4, 1/2, 1, 2, 5, 10W



anello	Colour coding									
1°	-	1	2	3	4	5	6	7	8	9
2°	0	1	2	3	4	5	6	7	8	9
3°	-	0	00	000	0000	00000	000000	0000000	00000000	000000000
4°										

Preferred values:

- 10%: 10 12 15 18 22 27 33 39 47 56 68 82
- 5% e 2%: 11 13 16 20 24 30 36 43 51 62 75 91

Moreover, we have only some preferred values of resistors, because other values can be reached with series and parallel between resistors. Moreover, due to tolerances, it might happen that, for instance, the 2k resistor and the 2.5k resistor have the same value (2.2k). So values of manufactured resistances' values are chosen so that the spreads due to tolerances don't overlap one with the other passing from one value to the other → also better to design electronics that doesn't work only with a specific value of resistance, or that doesn't change if the resistor drifts.

Technology: wire mould metal layer

Package: through-hole SMD, Surface Mounting Device

Variable: potentiometer trimmer

Sensors: photoR thermoR ...

To create capacitances with a very big value, we place two metallic plates one close to the other, we create oxide on the plates and we place the two plates one on the top of each other and we roll the plate. The two foils are isolated one from the other. Thus we achieved a very huge S and very small d, so the C is huge.



The issue is that the two thin foils are so close to each other that it can withstand small voltages, otherwise the disruptive discharge could make a hole in the capacitor creating a shortcircuit.

NB: if a units of measure is not specified for a capacitor, it means pF.

INDUCTORS



Values: 1nH ÷ 100mH

Tolerances: 20% ÷ 5%

Current ratings: 1mA ÷ 1A

An inductance is a wire with 0 resistance that is in a solenoidal configuration across a nucleus. When the current flows in an inductor, we generate a magnetic field that constantly changes direction because of the AC current across the coil. This field self-induces a counter force on the windings itself.

The inductor behaves as the opposite of the capacitor. In DC it behaves as a shortcircuit, whereas in AC it becomes as an open circuit.


As soon as we try to push current in the inductor, it reacts trying to reduce it. The signal at which we discriminate if the signal is AC or DC depends on the fpole $\rightarrow \tau = L/R$.

In an inductor we have to specify the current value (there is no voltage across it in DC).

NB: in general, the current-voltage dependency is not mediated always through a resistor, but there are nonlinear behaviours.


IDEAL VOLTAGE AND CURRENT SOURCES

 A current source provides a constant current whatever the voltage across it, while a voltage source provides a constant voltage no matter the current flowing through it.





REAL VOLTAGE AND CURRENT SOURCES

 The line is not exactly straight. If there is a voltage drop across the current source, the current through the current source starts decreasing → the real generators are modelled with Thevenin and Norton equivalents that take into account the voltage drop.




  Which one is a voltage source and which is a current one?



When a source is a voltage source or a current source. We cannot say it from the plot, but it is depending on the physical mechanism that underlines its behaviour. For instance, if we have a biological cell that generates 100 nA per excitation, if we want to measure the signal, we should measure the current. But sometimes the instrument can measure the voltage and not the current → we connect the cell to a resistor. However, this approach with the resistor is completely wrong, because we are converting a current into a voltage and we are reading the voltage but this voltage could change the intrinsic characteristics of the cell. The voltage drop across the resistor is reflected back on the cell, so the excitation current will be different (decreased).


So if the source is a current source better to read just the current and try to maximize the current, without developing any voltage across the current source. The amplifier to read the current should have an input impedance much smaller than the parasitic resistance of the real current generator. If so, there will be almost no voltage drop across the input impedance of the amplifier so the V_{in} across the cell itself will be almost zero, we don't lose any current due to the parasitic resistance.

 

The slope of the I-V curve is the equivalent resistor of the Norton equivalent circuit. The ideal current generator has an equivalent resistance in the Norton model that is infinite. So for a current source the best amplifier is the one with a zero input impedance, so that there is no voltage generated at its input.

As for the voltage source, the amplifier to amplify the signal should have an R_{in} much greater wrt the R_s of the Thevenin equivalent of my voltage source. In this way there is no current flowing in the circuit, so the voltage source will provide the voltage signal without any drop.

$v(t)$

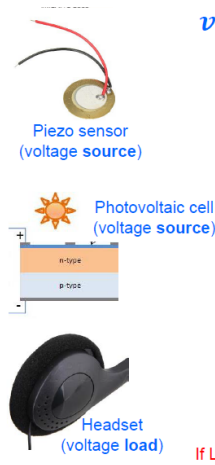

Piezo sensor (voltage source)

Photovoltaic cell (voltage source)


Headset (voltage load)

$i(t)$

- Read the source depending on what (either v or i) is **proportional to the actual signal to measure**
- Drive the load by means of what (either v or i) produces a **proportional effect to actuate**

LED and LaserDiode (???) load

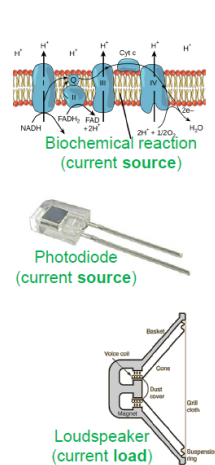A resistor "mediates" somehow i into v and viceversa, but it spoils the **proportionality** if the source/load changes!
If LED's light is proportional to current, then drive current into the LED"



Biochemical reaction (current source)


Photodiode (current source)

Loudspeaker (current load)

POWER SUPPLY

MILANO 1893

Typology: single- or dual- power supply

 


GROUND: local 0V reference
usually it is the copper plate of the PrintedCircuitBoard
it can also be the chassis connection and possibly **EARTH**

We have operational amplifiers that need power supply. The power supply refers to how we bias the circuit to have the circuit that operates. In the case of the image we have a dual power supply, meaning that there are two batteries that provide $\pm 5V$. To do so, we connect them in series and we consider the intermediate node as ground; if so one node will be $5V$ above ground, the other will be $5V$ below it. So ground is not necessarily $0V$, but the signal we want.


Of course, the KVL must always be respected, so the current that flows out the most positive power supply must be equal to the one flowing in the most negative power supply. Then the difference must flow through ground.

FREQUENCY RESPONSE

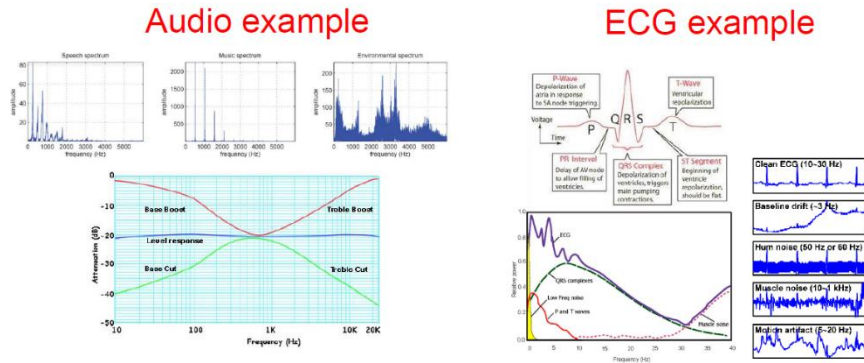We have to know which are the frequencies of the signals we are working with and we want to amplify.
Not just to Low-Pass, Band-Pass, High-Pass, Notch, but also for Integrators, Derivators...



Frequency analysis

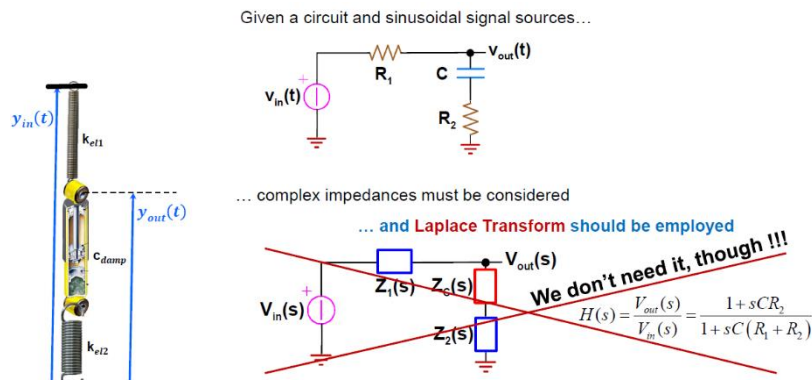


Let's start from a very simple schematic where we have a voltage source, two resistors and a capacitor. We want the output voltage in the time domain and frequency domain. We have seen the asymptotic behaviours of an inductor and a capacitor in DC and AC, but in middle frequencies, the current that flows in a capacitor has a specific value (the same for the voltage across the inductor).

$$i_c(t) = C \cdot \frac{dV_c(t)}{dt}$$


$$V_L(t) = L \cdot \frac{di_L(t)}{dt}$$

If at DC the variation of voltage over the capacitor is 0, then the current is zero. Similarly, in DC if the variation of the current in the inductor is 0, then the voltage across it is 0. Conversely, if the variation of voltage becomes very high across the capacitor, the current becomes infinite. The same and opposite reasoning for the inductor.

 Capacitor and inductor can also be seen in the frequency domain.



 
However, if the system has not a constant and finite frequency, but it varies the specific of the signal, with DC parts, AC and transients, we need to introduce the Laplace transform. It is another way to describe our system in the frequency domain ($s = \alpha + j*2*\pi*f$).




However, we are no longer using the Laplace transform because it's too complex, so we try to solve the circuit in another way.

Coming back to the previous circuit, we want to compute V_{out} given V_{in} . When we buy a voltmeter, we know that it has two wires and an infinite input impedance. The voltmeter reads 0 current, so it doesn't steal any current.

Let's solve the circuit through Laplace.

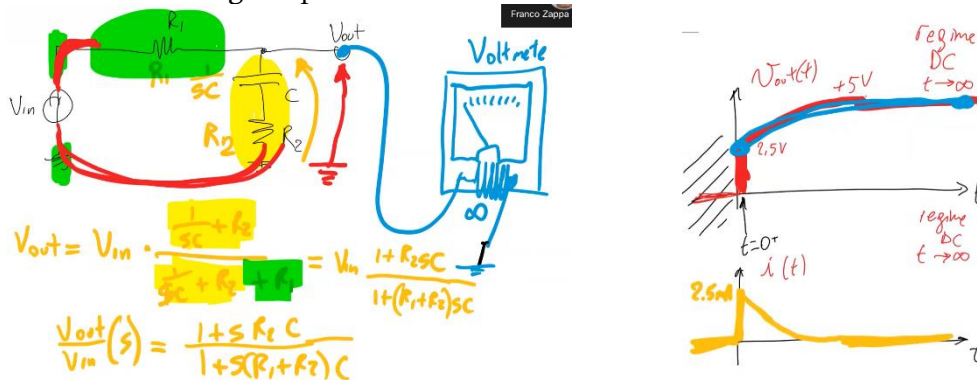


 Now we want to plot is how this gain varies with frequency f .




However, we can forget about the Laplace transform and study the frequency response of our circuit by using an asymptotic approach. Let's consider the circuit at DC (constant voltage applied at the input) or in AC (AC voltage at the input) and let's compute the gain.

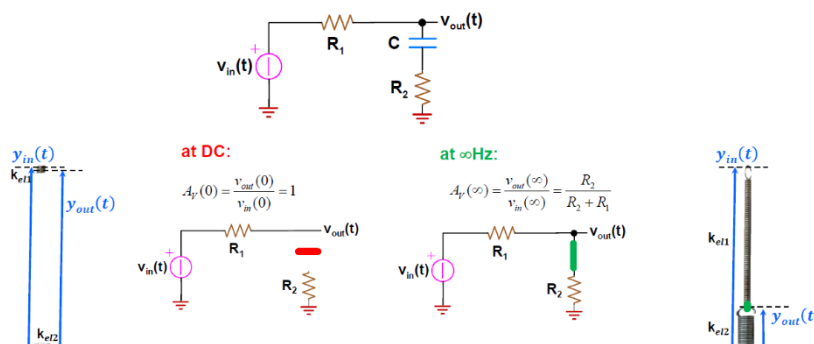1- We simply evaluate the circuit response at **0Hz** and **∞Hz**



Now we have to compute at which frequency the gain drops, that is when the reactive components start to display their behaviour. To do so, we have to compute the pole of the circuit, that is $1/\tau$, where τ is the time constant of the circuit, the speed at which the circuit relaxes down to a quite state. Imagine charging the capacitor at whatever voltage we wish. Then we switch off the voltage source

 
2- Then, we join the **0Hz** and **∞Hz** asymptotic trends through a **line** in log-log plot




(shortcircuited), the capacitor will spontaneously discharge because a current will flow through R1 and R2 and charges will recombine. This occurs at a speed that depends on the time constant tau of the circuit. In our case, the total R for the tau is R1 + R2 → tau = C*(R1+R2). The transient is typically over after 3 to 4 tau.

As for the frequency of the zero, we can compute it with the **GBWP**.

 In a Log-Log plot, the trend of increase or decrease is increasing or decreasing because as we can see in the Laplace transform, positive slope are associated to s (or f), negative to 1/s (or 1/f). This means that if we have a decrease of 75 in gain, we will have a shift in frequency of 75.



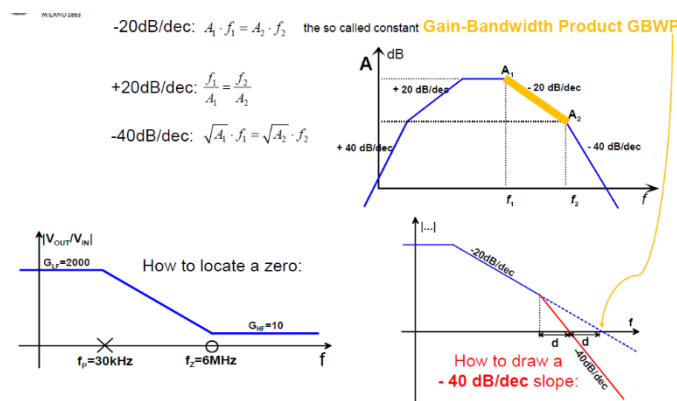Wrt the right Laplace equation we commit some errors where we have the poles and zeros, and they are of 3dB. In fact, **the pole is the frequency at which the gain drops by a factor 3dB**.



The inverse of seconds is Hz or rad/s? Given the period, f = 1/T is in Hz, but if we calculate f = 1/tau, in this case we are in rad/s. So one over period is actually in Hz, while since tau is not a period, 1/tau is in rad/s. 1/(2*pi*tau) is actually in Hz instead.


$$dB = \text{ratio} = \frac{V_{out}}{V_{in}} = G_{dB}$$

$$dB = 20 \log_{10} \frac{V_{out}}{V_{in}}$$


NB: the decibel (dB) is a ratio of something, e.g. Vout/Vin and applied like this.

The -20dB/dec slope can also be called a 45° slope because the slope has an angle of 45°.

Example

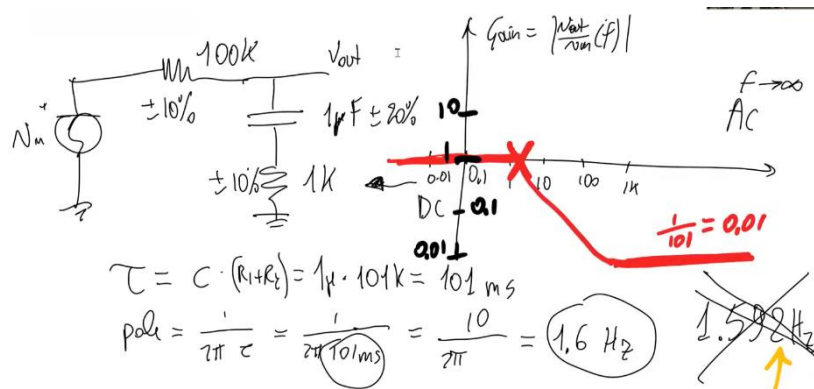

 How to compute the frequency when we have a -40dB/dec slope:





How to compute poles

Switch off all generators ($V=0$ is a short-circuit, while $I=0$ is an open-circuit)

Don't care where inputs and outputs are!

Compute the overall Resistance "seen" by the Capacitor!
  
$$pole_{Hz} = \frac{1}{2\pi \cdot R_{eq} \cdot C}$$



In order to compute the pole, we choose one capacitor, we remove it and look at the equivalent capacitor it sees. The hope is that one capacitor doesn't meet another capacitor because in this case we don't know how the other capacitor is affecting the one of which I'm computing the equivalent resistance. Hence so far **we assume capacitors that are not interactive**, like in the circuit on the left.

First of all, I have to check if the capacitor is actually introducing a pole in our circuit, and this happens if in going from the input to the output we pass through a capacitor. Moreover, if there are capacitors (e.g. 3 of them) connected in parallel, they don't give rise to three poles, but just one pole given by the parallel of the three.

To compute the pole of C1, we remove it and see the resistance we see from it. **When we compute the pole all the voltage/current sources must be off**, either power supply or input signal. Hence the equivalent impedance seen from C1 is $R_1 + R_2 \parallel R_3$ (in an ideal MOSFET the impedances seen into the gate and into the drain are infinite, whereas into the source I see $1/g_m$).

As for the capacitor C2, the $R_{eq} = R_4 + R_6$. For C3, $R_{eq} = R_8 + R_7$ (if the transistors are ideal).


In a MOSFET, if there is no degeneration at the source, we see r_0 from the drain, but if there is degeneration, hence a source resistance R_s , we don't see r_0 but more (not $r_0 + R_s$, because I have a feedback action in the transistor itself, it's much higher).



Hence the circuit has three poles, but we are not done, because there may be also some zeros. Moreover, we also miss the value of the DC gain.

As for the DC gain, all capacitors are open. Hence the DC gain is clearly 0, because the C1 is open; for sure C1 introduces also a 0 in the origin, but then also a pole later. In a Bode plot, gain equal to 0 means $-\infty$. Before the pole of C1 the signal is not passing, then after the pole of C1 the signal passes.

 Furthermore, also C2 introduces a zero in the origin, by the same reasoning. So we will have a +40 dB/dec slope at 0 Hz.




Above the two poles, the C1 and C3 will be shorted for the signal, so we can compute the flat gain of the circuit when C1 and C3 are shorted. Firstly we compute the transfer from the input to the gate of M1 through the resistive network, then gain of M1, from gate to drain is $-R_{\text{drain}}/R_{\text{source}}$, so $-R_4/(1/g_m + R_5)$ because C2 is open in this regime. Same reasoning for M2, $(R_7 || R_8)/(1/g_m)$.

Then we have to compute the pole of C2. If it is after the poles of C1 and C3 I'm ok and happy, but the problem is if the pole is lower than the other two. If so, the assumption we made on having the capacitors open or closed must be redone with the correct involved capacitors.

If by chance the pole associated to C2 is in the middle between C1 and C3, we cannot compute the gain going through the network because C3 would be open. But I know the value the gain could have with C2 after C3, I know the position of the first pole and the distance between C1 and C2, and with GBWP technique I can compute the gain.


Poles in Electronic systems

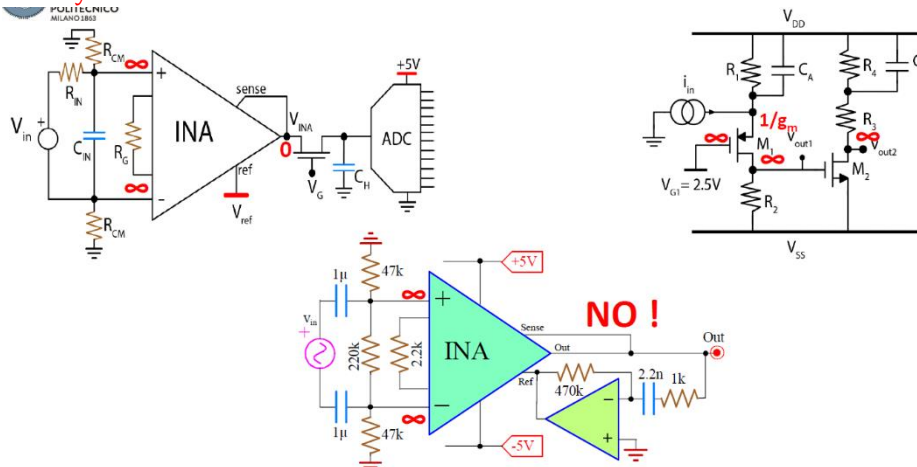

For the upper left circuit the pole of Cin is due to $R_{\text{in}} || 2 * R_{\text{cm}}$. Cin is introduced so that at DC it is open, and Vdiff at the input of the INA is not Vin, because we have the resistance Rin. We can rewrite the network as aside.

$$V_{\text{diff}} = V_{\text{in}} * (2 * R_{\text{cm}} / (R_{\text{in}} + 2 * R_{\text{cm}}))$$

 
So we have a flat DC gain. At infinite frequency, the Cin is shorted and Vdiff is 0 and hence the output is 0 → gain is 0 and it dies after the pole associated to Cin. Hence the Cin is introduced to perform a LP filtering action.



If we now move to the bottom circuit, the pole is computed considering the two capacitors in series because when the generator is off they are connected, so we have just one pole. $R_{\text{eq}} = 220k || 2 * 47k$.

As for the gain, at DC the two capacitors are open and the gain is 0, so we have a zero in the origin of the Bode plot. So the capacitors act to introduce a HP filtering.

Feedback action on poles

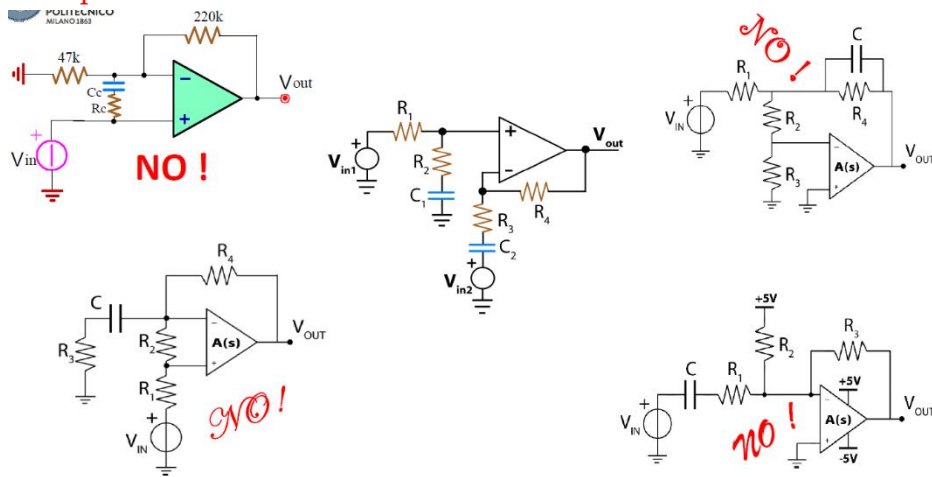

Feedback is useful but when it works something happens. Feedback means that if we have an amplifier and we apply a signal in input, the amplifier amplifies the difference, so the output moves but then, thanks to the network, also the other pin moves and hence the input difference decreases and the output decreases.

For instance, in the central circuit the - terminal is virtual ground, it doesn't change its voltage. If so, the pole associated to C2 is just associated to the R3 resistance.

For the upper right circuit, again the - terminal is virtual ground, the + terminal can move (but we decided to keep it fixed at ground). If so, R3 is in between VG and GND, so no current in it, so no current in R2, so no voltage drop across R2, so no voltage drop across R1 and hence C sees just R4.


For the bottom right circuit for the pole we have C*R1 (same concept on VG).

How to compute zeros

MILANO 1883


Switch off all generators ($V=0$ is a short-circuit, while $I=0$ is an open-circuit) **apart from the Input**

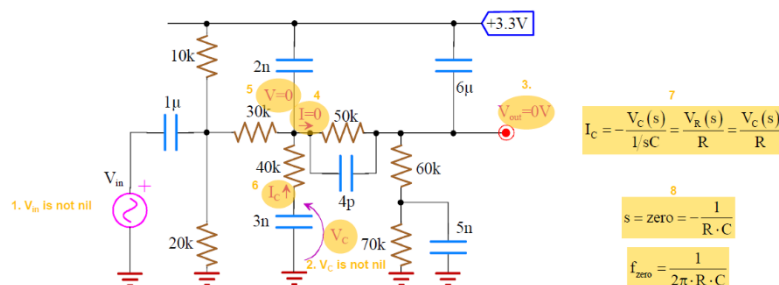1. Apply a generic (NOT NIL) signal to the actual Input
2. Pretend to have a generic signal $V_c(t)$ and $I_c(t)$ on the C under test
3. Check if the Output can indeed be NIL anyhow




The capacitor introduces a zero if the output stays at zero when we have an input signal. If the output is 0, there is no current through the 6µ capacitor and so no current in the parallel configuration at its left, so no voltage drop across 50k, so no current, so no current in 2n and 40k and so on. If I want to know if the capacitor introduces a zero I simply pretend that Vin moves, voltage across the capacitor moves and the output stays at 0, and node x stays at 0. Is it possible that Vin moves, Vc moves and node x does not and there is no current?

 A Capacitor **along the signal path**: a zero at the origin



 
Let's draw the simplified circuit and the equation of the capacitor.



It's actually possible to have I_c equal to zero whatever V_{in} is if $s = 0$. This that we found is the frequency of the zero (in this specific case it is a zero in the origin) → whenever we find a capacitor connected to the path of the signal we have a zero at $f = 0$.


The other possibility is the following.

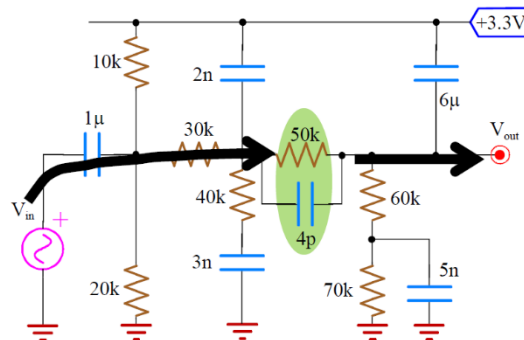An **RC-shunt along the signal path**: a zero at finite frequency



If we have a RC network along the path of the signal, we have a zero at infinite frequency. Again, if the output is 0, we have zero current flowing in the **RC shunt** from the output but at the same time a voltage across it because we have the input that is on. So we have actually a current from the input side of the RC shunt. This current recirculates in the RC shunt. *At which frequency the voltage across the capacitor causes a current through the resistor that is equal to the one through the capacitor?*

 
At infinite frequency, $s = -1/RC$. This is the zero of the network at a finite frequency.



Of course the pole of the capacitor 4p is not due to RC as the zero, but the resistance in the pole is the equivalent capacitor.

Then we have also another possibility, due to a **RC series** along the path of the signal.

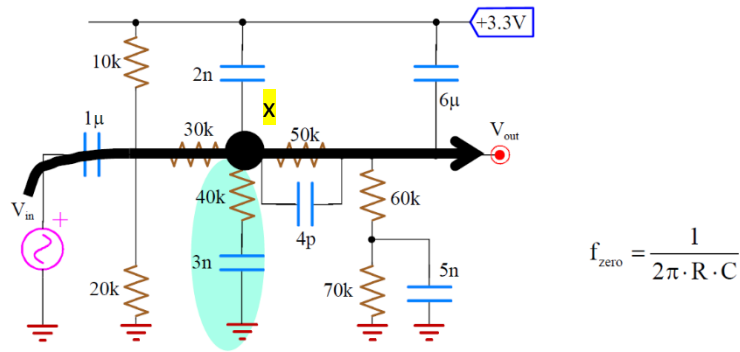An RC-series hanging at a node along the signal path: a finite zero




If we have an RC to ground we have a zero at finite frequency. If the output is 0V, there should be no current up to node x, because we have no voltage drop across the 50k resistance. *May we have a voltage across the 3n capacitor but 0V at node x?*

Yes, it happens if the current flowing through the resistance in series gives a voltage that is the opposite with respect to the one of the capacitor. Again, this happens if $s = -1/RC$. Again, related pole is different.


There may be, in the path of the signal, also capacitors attached to ground. These capacitor are not giving any zero, because it is not possible for the output to be zero if there is a voltage across the capacitor if we have just a capacitor to ground.

 A Capacitor hanging at a node along the signal path: NO ZERO



If we have a capacitor that is on another signal path, it introduces a zero at finite frequency.

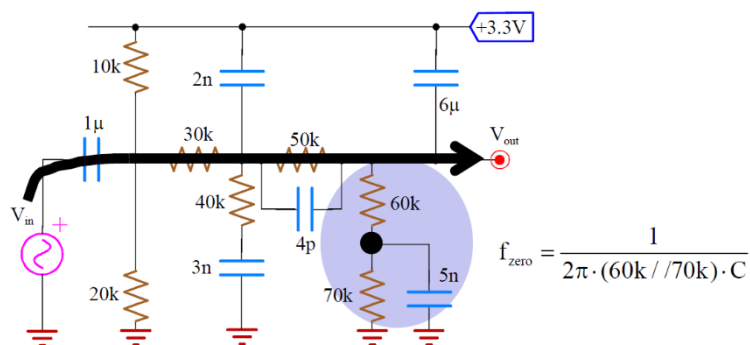A Capacitor hanging at a node off the signal path: a finite zero



To summarize, a capacitor along the path of the signal introduces a zero in the origin. If the capacitor is from one node to ground we have no zero; if we have a RC to ground or a RC shunt we have a finite zero, and also if we have more complex networks attached to the signal path. In the network in example we have for sure 4 zeros, of which one is in the origin.

As for the poles, capacitors here are interacting. So we cannot compute the pole assuming that all the other capacitors are not existing when computing the pole associated to one specific capacitor. In this

case, I cannot know the precise frequency of the pole, I'm just giving an estimation based on reasonings on resistances and having capacitors shorted or not.


The number of poles that we have is exactly the number of capacitors we have? At the most, they are 6, and we don't have any parallelisms or series of capacitors.

But are there any dependent capacitors (so do we have a loop formed just by capacitors)?

Yes, the 2n, 4p and 6u capacitors form this loop. So the other capacitances interact one with the other but they are independent one from the other, exception given for these three.

So we have just 5 poles, because the 3 dependent capacitors behave like two poles, because only 5 out of the 6 capacitors are independent (but still interacting).

 The final Bode diagram will be for sure something like below.



NEGATIVE FEEDBACK


Negative feedback improves the gain, the stability, the input impedance, output resistance and so on. We need to choose the proper amplifier depending on the input that we have.

VOLTAGE AMPLIFIER

In the example of the image, the input source provides a voltage that is proportional to the input signal. E.g. in input we might have a piezoelectric microphone that produces a signal proportional to the voice. We model the input source with the input resistance R_s that considers the voltage drop across the microphone if we force the microphone to provide a current.

Voltage to Voltage:
 
$$G = A_V = \frac{V_L}{V_S} \quad \text{V/V}$$



$$V_L/V_S = 0.99 \times 50,000 \times 0.24 = 12,000 \text{ V/V} = 12,000$$

Unfortunately there are **voltage drops**:

$$V_{in} = V_S \cdot \frac{R_{in}}{R_{in} + R_S}$$

$$V_L = V_u \cdot \frac{R_L}{R_L + R_u}$$

Hence a good **Voltage Amplifier** must have:

$$R_{in} \gg R_S \quad \text{very high input impedance}$$

$$R_u \ll R_L \quad \text{very low output impedance}$$

So we have our microphone, we model it with a voltage source $v_s(t)$ and we have across the mic, if we change the current of the mic, a voltage drop that decreases with an internal source resistor. The smaller the resistor, the more vertical the I-V characteristic, so more ideal.

We need to understand how to properly match the source with the load, and the load is modelled with a resistor.

In the first amplifier we want to amplify the voltage and provide the voltage to the load. It is the load that provide a physical reaction proportional to the voltage and not the current. To model the amplifier, we use two pins, the input and ground and the output and ground at the output.

We can **model the amplification as a voltage dependent voltage source**, that is a voltage source whose voltage v_u is proportional to the input voltage, so the output is $G \cdot V_{in}$.

Then we can model also the real behaviour of the output voltage source, so we place a resistance in series to it and also we introduce an input impedance. Let's see what happens due to the presence of an input impedance that, unfortunately, is not too high and an output impedance that, unfortunately, is not nihil. If the output impedance of the amplifier is not negligible with respect to the load impedance, if we compute V_{load}/V_S , the gain is not the gain of the amplifier but it is reduced due to the input and output impedances of the amplifier. From V_S to V_{in} we have the first path, then the amplification and then the final partition due to the output stage, due to R_u and R_L (load). If we compute V_{in}/V_S , it is like in the image (voltage partition).

In the final stage we have a great loss of signal because the output impedance of the loud speaker (load) is much lower than the output one of the amplifier. Hence, if current needs to flow, the current will cause


a voltage drop inside the opamp that will be higher on the load, simply because the output impedance of the amplifier is higher.

We realized that we loose signal not at the input, but in the output partition. To maximize the voltage gain, we should improve matching, to have an input impedance higher of the amplifier with respect to the voltage source input impedance, and the best way to provide a voltage is to have a load impedance that is much higher than the output impedance of the amplifier.

Since we know the amplifier that we bought, we have to choose a mic and a load coherently with respect to the already bought amplifier.

CURRENT AMPLIFIER

 
We need to amplify a current and provide a current. The source and load are both currents; the amplifier requires an input impedance as smaller as possible and an output impedance as bigger as possible, so that the current in input flows in the amplifier and not in the input impedance path related to the source (in the image a solenoidal load to be driven with a current, not a voltage).



We have a current source I_s , the amplifier with input impedance R_{in} , the output impedance R_u and the load R_L . Again, the source current I_s that enters in the amplifier is a current partition; if R_{in} is small, almost all the current will flow in R_{in} , and a small part in R_s (input impedance of the source).

Current to Current:

$$G = A_I = \frac{I_L}{I_S} \quad A/A$$

 

Unfortunately there are **current shunts**:

$$I_{in} = I_s \cdot \frac{R_s}{R_s + R_{in}}$$

$$I_L = I_u \cdot \frac{R_u}{R_u + R_L}$$


Hence a good **Current Amplifier** must have:

$$R_{in} \ll R_s \quad \text{very low input impedance} \quad R_u \gg R_L \quad \text{very high output impedance}$$

As for the output, the current that flows in the output speaker is still given by the partition. If R_u (output impedance of the amplifier) is bigger than R_L , it is good. It is exactly the opposite with respect to the voltage amplifier.

TRANSIMPEDANCE AMPLIFIER


Now for instance we have an input current and an output voltage to drive a load. Now the gain is V_{out}/i_{in} , so the amplification has a size of Ohms \rightarrow transimpedance amplifier because the gain is no more a pure number but an impedance, but it is not a resistor. It is not as the upper image, but as the lower image. The output should provide as much current as the output load wants, not just like as if it was a resistor.

 

The input is modelled as a current source, so R_{in} much smaller than R_s . In output R_{load} must be much bigger than R_u . If not, we could have a bad matching in the output stage as in the image.

Current to Voltage:
 
$$G = A_R = \frac{V_L}{I_S} \quad V/A = \Omega$$



$$V_L/I_S = 0.994 \times 2,000,000 \text{ V/A} \times 0.24 = 477 \text{ V/A} = 477 \Omega$$

Unfortunately there are **losses**:

$$I_{in} = I_S \cdot \frac{R_s}{R_s + R_{in}}$$

$$V_L = V_u \cdot \frac{R_L}{R_L + R_u}$$

Hence a good **Transimpedance Amplifier** must have:

$$R_{in} \ll R_s \quad \text{very low input impedance}$$


$$R_u \ll R_L \quad \text{very low output impedance}$$

TRANSCONDUCTANCE AMPLIFIER

It is exactly the opposite of the previous one.

Voltage to Current:
 
$$G = A_G = \frac{I_L}{V_S} \quad A/V = S$$



$$V_L/V_S = 0.99 \times 5 \text{ mA/V} \times 0.91 = 4.5 \text{ mA/V} = 0.0045 \Omega^{-1}$$

Unfortunately, there are **losses**:

$$V_{in} = V_S \cdot \frac{R_{in}}{R_{in} + R_s}$$

$$I_L = I_u \cdot \frac{R_u}{R_u + R_L}$$


Hence a good **Transconductance Amplifier** must have:

$$R_{in} \gg R_s \quad \text{very high input impedance}$$


$$R_u \gg R_L \quad \text{very high output impedance}$$

The gain is now in siemens (S).

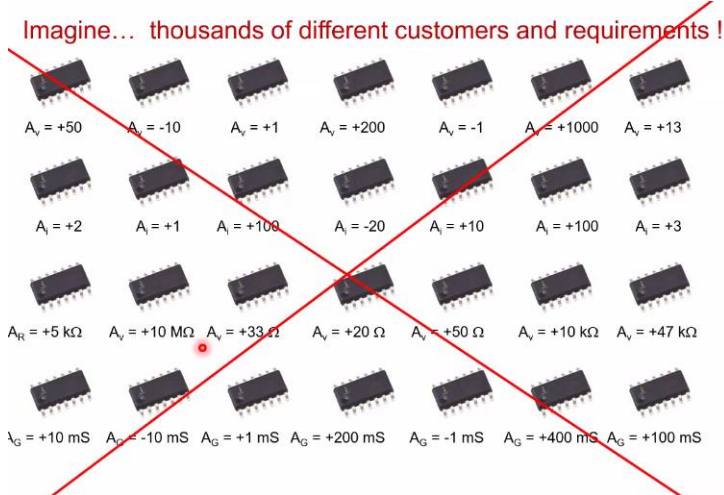So to achieve these results we can simply use an amplifier matched with the correct passive components and feedbacks.





 
Just one OpAmp suffices
(with few passive components) !






OPAMP WITH NEGATIVE FEEDBACK

The opamp is not used in open loop configuration (OL), because always feedback will be given to it.

Here is the "open-loop" OpAmp:

   

   Here is a basic "closed-loop" (negative feedback) circuit:




The idea is to buy one amplifier and use one input of it to give the input, and the output to provide the output. The gain will decrease if we use components in feedback to the amplifier with respect to the OL configuration. I like having a strong amplifier, but it could also amplify the noise and if it gets old or heats up, its gain will change a lot so it won't be used as before. Hence let's not use the opamps in OL configurations, but let's introduce feedbacks. If we subtract the feedback signal to the input signal, we get an output error signal that will be amplified in a lower way than before. So we can set the gain by choosing the attenuating network Sf.

The gain will be much lower but more stable and controllable and selectable with the passive components.

Mathematics

Let's model the amplifier with the Laplace transform of its voltage gain, $A(s)$. Let's use an attenuating network $F(s)$ and something known at the input, that is the sum of the two signals.

 If $A(s)$ is a non-inverting amplifier (positive gain) and the feedback network is not inverting, at the input I need to subtract, otherwise the overall feedback would be positive. Or I can put a + and having an inverting amplification.



Real (closed-loop) gain:

$$G(s) = \frac{S_u}{S_{in}} = \frac{A(s)}{1 - A(s) \cdot F(s)} \quad \text{X} = \frac{A(s)}{1 - G_{loop}} = -\frac{1}{F(s)} \cdot \frac{1}{1 - \frac{1}{G_{loop}}}$$

Real gain Correction factor Ideal gain

Loop gain G_{loop} : measures the **feedback effectiveness**, the higher the better !

if G_{loop} is very high, ideally infinite, the "error" ε gets nil

the negative feedback forces S_f to mimic S_{in} !

Indeed, the **ideal gain** does not depend on the OpAmp!


S_u ($u = uscita$) is epsilon multiplied by $A(s)$ OL gain of the amplifier (error in the slide, epsilon = $S_{in} + S_f$ with S_f negative).

The overall actual gain of the amplifier is x . Since I'm interested in negative feedbacks, either in input I have a minus, so the $-G_{loop}$ will have a G_{loop} negative to have a negative feedback so that $1 - G_{loop}$ is a big positive number.


Thus, the gain drastically reduces. Let's divide now the numerator and denominator by G_{loop} , that is $A(s)F(s)$. $-1/F(s)$ is the ideal gain. $1/G_{loop}$ must be smaller with respect to 1, so that if G_{loop} is strong the gain drops and the real gain is just $1/F(s)$, that is determined by the feedback and it won't be affected by temperature, age and so forth and so on like $A(s) \rightarrow$ the feedback must be precise to have a precise gain.

In the end the real gain is not the gain of the amplifier, but reduced by the negative feedback. G_{loop} represent the effectiveness of the feedback, if it is very high it is perfect, because it means that the output is bigger and in feedback there is the inverse of S_{in} , so that if the input is 2V, it returns in $S_f = 2V$, so $2 - 2 = 0$ so epsilon = 0, hence the feedbacks works in a way that the output will be moved by the feedback so that we will have the same signal as the input, still maintaining the output bigger than the input, thanks to the feedback.

Example

 


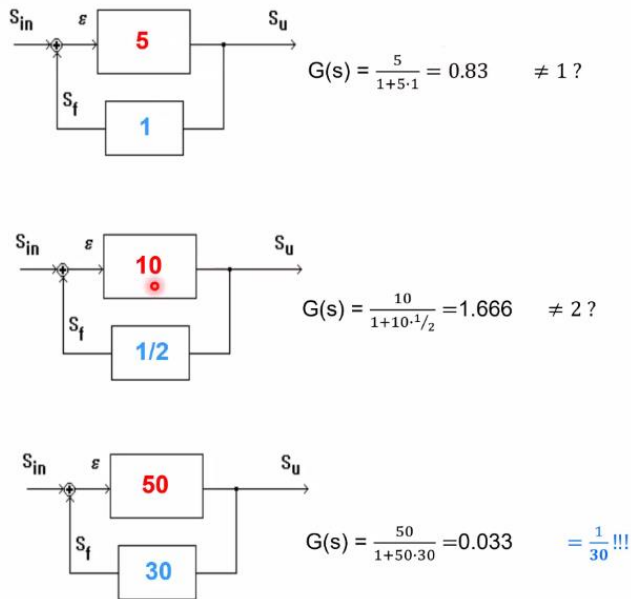The final gain $out/in = A/(1 - AF) = 0.83$. Other examples in the next images.



No practical use if $|G_{loop}|$ is not $\gg 1$

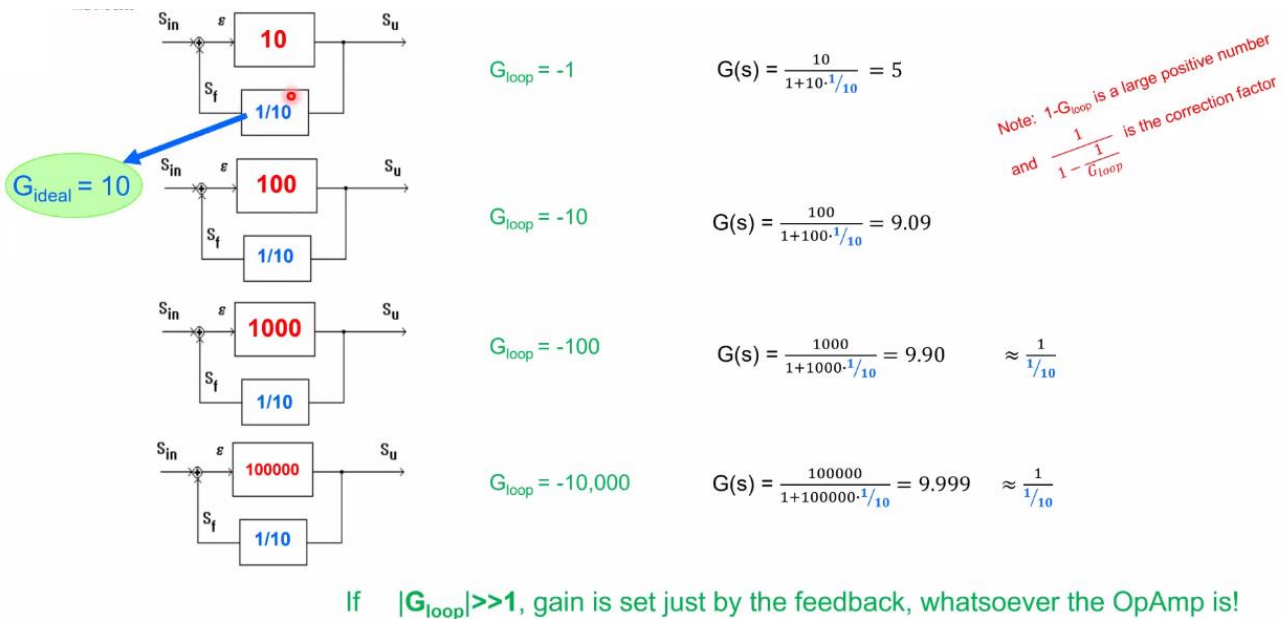Gloop was poor in case 1, 2, but strong in case 3. Hence $1/G_{loop}$ is small with respect to 1 and the gain is the inverse of the feedback network. If Gloop is much higher than 1, it makes sense to use the feedback, otherwise we should not use the feedback.



Now we have case 1, the gain is 5, and so on. Again, if Gloop is poor, it is not an advantage, while if we increase it, the gain arrives close to 10, that is the ideal gain.

So for negative feedbacks it is important to have whatever amplifier but a strong Gloop, which means much higher than 1 (e.g. a hundred).

NON-INVERTING AMPLIFIER

Voltage gain: $A_{vr} = 1 + \frac{R_2}{R_1}$


Input impedance: $R_{in} \approx \infty$

Output impedance: $R_{out} \approx 0$

It is NOT driven by the input, but eventually it "mimics" the input


We have a very small voltage source whose series resistance is very high (very bad source) and we want to 'move a load'. The amplifier needed is the one in the middle. The input source drives the input of the amplifier, then we use two resistors. The opamp doesn't require current from the input source. The feedback will be ok when the signal between input and feedback is 0. The current in feedback flows in R1 and R2.

 To have a 0 error in input (epsilon), we need $V_{in} = V_{feedback}$, which means that $V_{out} = V_f/F = V_{in}/F$ if Gloop is infinite.



Even if Gloop is not infinite, it should still be bigger than 1 to have a good feedback → we need resistances with small tolerance, 1% and not 10%. To the load, in this configuration, we can provide whatever current we want, because the opamp does it, either voltage or current. We don't need current in input because the opamp can provide whatever current we need without the need of it in input.

INVERTING CONFIGURATION

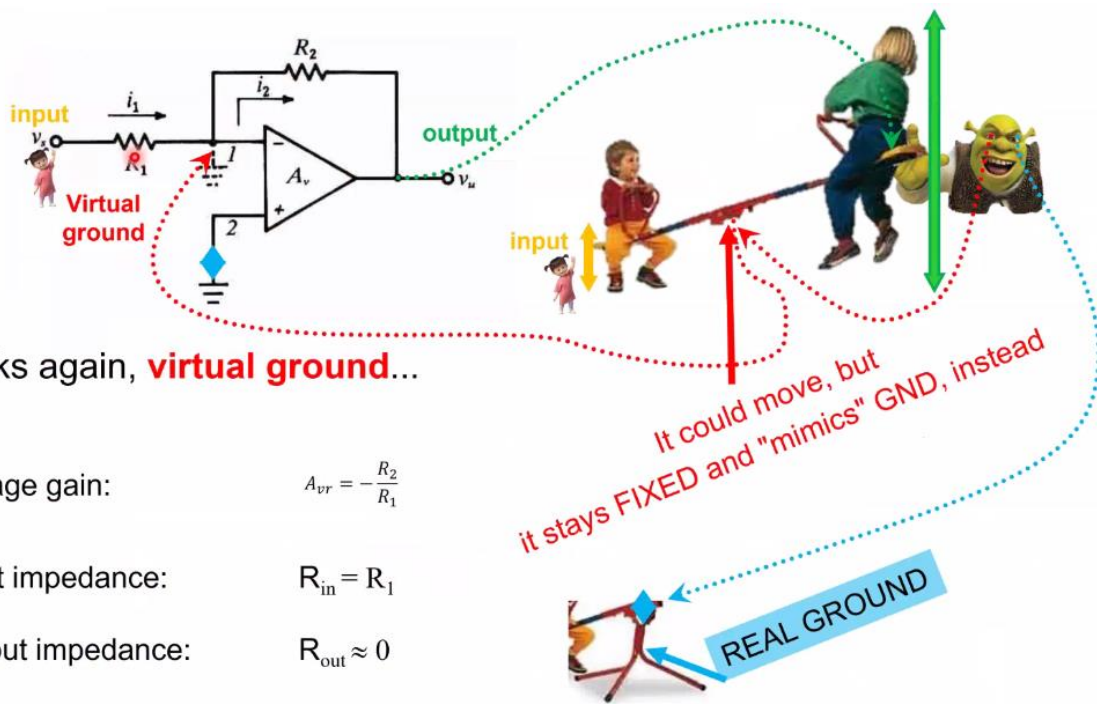

Thanks again, **virtual ground**...


Voltage gain: $A_{vr} = -\frac{R_2}{R_1}$

Input impedance: $R_{in} = R_1$

Output impedance: $R_{out} \approx 0$


REAL ELECTRICAL PERFORMANCES

Non-ideal **small-signal** specs:

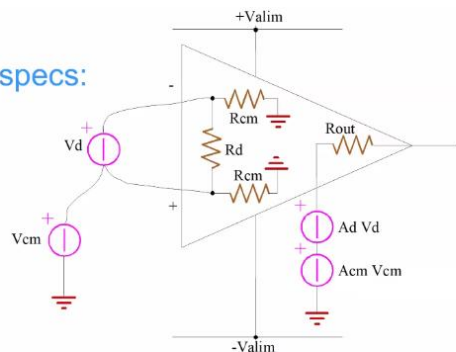

- Differential Gain (A_d) > 100'000 > 100dB
- Common-Mode Gain (A_{cm}) < 10 < 20dB
- Bandwidth (BW) 10Hz ÷ 1kHz
- Differential input impedance (R_d) > 100kΩ
- Common-Mode input impedance (R_{cm}) > 1MΩ
- Output impedance (R_o) < 4kΩ
- Temperature drifts some %/°C


Ideally, I want an output voltage of the amplifier proportional to the voltage input difference through the differential gain A_d . The I want a R_{out} close to zero, to be ideal. We are considering an amplifier that will be biased with e.g. $\pm 5V$, and it is made of different transistors. Depending on the number of components inside, the gain can vary. I hope to have a 0 output impedance, but it will be $1/g_m$ of the output transistor. I want the input impedance to be infinite, but it won't be in the real case. To measure if the input impedance is infinite or not, we can connecte + and - pins together and then apply a V_{cm} signal. If a current goes in, it means that the input impedance is not infinite.

 


I can also take the opamp and apply a differential voltage. If I measure a differential current I_d , then as in the image below.



 To model R_{in} in the two cases, in the case of common mode I should model it as if there were two resistance to ground, each equal to 2 times R_{cm} (they are in parallel).




 In the case of the differential source, I cannot use the same two resistors as above, but I should use a differential impedance R_d .




Output impedance

 Finally, we have the opamp, we drive it with the load, the output will be e.g. 3V with 0A, 2.9V with 0.1A and hence we can know the value of R_{out} .



This is the reason why I should model in the real opamps 3 resistors in input and one in output. Even if the differential signal V_d is 0, the output might be not 0 due to the common mode. So we need to consider a contribution of it to the output that is $A_{cm}V_{cm}$. I love to have a very high A_d but a very small A_{cm} .

 
In fact, different grounds can be not at the same potentials due to parasitism, we might have a voltage drop that can be assumed to be V_{cm} .




An ideal opamp should have $A_d = \infty$ and $A_{cm} = 0$. I also would like an infinite bandwidth, but typically will be in the range of tens of kHz. Moreover, all these parameters will vary with temperature with a certain percentage.

Hence even if we buy a bad opamp with not infinite R_{in} , bandwidth and so on, the feedback will improve all the parameters.

SINGLE ENDED VS DIFFERENTIAL AMPLIFIER

 

 - GND bouncing undistinguishable from signal
- ElectroMagnetic disturbance coupled through loop



$$v_o = A_d \cdot v_d + A_{cm} \cdot v_{cm}$$

- let's amplify just Differential signal
- let's reject Common Mode disturbance


$$CMRR = \frac{A_d}{A_{cm}} \approx 80-100dB$$

I can twist the cable so that if there is any electromagnetic disturbance is not coupled with the loop of the wires.

Moreover, in case of common mode signals (e.g. between grounds), the V_{cm} is applied to both inputs, so this is the reason why residual V_{cm} will be rejected if A_{cm} is 0, but this is not true in the real case. A_{cm} is more or less 10 for instance, and V_d is usually negligible because small and needs to be amplified and A_d is high because of the amplifier, whereas the V_{cm} is very high but with a very small A_{cm} . There is the risk that common mode signal overruns the useful signal \rightarrow we have a strong disturbance.

It is introduced the CMRR that should be the highest possible.

 Since we will never use the opamp in OL configuration, the feedbacks helps.



Closed-loop gain:

$$G(s) = \frac{S_u}{S_{in}} = \frac{A(s)}{1 - A(s) \cdot F(s)} = \frac{A(s)}{1 - G_{loop}} = \frac{1}{F(s)} \cdot \frac{1}{1 - 1/G_{loop}}$$

For example: $G_{loop} = -10$ correction factor = 0.9 $G_{loop} = -100$ correction factor = 0.99

Note: $1 - G_{loop}$ is a large positive number
and $\frac{1}{1 - 1/G_{loop}}$ is the correction factor between ideal and real gains

- and ... many more further advantages ...
 - larger bandwidth (excellent speed)
 - lower output impedance (excellent voltage source)
 - either ∞ input impedance (excellent voltage reader)
 - or 0 input impedance (excellent current reader)

The gain is reduced by G_{loop} , however it is more stable.

IMPROVEMENTS GIVEN BY THE FEEDBACK

Tolerances

In the upper image the gain is high, but if A changes of 15% (e.g. due to age), the gain varies of 15%.

Here is the "open-loop" OpAmp:

$$G = \frac{V_o}{V_d} = A$$

$$\frac{dG}{G} = \frac{dA}{A} \quad \text{e.g. } \pm 50\%$$

Here is the "closed-loop" circuit:

$$G = \frac{V_o}{V_d} = \frac{A}{1 - A \cdot F} = \frac{A}{1 + G_{loop}}$$


$$\frac{dG}{G} = \frac{dA}{A} \cdot \frac{1}{1 - G_{loop}} \quad \text{e.g. } \pm 50\% \cdot \frac{1}{1+100} = \pm 5\%$$

But what about $\frac{dG}{G} = \frac{dF}{F} \dots ??$

If we consider the same variation but with a feedback added, now it is better. The G (gain) is computed as always and now the variation of gain is dA/A divided by $1 - G_{loop}$, hence if G_{loop} is strong, even if A varies, it is mitigated by $G_{loop} \rightarrow$ external effects won't affect the performances.

Now if I compute dG/G as a function of dF/F , that is due to tolerances of components, if F changes by 10%, G changes by 10% as well \rightarrow the feedback reduces the dependencies on the tolerances of the opamp (forward dependencies), but not on the tolerances of the feedback components. We can buy a cheap opamp but we need very precise resistors, because they set the gain.

Input impedance

 

$$R_{in} = R_1 + R_A$$

$$R_A = \frac{\varepsilon}{i_1} = \frac{\varepsilon}{i_{in} + i_2} = \frac{\varepsilon}{\frac{\varepsilon}{R_{in}} + \frac{\varepsilon - A(s) \cdot \varepsilon}{R_2}} = \frac{R_{in} \cdot R_2}{R_2 + R_{in} - A(s) \cdot R_{in}}$$


$$= \frac{R_{in} \cdot R_2}{R_{in} + R_2} \cdot \frac{1}{1 - A(s) \cdot \frac{R_{in}}{R_{in} + R_2}} = \frac{R_{in} \parallel R_2}{1 - A(s) \cdot \frac{R_{in}}{R_{in} + R_2}}$$

The feedback is negative because if I have a positive increase, + terminal will go positive, hence if the output stays 0, the output will start to go negative so that node x is free to move up and down, and it is controlled by the feedback.

Every time we see a node in a feedback loop, the loop will try to maintain that node without voltage variations.


Again, since the + terminal is grounded, the amplifier will provide an output so that node x will be always at 0V. So V_{in} will see R_1 and then V_G , not actually a ground, because driven by the amplifier, and the amplifier drinks the current that the input is providing.

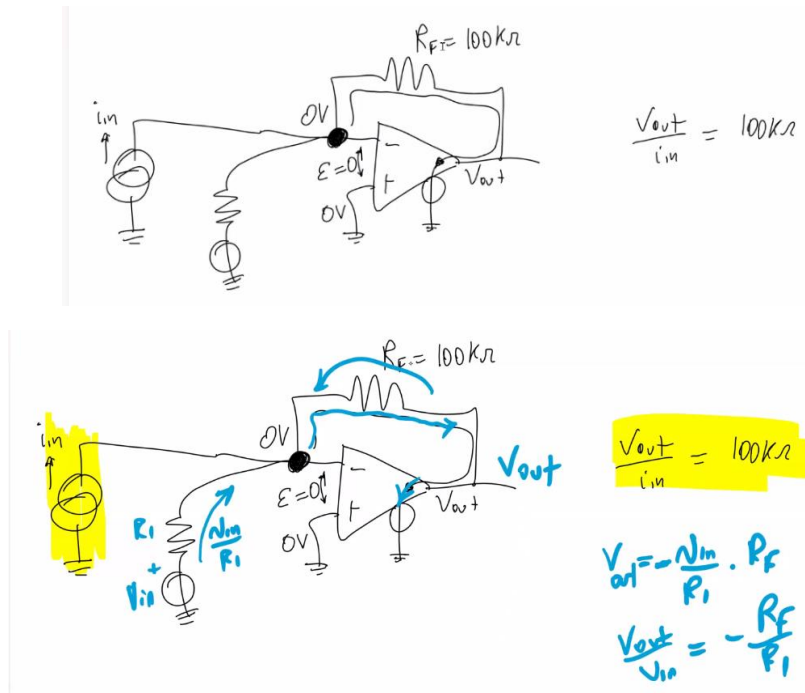Every time we have an opamp and the output of the opamp goes back to the input, if we enter with a current source or a real voltage source, that node will stay at 0 because thanks to feedback the error epsilon between terminals + and - is kept to 0, the injected current flows through the output.



The last blue equation relies on the presence of a virtual ground. So even if we introduce a resistor between + and - terminals, it won't have any effect because it will have no voltage across it and no current across it and its impedance won't be sensed. The current that goes in the virtual ground flows in the resistor between + and - terminals and goes to ground where it ends.

 Let's now compute the input impedance measured by the source.



Input impedance:

$$R_{in} = R_1 + R_A$$


$$R_A = \frac{\epsilon}{i_1} = \frac{\epsilon}{i_{in} + i_2} = \frac{\epsilon}{\frac{\epsilon}{R_{in}} + \frac{\epsilon - A(s) \cdot \epsilon}{R_2}} = \frac{R_{in} \cdot R_2}{R_2 + R_{in} - A(s) \cdot R_{in}} = \frac{R_{in} \cdot R_2}{R_{in} + R_2} \cdot \frac{1}{1 - A(s) \cdot \frac{R_{in}}{R_{in} + R_2}} = \frac{R_{in} \parallel R_2}{1 - A(s) \cdot \frac{R_{in}}{R_{in} + R_2}}$$

The input impedance considers everything off. We have R1 and two paths then, one through Rin and ground, the other thru R2 and ground. So it seems that Rin and R2 are in parallel. But this is not true because R2 is not connected to ground, since as soon as A moves, the output node moves.

How much Ra is? It is epsilon divided by current i1 that flows, and that is iin + i2. Then the computations are like in the image.


In the end, the impedance into A, that is Ra is actually Rin || R2, divided by a correcting factor that is 1 - Gloop. Every time we have such a circuit, the input impedance seen by Vin is: firstly there is R1, then I need to realize that there is a negative feedback and if Gloop is infinite, the input resistance is Rin || R2. If it is not infinite, we need a correcting factor.

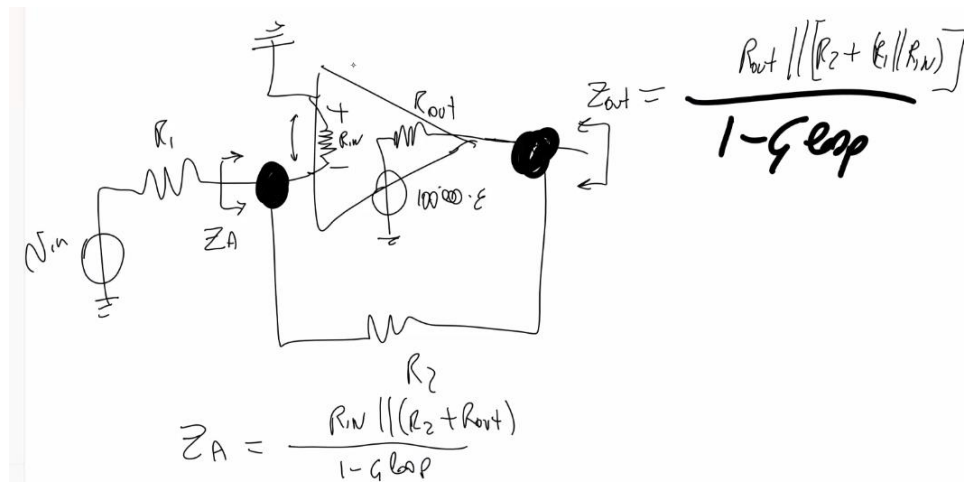The same reasoning can be done for the output impedance. In the ideal case I see 0 Ohm, but in the case of a real opamp, we have a Rout in parallel to a parallel of resistances.



If Gloop is strong, the output resistance is almost null.

IMPEDANCES THROUGH BRANCHES

 

Real transfer function:

$$\frac{V_{out}}{V_{in}} = + \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{1}{1 - 1/G_{loop}(s)}$$

Therefore, in case of FEEDBACK at a «NODE»:

Output impedance: $R_{out} = \frac{R_{out} \parallel (R_2 + R_1 \parallel R_{in})}{1 - G_{loop}(s)}$ $R_{out} \approx 0$

Instead, in case of FEEDBACK through a «BRANCH»:

Input impedance: $R_{in} = [R_{in} + R_1 \parallel R_2] \cdot [1 - G_{loop}(s)]$ $R_{in} \rightarrow \infty$

Let's consider the case of a real Rin (not infinite). If it is e.g. 1kOhm and I apply 1V, the opamp drinks mA of current from the source. But the loop gain Gloop will improve the impedance in input. In every

node of the loop the impedance is divided by $(1 - \text{Gloop})$, either the output node or the $-$ terminal of the depicted circuit.


Thanks to the Gloop the input impedance is the dummy one magnified by Gloop, because in the loop branches we have a magnification.

NB: when computing output and input impedances the generators are off, and so also the voltage generator inside the amplifier, hence we have like ground at the output of the amplifier.

We end up with an equation that, rearranged, it showing an input impedance that is the easy one $(R_{in} + R1 \parallel R2)$ multiplied by Gloop in the case of input on the positive terminal.

Again, the opamp gain is not needed to be infinite, it is sufficient to have good components.


FEEDBACK EFFECT ON BANDWIDTH

 

To have a very high gain, we need a lot of transistors in the opamp, but the higher is also the number of parasitic capacitances and hence the decrease in bandwidth. The bigger the amplification, the smaller the bandwidth in OL configuration of the amplifier.

If we use the opamp in OL, we are stupid, because we have a very huge amplification but with a very small bandwidth. To increase the bandwidth, we can shift the position of the pole with the feedback, because the tau is reduced with Gloop. In this way we kill the gain but we fasten the amplifier.

 Hence Gloop kills the gain by a factor $1 - \text{Gloop}$ but also pushes the pole of a factor $1 - \text{Gloop}$. Where the DC gain touches $A(s)$, there we have the new pole.




OPAMP STAGES



VOLTAGE AND CURRENT ADDER

We want to add several current sources. Let's consider different current sources, maybe with different performances (related to the parasitic resistance, with the smaller the R the worse the current source). In order to add the current, let's have the current flow in a load resistor. It is not good, because Rload has to be small, and if the parasitic R is low, it is not good, Rload should be small for all the related resistance. If a voltage develops over Rload, it generates a current that steals current from the sources. There is another possibility to have a resistor whose value is much smaller than all the others and it is the one with R = 0. In this case, iout is indeed the sum of all the currents. However, we sum the currents but we have no signal to amplify.

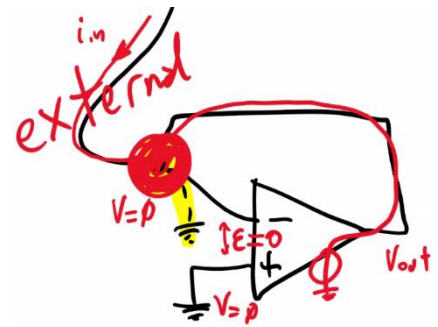Hence we need a ground, but not a ground, something that behaves like it without being a ground. The best solution is to use virtual grounds. Hence we use an amplifier with one input grounded and then the other node will be at virtual ground. We introduce a feedback circuit to force one terminal to virtual ground. Thus the current flows in feedback to ground.



  If we place a resistor in feedback, we will have a voltage drop on it, having hence Vout that is not 0, but Rf*iin (transimpedance amplifier).




Voltage gain:
$$v_u = -\left(\frac{R}{R_1} v_1 + \frac{R}{R_2} v_2 + \dots + \frac{R}{R_n} v_n\right)$$

Input impedance: $Z_{in_i} = R_i$

Output impedance: $Z_{out} \approx 0$

 Vout is equal to the sum of all the input currents (Vi/Ri) multiplied by R in feedback. Hence having a resistor instead a virtual ground is bad because if we have different voltage sources and we want to sum them, if we use a resistor, we will have a voltage on the resistor that is also applied to the other sources, so we have a sort of cross-talk. The amplification for each line is R/Ri.




This might damage the voltage source. For this reason is much better to use a ground, and not a resistor.

The output impedance, if the opamp is ideal it is 0. If Rout is not zero, the impedance we see is not just Rout || R + (R1 || R2 || ...), but it is this one divided by 1 - Gloop, with Gloop = A(s)*(R + (R1 || R2 || ...)).

As for the input impedance, every generator sees R_1 , R_2 etc, and then virtual ground. So it just depends on the input source resistance. This is not ideal because the feedback R is common to everybody, to change the gain relate to a source we need to change R_1 , R_2 etc. To overcome these mismatches, we better use another amplifier, that is the following one.

 The source is not applied straight to the R_1 , R_2 etc, but it is applied to an opamp whose gain is equal to 1, that is a **buffer**. An inverting buffer, that inverts the signal, has always the feedback on the $-$ terminal.




With the added buffers, the impedance in output of it is 0, whereas the input impedance the sources will see is infinite.

VOLTAGE SUBTRACTOR



The non-inverting configuration has a gain of $(1 + R_2/R_1)$, where R_2 is in feedback \rightarrow gain always >1 , so we will always have an amplification and never a decrease in signal.

Another possible configuration is the inverting amplifier, whose gain is $-R_2/R_1$. The gain is always negative and can assume any value greater or smaller than 1.

 We use one source to the $+$ terminal, and one on the $-$ terminal. We want to make the subtraction. The source V_1 experiences a gain of $-R_2/R_1$, the other $1 + R_2/R_1$, and this is not good because the gains are different, so we don't subtract the signals. Hence we need to introduce an attenuation.



With the attenuation.

  

$$v_{u1} = -\frac{R_2}{R_1} v_1$$

$$v_{u2} = \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right) \cdot v_2$$

Differential gain (when $R_2/R_1 = R_4/R_3$):

$$v_u = -\frac{R_2}{R_1} \cdot v_1 + \frac{R_4}{R_3} \cdot v_2 = -\frac{R_2}{R_1} \cdot v_{diff}$$

Common-mode gain:

$$v_u = 2 \cdot \frac{R_2}{R_1} \cdot v_{cm} \cdot tol$$


Input impedance: $R_{pos} = R_3 + R_4$
 $R_{neg} = R_1$

$R_{neg} \neq R_{pos}$


Let's solve this issue...

Output impedance: $R_{out} \approx 0$

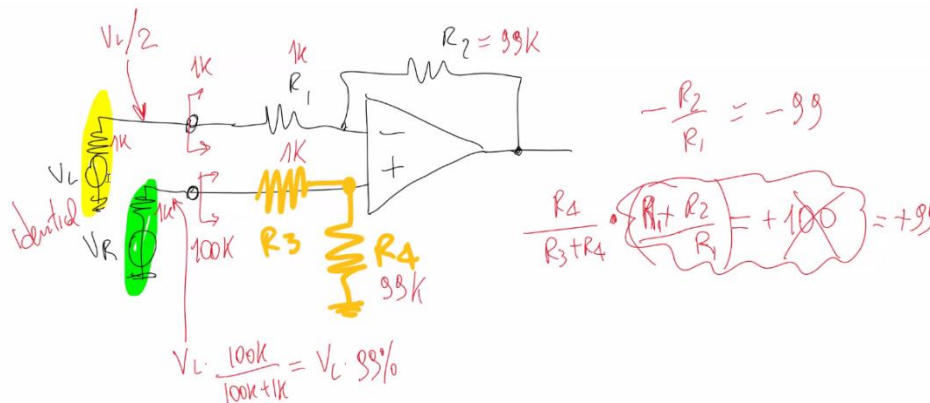The + terminal can move, whereas the - terminal is the slave (VG) and is linked to the + terminal. On the - terminal I see R1 as impedance, on the other branch R3 + R4. Hence even if the inputs source resistances are equal, the output is not 0 because of different input impedances on the two branches in input to the amplifier.




 We solve this mismatch by using buffers in input. - terminal is still at virtual ground and now the output is perfect.



IDEAL VOLTAGE INTEGRATOR

 We apply a V_{in} and node at terminal - will be fixed if I consider a strong feedback. The output is always the one that allows the virtual ground to be actually a virtual ground. We apply whatever V_{in} we wish but then the current that flows in must flow in the feedback.



Now in feedback we use a capacitor. In the capacitor, $V_{in}(t)/R = i_c(t) = C \cdot (dV_c(t)/dt)$.

$V_c(t) = (1/RC) * \text{Integral}(V_{in}(t)dt) = -V_{out}$. V_c is the opposite than V_{out} .

$$\dot{v}_c(t) = \frac{V_{in}(t)}{R}$$

$$\frac{V_{in}(t)}{R} = \dot{i}(t) = \dot{q}_c(t) = C \cdot \frac{dV_c(t)}{dt}$$


$$-V_{out}(t) = V_c(t) = \frac{1}{RC} \cdot \int_0^t V_{in}(t) dt$$

$$V_{out}(t) = -\frac{1}{RC} \cdot \int_0^t V_{in}(t) dt$$

The same reasoning can be done in the Laplace domain.

$$V_{out}(s) = (1/sRC) * V_{in}(s).$$

 Since there is the $s = \alpha + j2\pi * f$, the plot is the one below, with a decrease of -20dB/dec.



Every time we encounter this decrease, it means we have an integrator. This also means we have a pole in the origin (0 Hz) and no zero. The placement of the slope depends in the frequency where the plot intercepts the x axis, that is $1/2 * \pi * RC$. It is not a pole, but the frequency at which the gain is 1.

POLITECNICO MILANO 1863

Basics: $i_c(t) = C \cdot \frac{dv_c(t)}{dt}$


Time-domain: $v_o(t) = -\frac{1}{C} \int i(t) dt = -\frac{1}{RC} \int v_i(t) dt$

Frequency domain: $A_v(s) = \frac{V_o(s)}{V_i(s)} = -\frac{1}{sR} \quad \text{Laplace analysis}$

Issues: DC gain trends to infinity $A_v(0) = -Z_2 / Z_1 = \infty$
 hence eventually the OpAmp always saturates


The gain is $-(1/RC)$, that is not a pure number, but $1/[s]$, 1 over seconds, so that in output we still have a voltage. In the upper right plot we can see that we are integrate the signal in black resulting in the signal in green.

Example

 


The input is the black signal.


Let's now compute V_{out} . We need to know the charge accumulated in the capacitor. At time 0, it $V_c = 0V$, since V_{out} is ground and then we have the virtual ground. The output is the area of the voltage multiplied by the gain. So initially is 0, but then at a certain time we should compute the integral of V_{in} multiplied by the gain $1/RC$. If time passes, the area increases in the first 10 μs , and since there is a minus in the equation, the output will be negative; since the input is constant, the output will be a straight line. The total area of the first part is $10 \mu s * 10 mV$.

 

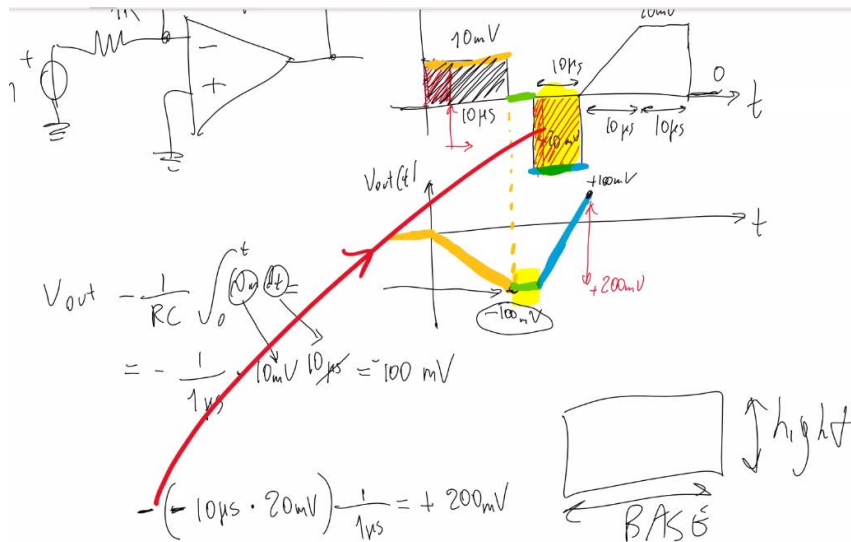Then we have a 0 to integrate \rightarrow the output will not move, and then we have to integrate something that is negative. Since the gain is negative, we will find a transition that will be increasing. The computed area must add to the previous value of V_{out} we had, that was $-100 mV$, so since it is of $200 mV$, we end up at $100 mV$.




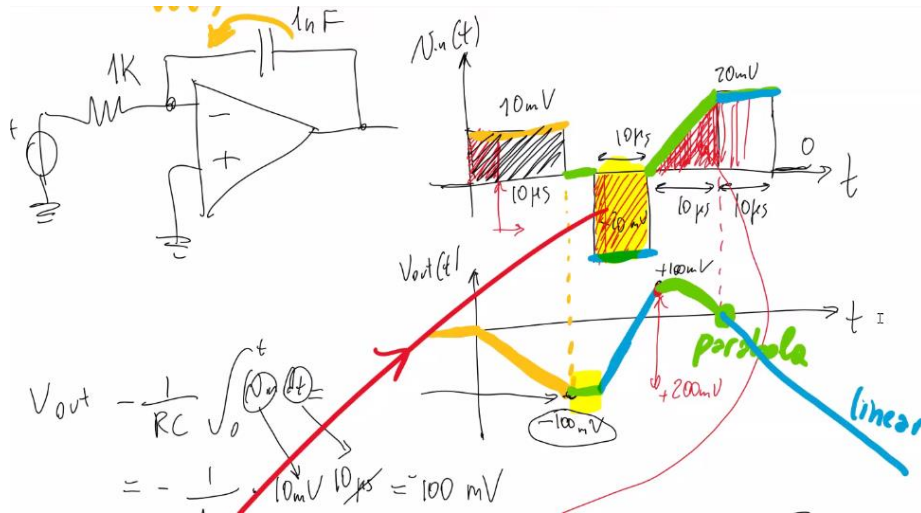Then we have the triangle: $-(10 \mu s * 20 mV) / 2 * (1 / 1 \mu s)$, so we must add $-100 mV$ from the $100 mV$ point. Since the trend is linear, we will have a paraboloid decrease.



The problem of the ideal integrator is that the current is 0 in DC if the capacitor is not charging up, whereas it should be present a current if I apply a constant voltage at the input. The opamp tries to drink a constant current in DC, but a constant current through a capacitor in DC causes $dV(t)/dt$ to be not nihil.

If in this integrator we have a constant signal due to the input or an offset, due to the virtual ground concept a current will flow through the 1k resistance, the current in DC flows through the capacitor, and if i is constant, voltage on the capacitor keeps increasing with an incredibly big rate, so the output starts from 0 and then when an offset is present the output continues to increase up to the saturation of the power supply of the opamp. Once it is saturated, it won't work anymore → problem of saturation with constant currents.

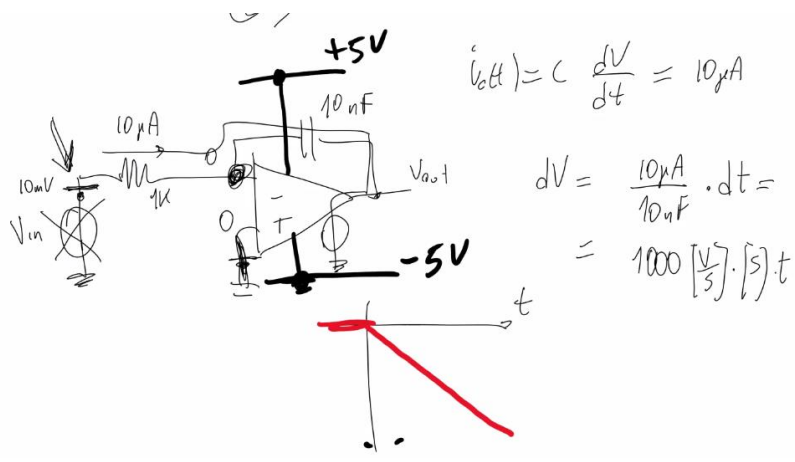


To avoid saturation, we should introduce a component that doesn't let the feedback to degenerate → we put a resistor in feedback, so that the gain doesn't saturate.

REAL VOLTAGE INTEGRATOR


In DC the capacitor is open, so the gain R_p/R , whereas at HF it is 0 because the C is a shortcircuit. Hence we start flat with a constant gain and then goes to 0 → we have one pole, not at the origin.

 The frequency of the pole is $1/2 \cdot \pi \cdot R_p \cdot C$. But let's compute it. We need to find the total R related to the C. C sees R_p parallel to the green path, that is made of R_i and R_{out} . Otherwise, I can see R_p and then virtual ground on the left and R_{out} on the right. But also this




is incorrect.

 When studying the pole, we switch V_{in} off, but not the one related to V_{out} inside the opamp. The correct analysis is the one below.



 
But then the capacitor cannot move as it wishes? One end of the capacitor touched the virtual ground, so as soon as the virtual ground moves, the opamp moves the output and hence the capacitor is in between constant and equal changes. So the output node can go up and down in order not to let the other arm (where the virtual ground is) change.



~~Laplace analysis:
 $A_v(s) = -\frac{Z_p(s)}{R}$
 $A_v(s) = -\frac{R_p}{R} \cdot \frac{1}{1+s \cdot R_p \cdot C} = \frac{A_{v0}}{1+s\tau}$~~
 No more, thank you!

Asymptotic analysis...

 
in DC: $A_{v0} = -\frac{R_p}{R}$
 at ∞ frequency: $A_v(\infty) = 0$
 there is a pole: $f_1 = \frac{1}{2\pi \cdot R_p \cdot C}$



The frequency at which the gain is equal to one is given by the GBWP: $1/2 \cdot \pi \cdot R \cdot C$, that is the same frequency of the ideal case.


The ideal integrator saturates at DC, so we added a resistor to get a real integrator. I could have also considered a normal amplifier and later added a capacitor, obtaining a low pass filter. Hence the LP filter and the real integrator have the same behaviour. But which is? It is an amplifier when the gain is flat,

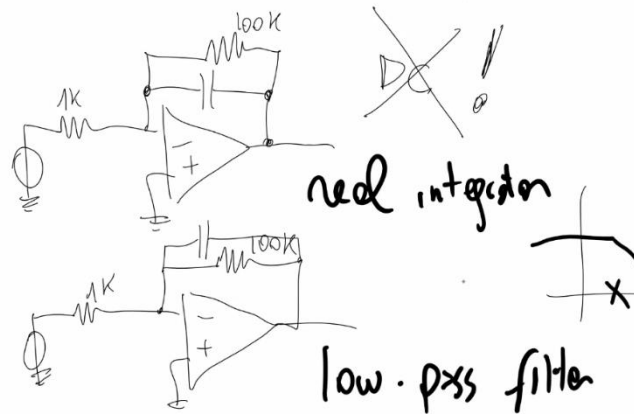hence from 0 to the pole, and then it is an integrator when the gain is no more flat, whereas it is a LP filter when the pole is in the middle of the frequency range.




IDEAL DERIVATOR

In feedback we place a resistor.

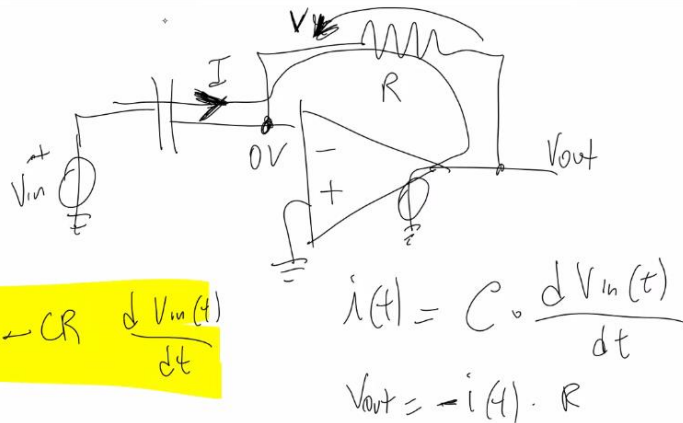

This time the gain is in seconds.

 

Basics: $i_c(t) = C \cdot \frac{dv_c(t)}{dt}$

Time-domain: $v_u(t) = -RC \cdot \frac{dv_i(t)}{dt}$

Frequency domain: $A_v(s) = -s\tau$


Issues:

gain at ∞ frequency diverges, since $A_v(\infty) = \infty$
 hence eventually the OpAmp is too sensitive to noise

If the signal in input increases, the output decreases and vice versa. If the transition happens in 0 time, in output we will have a Dirac delta.

 Example

The derivative in the first phase is the ratio between the two delta; since the slope is constant, the output will be constant. When the input is 0 the output is 0. When we have the sharp transition, the slope is




infinite, so we have a Dirac delta (lasting 0 time). However is not exactly infinite, but it goes to a finite value because it will, in reality, have a very very small duration.

The problem with this stage is the lack of control at HF, and we are shortcircuiting a virtual ground with an input. In the ideal derivator, we have a zero in the origin, with the frequency where the gain is 1 that is $1/2 \cdot \pi \cdot RC$.


We want to force it in saturation soon or later with a pole, placing a resistor in series with the capacitor.

REAL DERIVATOR

 


Asymptotic analysis...

 - in DC: $A_v(0) = 0$
- at ∞ frequency: $A_v(\infty) = -R/R_s$
- bandwidth: $f_1 = \frac{1}{2\pi \cdot R_s \cdot C}$




Now the pole is $1/2 \cdot \pi \cdot RC$, whereas where the gain is 1 we have R_s . Also in this case we can consider either a real derivator or a HP filter. Again, the reasoning on when it is an amplifier or a derivator holds as before.


Recap

 

BANDPASS FILTER

 


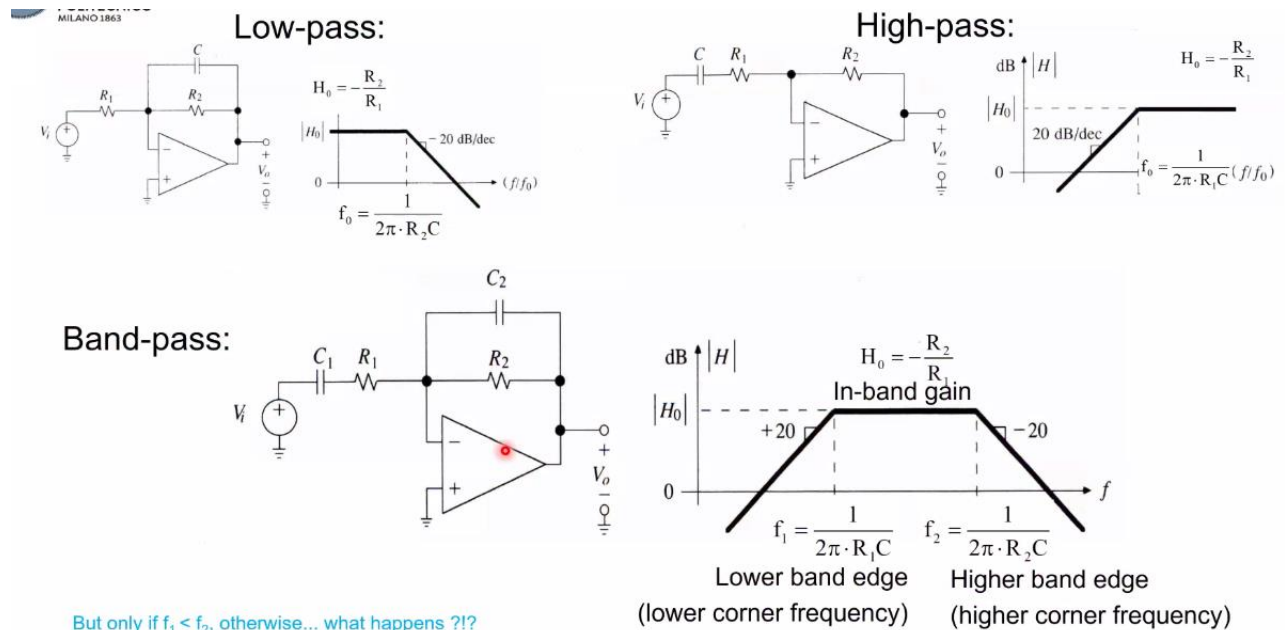With symmetrical slopes in the Bode plot. The gain is $-R_2/R_1$, only if the input path has the pole at lower frequencies than the feedback pole. If we do the opposite, the capacitor C_2 kills the signal with the capacitor C_1 that instead lets the signal pass \rightarrow the signal will die soon, so it's us that need to choose the pole correctly.



Band-pass wrong sizing


Band-pass (**wrong sizing!**):

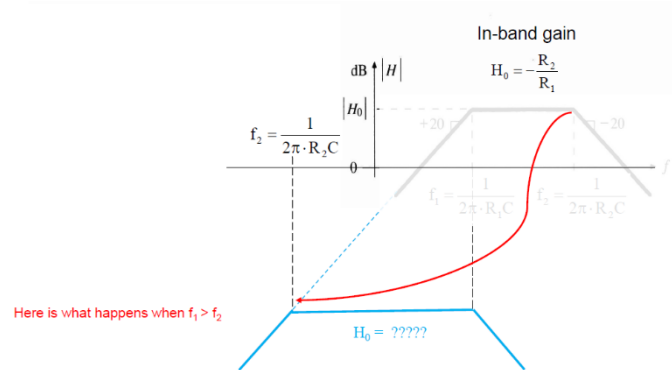

We have to size the poles so that one happens at LF at the frequency we wish so that at midrange we are in a configuration where the input capacitor is shorted and the feedback one is open, so the gain is $-R_2/R_1$. If the pole related to the feedback capacitor is at LF, so we do the wrong sizing (as in the image above), we have an intermediate range very bad, because if we increase the frequency of the signal, instead of having the input capacitor shorted and the other one open, it is the opposite.

To compute the gain in the midrange in the case the poles are inverted, we can use the products. We know that in the case the poles are correct the gain is $-R_2/R_1$, and we have to put together the two trends.

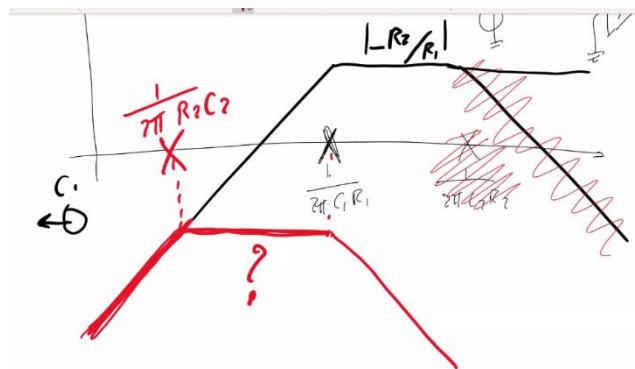Let's compute the height of the filter in case of bad conditioning, hence the pole related to C_1 at higher frequencies than the one related to C_2 . In red what happens in case of bad conditioning, in black good conditioning.



The gain of the red flat part is not $G = -R_2/R_1$, but it is this quantity multiplied by a scaling factor.



$$G = \left| -\frac{R_2}{R_1} \right| \cdot \frac{\frac{1}{2\pi C_1 R_1}}{\frac{1}{2\pi R_2 C_2}} = \frac{\frac{R_2}{R_1} \cdot C_2 R_2}{C_1 R_1} = \left(\frac{R_2}{R_1} \right)^2 \cdot \frac{C_2}{C_1}$$

Depending on C_2 and C_1 we will have a lower gain than expected.

TRANSIMPEDANCE AND TRANSCONDUCTANCE AMPLIFIERS

Transimpedance amplifier

  The input impedance of the right circuit is 0 because we have a virtual ground at the - terminal. Also, the output is a very low impedance, and if we have an amplifier with low input impedance, we can connect a current source, whereas if the output impedance is low, it is a very excellent voltage source, so it is actually a I to V converter.



Gain (transimpedance): $-R_2$
independent of the load R_L

Input impedance: $Z_{in} \approx 0$


Output impedance: $Z_{out} \approx 0$

Gain (transconductance): $-1/R$
independent of the load R_L

Input impedance: $Z_{in} \approx \infty$


Output impedance: $Z_{out} \approx \infty$

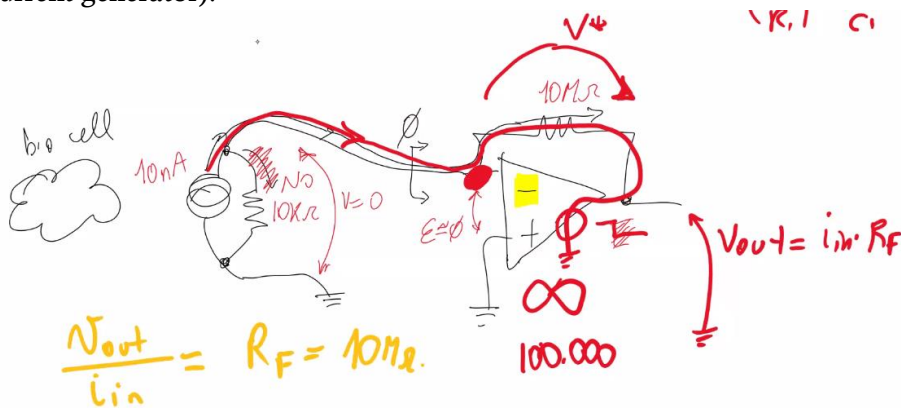The following an example. Since - terminal is virtual ground, no current is lost in the source (resistor in parallel to the current generator).



Transconductance amplifier

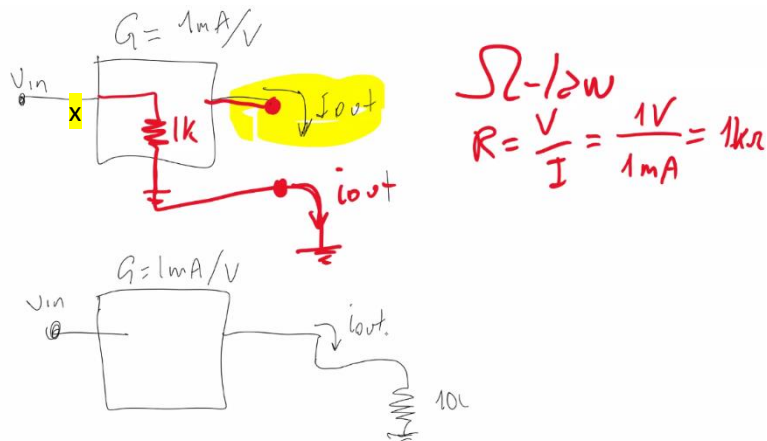I want to convert a voltage into a current. I want an output current proportional to the input voltage, with a gain that is for instance 1mA/V. The typical erroneous solution is the ohms law, because it is not n amplifier, because I would have the output node for the current attached to ground if I use a resistor,



while now I want a floating output to be attached to whatever the customer wants, and if I use a simple resistor the current in output depends on the load. So x is wrong.

I want an amplifier with infinite input impedance so that if the input impedance of the source is whatever, the input impedance of the amplifier will dominate. Then I want the output to be a current generator, so the output impedance also infinite, so that it is a perfect current source.




If we consider an amplifier, connecting directly the source to the terminal of the amplifier is ok, because we verify the condition of infinite input impedance. However, in output to an OL amplifier we have 0 impedance, so it is a perfect voltage source, not a current source in output. So I put a feedback signal in output, as below. If Gloop is infinite, I return to the input what I've applied. Since the loop is negative, I have epsilon = 0 across the terminal, and so Vin is also applied to the output.

However, I want the current to flow through the output resistor of 1k and the load. Now, the current is however no more Vin/1k, but Vin/(1k + RL). So how can I do it?



 The current comes from the amplifier, that is a voltage source. To solve the problem, I attach the load to the output load and then I connect the output load to the feedback and the 1k resistor.



The load is in series with R as in the transimpedance amplifier, but the current is independent on RL.

However, a limitation of this circuit is that (gain of 1mA/V), if RL is huge, such as 100k compared to the 1k of R, the 1mA through a 100k resistor means 101V provided by the amplifier, and no opamp can provide such a high voltage.


Conversely, if RL = 2k and we want a higher gain, such as 200mA/V, I can use a 5ohm resistance as R. But the 200mA should go through RL and maybe the amplifier cannot provide it. Hence this stage is good but not always works due to the current and voltage limiting capabilities of the amplifier. However, it is good if we want to force a current in a cell.

How can the current be high in the load but not in the opamp?

Final implementation

I still need the resistor and I don't connect the opamp to the resistor, but I use a transistor in output, and the transistor will provide the huge current I need. The opamp provides no current but the voltage required.

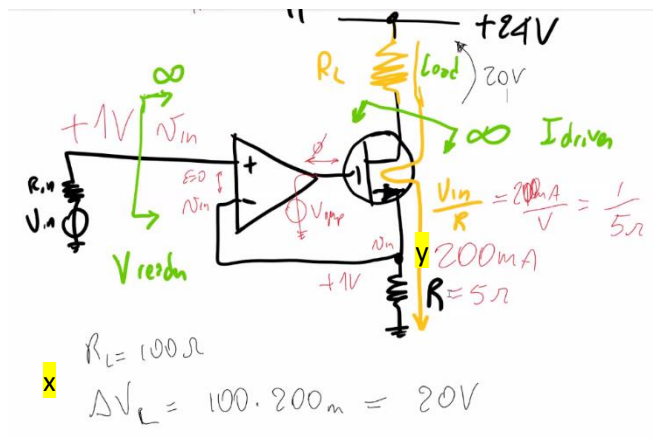The load is connected somewhere to have high voltage. The current through R is fixed by the stage. So the input impedance is infinite, the output impedance seen by the load is infinite, so it is a perfect voltage reader in input and current driver in output (24V power supply are given by the computation).




What is the voltage in output of the opamp?

The transistor is a very nice slave, so the buffer gives the voltage to it and the transistor gives the current that is ok with my requirement. If I apply V_{in} , the opamp output voltage increases, V_{gs} of the transistor increases and also the current flowing through it. If current increases voltage at $-$ terminal increases. If $-$ terminal voltage is different than $+$ terminal, the output is still high, up to the point the two input voltages are the same and the epsilon is 0.

Eventually, if G_{loop} is infinite, epsilon is 0, but if the gain is finite, epsilon will be e.g. 10nV, that are however negligible when transferred in output.

In output of the opamp, we need to consider MOS transistors. They are devices using a p-doped silicon with n+ doped introduced with diffusion. With no voltage to the gate, if we apply a V_{ds} voltage, no current happens because we don't have current. So we need to apply a positive voltage to the gate so that the holes of the p-doped material are pushed down and electrons start to pass across the material. The current is between drain and source (I_D).

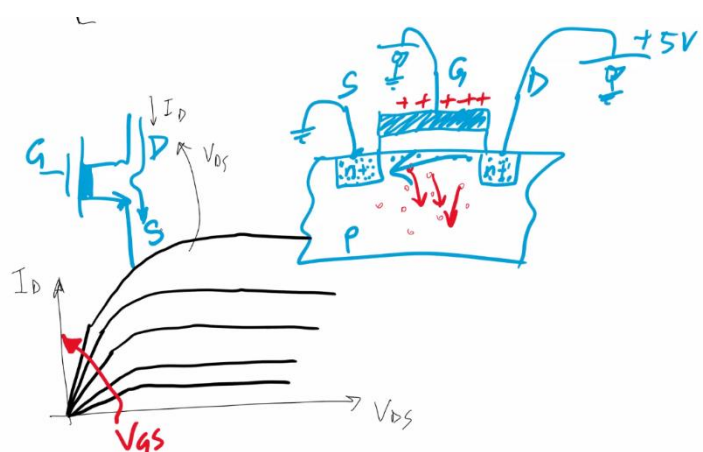

If V_{ds} is increased too much, we suffer from a saturation of the current I_D .

The minimum voltage to be applied to the gate to have a current is called threshold voltage (V_t). The difference $V_{gs} - V_t$ is called V_{ov} , overdrive voltage.

The typical equation of a MOS transistor is the following, in the saturation region.

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$

It is proportional to the squared V_{ov} , while μ is the electron mobility of the channel, C_{ox} is the parasitic capacitance of the Silicon dioxide insulator, while W and L are the physical dimensions of the transistor.


So going back to the previous circuit transconductance amplifier, if we apply a $V_{in} = 1V$:

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs} - V_T)^2$$

$K = 10 \frac{mA}{V^2}$

$$200 mA = I_D = 10 \frac{mA}{V^2} \cdot OD^2$$

$$OD = \sqrt{\frac{200 mA}{10 \frac{mA}{V^2}}} = \sqrt{20} = 4.2 V$$
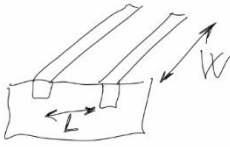
$$V_{gs} = V_T + OD = 1.1 V + 4.2 = 5.3 V$$


Hence between the upper terminal of R and the output voltage of the opamp we have to apply V_{gs} . Since we have V_{in} in the upper node of the resistor R, so we perform the Kirchhoff law and V_{out} of the opamp is $6.3V \rightarrow$ we need a power supply higher than $5V$ for the transistor.

NB: if we apply a V_g and $V_{ds} = 0$, we are in the ohmic region, where the current varies depending on V_{gs} and also on V_{ds} and the channel is uniform. If now we increase V_d , e.g. to $2V$ and we apply $5.3V$ at the gate, we have a very high V_{gs} , but a lower V_{gd} ($3.3V$) \rightarrow if we increase the drain voltage then we have channel at the source side but no more at the drain side \rightarrow pinch-off condition if we reach V_t , and the green equation holds. So in the saturated region I MUST have channel at the source but NO CHANNEL at the drain.


Hence I should not have V_t , but a smaller value for V_{gd} . If $V_{gs} > V_t$ and $V_{gd} < V_t$, it is ok and we are fine (channel at the source and no channel at the drain), and it is ok because the current doesn't depend on V_{ds} . But we have to verify we are in this condition.

We want the two inequalities before, meaning that the condition to be satisfied is $V_{gs} - V_t > V_{ov}$. The saturated region is perfect because if I change R, I don't want the current to change, so eventually V_{gs} changes but I_d remains constant.

NB: we must verify the MOS in the saturated region in the end, that occurs if $V_{ds} \geq V_{ov}$. Let's see from the example. $V_s = 1V$, $V_{ov} = 4.2V$, so V_d must $> 5.2V$ to have a working stage that acts as a current source.

If we let the transistor operate in the saturated region we are sure that it acts as a current source, so that if voltage at the drain changes the current will never move. But if for any reason we are in the ohmic region, then the current through the source won't be the value above, so if current reduces, voltage y would change and be lower than expected, so an epsilon will appear at the input of the opamp. So even if the transistor enters the triode region, since there is feedback the opamp will start to increase V_{gs} so that the current in the MOS is enough to enforce the overall feedback.


When we apply $V_{in,max}$, the circuit is the one aside. V_{in} can move from 0 to $5V$, the bottom resistor is 5 ohm so with $1V$ in input we have 200 mA , but if we apply $5V$ the current should be $1A$ ($5V/5\text{ohm}$). If the current is $1A$, we can compute the required V_{gs} , that is for instance $9V$, so we run the risk that if we apply $5V$ in input the voltage at the output of the opamp should be $14V$ (KVL), so PS has to be higher than $12V$. Moreover, if on the drain of the

 


MOSFET we have our load that is for instance a 100ohm resistance, forcing 1A in 100ohm means that in the worst case the voltage drop across the load will be 114V, so PS of 24V is not enough. Moreover, we have to try to enforce saturated region, so at least one overdrive at the drain node → too high power supply for this application.

Hence if we want the drain node to be above of at least one overdrive, then we require the PS to be too high, so maybe the design constrain can be relaxed and instead of operating the MOS transistor in the saturated region but in the ohmic region, with a very high V_{gs} . If the opamp can do this, current will be the one we want anyhow and everything will work, but we have to be sure that the opamp can do this and that the MOSFET can withstand such high voltages → as a rule of thumb let's try to operate with the transistor in saturation, the opamp with a proper value and also the PS.

 There are some application where the load is connected to ground. Hence we cannot connect it directly to the power supply, because one end of the load is to ground. We simply use a p-MOS transistor and invert everything. When $V_{in} = 5V$, across the resistor I have 0V and 0 current. Whereas if $V_{in} = 0$, the current is the maximum.



 
So if V_{in} varies between 0 and +5V, i_{out} changes as on the left (condition of n-MOS), whereas in the other case it is the right plot.



LOGARITMIC CONVERTER

Let's consider an opamp with a signal applied, e.g. entering in the - terminal and placing a non-linear component in feedback, e.g. a diode. In forward bias, the diode has the displayed characteristic, with a current of more or less mA in the forward region and in the order of uA in the inverse region.

When V_{in} is high, the voltage at the - termina increases, so the output start to becomes negative and hence the voltage across the diode rises in forward direction. Let's imagine to apply 1V as V_{in} and use a 1k resistance. The current is 1mA, will flow through the diode and since it is on, the output voltage will be 0.6V. If we now apply $V_{in} = 5V$, the current will be 5mA, so V_{out} will be like 0.63, because the voltage increases a little bit across the diode.

 

So the output stays almost constant. If we consider the equation of the diode, the current has an exponential trend depending on V_{th} where $V_{th} = kT/q$ (25mV at RT) $\rightarrow I_D = I_s \cdot [e^{(V_d/V_{th})} - 1]$. So V_{th} compared to V_d causes an exponential increase of I_D in reverse bias. In forward bias, we can forget of the -1.

Small signal analysis

Let's consider a small variation around a central point and see what happens in output.

If we apply something positive at the input, the - terminal of the opamp goes positive, but then the output goes negative \rightarrow the diode turns on and the voltage at node - is pushed back to a negative value. So the feedback is negative and node x acts as a virtual ground.


Hence the current that enters the feedback circuit is V_{in}/R , and we are forcing the opamp to drive the current and let it flow through the diode. Now let's compute the dependency of V_d over V_{in} .

$$\frac{V_{in}}{R} = I_D = I_s \cdot e^{\frac{V_d}{kT/q}}$$


$$V_{out}(t) = \frac{kT}{q} \ln \frac{V_{in}}{R \cdot I_s}$$

The relationship between V_{in} and V_{out} is no more an amplification but it is a logarithmic scaling. So the stage behaves like a **logarithmic amplifier**, meaning that a compression is performed over the input signal.

 However, if I forget the - 1 in the equation of the diode, the logarithm is equal to 0 when $V_{in} = I \cdot R_s$. This is not true because the real curve of a logarithmic amplifier never goes towards negative values of V_{in} , otherwise the current would flow in the opposite direction, but this is not possible. So the system works if V_{in} is positive (green curve).





Similarly, we could use a BJT transistor (eventually with base and collector shortened). This transistor must be inserted into the circuit in a proper way. We want to apply a voltage and convert it into a current, and the transistor in feedback must go as the feedback acts. For instance, a transistor connected as below cannot work, because we have a pnp transistor where the collector is brought to a negative value. The best thing is to apply something on the transistor that acts on the base-emitter junction, because it's this junction for a npn that is a lovely forward bias, while in a pnp transistor the other way.

 

So the output of the opamp must act on the input of the transistor, that is the base emitter junction.


EXPONENTIAL AMPLIFIER

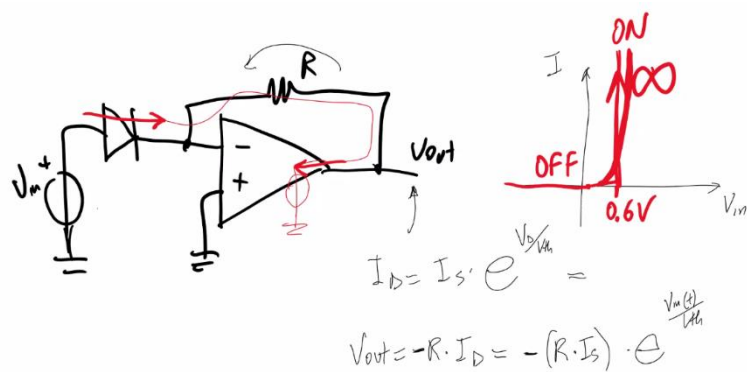 In this configuration, if V_{in} is negative, the current is 0, whereas for positive V_{in} the current is infinite. As soon as the diode turns on, we have the maximum current that can flow through the diode. Still, V_{in} has to have reasonable values, so e.g. 2V is too much, it must be reasonably close to 0.6V otherwise the diode breaks or the opamp isn't capable of providing an output.




The final result is an exponential processing of the input signal. It is not an amplifier with a gain of 1, but something that has a higher and higher gain as V_{in} goes close to 0.6V.

 With this stage we are not compressing the dynamics as in the previous case, we are expanding it.



 
As before, the V_{in} can be connected to the opamp also with another component, e.g. a BJT transistor. Since we want to move the pin, the input should be attached to the terminal of the transistor that is not the collector, but the base or the emitter of the BJT.




If the V_{in} is negative, the diode should be reverted and consequently the configurations of the transistors.

Gloop computation in the Logarithmic converter

When i want to study the Gloop we have to turn off the source, wherever it is and we cut in the loop, applying then an epsilon to the circuit to then see what is the signal that returns back to the input. At the output, in a general resistive case, we have $\epsilon \cdot A_0$ and eventually at the $-$ terminal we have $\epsilon \cdot A_0$ multiplier by the resistive partition. Hence then Gloop is v_f/v_{test} .

 


Now, if we have the diode we have to study a completely different circuit, but with the same procedure. Unfortunately, we have a non-linear component. So in output of the opamp we will have $v_{test} \cdot A_0$, but then we apply a voltage to a series of a resistance and a diode. If we consider small variations, we should substitute the diode with its proper small signal equivalent. We know the i/o curve of a diode, and if we fix a given position on the curve, e.g. at 0.6V, we can compute the slope of the curve, so how the diode behaves around that position, calculating the derivative.

 


dI/dV is defined as the transconductance (g_m) of a diode, that is the inverse of the resistivity of a diode and related to the I-V curve slope. Hence around the position we can consider the diode to act as an impedance whose value is $1/g_m$, that with 2mA and $V_{th} = 25mV$ at RT is $1/g_m = 12.5 \text{ ohm}$. Now that we have substituted the diode with a resistance, we can calculate the Gloop with the resistive divider.

 This is done assuming a signal in input that has a DC value with some high frequency signal superimposed to it. If for instance the DC value is 2V, it means that we have 2mA flowing through the diode in DC, so I know in which position of the i/o diode curve I am. Then on the top of the DC value I superimpose my AC signal.





Inverted Diode

 


If I invert the positioning of the diode, if in input we have 2V, we try to increase the - terminal value, and in principle the feedback should go negative. If there was a resistor in place of the diode, we have a negative feedback, but since we have a diode, the diode cannot work because it's reversed biased, so no current flows and there in also no current in the input resistance. Hence the whole

V_{in} is transferred at the - input of the opamp, and at the + terminal we have GND. So the feedback in this case is off, not broken but off and the output will saturate to the positive power supply. Conversely, if a negative signal is applied in input, the feedback is on again.

  
Recap – Exponential and Logarithmic Converters



 To have an output that is theoretically equal to the input it would be sufficient to put an exponential stage followed by a logarithmic stage.




 But in this configuration above the system won't work because with an input positive signal, the output goes negative, and hence the second diode in that direction won't be on → need to invert it.



We can see that into the first opamp we have two currents, one from its resistance, the other one coming from the other diode. Eventually, if the two resistances are the same, $V_{out} = V_{in}$.

VOLTAGE MULTIPLIER

 

And what happens with MOSFETs?


It's an analog processing to multiply two signals.

We apply the V1 and we compute its logarithmic, and the same for V2. Then the outputs are summed and the intermediate sum is exponentially amplified.


So the V_{out} is the exponential of something and that something is the sum of two logarithms. So we have the multiplication between the two input signals $\exp(\ln(1) + \ln(2)) = 1 \cdot 2$.

SQRT AND POWER2 CONVERTERS

We use MOSFETs instead of BJTs.

 

 The V_{gs} vs I_d relationship is quadratic in the MOSFET. In the BJT I like to keep the base-emitter on, while here I like to have a charge channel between gate and source. So the BJT curve is proportional to $e^{V_{be}}$, while the MOSFET to V_{gs}^2 .



SQRT amplifier:

$$v_{out} = -V_{TH} - \sqrt{\frac{v_{in}}{\frac{1}{2} \cdot \mu_n \cdot C_{ox} \cdot \frac{W}{L} \cdot R_{in}}}$$

$$i_d = \frac{1}{2} \cdot \mu_n \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})^2$$

POWER2 amplifier:


$$v_{out} = -R_f \cdot \frac{1}{2} \cdot \mu_n \cdot C_{ox} \cdot \frac{W}{L} \cdot (v_{in} - V_{TH})^2$$

If I apply a positive input, node x tries to go positive, so the output is negative, but if so, since the gate of the MOSFET is grounded, the source goes negative and $V_{gs} > 0$ and channel forms, so a current flows top bottom. If so, node x tends to decrease \rightarrow negative feedback.

Hence the current V_{in}/R_1 must flow in the MOSFET thanks to the feedback action due to the opamp on the source of the MOSFET, we aren't "pushing" anything from the drain.


Of course, the sqrt operation is not just on V_{in} , but on V_{in} divided by something that is a voltage. Again, the positioning of the MOSFET is crucial, also depending on the sign of the input signal.

Furthermore, if the transistor is in the input branch we have a power2 amplifier. But in this case is V_{in} that wants to drive the transistor, so we cannot put V_{in} attached to the drain of the MOSFET, but to the source. Again, the choice of the MOSFET depends on the sign of V_{in} . If V_{in} is positive, current must flow from left to right, so the first two configurations are fine, vice versa if $V_{in} < 0$.

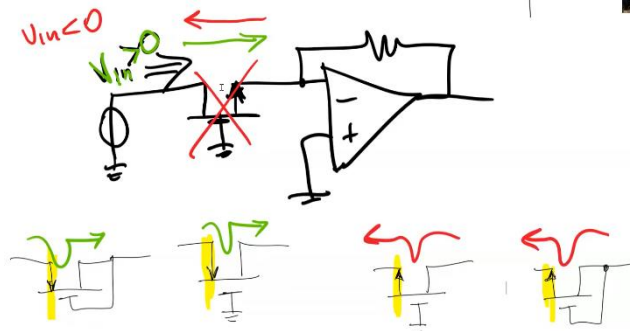


SIGNAL RECTIFICATION

 We have a signal and we have a load where we want to apply only the positive (or negative) part of the signal. This action is called rectification; in the time domain we can introduce the diode, which is a rectifying component. Thanks to its i/o characteristic that is an exponential curve that increases around 0.6V and we have a negative reverse current below 0. At RT the thermal voltage is 25 mV.




 
When V_{in} is positive through the network, trying to impose a clockwise current, this current can pass because it is a forward current, the diode is turned on and it has a 0.6V across it. If the negative voltage is applied, no current will flow.




In the exponential amplifier, we considered V_{in} small enough to have the diode always on and to move around it slightly around the bias point.

Let's simplify the conditions; when the diode is off no current flows, whereas when it is on it has a voltage of 0.6V across it. Only if the signal is sufficiently high it can pass through the diode, otherwise if it is like mV, it won't turn the diode on.

So we need to define a diode that is a shortcircuit when V is positive and that has 0 current in the off condition. To do so, we don't want to use a diode directly, because it requires too much signal to be turned on. So we can use an opamp that will drive the load, to reach a 0 difference in voltage between the input terminals. To have only positive currents in the load, we introduce a diode in the loop (it is driven by the opamp) and in series with the load. It is the **superdiode configuration**.

  


The 0.6V to the diode are provided by the opamp. If V_{in} is negative, the current cannot flow this time, because the diode won't turn on, the opamp won't drink the current in \rightarrow the diode behaves like an open circuit, so the voltage on the load will be 0, and the opamp tries to go as low as he can, but since there is no current, in the $-$ terminal we have 0, so the epsilon in input to the opamp is -2V.

 


We have no more a negative feedback, because the diode is open and so there is no virtual ground and no loop.

Input-output characteristic

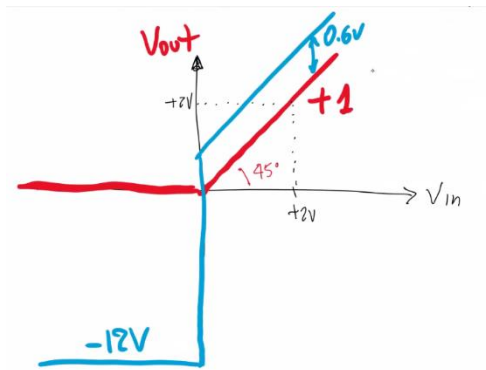


The slope if the diode is on is +1, whereas when V_{in} is negative, V_{out} is 0. Let V^* be the output of the amplifier at node x. It is the blue curve. With negative input, it saturates to the negative biasing voltage of the amplifier.

In time domain, if I have a certain signal, the signal in output will be the positive V_{in} , nothing if the signal is negative for V_{out} . Conversely, V^* will be 0.6V above V_{out} . As soon V_{in} is negative, V^* collapses down to the negative power supply. This is a bad behaviour because I don't see it in output but the amplifier does it. We have to improve this because we don't want to have a saturation behaviour.

 

IMPROVED VERSION OF THE SUPERDIODE

 

Now the OpAmp no longer saturates

The two configurations are the same. In the inverting one we enter on the $-$ terminal branch and the other is at ground, while in the non inverting the $-$ terminal branch is grounded and we enter from the $+$ terminal.

Inverting configuration


When V_{in} goes positive, node x (circuit above) goes positive and if so the opamp has a negative output. If so, D2 is in forward bias and becomes a short. Conversely, D1 has negative voltage on the left and ground on the right, so it is reversed biased, so open circuit.

For every positive input signal D2 is on and D1 is off. But if so, the buffer that we have created acts as a voltage source. In reality, a diode is not a perfect switch, because it requires 0.6V across it, so we should model the diode with a battery of 0.6V battery to be taken into account.

When D2 is on, there is something (the created buffer) that brings something back to the input, so we have a negative feedback. So there is V_g at node x. Hence if we apply a V_{in} , we have V_g and we generate a current on R_{in} that will flow maybe in the R_f resistance. But D1 is open and the series of R_f and R_L has V_g and ground on their sides. So no current could theoretically flow through the two resistors.


Instead, when $V_{in} < 0$, D2 is off and D1 (one side of D1 is at very positive voltage, the other is attached to a resistor, R_L , to ground) is on because the output of the amplifier is very much positive. So we have a current through D1 that goes in R_L and maybe in R_f . If current flows in R_f , the circuit has negative feedback. Hence the V_g concept applies and at $-$ terminal we have V_g . If so, D2 is off, R_f is in between V_g and a positive value \rightarrow we have a current in R_f . Hence the current V_{in}/R_i will flow in R_f . But then this current will also flow in R_L . If so, being V_{in} a negative value, the output is an amplified positive value.

 So for positive V_{in} the overall output of the stage is 0, while for negative V_{in} the output is the opposite version of V_{in} and eventually amplified if $R_f > R_i$ (eventually equal if $R_f = R_i$ or attenuated if $R_f < R_i$).



Non inverting configuration


The same diode positioning is in the non-inverting configuration, but now the input is different. If V_{in} is positive, $+$ is positive. The $-$ is still at 0, because I have applied to $+$ the signal \rightarrow output of the opamp is very much positive. If V_o goes positive, since $-$ is at 0, D2 is reverse bias and open. Most probably, D1 is instead high positive on the left and on the right side positive. If so, v_1 is high and positive and so if we look at the feedback through R_f we have a negative feedback and V_g applies. So we have the $-$ terminal equal to V_{in} .

 

So when the input is positive, the output is positive and it gets amplified by $1 + R_f/R_i$, whereas when V_{in} is negative, V_o is negative, and so D1 is off, it is reverse bias; $-$ terminal was maybe at 0, so D2 is forward bias and it is on, and we have a buffer. So $-$ terminal is now equal to V_{in} because we have the feedback and nobody touches R_L . But the output is not 0, because R_f and R_L are in series and we are

moving the - terminal copying the + terminal input signal because of the feedback. In this case, the output goes to $V_{in} * R_1 / (R_1 + R_f)$.

 
So for positive signals the output gets positive and it is amplified, while for negative signals we have a certain leakage and we get an attenuated version of the input, not 0.



With positive signals at node x, $V^* = V_{out} + 0.6 V$.

With inverting configuration, $V^* = -0.6V$ for positive signals, whereas it is $V_{out} + 0.6V$ for negative signals.


The first circuit has to be preferred because it kills the signal when not useful, but it is inverting \rightarrow we might change the orientations of the diodes in order to have not only the negative parts of the signal amplified but also the positive part and the negative suppressed instead. For example, we can invert D2. If input is positive, on the left side of D2 we have a positive signal, and on the right side a negative one. So D2 is off. If the output of the opamp is negative, nobody is touching the right side of D1 and so D1 is off as well. Hence for positive signals the circuit (left) is with both diodes off \rightarrow there is not a negative feedback, we have a series of R_i , R_f and R_l .

 


For negative signals, D2 is on and also D1 is on. Hence thanks to virtual ground the - terminal is at 0. This is a bad circuit because the output is slightly 0.

SUPER DOUBLE RECTIFIER

NICO

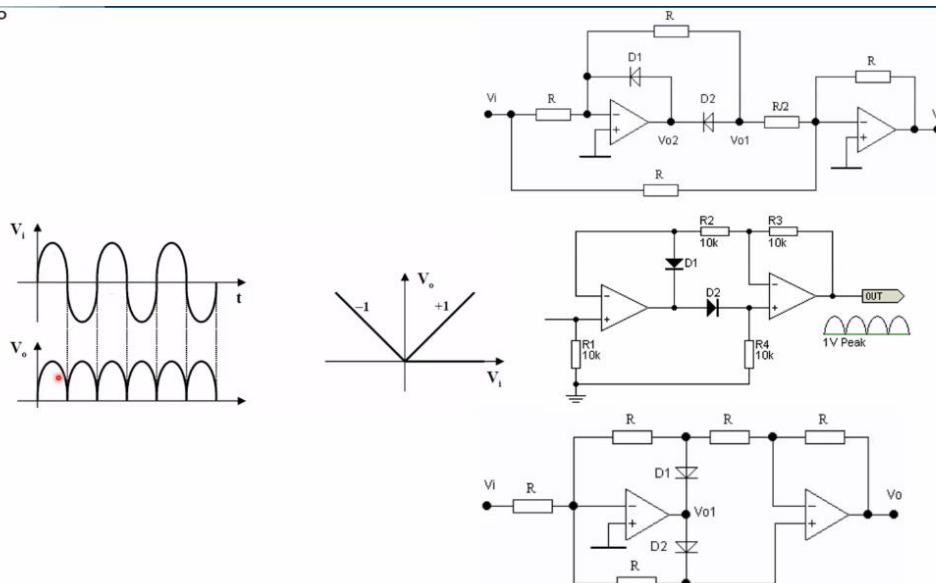

We want both the positive and negative signals to pass through and be inverted. To do so, we take the previous inverting circuit and in the other we invert D1 and D2, then we sum their outputs, we get a double rectifier. With positive V_{in} the upper circuit gets 0 in output and the bottom one V_{in} , the opposite if V_{in} is negative. The gain will be R_f/R_i and hopefully we select the two R_f and R_i of the top and bottom branches to be the same. The problem is that we are using 3 opamps, and a similar solution can be found with just 2 opamps and 2 diodes (configurations in the previous image).

 


The three configurations differ one from the other but the good thing, for instance, of the second configuration, is that the input is high impedance. In the first circuit the input stage is $R/2$ (two R parallel to ground). In the third circuit the input impedance is R .

We introduced these configurations with two diodes to avoid saturation towards negative power supply, and now we have 3 circuits where this saturation is not occurring.


COMPARATOR

It is an opamp with no feedback at all or a positive feedback. If we don't have a feedback, if the $-$ pin (V_{ref}) is for instance higher than the $+$ terminal, the output will be low to the lower power supply of the opamp. There is of course a transition region but if the gain of the amplifier is huge, the transition region is small, it depends on the swing I want (that is the swing of the PS) divided by the gain of the opamp.

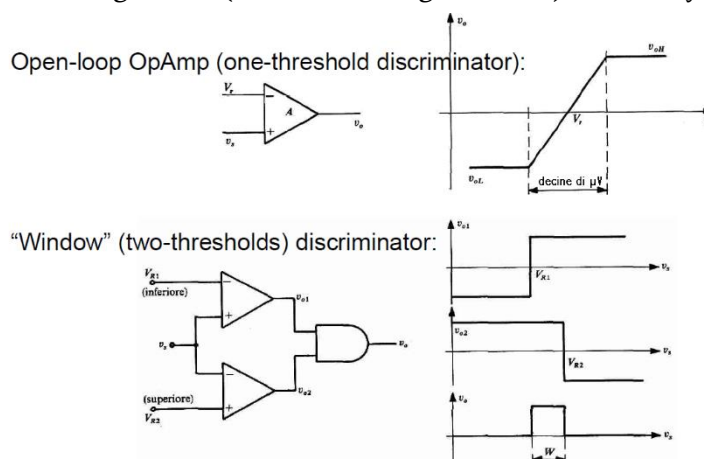


We use a comparator in the case where we have a sensor, e.g. a photoresistor whose value changes with light. The photoresistor value is about 10 kOhm, and we use a comparator to get the output saturated to the positive or negative power supply depending on the reference voltage value on the $-$ terminal. If the threshold is e.g. related to 10 kOhm, I can place a 10 kOhm resistance in series and the crossing point is 2.5V from the voltage partition, obtained with a resistive partition with the 33k resistances.

 If the sensor's resistance increases, the voltage will decrease compared to 2.5V, so the $-$ terminal will win and the output will saturate at 0.



 If we want the LED to turn off when the weather is sunny, so the sensor's resistance increases, we connect the LED as below. Typically, to be on, the LED requires 1.5V across it in forward bias.



To invert the behaviour of the circuit, we simply can change the position of the input terminals of the opamp, or we could change the positioning of the input sensor, swapping it with the resistor. If in output we have a led with a resistor, we can also invert the biasing of the led.


There is a problem, that we could have minor fluctuations on the input signal that cause the output to display some undesired commutations because the threshold is crossed every other time.

In order to solve this problem, we can introduce hysteresis.

SCHMITT TRIGGER


We implement two different thresholds and we use one or the other as we like. Only when the signal goes higher the higher threshold the output commutes. Conversely, it goes down only when the input is smaller than the lower threshold.

 To avoid triggering "undecisions", let's implement **two** switching-thresholds




This can be achieved very easily. A possible implementation is the one below. Let's consider a V_{in} fed to the negative input of the opamp, and the threshold applied to the positive input. On the left we have the classical comparator with a threshold of 2V. On the right we have the circuit with two thresholds.

 As soon as the opamp is triggered, I want to change the threshold \rightarrow I need to introduce a positive feedback connection. In this case, if V_{in} is very small, e.g. 0.3V, the threshold wins and the output saturates to +5V.



 Now the threshold voltage is no longer 2V, but higher and $V_{th-high}$ is given by the following network (right case).




V_{th_high} is as in the formula in the image. When V_{in} is very high, e.g. +4V, the minus wins and the output goes negative and hence to 0 (negative power supply). So, thanks to the feedback due to the resistor R, the threshold of the stage reduces, because now the R resistance is not connected to +3V but to 0V (thanks to the opamp) in output. We get that the equivalent circuit is the following now.



Now we have a brand new threshold, V_{tl} . We can also quantify the **hysteresis** that is $\Delta_H = V_{th} - V_{tl}$.

However, the hysteresis can be computed also in another way. In the network, we have the series of 33k and 22k and in the middle we attach a resistor R that is driven by the opamp, which can be either 0 or 5V. So the opamp swings its output of 5V.

 The corresponding swing that we have in the node where the R is attached is the hysteresis.




$$\Delta_H = V_{TH} - V_{TL} = 5 \cdot \frac{22k \parallel 33k}{(22k \parallel 33k) + R}$$

The higher the R the smaller the difference between the two thresholds and hence also the hysteresis. For R that tends to inf, hysteresis is 0.

Inverting Schmitt trigger

 When the OpAmp output swings, the threshold changes to opposite direction, therefore let's exploit POSITIVE feedback !



Usually let's choose $R_f \gg R_r$
 so ...

Upper threshold: $V_{th} \cong V_r + \frac{V_h}{2}$


Lower threshold: $V_{tl} \cong V_r - \frac{V_h}{2}$

Hysteresis: $V_h \cong (V_{OH} - V_{OL}) \frac{R_r}{R_f}$

Let's compute the thresholds. We have a positive feedback configuration. Since the feedback is positive, the output is either 5V or 0V (limits of the power supply). Now let's compute the value of V_{in} that causes V_{out} to commute, hence the threshold. If the signal enters at the minus, it is an inverting Schmitt trigger. If we cross V_{tl} , the output goes high, while if we cross V_{th} , the output goes low.

To compute the threshold in the case of V_{tl} , let's consider to have the same V_{in} at the negative and positive inputs of the amplifier (it is not an effect of the feedback, but we are making the assumption because we want to find the threshold).

The voltage at red node is $V_{tl} = 5V * (R_2 || R) / (R_2 || R + R_1)$.

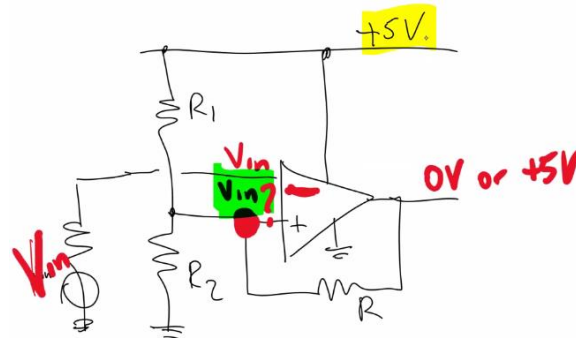

Conversely, when the input is high, the high threshold is:

$$V_{th} = 5V * R_2 / (R_2 + R_1 || R)$$


$$V_{inL} = +5V \cdot \frac{R_2 || R}{(R_1 || R) + R_1}$$

$$V_{inH} = -5V \cdot \frac{R_2}{R_2 + (R_1 || R)}$$

$$\Delta = 5V \cdot \frac{R_1 || R_2}{(R_1 || R_2) + R}$$

Non-inverting Schmitt trigger

 Let's compute the i/o characteristic. When V_{in} increases, the + terminal goes positive, so the output will go positive soon or later. The output can only have two values, 0V or 5V.




The computation of the threshold is not so easy. Voltage at node x is $5V \cdot R_2 / (R_1 + R_2)$. What is the value of V_{in} to have V_y slightly higher than V_x ? If so, the output of the opamp commutes.

In order to compute the input threshold, let's consider when $V_y = V_x$. In this configuration, the output is either 0V or 5V. The current that flows in R_i must also flow in R , because no current enters in the + terminal. This current equation over the resistance R_1 and R is:

$$\frac{V_{in} - V_x}{R_i} = \frac{V_x - V_{out}}{R}$$

With V_{out} equal either to 0V or 5V. For $V_{out} = 0V$ we get V_{tl} , for $V_{out} = 5V$ we get V_{th} .

Example 1

 

$R_1 = 20k\Omega$ $R_4 = 10k\Omega$ $R_2 = 30k\Omega$ $C_1 = 200nF$ $R_3 = 1k\Omega$ $C_2 = 1nF$
 $A_0 = 10^6$ $I_B = 10nA$ $f_0 = 10Hz$

- Plot the ideal gain $V_{OUT}(f)/V_{IN1}(f)$
- Plot the ideal gain $V_{OUT}(f)/V_{IN2}(f)$

Request a)

We have to consider the frequency domain. V_{in2} is grounded. To compute the gain, we have an RC towards ground (x) that causes a zero for sure, and then we have an amplifier stage with gain $1 + R_4/R_3$. In DC, all the capacitors are open, so V_{in} is directly attached to the + terminal of the amplifier. Then the amplifier is a buffer because there is no resistor to ground, R_3 is not to ground. So the DC gain is +1.

The RC net at node x causes a zero that is given by:

$$Z_{p0_1} = \frac{1}{2\pi \cdot 30k \cdot 200n} = 26Hz$$

$$pole_1 = \frac{1}{2\pi \cdot 200n \cdot (30k + 20k)} = 16Hz$$

Then there is also a pole given by the total resistance that is the R_1 in series with R_2 .


Also the other capacitor has a pole, where the total resistance is given just by R_3 , because the impedance of nodes y is 0.

$$pole_2 = \frac{1}{2\pi \cdot 1n \cdot 1k} = 160kHz$$

But does C2 introduces a zero? If the capacitor is open, the gain is 1, whereas if it is shortened, the gain of the amplifier stage is something. Hence it has for sure a zero to switch from a small gain to the higher gain.


To compute the gain we use the GBWP. Zero = pole/gain_high.

 From an empirical point of view, the zero of this stage can be computed as the C2 multiplied by the series of resistances looked from the output, because if I look from the capacitor they are not in series, but if I look at the feedback from the output, they are.



The HF gain is $R_2 / (R_2 + R_1) \cdot (1 + R_2 / R_1)$.

Bode plot:

 


So in the circuit at middle frequencies we have attenuation. It is true because if we look at the circuit, in DC both the capacitors are open, but then at middle frequencies the attenuation is caused by C1 that have an RC circuit that enters into action before the other capacitor → attenuation of C1 is before amplification due to C2. This sizing of the circuit is not ideal, because we have attenuation in between, but we want to achieve amplification. If it was in the opposite case, with C2 acting before C1, I would have had a gain of 11 in the middle frequencies, and 6,6 gain at HF.

Request b)

Now Vin1 is in shortcircuit. We are in an inverting configuration, I don't touch the portion of the circuit that has the RC branch.


In DC, $G = 0$, whereas at HF, $G = -R_4/R_3$. We have a zero at 0Hz and a pole at $p = 1 / (2\pi \cdot R_3 \cdot C_2) = 160 \text{ kHz}$.

Bode diagram:

 

Example 2

AILANO 1863

 


Calvin measures his bike's speed S , by employing Hobbes' speedometer ($v_s = S \cdot 50 \text{mV/m/s} + 200 \text{mV}$) and 10V FSR voltmeters

- Design a circuit for displaying the speed, up to 40km/h, with 3s smoothing
- Display acceleration/deceleration, up to 2 g ($g=9.81\text{m/s}^2$)
- Measure and display the ride distance, up to 1km


Request a)

 So the dynamo gives a constant voltage and I want to see it on my voltmeter and see the speed. The white box is the circuit I have to design. 200 mV is a constant offset that I have.



So I need an amplifier with a 18 gain. I choose an inverting amplifier, i could use a 17 kOhm and 1 kOhm resistances. But if the input is 0, the output is not 0 due to the DC offset of 200 mV. How can I subtract it?

 Let's go to speed = 0, I will have 200 mV in input that corresponds to 3.6V output in DC.




With 200 mV in input I want the output of the amplification stage to be 0V. To remove the 3.6V due to the 200 mV, I could take node x and put it to a specific voltage, not grounded, so that its value per 17 is equal to 3.6V \rightarrow 212 mV.

$$N(40 \text{ km/h}) = 50 \frac{\text{mV}}{\text{m/s}} \cdot \frac{40 \cdot 1000}{3600} + 200 \text{ mV} = 0.555 \text{ V}$$

$$G = \frac{10 \text{ V}}{0.555 \text{ V}} = 18$$

But using a battery to remove the DC value is not useful → I create this voltage from the power supply with a voltage partition. Thanks to this, V_{out} is 0 when there is no speed.

 Another possibility is that we have the amplifying stage with two resistors of 17 and 1 kOhm because we want a gain of 18, but if we have the 200 mV, to remove the 3.6V in output, I could take the PS and use it to inject current at the - terminal.



The current flows in the R resistance, so I choose this resistance to have a voltage drop across it of 3.6V. In the case of the image:


$$V_{out} = -3.6V = +12V \cdot \left(\frac{-17k}{R} \right)$$

$$R = 12V \cdot \frac{17k}{3.6} = 56.666 \Omega$$

In this way the output is zero for a 200 mV offset input signal.

Request b)

 The dynamo produces a velocity, and we know that the acceleration is the derivative of the speed. So to perform the derivation we use the derivator circuit. So if I consider V_{in} and I derivate it, I get the information related to the acceleration.




Let's now size the components. If $a = 2g = 2 \cdot 9.81$, I want $V_{out} = 10V$.

Now we substitute back the values $10V = -RC \cdot 50mV \cdot 2 \cdot 9.81m/s \rightarrow RC = 10.2 s$

Hence the circuit correctly converts the dynamo in a voltage if we choose $RC = 10s$ (we select the value of R and C as we want).

 Let's now draw the full schematic of the first and second stages of requests a and b. The signal from the dynamo is proportional to the velocity; in the first stage we used a non inverting configuration, and the DC offset is killed by injecting a current in virtual ground from the power supply.




Negative power supply can be ground, while the positive one has to be 12V because we want to reach 10V in output.

As for the second stage, it has to be a derivator, in particular a real derivator. Indeed, V_{out} is a function or $-RC \cdot dV_{in}(t)/dt$. When we reach the maximal acceleration of 2g, the output should be equal to 10V FSR. Since we have a minus, this means that when the input is positive, the output is negative \rightarrow we can simply connect the voltmeter driving the negative input, while the positive one is to ground. For the previous stage it was the opposite.


However, this circuit is capable of measuring only positive accelerations, not also negative, because when we have no acceleration the output is 0, and then if we have a deceleration we cannot go below 0. So we need a double rectifier.

 The double rectifier circuit is the one at the end of the bottom branch. Negative signals and negative ones are amplified by 1 and the output is the inverted version of V^* .



Given V^* , the output is $-|V^*|$. Since when the acceleration is negative and V^* is negative, the output is positive, while in the opposite case it is negative \rightarrow no need of inversion in the voltmeter.

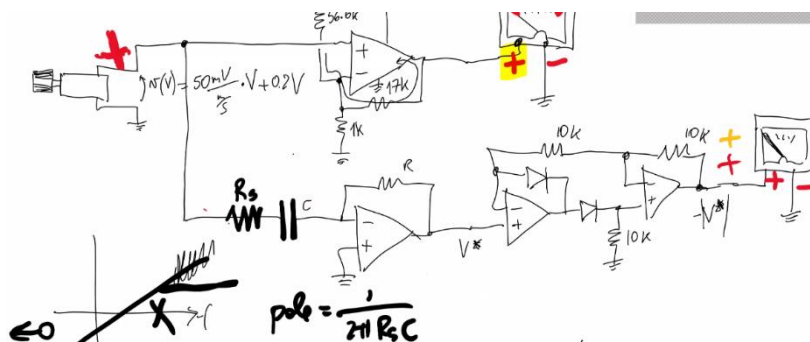The real derivator is needed because if we have noise at HF, the output is incredibly high (saturated), so we need a resistor to prevent this problem and have a finite gain at HF.




We can choose the pole depending on the position when I don't want anymore the derivative action to be done, e.g. every time I simply press the pedal I don't want the derivative, whereas I want it when I'm accelerating over some seconds \rightarrow I can operate for example up to 1Hz, so I set the pole at 1Hz. If $C = 100 \mu F$, $R_s = 16 \text{ k}\Omega$.

We need a double rectifier to rectify the signal because the input signal is either positive or negative, so instead of two diodes we can use two LEDs in place of the diode, in this way the two activate alternatively when we have acceleration or deceleration. The LED activates very bright or not?

If the signal increases at the input, V^* is negative, so the green diode turns on because the output goes negative. The current flowing through the diode is $V^*/10\text{ k}\Omega$ because in the upper branch we don't have current \rightarrow if I want the LED to be much brighter I need to reduce the resistor to provide more current.

 
As for the LED in blue, I have to reduce the resistors in the upper branch, because they regulate the current.



The opamp must be biased between -12 and 12 V (the one of the derivator), whereas the one of the rectifier one (the first) between +- 12V and the other between +12V. Since it is all a mess, it is better to bias them all between +- 12 V.

Request c)

 The distance is the integral of velocity, so I need an integrator stage.



If I have a constant input in the integrator, the output is increasing with a ramp, it is proportional to minus time (because it is inverting). Moreover, the output is negative, so we need to plug it into the - input of the voltmeter.

So we need to get rid of the DC signal. Moreover, I want to get 10V when I've done 1km.


$$10V = V_{out}|_{max} = -\frac{1}{RC} \cdot 50 \frac{mV}{s} \cdot 10 \frac{km}{h} \cdot 1000 =$$

$$RC = \frac{50 \frac{mV}{s} \cdot 10 \cdot 10^3}{10} = \frac{500}{10} = 50s$$

Let's choose a very big capacitor, e.g. 40 uF and a 100 kOhm resistance. But if we do so, the problem is that after 1km the voltage displayed is not 10V but a little bit small \rightarrow so we sell the device at lower price, while if I want precision I size the components correctly.

Now I want to avoid that if the input is constant, the output is not a ramp, but a constant 0. So I need to remove the current generated by the constant V_{in} , so I add a resistor. - terminal is at 0V, so the resistor should be biased with a negative voltage. Also the opamp should be biased with negative values and the positive ones with ground.

 
To choose the value of R, we know that the input resistor has 200mV applied to it, whereas the R experiences 12V.



$R = 6.4 \text{ MOhm}$. If I choose the most close value to the value I need, there still could be mismatches due to tolerances \rightarrow there will be a current moving in the feedback and if there is a DC mismatch, the output will ramp up or it will ramp down. So the voltmeter in output still will be increasing.


So the integrator, to decrease the bad gain in DC, adds a pole to limit the DC gain \rightarrow we add a parallel resistance in feedback, R_p . Thanks to R_p the integrator has now a pole that saturates the gain. Thus, even if we have a DC signal we don't have amplification. So the resistor R steals away the DC component, whereas the feedback resistance decreases the gain. We need both the two configurations to limit the DC effect.

So for the last branch of the circuit we have the following Bode Plot.

 

Example 3

POLITECNICO MILANO 1863

 

MOSFET: $V_T = 0.5V$ $k = 1/2 \cdot \mu \cdot C_{ox} \cdot W/L = 12 \text{ mA/V}^2$

$V_{IN}(t)$ has 5V DC plus a $\pm 100\text{mV}$ sinusoid

a) Compute I_{LED}/V_{in} relationship at DC and I_{LED} for $V_{in} = 5V$


b) Plot the Bode diagram of $i_{LED}(f)/V_{in}(f)$

Resolution

If I apply positive V_{in} , the output goes positive. Then we have a nMOS so if we increase the gate we will create a channel and a current will flow and pump increasing V_s going to ground towards the 1k resistance and the 47k and 1k series and voltage at $-$ terminal increases.

So the feedback is negative. If G_{loop} is very high, then the virtual ground concept applies, so the V_{in} applied on the $+$ terminal will be also applied to the $-$ terminal.

At DC, we find V_{in} also on the $-$ terminal, and the C is open, so we find $V_s = V_{in}$. If we have this, we must have a current on the 1k resistor (5mA), that must be provided by the transistor and hence must be drawn from the drain. Since a current flows through the LED, the LED turns on, not because I'm applying a voltage of 12V but because I'm applying a current through the transistor that is driven by the opamp.

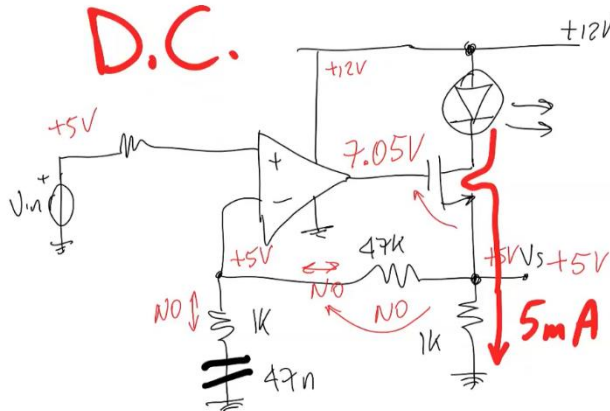

$$I_D = k \cdot 0.5^2 = 12 \frac{\text{mA}}{\text{V}^2} \cdot (V_{gs} - V_t)^2 = 5 \text{mA}$$

$$V_{gs} = V_t + \sqrt{\frac{5 \text{mA}}{12 \text{mA}}} = 1.15 \text{V}$$

Of course, the opamp will be biased so that it can be provided a proper V^* . to compute V^* , we know the current through the drain that is $k \cdot V_{ov}^2$, and I want it to be 5mA. So we can compute V_{gs} .

In the end $V_{gs} = 1.15 \text{V}$ and $V^* = 5 + 1.15 = 6.15 \text{V}$.

This value of V^* is possible because the opamp is biased at 12V so it is able to provide this value of voltage.

Now we can compute the gains at DC and AC. In DC I find V_{in} at node V_s , because the $+$ terminal V_{in} is copied on the $-$ terminal and the capacitor is an open, so no current flows. The gain we get is a transconductance gain, because we have a voltage to current converter. The input is a voltage and the output is a current.

In AC, the capacitor is shorted, so we have V_{in} across the 1k resistance on the left, which generates a current. So we can say that $V_s = (V_{in}/1k) \cdot (1k + 47k)$. Hence we also know the voltage on the right 1k resistance and we can compute the current through it.

$$\text{@DC} \quad G = \frac{i_{LED}}{V_{in}} = \frac{V_{in}/1k}{V_{in}} = \frac{1}{1k} = 1 \text{mA/V}$$


$$\text{@AC} \quad \tilde{i}_{LED} = \frac{\tilde{v}_{in}}{1k} + \frac{v_s}{1k} = \frac{\tilde{v}_{in}}{1k} + \frac{\tilde{v}_{in} \cdot 48}{1k} = \frac{\tilde{v}_{in}}{1k} (1 + 48) = \frac{\tilde{v}_{in} \cdot 49}{1k}$$

$$G = \frac{i_{LED}}{\tilde{v}_{in}} = \frac{49}{1k} = 49 \text{mA/V}$$

Let's now draw the Bode plot. The gain now has a size, we are not computing V_{out}/V_{in} and hence getting an adimensional value. Since the AC gain is higher than the DC gain, we have a zero and a pole.

The R_{eq} of the pole is just the 1k resistance on the left, because in computing the pole the input signal is 0, and if so also the $-$ terminal is at 0V. The pole results at 3.4 kHz

 
As for the zero, since I know that the ratio between AC and DC gain is 49, also the ratio between pole and zero must be 49, hence the zero is at $3.4 \text{ kHz}/49 = 70 \text{ Hz}$.



Let's now see in the time domain what happens.

If the input is 0, the output is 0 ($0 \cdot 1 = 0$), so no current in the LED ($i_{led} = 0$). If now V_{in} goes to 5V, i_{led} will go to 5mA. In the time domain, shifting between these two values we have a transient, but we will discuss about it later.

 
If now we apply a small signal over the DC value, e.g. 1Vpp AC, the gain is 49 V/A, so we should multiply this value for 49.



Hence in output we get 49 mA peak to peak superimposed to the 5mA DC.


Theoretically this reasoning is correct, but practically it's wrong. Firstly, we cannot have negative currents, because it should go in the direction down to up in the MOSFET, and to have so, the drain must be negative and the output of the opamp should hence be negative. However, this cannot happen because the PS of the opamp is 12V – 0V. Hence we have a saturation at the bottom, we have no negative portion of i_{led} . Moreover, the signal cannot reach about 50mA. If the i_{led} was $49\text{mA} + 5\text{mA} = 54\text{mA}$, because the voltage V_s should be 54V. This cannot be feasible again for PS limitations. Hence we have also a upper-side limitation due to the upper part of the PS. The maximum current we can have at the output is when V_g is the maximal possible value, that is 12V.

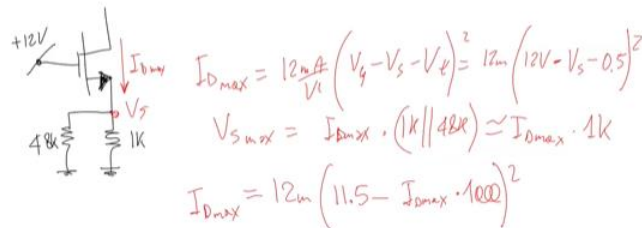To compute the maximal current that can flow, I have to write the equation of the network.



Maybe in the end we find that $I_{d_max} = 25\text{mA}$.

 We can now redraw the time diagram. The limitation is provided by the opamp that cannot provide higher voltages than the PS and by the k of the MOSFET that requires a high V_{gs} to provide a high current.




So this circuit is a voltage to current converter with a low gain at DC and a high gain in HF.

Let's revise the concepts of AC and DC. Let's consider the circuit and an AC signal in input with a DC value of 5V. At DC, no current across the capacitor so it charges to 5V DC, and we have 5mA DC current through the transistor.


Now let's consider AC that is on top of the DC (+100mV), it is not around zero, but around the DC value. The capacitor is now a shortcircuit because it cannot charge or discharge, so it cannot change its voltage. Which voltage? The voltage it has in DC that is 5V. So the capacitor won't change and it will be like 0V in terms of DC (but in reality it will be at 5V), so I see a current that flows through the resistors

(1k and 47k). In output we will see a fluctuation higher than in input (48 times higher than the input). This fluctuation causes a current that can be in one of the two possible directions, up or down in the mosfet. This current is like seeing $48k \parallel 1k$ at the output node. So for the signal the current can be positive or negative (I'm considering fluctuations at the top of the DC value).

The current can be either positive or negative but on the top of the DC value that was of 5mA, so the real actual signal will be always positive, it is 5mA in DC, it reaches 9.8 mA at top and 0.2 mA at the bottom. If I further increase or decrease the input signal, I reach a saturation.

 

Example 4

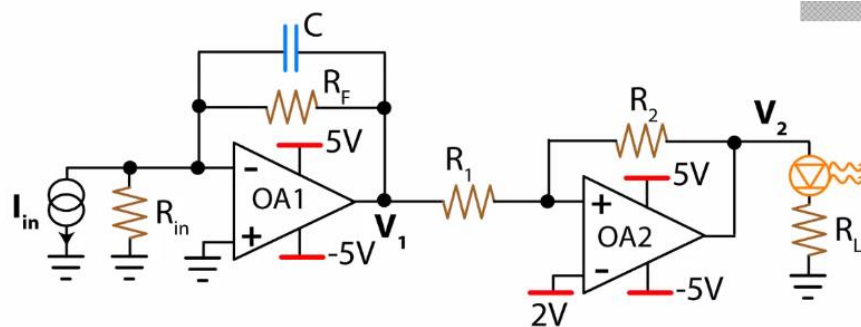

$$R_{in}=100k\Omega \quad R_F=10k\Omega \quad C=10\mu F \quad R_1=2k\Omega \quad R_2=20k\Omega \quad R_L=1k\Omega$$


- Compute the effect of $I_B=100nA$ and $V_{OS}=3mV$ of OA1 on V_1
- Plot the static curve V_1 vs. V_2
- Compute the minimum amplitude I_{in} (20Hz sinusoidal) to switch on the LED

Resolution


I always need to check if the loop is negative. If the OA1 – terminal increases, the output decreases, so the left end of R_f decreases with respect to my increasing perturbation \rightarrow It is a negative feedback and the concept of virtual ground applies. If so, R_{in} is making no effect because no current will flow through it and I_{in} will go all to virtual ground.

Then I have OA2, and we have a positive feedback, so it is a Schmitt trigger. So the two terminals are one fixed, and the other one moving, whereas in the negative feedback they move together. So the output is either + or – 5V.

 The first stage is an integrator, so at DC we have $V_{out} = -i_{in} \cdot R_f$, while at HF $V_{out} = 0$, so the gain is 0. Both in DC and AC the current is not coming from the right branch, but the current comes from the output generator of OA1. Then if I have an output resistor also the generator will provide a current, but it is not the i_{in} current goes as in blue.




So the Bode plot of this stage is:

 

Once we have V1, let's study the second stage. The OA2 is a voltage source, so I don't care about the output because the opamp does what it wants to do plus taking care also of the output.

We have a Schmitt trigger (non-inverting because I enter in the +) biased between +5V, so the output will be one of these two values. Now I want to compute the values of V_{th} and V_{tl} , that cause the comparator to trigger.

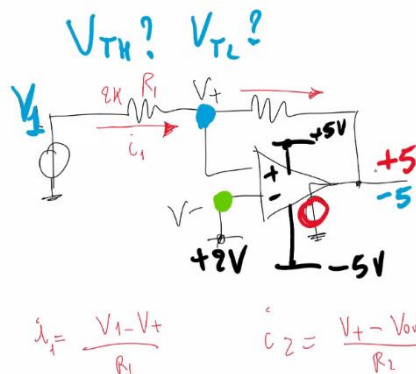I want the condition when V_+ is equal to V_- or when $i_1 = i_2$.



Then I want $V_+ = V_- = +2V$.


$$\begin{cases} i_1 = \frac{V_1 - V_+}{R_1} \equiv i_2 = \frac{V_+ - V_{out}}{R_2} \\ V_+ \approx V_- = +2V \end{cases}$$

$$\frac{V_1 - 2}{2k} = \frac{2 - V_{out}}{20k}$$

We will find two values of V_1 depending on having either + or - 5V in output.


$$V_1 = \frac{(2 - 5V) \cdot 2k}{20k} + 2 = -3 \cdot \frac{2}{20} + 2 = 1.7V$$
 
$$V_1 = \frac{(2 + 5V) \cdot 2k}{20k} + 2 = +7 \cdot \frac{2}{20} + 2 = 2.7V$$



When the output is high, the output LED emits light, otherwise it is off. The one in red is the static curve V_1 vs V_2 .

Request c)

 


Usually the LED requires 1.5V, so the voltage across the resistor in output will be 3.5V, so the current across the LED is 3.5mA (when on) because $R_1 = 1k$.

When will the LED turn on? It will be in the off condition before, so in the off condition we have -5V at node x and if so, the voltage across the diode will be very negative. I know that the threshold to turn the diode on is the high threshold of 2.7V, so we will experience the commutation between -5 to +5V only when the voltage at node y becomes higher than 2.7V. This happens depending on the gain, which is frequency dependent. The pole is at 1.6Hz (C and Rf).


We want the minimum amplitude at 20Hz, with the pole at 1.6Hz. so the gain is given by the GBWP and it is: $G(20Hz) = (10mV/uA, \text{ that is the DC gain}) / (20/1.6) = 0.8 mV/uA$.

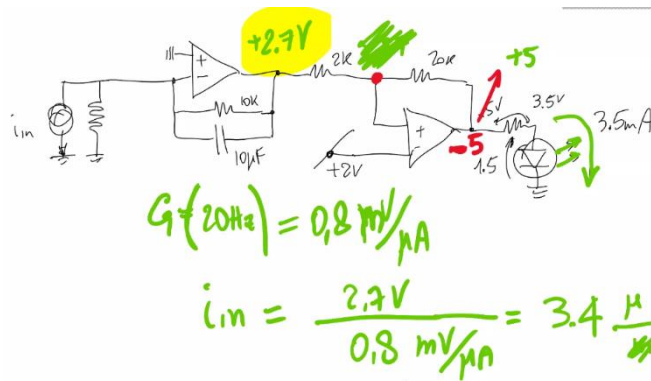So in input I will have $i_{in} = 2.7V / (0.8mV/uA) = 3.4 mA$.



So i_{in} must reach 3.4mA at 20Hz to have the LED on. If the frequency was higher, I would have needed a higher value of i_{in} .

Example 5

 


Rail-to-rail OpAmp biased at $\pm 5V$. At $t=0s$, the capacitor is discharged.

a) Plot all waveforms

b) Write the equation of output frequency vs. R and compute the value for $R=220k\Omega$

There is no input in this circuit. There is a first opamp, then a negative feedback through a capacitor, so maybe the first opamp is an integrator. In fact, if we apply an input at node x, the first opamp behaves as an integrator. Then the second stage is not an amplifier because the feedback is positive, so its is a Schmitt trigger, whose output will be saturated to the lowest or highest power supply. Moreover, it's a rail to rail opamp, meaning that the microelectronics of the opamp is in a way that the lower and higher PS can be reached. Furthermore, since the first stage is an integrator, at - terminal of the opamp we have VG; this integrator is fed with either + or - 5V from the trigger.

Let's redraw the circuit.

 


Let's start with the input +5V, I don't know which is the output of the trigger at the beginning. If we have +5V, since the voltage at the - terminal of the integrator is 0V due to the negative feedback, it means that when we have +5V there will be a constant current provided by the opamp equal to $+5/220k$. This current must flow through the capacitor because the opamp drinks it because of the negative feedback. I can then write the equation into the capacitor $I = C \cdot dV/dt$, and dV/dt will be a constant number, so the V will be a ramp. V_{out} will start from 0 at the power on and then will go down after it with a slope $I/C = 5/(220k \cdot 100n) = 227 \text{ V/s}$.

The output goes negative and eventually it will saturate to the power supply, but no, because the output feeds back the input of the circuit. The first trigger in fact monitors the output voltage because it's a Schmitt trigger, so we need to compute at which voltage the commutation occurs.

The trigger will have 5V in output and the input will go so negative that the + terminal of the trigger, which at the beginning was positive (we started with 0V at the output of the integrator), will reach a value less than 0 and if so the epsilon in input to the trigger will go negative and soon or later I will trigger the commutation of the output to -5V. let's compute the threshold value at which the trigger commutates.

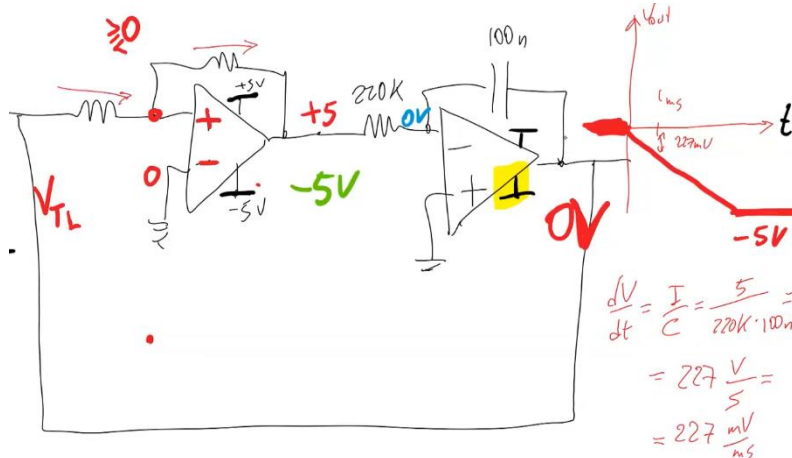The threshold can be easily found by assuming the + terminal equal to 0 and the output is +5V. this happens if V_{tl} causes a current in the feedback resistance that is equal to the current in the input resistance.




We write the balance of currents $(V_{tl}-0)/33k = (0-5)/33k \rightarrow V_{tl} = -5V$.

Hence this circuit causes a ramp at the output and when the ramp reaches -5V the + terminal of the Schmitt trigger reaches 0 and the trigger probably commutes. However, I'm not sure this commutation happens because it is not so likely that the output reaches -5V, so I can slightly modify the circuit, for example by changing the resistors.


In this case $V_{tl} = -3.3V$.

 When the output ramp reaches -3.3V, then the trigger commutes and the output moves suddenly from +5V to -5V. If so, we will have a current in the opposite direction charging the capacitor and so we will have an increasing




ramp. The current is still with the same slope, but with the opposite sign. We will move from -3.3V up to eventually +5V. But before the saturation at the output we have the commutation of the trigger. As soon the + terminal of the trigger goes slightly above zero we commutate the output.

To sum up, when we start we don't know where the capacitor will be after power on. Let's suppose the output of the trigger is positive. If so, then the integrator starts integrating charge, and I will have a decreasing slope on the capacitor. Eventually, when I will reach V_{t1} , we have commutation, and from +5V the trigger saturates to -5V. If so, the current reverts and the capacitor charges. Soon or later we will reach the new threshold V_{th} , that will be equal to +3.3V (because of symmetry).

 

I can conclude that we have a bistable oscillator that keeps running.

 NB: only the first transition is short because the signal moves from 0V to -3.3V, the other ones are larger. We can compute the period of oscillation, and since the two commutations are symmetrical, I can compute the time from $dV/dt = I/C \rightarrow t = dV/(I/C)$.



I can conclude that $T = T_{on} + T_{off} = 58 \text{ ms}$.


Hence this circuit oscillates with a $f = 1/T = 1/58 = 17 \text{ Hz}$.

If we exit at the output node after the trigger we have a square wave oscillator, while if we exit after the integrator we have a triangular wave.

However, sometimes we may want to change the duration of T_{on} with respect to T_{off} and this can be done in different ways. Knowing that the slope depends on I and C , I then depends on R , to change the duty cycle $DC = T_{on}/T_{off}$ we can design a new circuit.

We need for sure an integrator and then a Schmitt trigger. To change the duty cycle I can change the charging current I with two resistors. One for charging and the other for discharging.

 
When the output will be +5V or -5V the current will flow in one path or the other. We have always to remember that we have still a voltage drop on the diode (e.g. 0.7V).



$$\frac{dV}{dt} = \frac{I}{C} = \frac{0 - (-5V + 0,7)}{100k \cdot 100n} = 430 \frac{V}{s} = 430 \frac{mV}{ms}$$


$$\frac{dV}{dt} = \frac{I}{C} = \frac{+5 - 0,7 - 0V}{1k \cdot 100n} = \frac{4,3}{1 \cdot 100} = 43000 \frac{V}{s}$$

 We can see that the transition with +5V has a much steeper slope simply because the resistor associated to that path is much smaller, 1 kOhm. So what happens is the following (thresholds remain the same because they are related to the resistive network of the trigger).



$$DC = 77\mu s / 15ms = 0.5\%$$

 
Another way to change the circuit is by changing also the thresholds. So let's introduce another branch with two different resistors and we use one resistor or the other thanks to diodes. When the output is positive the current will flow in the upper branch, if negative in the lower branch. Thus the two thresholds will differ.



In general term, we may have a circuit that has thresholds in two different points to have a different duty cycle. We can also change $V_{out,high}$ and $V_{out,low}$ by changing the biasing of the trigger.

We could also use two capacitors in parallel (always with diodes). Eventually, we can also have variable resistances that changes according to a potentiometer.

 
In this case, since the sum of the two resistors doesn't change, the oscillation frequency of the circuit is constant



(apart from the first short commutation). But we can change the duty cycle by acting on the potentiometer.

NB: if the input resistance of the trigger was higher than the feedback resistance, the circuit would never oscillate, because to bring the + terminal below 0 it would require a voltage in input smaller than the PS limit (same reasoning for the V_{th}).

In the previous circuit, the capacitors are placed like that because, when the Schmitt trigger commutes, e.g. to +5V, we have a current in the potentiometer. Once the current flow in that direction, it means that it should also flow in the capacitor, and only through the bottom capacitor because the diode stops the current. Vice versa, when the output commutes to -5V, current should follow the blue path in the opposite direction and through the parallel of the two capacitors, and the slope is slower, and so we can change the DC.

 


FREQUENCY COMPENSATION

We want to understand if the negative feedback is strong enough.

INSTABILITY

Let's consider a loop we set to drive a car. We want to drive at a specific velocity, we look at the speedometer, we know the speed we want to reach. The difference between what we want to reach and the actual speed determines our action on the pedal. The pedal drives the engine, the engine drives the traction wheel and the speedometer is connected to the wheel. If there is no delay, we reach the target speed soon. But if there is a delay in our system, we are in an unstable condition.

OPEN LOOP FREQUENCY RESPONSE

 

We have an opamp connected as a buffer. So far we considered the opamp as an amplifier with a very high gain in DC (120 dB), then a pole and then there will be a frequency where the gain of the opamp reduces to 1, the GBWP.

Let's imagine the connect the opamp that we have in OL. The opamp has a gain $A(s)$ that is DC gain and when the frequency increases to much there is a pole inside the opamp that causes the gain to drop. Every time we have a pole, the pole causes a phase shift between the input and the output. At the frequency corresponding to the pole the accumulated phase shift is 45° . 1 decade before the pole there is no phase shift, one decade after it there is a full phase shift of 90° .

So if we look at the OL opamp, we have the phase shift in the upper right plot. A phase shift of -180° is very bad, because if we take the opamp and we want to introduce feedback, we may have a negative feedback in DC, but if we increase the frequency we run the risk that the output has a shift. If the shift is remarkable, to the input of the feedback circuit it returns the signal with a shift, so the epsilon is no longer 0 at the input terminals of the opamp and the feedback could become positive.


NON-INVERTING STAGE

We want to compute the Gloop, so the amplification that a signal epsilon at the input of the opamp experiences before coming back to the input. Given a feedback circuit, we should cut the loop, excite it with a V_{test} and compute the ration of the voltage that returns over V_{test} .

Once we have the circuit as below, in principle we could cut wherever we wish. However, the good position where to cut the loop is just after a voltage source, e.g. after the output of the opamp.


In the case of the non-inverting stage, we have V_{test} , then the partition R_2 and R_1 , so we eventually have the V_+ voltage. Once we have it we multiply by the gain of the amplifier A_0 and we have reached V_{loop} . So we have G_{loop} .

 G_{loop} must be assessed, in order to check **quality** and **stability** of feedback



$$\beta = \frac{V_{feedback}}{V_{test}} = \frac{R_1}{R_1 + R_2}$$

 
$$G_{loop} = -A(s) \cdot \frac{R_1}{R_1 + R_2} = -A \cdot \beta$$



Real closed-loop gain:

$$G_{NI} = \frac{A}{1 - A \cdot \beta} = \begin{cases} 1/\beta & \text{if } 1/\beta \ll A \quad (\text{i.e. if } G_{loop} \gg 1) \quad \text{Ideal gain} \\ A & \text{if } 1/\beta \gg A \quad (\text{i.e. if } G_{loop} \ll 1) \end{cases}$$

 We could have decided to cut in other positions, like below.



This position is ok because we cut in a position where the impedance is infinite on the right, so we can leave it unconnected. Moreover, now I can drive the high impedance on the right with a V_{test} and see what returns. G_{loop} is negative because we pass through the $-$ terminal of the opamp.

The real gain of the non-inverting stage is the ideal gain divided by $1 - G_{loop}$. If $G_{loop} \gg 1$ we are left with G_{loop} and what remains is $1/\beta$. If G_{loop} is very high, the ideal gain is $1/\beta$, which means that $A \gg 1/\beta$. If we have a G_{loop} poor, so much smaller than 1, than the gain is A , so it acts as if it was no feedback.

Gloop ASSESSMENT

In order to assess G_{loop} , to check feedback **quality** and stage **stability**, and to be able to draw the **real closed-loop frequency response** and not just the ideal one, do follow these hints:


1. Draw $A(s)$ i.e. the frequency response of the OpAmp
2. Compute $\beta(s)$ NO Laplace, just asymptotic analysis at 0, medium and ∞ freq.s
then draw $1/\beta(s)$ remember: poles of $\beta(s)$ lift up, zeroes of $\beta(s)$ put down $1/\beta(s)$
3. The split between $A(s)$ and $1/\beta(s)$ is $G_{loop}(s)$; the larger the split, i.e. G_{loop} , the better the feedback **quality** instead, at frequency f^* , where $A(s)$ intercepts $1/\beta(s)$, $G_{loop}(f^*)=1$
3. Draw the expected ideal gain don't care about $A(s)$ nor $1/\beta(s)$
4. The **real closed-loop frequency response** follows the ideal one when "there is G_{loop} ", i.e. $G_{loop}(s) > 1$, instead, beyond f^* there is no more feedback, hence the real gain rolls off from the ideal trend, experiencing all following poles and zeroes of $A(s)$; "the real gain dies as $A(s)$ is dying"
5. Stage **stability** depends on the "closure angle" between $A(s)$ and $1/\beta(s)$ around f^* stable when 20dB/dec before and after f^*
marginally stable when 20dB/dec before and 40dB/dec after f^* or viceversa
unstable when 40dB/dec or higher before and after f^*

In our circuits we usually have two blocks; one is an amplifier $A(s)$, and then a network $\beta(s)$. $A(s)$ is defined by the datasheet, and we design β , that is the attenuation and can also be frequency dependent.

We don't compute G_{loop} as $A(s) \cdot \beta(s)$, because I want to assess if $G_{loop} \gg 1$, so if $A(s) \cdot \beta(s) \gg 1$, and this happens if $A(s) \gg 1/\beta(s)$. So we draw the Bode diagram of $A(s)$, the one of $1/\beta(s)$ and we check this condition. So we don't compute Laplace transforms but we simply plot the two.

When $A(s) = 1/\beta(s)$, there $G_{loop} = 1$. Before it, G_{loop} is good, after it G_{loop} collapses.


Non-inverting stage computations

 

The ideal gain is $1 + R_2/R_1$. Let's now study the loop by cutting at the output and let's drive it with a voltage source and compute $\beta(s)$. We remove $A(s)$ and see what returns at the input of the $A(s)$ block, and then we draw the inverse of $\beta(s)$.

Since we are in a log-log plot, the ratio between $A(s)$ and $1/\beta(s)$, so $A(s) \cdot \beta(s)$, is the distance between the two curves.

 Up until f^* , where $A(s)$ and $1/\beta(s)$ touch, the real gain is equal to the ideal gain, $1 + R_2/R_1$. Just



by chance it is equal to $1/\beta(0)$ in this non-inverting configuration. Then after f^* , G_{loop} dies and the real gain proceeds like the $A(s)$ because the real gain dies by G_{loop} . In the formula we have the + at the denominator, but in reality it's a minus and G_{loop} is negative.

Ideally, there are no poles and so the gain is 10, but actually there are poles and they are inside the opamp, so after f^* G_{loop} dies. Hence after f^* I don't proceed like the ideal gain, but it depends on $A(s)$ also. So since $1/\beta$ is not dying and $A(s)$ is, the maximum death rate is the one of $A(s)$. The frequency at which the gain dies is at f^* , and it's not dying due to the poles, but because the overall G_{loop} dies.

Stability of the circuit

I want to know if the stage is stable or not. In fact, if G_{loop} gets a too high phase shift, then the feedback is no longer negative and becomes positive. This happens if the phase shift accumulated is 180° . Hence I want to check the phase margin that is left before reaching 180° of phase shift.

Every time in the path there is a pole, the pole will introduce the full phase shift of -90° one decade after its frequency.

To do so, it's sufficient to look at the Bode plot of the modulus. If the closing angle between $1/\beta(s)$ and $A(s)$ is $20-20$ dB/dec, it means that before the frequency of f^* one pole acted in the loop, and that pole is the pole of the opamp in this case. But only one pole has happened and introduced 90° of phase shift. So the phase margin is still of 90° , so good.

Of course, then there will be another pole, but its phase shift will be limited ad HF. So we need to compute the phase margin with the formula of the image above.

Conversely, if the crossing is e.g. $20-40$ dB/dec, this is a bad situation because the phase margin is maybe not high enough, the system is marginally stable ($\text{phm} = 45^\circ$).

Finally, if the crossing is $40-40$ dB/dec, the system is not stable anymore, the phase margin could be different from 0° but very close to it, and consequently very close to instability.


STABILITY ASSESSMENT

The reason why "closure angle" matters on **stability** is straightforward:

- Given that the split between $A(s)$ and $1/\beta(s)$ is $G_{loop}(s)$
- The "closure angle" at f^* measures the slope of $G_{loop}(s)$ versus frequency at f^*
- If before f^* the G_{loop} experienced...

1 pole,	-20dB/dec slope
2 poles,	-40dB/dec
n poles,	$n \times -20\text{dB/dec}$
2 poles 1 zero,	-20dB/dec
p poles z zeroes,	$(p-z) \times -20\text{dB/dec}$
- 1 pole before f^* and 1 pole exactly at f^* , -20dB/dec before f^* but -40dB/dec after f^*
- Each pole (zero) adds a phase shift of -90° ($+90^\circ$) to the feedback signal after one decade from it; instead the pole (zero) adds just -45° ($+45^\circ$) if the f^* is coincident with the pole (zero) itself
- Therefore, by measuring the "closure angle" it is possible to infer the difference (p-z) and eventually the overall phase shift accumulated along the feedback path
- The stage is **stable** if the feedback stays negative and does not accumulate -180° phase shift, in which case it turns to be positive and the stage is **unstable**

CLOSED LOOP FREQUENCY RESPONSE

 


If we start from an opamp whose poles are the orange one, the root locus describes where the CL poles will appear. With the opamp open, I see just the orange poles. If instead I introduce feedback, then depending on the strength of G_{loop} , if G_{loop} is more or less 0, the poles of the loop will be equal to the poles of the OL opamp. If instead G_{loop} is different from 0 and gets stronger, the poles of the circuit move apart from the original poles and they move one close to the other (it happens also in the non-inverting configuration, see previous image).

If instead there are two poles and the G_{loop} is so strong that the crossing happens in a bad way, if we look at the root locus it means that we started with an opamp whose pole were separated but G_{loop} is so strong that the pole move across the imaginary axis. If the crossing is bad, 40-40, the system has to c.c. poles. They are so bad that the Bode diagram will see those two poles because it will collapse with -40 dB/dec and we have also peaking due to the instability of the circuit.

In the time domain, having a peaking it means that the output will have some resonance and it will settle after a certain time.



NB: every time we have a circuit that can be described with one pole, if we enter with a step at the input the output won't be an ideal step but an exponential curve. If we take the tau of this exponential, it is indeed the time constant of the pole.

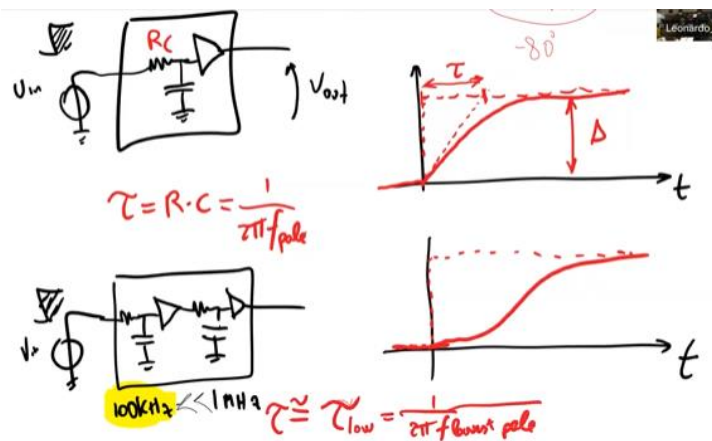If instead the circuit has two poles, if I enter with a step, the response won't be an ideal step but it will start flat and then have two exponentials curve. If one pole is much lower than the other, than the tau that dominates the transient is the one of the lowest pole and we are similar to a one pole response.



BUFFER CONFIGURATION

  ... the **BUFFER** (when G_{loop} is the highest)




$$G_{loop}(s) = -\beta \frac{A_0}{\left(1 + \frac{s}{GBWP}\right) \left(1 + \frac{sA_0}{GBWP}\right)} = +1$$

When $f_{p2} = GBWP$...

$$s_{1,2} = -\frac{GBWP}{2} \pm j \frac{GBWP \sqrt{3}}{2}$$

... Phase Margin = 45°

 


Some amplifiers are sold in order to be operated as a buffer, so the output is connected to the – terminal. The gain is 1. The opamp itself has an $A(s)$, and the beta is 1 (as well as the $1/\beta$). If the second pole of the opamp is before GBWP, the system is unstable because the crossing between $A(s)$ and $1/\beta(s)$ is with 40-40.

To avoid this problem, some manufacturer designed the amplifier with the first pole move backward to lower frequencies so that the second pole happens after the GBWP and the closure angle is 20-20. If there is no second pole it's even better, we are perfectly stable. If the second pole gets closer to GBWP we are still stable, so we reduce the frequency of the dominant pole so that the second pole is just after the GBWP, not far away from it or we reduce too much A_0 .

An opamp that has the second pole after the GBWP is called **compensated opamp**. If the second pole is before the GBWP the opamp is **uncompensated**.

If the manufacturer places the second pole just after the GBWP, the closure angle is no more 20-20, but it's almost 20-40. But if this is the case, it's still reasonable because the phase margin is still 45° , which means that the two poles are c.c. but the angle in the root locus is just 60° , so they are not that much c.c., we have just a small peaking, not perceptible. Bad c.c. that cause peaking have an angle in the root locus higher than 60° .

INVERTING STAGE

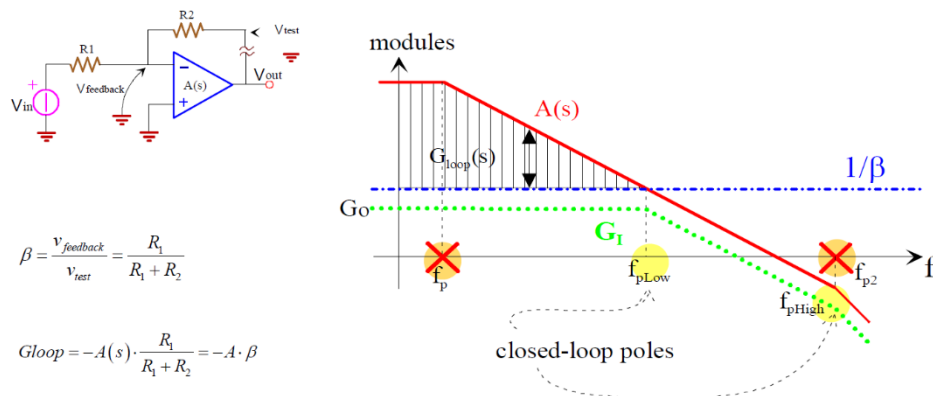

It differs from the non-inverting stage. When we switch off V_{in} , however, the two circuits are the same, so the G_{loop} of the non-inverting and inverting stages is the same. We can see that the opamp is compensated. We cut it after the opamp, we put a voltage source and check V_f to get $1/\beta$.

So we plot the ideal gain that is $-R_2/R_1$, that IS NOT $1/\beta$. Then the real gain is the ideal one up until f^* , when $A(s)$ touches $1/\beta(s)$, and then we will dye as G_{loop} dies. Hence f^* is the pole of the close loop gain.

Uncompensated opamp




Sometimes datasheets quote the first pole, A_0 and the height A_{min} . Then we can compute the second pole because $A_0/A_{min} = f_2/f_1$. They give us the height A_{min} because if we connect a feedback to that opamp, e.g. in the non-inverting configuration, if we have an ideal feedback smaller than A_{min} we are unstable, because we are in the portion of the Bode plot where the crossing will result in 40-40.

So when we use an uncompensated opamp we run the risk that, with the same configuration but with different values of resistances, one configuration is stable, the other not.



There exists a "Minimum Gain" A_{min} and two major poles f_0 and f_1

   Example



Compensated:
OPA 27 SR = 2V/ms
Uncompensated:
OPA 37 SR = 17V/ms




ROLE OF FEEDBACK CAPACITANCE

  

  The $1/\beta(s)$ has a low-pass shape, which increases G_{loop} at high frequencies




2 11:20

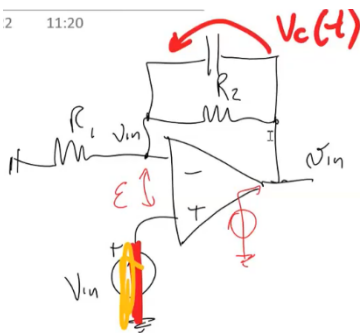

IDEAL

 
$$G_{ideal} = 1 + \frac{R_2}{R_1} = \begin{cases} @DC & G = 1 + \frac{R_2}{R_1} \\ @\infty & G = 1 \end{cases}$$



To compute the pole, we consider the input generator off, so we have 0V on both the - and + terminals of the opamp (epsilon is 0). So no current through R1. So the current recirculates on the C - R2 network → the pole will depend just on $R_{eq} = R_2$.

Then we can compute the zero in a graphical way. It will be at the frequency of the pole multiplied by the distance between the DC and AC gains.

 But we are studying the ideal gain. So we define an $A(s)$ and $\beta(s)$. We excite with a voltage source the $\beta(s)$ in the same position where the opamp touches the feedback network and then we measure the signal that returns at the input of the opamp. We consider two regimes, DC with C open and AC with C shorted.




To study the real behaviour of the circuit. We remove the opamp and the plot $A(s)$, and the second pole is set coincident with the GBWP. So the crossing may be 20-40, the phase margin is 45° and the poles are c.c. with an angle of 60° in the root locus. Hence we will have a negligible overshooting in the time domain.

Then we compute β and we plot $1/\beta$ and we see that the crossing is so that the phase margin is 45° and poles are c.c. with 60° in the root locus. The response is ok, I like it. To compute the ideal gain of the circuit we have to compute the ideal gain, that in this case overlaps with $1/\beta$, but in this case it happens just by chance.

The real gain is equal to the ideal one up to f_{loop} , and then it dies like $A(s)$. Hence the real circuit has two poles, not just one. The pole of the CL gain is coincident with the zero of the β , that was $1/(2\pi RC)$.

 
The circuit is well designed if the pole of the beta network happens before we reach GBWP. If we make the wrong sizing and e.g. the pole of the opamp is at too low frequency, we may have another configuration in which the pole of the circuit is due to f^* and not due to the feedback network.



DERIVATOR STAGE

Ideal derivator

 The gain of the stage in the frequency domain is $-sRC$. Hence we have a zero in the origin in the Laplace domain, and so a derivation in the time domain. This is the ideal gain of the stage. The frequency at which the gain is 1 is $1/(2\pi RC)$.




Let's now study the circuit with the Gloop considerations.

We have an opamp that will be our A(s), and then we remove it and compute the beta(s). Let's suppose the opamp is compensated.

To compute beta(s), we should shortcircuit the voltage generators and open the current generators, cut at the output and excite with a v_test and I want the v_feedback that returns to the opamp. Of course, beta(s) is frequency dependent. At DC, beta is 1 (C open), while in AC beta dies.

Now we plot A(s) and 1/beta(s).

 


f* is the frequency above which the loop is not working in the proper condition because with increasing frequency the opamp amplifies less (A(s) decreases) and beta is attenuating more and more, so A*beta decreases.

The crossing in this derivator is at 40-40, so we have two c.c. poles, the residual phase margin is almost zero and the circuit is unstable → in the Bode diagram we will have a strong peaking.

As for the real gain, firstly we need to plot the ideal gain, that is a straight line with a zero in the origin. To put it in the plot, we know at which frequency the ideal gain crosses the 0 dB axis. This frequency is the pole of the beta network in this case.

 As for the real gain, we follow the ideal one up to f* and then we decrease as Gloop dies, so with -20 dB/dec (because A(s) dies by -20 dB/dec and 1/beta increases +20 dB/dec, and so compared to the previous trend we need to go down by -40). The real gain is the green one, it is a derivator up to f* and then it dies.



Moreover, since the closure angle is bad, the poles are c.c. and the circuit is unstable, so I also display a strong peak in correspondence of the f*.


The part up to f* is good, the one after is bad, because if A(s) changes (e.g. due to time, temperature ecc.), the falling side of the Bode diagram can change. And example of the response we may have is in the plot on the right.

Real derivator

We add a resistor in series with the capacitor. Now we have again a zero in the origin but we have a pole that causes a saturation at HF.


Previous issue possible solution

To improve the crossing of $A(s)$ and $1/\beta(s)$ like 40-40, what we can do is to move far away the pole of the beta network so that the crossing is 20-20, and the f^* will be at GBWP. But the problem is that in this case, still in the case of the ideal derivator, the real gain will go from +20 to -20 as slope. After the pole of the beta then, it will die with -40 dB/dec. Technically we removed the instability condition, but the behaviour is bad, because I expect the derivating action from 0Hz up to the pole of the beta network but it is not like that, because it is up to the GBWP of the opamp.

 


Another possibility is to change the opamp so that the GBWP is aligned with the pole of the beta network. But decreasing the performance of $A(s)$ to gain stability is not a smart move.

 
So in reality what we should do is to keep the same opamp, and in the beta network we add a zero thanks to the resistor in series with the capacitor, because we are causing $1/\beta$ to saturate. The zero is given by $C \cdot R_c$.



 
Now the ideal gain of the stage is different with respect to the case of the ideal derivator, because we have a saturation of the gain at infinite frequency (blue line). In this case the curve of $1/\beta$ and ideal gain differ by 1.



 We introduced the resistor R_c , but if the zero happens at the wrong frequency, the circuit is still unstable, like in the case above, because the crossing is still 40-40. The orange one will be the real bode diagram.




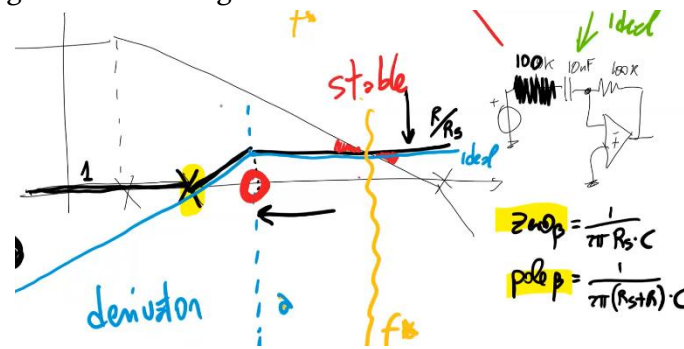Conversely, if the zero of the beta is placed at too low frequencies it happens as below. Now the stage is stable because C is so big that the crossing is 20-20.



If now we increase the resistor value, for instance from 10k to 100k, it happens that the zero moves to lower frequencies and also the saturation value decreases and the one above is our new Bode plot. It is stable and the circuit is now a derivator but up to a certain frequency that is the zero of the beta, and then it behaves as an amplifier up to the f^* . The problem is that this stage is bad because it is not a derivator across the full stage, even if it's stable.

 We need to find a compromise; let's put the resistor such that the zero and f^* have the same frequency.




The real behaviour is a derivator up to where the circuit collapses, so it doesn't show an amplifier region. Now the derivating gain collapses at the highest frequency. Given the value of the GBWP, we set the zero at the following frequency.

$$z_{w0} = \frac{1}{2\pi R_c \cdot C} = \sqrt{\frac{1}{2\pi R_c \cdot C} \cdot GBWP}$$


Moreover, now the stage is also stable because the crossing is 40-20, so we have a marginally stable circuit.

EFFECT OF AN INPUT CAPACITOR

 This capacitor can be the parasitic capacitance of the opamp or something that we have in the circuit. If the circuit was ideal, in C_i there should be no current because VG concept applies and C_i is between VG and ground.



 
It threatens stability because it alters the feedback β



$$\beta = \frac{R_1}{R_1 + R_2} \cdot \frac{1}{1 + \frac{s}{(C_i \cdot (R_1 \parallel R_2))}}$$

Hence the capacitor is like having no role, like if it was not connected there. The ideal gain of the previous circuit is $1+R2/R1$, constant in frequency.

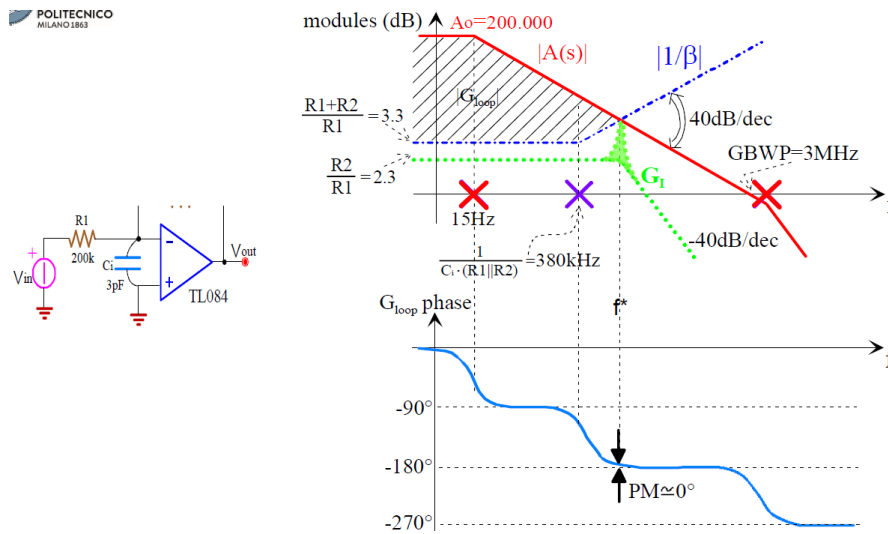
Let's now study the real gain, with $A(s)$ and $1/\beta(s)$ (in the image v_{test} is $v_{feedback}$ and v_{out} should be v_{test}).



We see that the real gain, instead of proceeding flat, dies with -40 dB/dec. Moreover, the circuit is unstable and if the second pole happens 1 decade before f^* , the phase margin is almost 0. So it is not correct to add a capacitor just at the input of the amplifier, because it causes instability.

However, we can bring the circuit back to stability either by removing the capacitor (so that $1/\beta$ is constant for any frequency) or we can perform components' sizing, because maybe the capacitor cannot be removed and it's simply there because of parasitisms. If C_i gets smaller, the pole of the beta moves to higher frequencies and maybe the crossing returns good. Thus we achieve a 20-40 crossing and achieve marginal stability.

 
Re-catch stability: no additional component, but simple value adjustments



If C_i cannot be changed, we can still act on the resistive network. $R1$ and $R2$ are needed to set the gain, but we can change them by scaling them of the same factor so that the gain remains the same, because it depends on their ration, while the pole, that depends on their parallel, moves at higher frequencies. Now we are changing both $R1$ and $R2$.

Another possibility is to change just $R1$ or $R2$ so that the pole stays the same but the gain changes. We increase the gain.

 Re-catch stability: no additional component, but simple value adjustments





The last possibility is to regain stability by adding components.

Compensation of instability by adding components

POLITECNICO MILANO 1963

Compensation is needed !

  


The opamp is ok because it is compensated, it is the beta(s) that is bad.


To guarantee a good crossing, we may want the beta to saturate, so we want a zero in the beta that causes saturation, but it must be positioned correctly to gain stability, so that the crossing with A(s) is 40-20 or 20-20.

A possible way to introduce a zero is by adding a capacitor in parallel to R2 (Cc). In fact, every time we have a C in parallel to a R and the signal has to propagate through there, this portion of the circuit generates a zero with $\tau = R \cdot C$. Instead, we don't have two poles because the two capacitors are in parallel and not independent. Hence we have just one pole with $\tau = (C_i + C_c)(R_1 || R_2)$.

 
In the beta network, we may have different possibilities. In DC, 1/beta is $1 + R_2/R_1$, while at AC impedance depends on the two capacitors, because their impedance is much smaller than the one of the resistors, so it will be $1 + C_i/C_c$. Depending on the values of Ci and Cc we may have a higher, equal or lower value with respect to $1 + R_2/R_1$.



 
In general, in a voltage partition network, if the product between $R_1 \cdot C_1 = R_2 \cdot C_2$, the voltage partition is said to be compensated. This means that if the previous equation holds, then the Bode diagram, is flat.



The compensation is important because if for instance we enter in the circuit with a step and we have no C_i or C_c , the output of the circuit will be for sure a step attenuated (in the time domain). If instead we have just C_i , C_i causes LP filtering action. If we have C_c but not C_i we have a HP filtering action. If we have bot C_c and C_i and the network is not compensated, then either the LP will prevail or the HP will prevail, so we will have a trend with a step and then regime or with an exponential increase. Eventually, if the C_i and C_c are matched, if we enter with a step the output will still be a step because we will have a perfect compensation of the LP transition and of the HP transition.

 

Hence with the C_c capacitor we can regain stability. The zero is not to be placed at too low frequencies, nor at high frequencies, because the best way is to place it where $A(s)$ and $1/\beta(s)$ cross each other. Thus the real gain is the green one; in fact, the ideal gain is the one of a non-inverting stage in DC, then it collapses with a pole that is the zero of the beta network. If C_c was placed so that the zero is before f^* , than in the operation range of my amplify I would introduce a LP filtering action that is not required.

 


The gain dies with -40 dB/dec with a minor peaking because we are marginally stable, and $C_c > C_i$. If we draw the phase plot, we notice that it is the zero that recovers the stability. However, just before the zero we have a portion of the plot where the phase margin is 0, so theoretically we should be unstable in that region where Gloop is higher than 1. However, there is not the problem because it is only where Gloop = 1 that the phase is important, because if we have poor phase margin even before it doesn't matter.

Eventually, if C_c is too big, the zero is at a so low frequency that we see the low pass filtering action, and the output transition to the steady state value becomes so slow that the stage is unusable.


TRANSIMPEDANCE AMPLIFIER

Example: **photodiode amplifier**

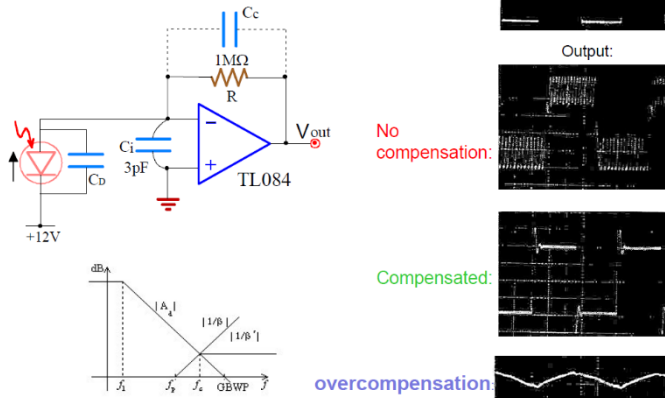


This stage is introduced to demonstrate that the ideal gain is not coincident with $1/\beta$. The photodiode can be modelled with a current generator in parallel with a parasitic capacitance. The I_{ph} in DC passes through the feedback resistor R and $V_{out}/I_{ph} = R$.

 If we study the stability, $A(s)$ is compensated, and the β is 1 at DC, then we have a pole.




Hence a standard transconductance amplifier is always unstable, because the crossing will be bad, 40-40. Since we have peaking, we have two c.c. poles. Hence for sure we need to introduce a C_c capacitor. If C_c is too small, we don't grant enough compensation. If it is too big, we are overcompensating.

EFFECT OF AN OUTPUT CAPACITOR

 

 It threatens stability because it alters the forward gain $A(s)$



... due to the additional output pole: $f_{out} = \frac{1}{C_L \cdot R_0} = 530 \text{ kHz}$


The output capacitance, as well as it was for the input one, could be added on purpose or it can be a stray effect.

The amplifier can be either in a non-inverting or inverting configuration and for instance if we drive the load with a long coaxial cable we introduce a stray capacitance.


Of course, if the opamp was ideal with a zero value of R_{on} (output resistance), then the C_l won't have any effect; however, if we use an OA with a given value of R_{on} , it is not negligible.

So we start with a compensated opamp but then, due to R_{on} and the C_l we add a pole. The new $A(s)$ can be considered not just the $A(s)$ of the opamp but the combination of the opamp and R_o - C_l network.

 The idea is to consider the following circuit with an OA with $A(s)$, then we add a pole due to R_{out} (R_o) and C_l and then we have the feedback network due to R_1 and R_2 . We consider a new $A(s)$ and the remaining part is the beta network.




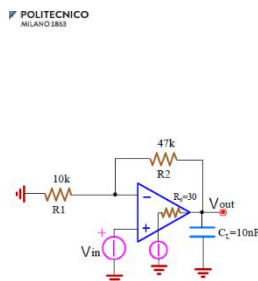Let's plot $A(s)$ -tilde. It will be due to the typical response of the compensated opamp but then, due to R_o and C_l we have a pole that is at the frequency with $\tau = R_o \cdot C_l$ and so we decrease with -40 dB/dec after this pole. Now the $A(s)$ -tilde is similar to the frequency response of an uncompensated opamp with the second pole before the GBWP.



$$f_{out} = \frac{1}{C_L \cdot R_o} = 530 \text{ kHz}$$

 
$$f_{pole} = \sqrt{f_{out} \cdot \beta \cdot GBWP}$$




Now we should study beta, but it is simply a resistive network, so it will be constant in frequency. We see that we are unstable because the closure angle is $40-40 \rightarrow$ there will be peaking. In this case the ideal gain is equal to $1/\beta$, just by chance.

As for the real gain, it is equal to the ideal one up to when $A(s)$ -tilde and $1/\beta$ touch, then it dies by -40 dB/dec.

 If we study another circuit, the inverting configuration, in this configuration we cannot model the circuit with the typical block diagram of automation and control. This modelling applies only if we study the non-inverting configuration.



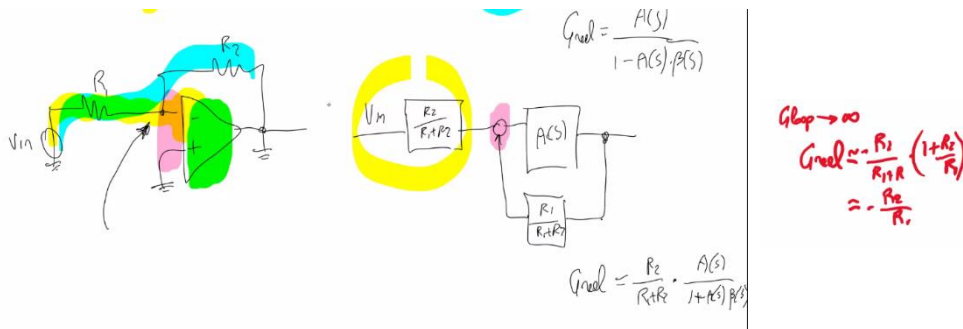If we use the inverting configuration, V_{in} gets attenuated by R_1 and R_2 , so the signal that reaches the loop is not V_{in} but its attenuated version. Then we have the subtracting node and then we enter in the opamp with $A(s)$, then we have the attenuating network β and then the signal gets subtracted from the previous one. Hence G_{real} is different.




In this case, when G_{loop} is very very high, in the noninverting configuration, if $G_{loop} \rightarrow \infty$, the G_{real} tends to $1/\beta$. In the inverting one, it tends to $-R_2/R_1$.

So the classical automation control blocks diagram happens only for the non-inverting configuration, in all the other cases and circuit we cannot do this. So we have to compute the ideal gain and then study G_{loop} , that is instead the classical automation and control diagram with $A(s)$ and $1/\beta(s)$. Ideal gain is $1/\beta(s)$ only for the non-inverting configuration.

Compensation

Let's try to compensate. An easy idea that we could use is (I know that it is unstable because we have a resistance R_{out} and a capacitor C_1 , so the overall $A(s)$ -tilde (the red circle) goes as in the red plot, so since the $1/\beta$ crosses at -40db , the system is unstable). To compensate, we could add a C_c capacitor in parallel to R_2 . But this C_c causes β to be equal to 1 at HF, hence C_c is not recovering stability.

 

Anyhow, the crossing will still be bad, so C_c cannot guarantee stability. C_c tries to modify the $1/\beta(s)$, but it decreases so much that the crossing is so bad, because the R_o and C_1 create the pole. So to compensate we can do something different.

The best idea is to feed the node between the voltage output generator and R_o and feed it back at HF (e.g. with a capacitor) to the input. But this cannot be done because the node is inside the amplifier, so we cannot have access to it.

Hence what we do is that we put a resistor (R_c) in series with R_o , eventually even worsening the effect of R_o because the pole decreases in frequency, and then I use a capacitor to feed back to the input.

So nothing changes in DC but in HF C_I goes in short, so $A(s)$ -tilde should die, but since we have R_c in series with R_o , we can have access to node x and we can take it and feed it back to the input through C_c to regain stability.



First **compensation** approach:



Sizing (empirical? Not at all!):

$$R_c \cong R_o$$

$$C_c = C_L \cdot \frac{2R_o}{R_2} = 13 \text{ pF}$$

Disadvantage:

R_o leads to voltage drop !

 
 


The advantage of this solution is that at AC we will have just $A(s)$, not $A(s)$ -tilde, the $1/\beta$ is 1 at HF and now we grant stability.

COMPENSATION WITH NEGATIVE FEEDBACK

This approach is suitable for the compensation of any pole of $A(s)$

It improves the Slew-Rate too

  


$$\beta = \frac{R_1}{R_1 + R_2} \cdot \frac{1 + sR_c \cdot C_c}{1 + s(R_c + R_1 \parallel R_2)}$$

We introduce a further negative feedback. Let's imagine that the stage in the image is unstable. Let's imagine to have an uncompensated opamp (so $A(s)$ of the opamp has two poles). If we introduce the couple R_c - C_c we can regain stability.


Let's imagine $A(s)$ is uncompensated and let's study beta. At DC the capacitor is open and beta is $R_1/(R_1+R_2)$, the usual one. Then in AC we have the capacitor shorted.

 To compensate this stage, and $A_{min} = 100$, for example, and I want an amplification of 2.3, the crossing will be bad and the stage unstable because $\text{Gain} < A_{min}$. To regain stability, we could increase the gain to have a good crossing. But I don't want to change the gain, so maybe I could use a




compensated OA. If I don't want to change neither the gain nor the OA, we can change the position where the crossing occurs.

So at DC we use the gain we want, e.g. 5.3, but then we introduce a pole and a zero in the beta network to shift the gain up and compensate everything. To do so, having a beta high at low freq and low at high freq (in the plot I have $1/\beta$), I cannot use a capacitor in feedback, because it causes $1/\beta$ to be ok at LF, but then it goes to 1 at HF, so it's even worse. So C_c is not the solution because it cause the stability to be even worse.

 

 If we want beta to decrease, we could place something in the input branch, because we want beta to decrease at HF is we want a high $1/\beta$. Hence we place a R-C series.




This solution could work, but the problem is that we are changing the gain of the circuit. The new ideal gain is no more flat, but it has a pole and a zero, and we want it to be constant.


The new ideal gain is not flat, but it is flat, rises and goes flat again, and this is not good for the customer, because the customer what a constant gain. So if I want the ideal gain to be constant, I can include the compensating network connecting it between the terminals of the OA. If so, thanks to VG the two don't play any role in the ideal gain, and it remains constant in frequency.

If epsilon is 0, they don't play any role in the ideal gain. As for the Gloop, I have the OA, it's $A(s)$ and to study beta I shortcircuit V_{in} so the two branches in input are in parallel. Thanks to this smart connection I've compensated the stage.

 So ideal gain is something, the $1/\beta(s)$ is something different and also the actual Gloop is different. So ideal gain is never equal to $1/\beta$ except for the ideal non-inverting configuration.




 If we remove C_c , thanks to the feedback, ideally in R_c no current flows if G_{loop} is strong enough, so R_c doesn't impact in the computation of the ideal gain. However, if the ideal gain is not changed, the beta is changed. $A(s)$ is still the same, but now beta is always high and constant \rightarrow we are losing the low $1/\beta$ at low frequency, so now G_{loop} is lower than before.



However the circuit is still stable and the ideal gain (green) is the same as before, and the real gain as before.


Having a smaller G_{loop} means that the feedback is less strong. Having a high feedback is a good thing because if we have for instance a real OA with its R_o and we want to compute the R_{out} , the $R_{out}(0)$ is equal to the $R_{stupid}/(1 - G_{loop})$, where the R_{stupid} is the impedance I see from the output (A_0 is $A(s)$ at 0 freq from the input to the upper node of the output generator, so R_o must be considered).

 

If the G_{loop} is sufficiently high, the R_{stupid} is reduced a lot. If we remove C_c permanently, now also at DC the equation changes, because we won't have $R_1 * A_0$ but $(R_1 || R_c) * A_0$, so G_{loop} is lower and R_{out} is higher than before, because the action of G_{loop} is not that much strong.


What about the input impedance if we place C_c and R_c (or just R_c)? Is it no more infinite?

 No, it is still infinite because epsilon across the $R_c C_c$ series is zero, since we have V_{in} both at the + and - terminals. The impedance we see is the stupid one but magnified by $1 - G_{loop}$.



So if R_c is infinite, the input impedance is infinite, but if it is not infinite, thanks to the feedback it gets really big.

 Let's redraw the schematic with Rc outside the OA and modify the circuit a little bit.



I have a circuit, a loop, a node and so the input impedance is the stupid one divided by $1 - \text{Gloop}$. But if I divide by $1 - \text{Gloop}$, it means that the result is less than before, because Rin was Rstupid was magnified by Gloop. However, the two equations are correct anyway! The two equations in fact refer to two different Gloop.

The two equations are correct but the Gloop is not the same for the two, they differ from each other. In the previous equation when the impedance Rc gets magnified by Gloop, Gloop is given by the feedback of the OA (negative feedback).

In this other case the loop is given by another net, the new $\text{Gloop} = \text{Gloop}^*$ (blue). Let's compute Gloop^* . The gain of the part inside the black circle is not $1 + R2/R1$, because our 'output' is not at x, but it is at the - terminal of the opamp. Ideally, epsilon is 0, so the gain is +1.

So we can compute Rin.

$$R_{in} = \frac{R_{stupid}}{1 - \text{Gloop}^*} = \frac{R_c + (R_1/R_2)}{1 - A^* \cdot 1}$$



Hence we have a division by 0, and Rin becomes infinite. And this is the exact same result than before, when the resistance is amplified by Gloop and so still becomes infinite.

In reality, the gain A^* is not exactly 1, but it is 0.99, because the loop is not ideal, so we are dividing by 0.01, so we get a very high value but not infinite.

COMPENSATION WITH POSITIVE FEEDBACK


MILANO 1863

  For buffers, previous approaches cannot be applied... therefore




$$R_c = \frac{R_2}{A_{min} - 1}$$
 
$$C_c = \frac{1}{2\pi \cdot f_c \cdot R_c}$$




 We have an opamp and let's suppose we want to use it as a buffer. The problem is that the opamp I bought is uncompensated, so we are out of stability.




Hence we may want to add a compensation network. If I add a compensation capacitance in feedback it is not good, I'm changing the circuit. So can I eventually introduce the Rc-Cc couple? No, because at 0Hz beta is 1 and at HF it is still one, so not compensated. Hence we need to introduce also an additional resistance. Now it works.

 Now in DC beta is 1 (capacitor open), instead, at HF, the capacitor is short circuit and the beta network is the one two images ago. The $v_{feedback}$ I'm interested in is the one between the input terminals of the opamp. $\beta(\infty)$ is the beta at the minus node (-) plus the beta at the plus node (we can also compute simply the voltage divider and we achieve the same result).




In this case the beta is the sum of the contributions because the + terminal of the opamp is not connected to ground like in all the other previous cases.

 Since now beta is < 1 at HF, $1/\beta$ will be high, so eventually we can cross the uncompensated opamp in the 20-20 or 20-40 crossing. We prefer the first case because f^* is higher, and the higher f^* is, the better is the bandwidth.



 
If we have a situation like below, we are still out of stability because we are still maintaining a 40-40 closure angle.



The circuit is stable if the zero of the beta network is at least 1 decade before the second pole of the uncompensated opamp, so that the phase margin is 45°.

C_c can be removed, but it is better to keep it to have a very large Gloop in DC, because if we remove it $1/\beta$ will be constant and equal to the HF value in the case we have the C_c .

Example 1

 


$R_1=10k\Omega$, $R_2=100k\Omega$, $R_3=220k\Omega$, $R_4=1k\Omega$, $R_5=10k\Omega$, $R_6=47k\Omega$, $C_1=1\mu F$, $C_2=100pF$.

- Plot the ideal $|v_{out}(f)/v_{in}(f)|$ gain.
- Compute i_{out} when $V_{in}=-100mV$.

Let's check if we have a negative or positive feedback. We enter at the minus node, the signal propagates at the output and then it returns back to the input and it is negative, so the minus terminal will be VG. We can compute the input current. If in feedback we would have had just a resistor R_f , then the DC gain would have been $-R_f/(R_1+R_2)$ and at AC, the gain would be $-R_f/R_1$, so it would have been a high pass circuit.

We have now a resistor R_4 connected to ground, that is used to increase drastically the gain. The input current $i_{in}(f) = V_{in}/(R_1+Z_1)$. At DC, $i_{in} = V_{in}/(R_1+R_2)$, at HF it is V_{in}/R_1 . Then this current flows through the feedback. Voltage at node V^* above R_4 can be computed in DC and AC. Once we have it, we can compute the current that flows in R_5 , i_5 ; consequently we can also compute V_{out} .

 

$$V^*(0) = -\frac{V_{in}}{R_1 + R_2} \cdot R_3 \quad i_5(0) = \frac{V^*}{R_3} + \frac{V^*}{R_4} \quad V_{out}(0) = V^* + R_5 \cdot i_5$$

$$V_{out}(0) = V^* + R_5 \cdot V^* \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = -\frac{V_{in}}{R_1 + R_2} \cdot R_3 \left[1 + R_5 \cdot \left(\frac{1}{R_3} + \frac{1}{R_4} \right) \right]$$

The current that the opamp should provide is not just the input current, but also the one that flows through R_4 . We can finally write the gain in DC.

$$G(0) = \frac{V_{out}(0)}{V_{in}(0)} = -\frac{R_3}{R_1 + R_2} \cdot \left[1 + \frac{R_5}{R_3 \parallel R_4} \right] = -\frac{220k}{10k + 100k} \left[1 + \frac{10k}{1k} \right] = -2.11 = 22$$

The gain doesn't seem so high, but it is already increased by R_4 .

As for the rest, we have two capacitors, so we are prone to think that we will have two poles. For sure R_1 and C_1 introduce a pole because they are in the path of the signal towards ground (actually, towards VG), and the same for C_2 and R_3 .

When computing the pole values, the concept of virtual ground applies, so C_1 sees $R_1 \parallel R_2$. Since we have a parallel configuration of a C_1 and R_2 we will have also a zero with a tau $C_1 \cdot R_2$.

$$pole_1 = \frac{1}{2\pi C_1 \cdot (R_2 \parallel R_1)} = \frac{1}{2\pi \cdot 1\mu \cdot (10k \parallel 100k)} = 18 \text{ Hz}$$


$$zero_1 = \frac{1}{2\pi C_1 \cdot R_2} = 1,6 \text{ Hz}$$

$$pole_2 = \frac{1}{2\pi C_2 \cdot R_3} = 7,2 \text{ kHz}$$

Now let's compute the pole and eventually the zero introduced by the other capacitor. No current will flow in the input branch because V_{in} is shorted, so no current flows in the feedback.

Again, now we should consider if C_2 introduces also a zero. It will do for sure because at DC the gain is different from AC when C_2 is in short circuit. At AC, $V^* = V_G$, so there is no current in R_4 and so the gain will be provided only by the current in the input branch and through R_5 . Since there is a current in R_5 , the gain won't be 0. Hence C_2 should introduce also a zero.

 The procedure to understand if the capacitor introduces a zero is to suppose a signal on the capacitor, a signal in input and check whether the output is 0. Is this possible? The circuit of course is operating, so the V_G is provided. Let's study the yellow circuit.




The current that flows in the capacitor is $V/(1/sC_2)$. This current should be such that the output is 0. So the resistances R_3 , R_4 and R_5 are seen as in parallel.

$$\frac{V}{1/sC_2} = -\frac{V}{R_3} - \frac{V}{R_4} - \frac{V}{R_5} = -\frac{V \cdot (R_4 R_5 + R_3 R_5 + R_3 R_4)}{R_3 \cdot R_4 \cdot R_5}$$

The zero is at the frequency where this equation holds.

$$s = zero_2 = \frac{\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}}{C_2} = \frac{1}{2\pi C_2 \cdot (R_3 \parallel R_4 \parallel R_5)} = 1,8 \text{ MHz}$$

 Let's now plot the Bode diagram. Of course, the zero could also have been computed with the graphical representation of the Bode plot.



The gain at infinite frequency is:

$$G(\infty) = \frac{V_{out}(\infty)}{V_{in}(\infty)} = -\frac{R_5}{R_1} = -1$$

NB: R_6 has no effect because the opamp is producing its V_{out} that is the one we need to find, and then it's the opamp that is providing the additional current on R_5 , but it is on the top of the feedback network, it is additional. It is wrong to say that the current that flows from the feedback goes in R_6 and then in the opamp, because it is the opamp that provides the current to the feedback and to the load.


V_{out} then depends only on the feedback and input network and not on the amplifier and load resistor.

As for request b), $V_{in} = 100\text{mV}$ is a DC value.

$V_{out} = 22 \cdot V_{in} = -2,2V$. To provide this voltage, the opamp should be able to provide the current $-2.2/R_6$ and the other current that flows in the feedback, that is the current that we have in input and the extra current that should flow in R_4 . So we should recompute the value of V^* to get the current. We already have the formula for it from the beginning, and we get $V^* = +0.2V$.

Hence we can compute the current in R_5 . So we finally get to $i_{out} = i_5 + i_6 = 0.5mA + 47\mu A = 247\mu A$.

Example 2

 


$A_0 = 100dB$, $GBWP = 100MHz$.
 $R_1 = 22k\Omega$, $R_2 = 1k\Omega$, $R_3 = 1k\Omega$, $R_4 = 47k\Omega$, $C = 1nF$.

- Plot the Bode diagram of the **ideal** and **real** $V_{OUT}(f)/V_{IN}(f)$.
- Compute the range of GBWP values that guarantees stability with a P.M. better than 90° .

The opamp is compensated because the GBWP is specified.

- Again, we have a negative feedback. So epsilon is $0V$, so no current through R_2 , and so no current in R_1 and hence I will have V_{in} both on the $-$ and $+$ terminal. Since in DC the capacitor is open, there is no current in feedback and $G(0) = 1$.
 $G(\infty) = 1 + R_4/R_3$.

 Hence the circuit will have a pole and a zero. To compute the pole, V_{in} is off, so since R_2 is between $0V$ and $0V$, C sees only R_3 . $f_{pole} = 160 kHz$. The zero can be computed dividing $160kHz$ by 48 , so at $3.3kHz$.




To compute it analytically, I put a voltage on the capacitor and the output to 0 . The current in the capacitor will flow in R_3 but won't go in R_2 because epsilon is 0 , so it will flow in R_4 . $-$ terminal will be at V_{in} (not V_G).

$$\frac{-V}{sC} (R_3 + R_4) + V = 0$$

$$sC(R_3 + R_4) + 1 = 0$$

$$s = \omega_{po} = -\frac{1}{\pi C (R_3 + R_4)}$$

 To compute the real gain we need now to study Gloop. We have the following beta network.



$$\beta(0) = \frac{V_E}{V_{out}}(0) = \frac{-R_2}{(R_2 + R_1 + R_4)} = \frac{-1k}{22k + 47k} = \frac{-1}{69}$$

$$\frac{1}{\beta(0)} = -69$$


$$\beta(\infty) = \frac{-R_2 \parallel (R_1 + R_2)}{[R_3 \parallel (R_1 + R_2)] + R_4} \cdot \frac{R_2}{R_2 + R_1} = \frac{-1k \parallel 23k}{1k \parallel 23k + 47k} \cdot \frac{1}{23}$$

$$= -870 \cdot 10^{-6}$$


$$\frac{1}{\beta(\infty)} = -1151$$

As for the poles and zeros of the beta, the pole has a $R_{eq} = R_3 + (R_2 + R_1) \parallel R_4$. As for the zero, we have a node and an R-C hanging from that node (C and R3). So it is easier to compute the zero, because its tau is $C \cdot R_3$.

 
Now we can plot the Bode diagram to retrieve the real gain and to compute stability.



 To compute f^* , we prolong the DC value of $1/\beta$ so that we get a triangle (green one) that has the base divided in half by f^* . So we compute f^* with the geometric average.




 We see that the closure angle is not good, 40-40, even if there is a zero of beta that tries to help. We can compute the phase margin.



We are left with a phase margin of 36° , so the system is unstable. Let's now plot the real gain. Firstly, we need to plot the ideal gain.

 
When we reach f^* we drop by -20 dB/dec and then still -20 dB/dec after the zero of the ideal gain.



To solve the problem we need to let the circuit reach the HF gain. A solution could be to change to opamp to have the crossing between $1/\beta$ and $A(s)$ with 20-20. But it is better not to change the opamp, so we can reshape the β so that the crossing with $A(s)$ happens at the frequency I want. To decrease $1/\beta$ we have to increase β at HF, and to do so we should not kill β at HF. At HF, β dies because there is the capacitor C. Maybe, in this circuit it was an incorrect thing to add that capacitor.


To regain stability we can change R_2 , which is not impacting on the ideal gain, but it can change β . Reducing $1/\beta$, f^* increases, and to increase β we have to increase R_2 . If we completely remove R_2 , the real gain will be the same, but β will be 1 at LF and at HF it will be just the R_3 and R_4 partition, 48. So it is overlapping with the ideal gain.

Maybe now the situation is ok.

 

Example 3

POLITECNICO MILANO 1863

 

Compensated OpAmp: $A_0=120\text{dB}$, $\text{GBWP}=10\text{MHz}$, $I_B=10\text{nA}$, $V_{OS}=5\text{mV}$. $R_1=47\text{k}\Omega$, $R_2=33\text{k}\Omega$, $R_3=22\text{k}\Omega$, $R_4=680\text{k}\Omega$, $C=330\text{pF}$.

- Plot the real $v_{out}(f)/v_{in}(f)$ gain and comment stability.
- Compute the output static errors due to the OpAmp.
- Let the OpAmp be a Norton Amplifier instead, with $A_1=5$, compute the $v_{out}(f)/v_{in}(f)$ gain.

Opamp is still compensated.


- a) Again we have a negative feedback. Because of this, I can say that I have virtual ground at - terminal. Hence no current flows in R3 and R2, so also node x is at 0V.

$$G(0) = -R4/R1 = -14.5$$


$$G(\infty) = 0$$

The Bode diagram of this circuit is the one of a LP filter, so the circuit has no zero and one pole. The Req of the pole is $C \cdot R4$. $f_{pole} = 710 \text{ Hz}$.

 
As for the real gain, we need to compute the $1/\beta(s)$. Of course everything is negative because we return to the - terminal of the opamp.



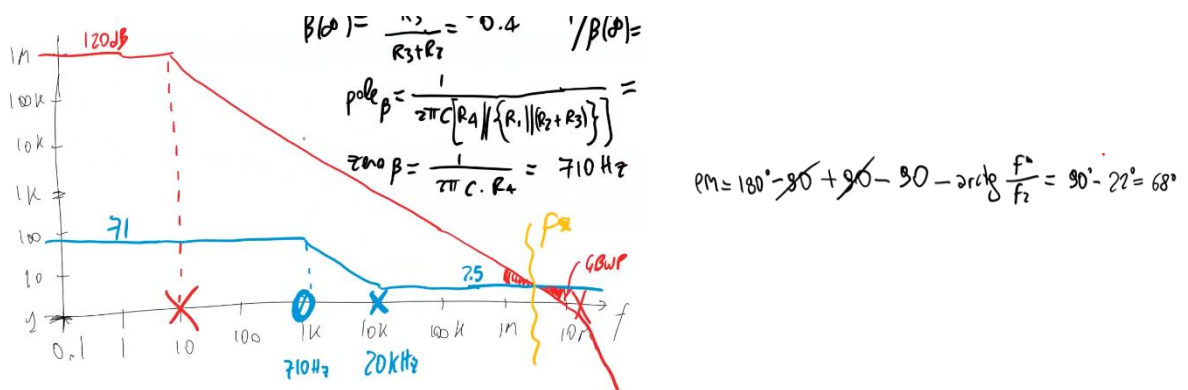We can now plot the real gain. f^* is very close to the second pole of the opamp, so we might be unstable. So let's compute the phase margin.




The phase margin is ok, very good.

 

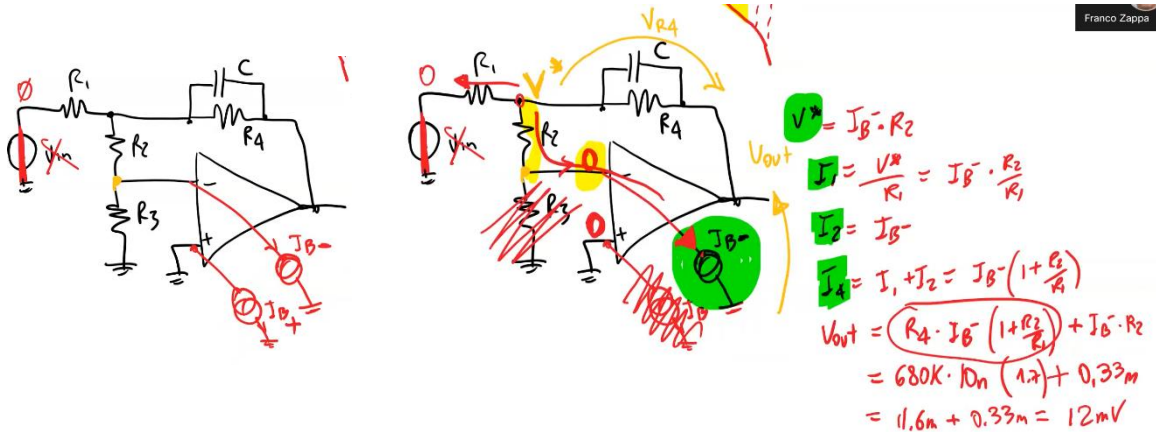
- b) Output static errors of the opamp. Since the opamp has components inside, the impedance in input is not infinite, but there is some. Moreover, even if the input was infinite, maybe at DC we still need an input current for the opamp to operate, e.g. in the case of BJTs. The two bias current causes a current intake but the opamp, but still with infinite impedance.

When we consider the effect of the bias, we switch off the input and we consider just the bias effects, with the superposition of effects, hence considering one bias current at a time.



If I consider I_{B+} , the other one will be open circuit. I_{B+} is pumped into a ground, so it doesn't give rise to any signal, so no error at the output. As for I_{B-} , due to virtual ground we have no current in R_3 . If so all I_{B-} flows in R_2 ; if the opamp is sinking current, V^* is positive. So we will have a current I_1 in R_1 . Since the bias current is a DC contribution, the capacitor will be open. To kill this contribution, we should add a resistor, properly sized, between PS and V^* .


Example 4

 

OpAmp with $A_0=100dB$ and $GBWP=100MHz$. $R_1=47k\Omega$, $R_2=220k\Omega$, $R_3=110k\Omega$.

- a) Compute the real $v_A(f)/v_{in}(f)$ and $v_B(f)/v_{in}(f)$ gains and the input impedance.
- b) Compute the output static error on V_A , due to $I_B=10nA$ and $V_{OS}=5mV$ of both OpAmps.

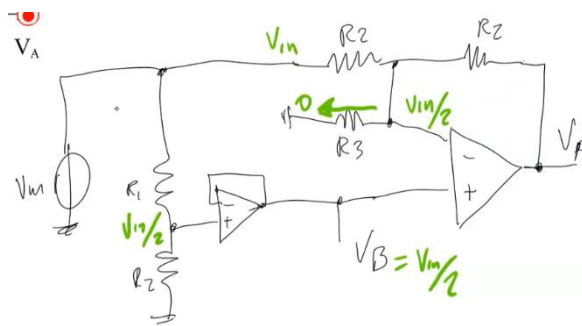
- a) OA1 is a buffer that goes to the + terminal of OA2. So we have two local negative feedbacks, but is there a global one? No, because no one can counteract on the node where the voltage source V_{in} is placed. Let's redraw the circuit. The second stage has VG.



$$V_A = \left(\frac{V_{in}}{2} + \frac{V_{in} - V_{in}}{R_2} \right) \cdot R_2 + \frac{V_{in}}{2} = \frac{V_{in}}{2} \left[\left(\frac{R_2}{R_3} + \frac{R_2}{R_2} \right) + 1 \right]$$

$$G_{\text{real}} = \frac{V_A}{V_{in}} = \frac{1}{2} \left(1 + \frac{R_2}{R_3} + 1 \right) = \frac{1}{2} \cdot \frac{R_2}{R_3} = +1$$

 
To compute the real gain of OA1 we know that it is a buffer, so I expect it to have a gain of 1, but it is not, because we have a $A(s)$ and a $\beta(s)$. The β for OA1 is 1, just the feedback network. The real gain is as below.



If the second pole of the amplifier is too close to GBWP I run the risk of having a phase margin poor, of 45° . For this reason we have a minor peaking.


As for the real gain of V_b/V_{in} , it won't be 0.5, but at $\text{GBWP} = 100 \text{ MHz}$ it will experience two c.c. poles, so a minor peaking and a -40 dB/dec decrease. The two poles are due to a crossing 20-40 in OA1.

 Let's now study the second opamp with its β . f^* will be at a frequency 3.9 times before GBWP.



Hence the real gain won't be flat, equal to 1 for almost all the frequencies of interest, but then there will be a first pole at f^* and a second pole where the second pole of the opamp is.

 b) Static error due to I_{bias} and V_{os} .



Let's compute the V_{out} due to the bias generator. I_{b+} of OA1 have a current that flows in a parallel of $47k \parallel 47k$ (V_{in} is off). Once we have V^+ of OA1, that will be also at the $+$ terminal of OA2. That value get's amplified to the output with a gain of the non-inverting configuration. Eventually, the contribution due to I_{b+} gives 0.9 mV .

As for I_{b-} of OA1, the current comes from the opamp itself, and since the opamp is providing 0V at the output (V_{in} is 0), so that voltage doesn't move and because of this, the contribution of I_{b-} on the output is nihil.

Let's now consider I_{b+} of the second stage. Same reasoning as before because it pumps again in a voltage generator of OA1 output. Also for this current the contribution is 0.

Finally, for I_{b-} of the OA2, we have V_- of OA2 at zero because of the propagation of the $V_{in} = 0$. If so, there is no current in the 220k and 110k resistors. Hence the I_{b-} is provided by the voltage source of the opamp and causes a voltage drop across the feedback resistor.


$$I_{b1} \cdot (R_1 \parallel R_i) \cdot \left(\frac{220k \parallel 110k + 220k}{220k \parallel 110k} \right) \left(1 + \frac{220k}{220k \parallel 110k} \right) = 0,9mV$$

$I_{b1} \cdot \emptyset$ no effect
 $I_{b2} \cdot \emptyset$ no effect
 $I_{b2} \cdot 220k = 2,2\mu V$

$$V_{out \epsilon} = 0,9mV + 2,2\mu V = 0,9022mV \approx 0,9mV$$

We can see that the opamp that mainly affects the offset in the case of the bias current is OA1.

 
As for the offset, it is due to the mismatch between components. Offset voltage is unpredictable, it can be positive in one or the other side, differently from the bias current that can be positive inward going or outward going. The V_{os} is a statistical error, with a statistical distribution (e.g. Gaussian) around a given value.



If we consider the offset of OA1 (input still off), we have an amplification due to the second stage, so the error is $V_{os1} \cdot G_2$.

As for V_{os2} it is exactly the same of V_{os1} , because in the second opamp enters just V_{os2} .


Total error is $\pm 36mV$.

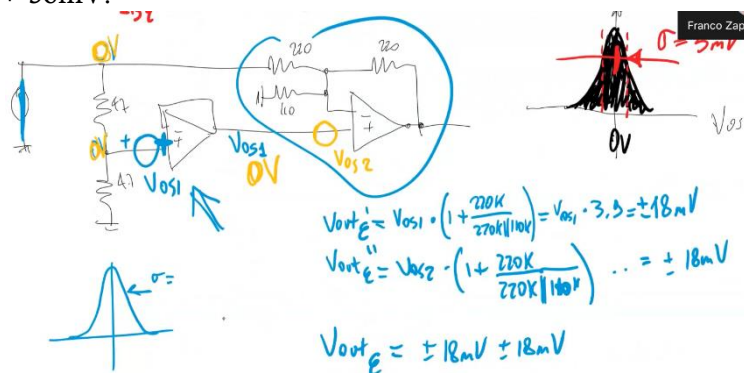

We can notice that I_{bias} contribution is negligible with respect to V_{os} contribution.

Example 5

POLI TECNICO
MILANO 2013

 


Uncompensated OpAmps with $A_0=120\text{dB}$, $f_0=5\text{kHz}$ and $f_1=50\text{MHz}$, $I_B=1\text{nA}$ and $V_{OS}=3\text{mV}$.

- Without** C_C and R_C , compute stability and PM.
- Properly size C_C and R_C to attain $\text{PM}=90^\circ$.


We start from the input signal, and then it touches node +, it gets amplified and the output is sent to the input \rightarrow we have a feedback. Is it positive or negative? If + increases, the output increases, so due to the feedback network also - increases, so the error signal decreases and we have feedback \rightarrow we can apply the concept of virtual ground, so the voltage on the + and - terminals are the same, so no drop on C_C and R_C .

$$G_{\text{ideal}} = 1 + R_2/R_1 = 1 + 110/47 = 5.7$$

 - Let's compute the phase margin. The first pole is at 5kHz and the second at 50MHz, the opamp is uncompensated. Let's draw the Bode plot. The attenuation between first and second pole is 1000, that is 4 decades, so I will decrease by 4 decades in amplitude of the gain.



 The crossing frequency is $50\text{MHz} \cdot \sqrt{100} = 500\text{MHz}$. This in red is $A(s)$. Now we have to study beta. Since R_C and C_C has to be neglected it is 5.7 and constant.




We can see that the crossing with $A(s)$ is at -40dB/dec , so we can compute the phase margin. To compute f^* , the crossing frequency, the ratio in gain is $100/5.7$ but we have -40dB/dec , so $f^* = 50\text{MHz} \cdot \sqrt{100/5.7} = 209\text{MHz}$.
 $\text{PM} = 90 - 77 = 13^\circ \rightarrow$ not stable.

$$PM = 180 - 90 - 2 \cdot \arctan \frac{f^*}{50 \text{kHz}} = 90 - 2 \cdot \arctan \left(\frac{20 \text{kHz}}{50 \text{kHz}} \right)$$

The ideal gain is 5.7, that just by chance overlaps with 1/beta, and let's plot the real gain, that is equal to the ideal up to f^* , where it then follows $A(s)$ because 1/beta is constant and $A(s)$ is -40. If 1/beta was -20 after f^* , the real would go with -20 after f^* (REG).

 - b) Let's see the role of R_c and C_c . We are adding something that is not changing the ideal gain, because the voltage across them is ideally 0, but it impacts on the beta. In DC 1/beta is the same because the capacitor is open, but then we have a pole and a zero. Every time we enter in a circuit and we have a RC to ground, that RC introduces a zero = $1/(2 \cdot \pi \cdot C_c \cdot R_c)$. To compute the pole, we switch everything off.




$$z_{RC} = \frac{1}{2\pi R_c C_c}$$

$$p_{RC} = \frac{1}{2\pi C_c (R_c + 47k \parallel 220k)}$$

We have to size C_c and R_c to cross $A(s)$ in the -20 region but not in a decade within the next pole, otherwise we are still experiencing the effect of the following pole. We have to stay one decade before the second pole of $A(s)$.

 The important thing is that the crossing is with a 0 slope, because if it is with a +20 slope for 1/beta we are not compensating anything.



Moreover, as to the 1/beta at infinite frequency, should be 1k that is $10 \cdot A_{min}$, because we know that the gain difference between the value at f^* and at f of the second pole is 10.

$$\frac{1}{\beta(\omega)} = 10 \cdot A_{min} = 1k \approx 1 + \frac{270k}{R_c}$$


$$R_c = \frac{270k}{999} = 270 \Omega$$

Then since I want the zero one decade before to be sure that we don't suffer of the presence of the second pole, we can compute the value of C_c .

$$\frac{1}{2\pi C_c R_c} = z_{RC} = \frac{f^*}{10} = 500 \text{kHz} \quad R_c$$

$$C_c = \frac{1}{2\pi \cdot 500 \text{kHz} \cdot 270} = 1.4 \text{nF}$$

 
In this situation, we are sure that the PM is more or less 90° (we are adding the two poles and then a zero of 1/beta). Then of course we have another pole, but we are interested in the phase shift only at the frequency where $G_{loop} = 1$.



The pole of this circuit is when the real gain decreases, that is at f^* , and this is the pole of the closed loop configuration.

Example 6

MILANO 1983

 


OpAmp with $A_0=120\text{dB}$ and $\text{GBWP}=20\text{MHz}$, with $I_B=10\text{nA}$ and $V_{OS}=5\text{mV}$.

$R_1=1\text{k}\Omega$, $R_2=50\text{k}\Omega$, $R_3=2\text{k}\Omega$, $R_4=50\text{k}\Omega$, $R_5=1\text{k}\Omega$, $C=10\text{nF}$.

- Plot the Bode diagram of the $v_{out}(f)/v_{in}(f)$ real gain, when OA2 is still ideal.
- Discuss circuit stability when also OA2 is real.
- Compute the output error due to bias currents and offset voltages of both OpAmps.

If we apply something positive, the output of OA1 goes positive, and then we have a standard inverting amplifier in the feedback, so the output of OA2 (stage with $G = -25$ in DC and -0.48 in AC) will go negative (node A) and hence we have a negative feedback because the negative on node A opposes on the positive increase in the + terminal of OA1.

 OA1 is an amplifier with a very large gain because it is open loop, so the gain is $A(s)$, while OA2 has a feedback that causes a gain that depends on the frequency. We have the following configuration.



The beta network is not just resistors in this case but it is an amplification, and since it is a negative amplification, the output can return to the positive terminal of OA1.

- So OA1 has infinite gain (or at least $A(s)$), and if so, between its two input the epsilon is 0, so there there is the concept of virtual ground \rightarrow + terminal of OA1 will be at 0V. If + terminal is at 0V, this voltage is set by the feedback, whatever we apply at V_{in} . Thanks to feedback, we apply a signal V_{in} that tries to move node x but then Shrek moves the output so much that the beta stage will respond causing a negative signal to appear so that there is no movement at node x, remaining 0 (virtual ground). A current will flow in R_1 that is V_{in}/R_1 . Voltage $V^* = V_{in}/1\text{k} * 50\text{k}$.

We are interested in V_{out} that is, at DC: $V^* = -25 \cdot V_{out}$.

At AC: $V_{out} = V^* / -0.48$.


As for the final transfer function:

$$\frac{V_{out}}{V_{in}}(0) = \frac{-50}{-25} = +2$$


$$\frac{V_{out}}{V_{in}}(\omega) = \frac{-50}{-0.48} = +100$$

Let's plot the ideal gain, it will have a zero and a pole. To locate them, we cannot exactly say where they are, since C causes something but not in a clear way. If there were a capacitor in series to R1, I would exactly know the position of the pole and zero.

 To understand where pole and zero are, we must study stability. First of all, let's complicate the circuit.



We start from V_{in} and then I move. I cannot go in OA2 output because it is a voltage source the output of an opamp, so I go in OA1. Given the +, the output increases, and since we are increasing the base of a transistor, the emitter is increasing as well (common collector configurator, emitter follower). But then we have an opamp with an inverting configuration. Then we have a BJT where we are entering in the base and exiting at the collector we are in an inverting configuration. The infinite gain is still related to OA1, because the gains of OA2, OA3 and the two BJTs are limited. So on OA1 applies the concept of virtual ground. Let's compute the gain. The current in input flows in the OA2, so $V^* = -V_{in} / 1k \cdot 50k$.

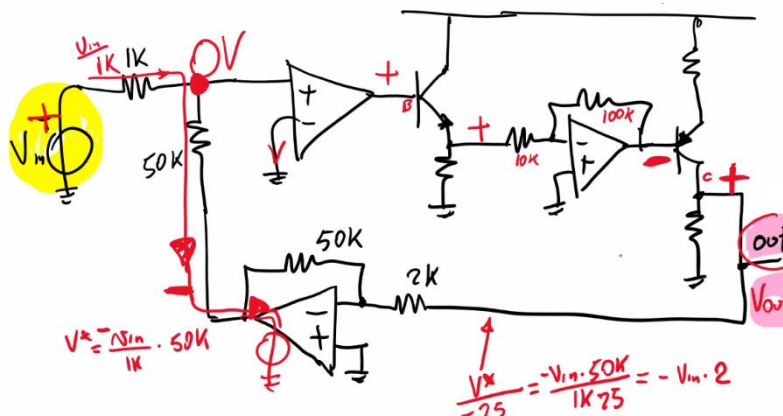


So we don't need to pass through the upper network to get the output. The signal propagates firstly in the upper branch and then in the feedback, but we can analyze it in the way we want.


So I don't care if the opamp is ideal or if there are non linearities, I don't care about what $A(s)$ is (indeed, $A(s)$ is not necessarily only the one of the single opamp, but it can be the whole forward branch), because the important thing is the beta network, that is the one that sets the real gain

(from the output back to the input). We can choose whatever beta and A(s) network we want, the important thing is that the f^* is always the same, as well as for the close angle in the crossing between $1/\beta$ and $A(s)$. Now we return to the original circuit.

 OA1 is the open loop opamp and let's call it $A(s)$. It is uncompensated.




Now let's plot beta. We cut at the output of OA1 and place V_{test} . Then we have the gain of the classical inverting configuration. We have also a pole and a zero because we have the C capacitor. The pole is not the one of the overall circuit, nor of the beta, but of the inverting configuration in which OA2 is. In the CL config of the inverting, we recall that the pole is given by the two resistances in series (we have to switch off all the input signal when computing the pole).

 


$f_p = 312 \text{ Hz}$.

 
As for the frequency of the zero, it is a factor $25/0.48$ higher than the pole.



 Apart from the gain of the inverting stage, the beta network is also composed by the resistive divider that we have in output to the inverting stage. So the gain of OA2 must be multiplied by an attenuation factor $R1/(R1+R2) = 1/51$.




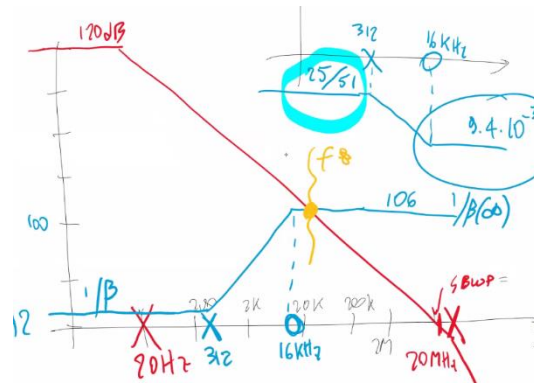Overall, the beta network has a gain of $25 * (1/51)$ in DC and $0.48 * (1/51)$ in AC.




But I don't want beta, but $1/\text{beta}$, so I have to revert all the gain values. Now we have to compute the $f^* = \text{GBWP}/106 = 189 \text{ kHz}$. The zero is at lower frequency, so the plot is correct. If f^* was 189 kHz and zero was at a higher frequency, the plot was wrong.

 We could also study the circuit in another way. Now I change what is $A(s)$ and what is beta. In fact, if we switch off the source, output disappears, so the loop is a loop, so we can define whatever we want.




In this case, $A(s)$ has a gain of 25 at LF and 0.48 at HF. Now we have to plot beta, that is firstly an attenuation due to the resistive divider, and then the t.f. of the opamp. In DC, $\text{beta} = 1/51 * 1'000'000 = 19'000$, while in AC it dies as the t.f. of the opamp. We want the inverse of beta, of course.

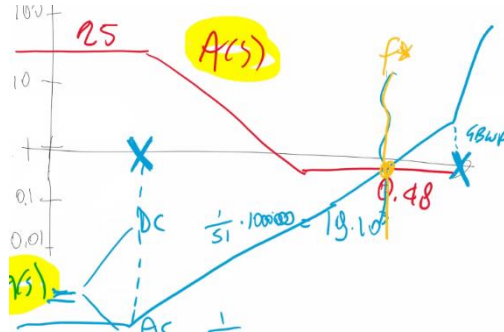DC: $51 * 10^{-6}$. Even with this method, I find f^* that is exactly the same of the previous case.



 b) (It is request c).

Bias currents are a DC concept, so the capacitors are open. Offset can be put where I wish, it is easier if placed as in the image.




Let's consider $V_{os,OA1}$. V_{in} is off, so node x I have V_{os} . So a current flows in R_1 and through also R_2 . Then it goes to the source that is the OA_2 , whose output generator is providing the current. $V^* = V_{os}/1k * (50k + 1k)$.


Hence the output error due to V_{os1} is $V_{os1} \cdot 2$ more or less.

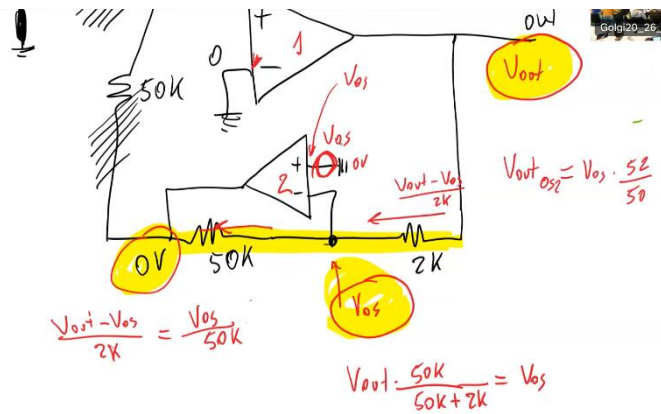(1:26:10)


Let's consider now the second offset related to OA2. The typical error is that we suppose the V_{os} propagates clockwise in the network to the output with all the different values of gain and everything, but to investigate the circuit I have to move the other way round.
So the input is 0, so I have no current in the 1k resistor and no current in the 50k resistor. Hence output of the feedback opamp is 0. We will have a current in the 50k resistor due to V_{os} . And this current must be equal to the one in the 2k resistor.



Let's consider the following circuit.

 

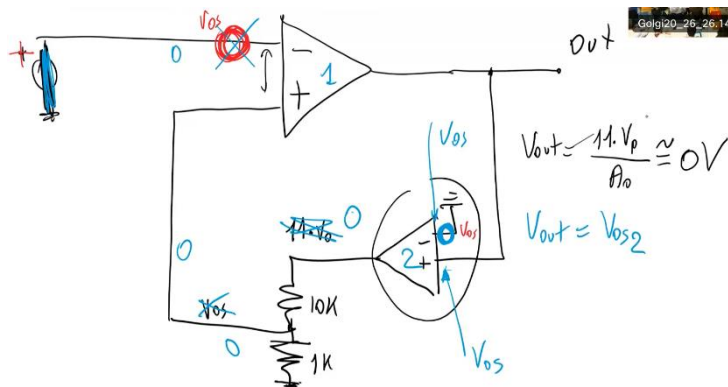There is not a negative feedback, the feedback is positive. To have a positive one it's sufficient to switch the input terminals. The contribution of the offsets of the two opamps are the following.




NOISE

Noise is a disturbance that can be considered white or not. It is a problem both in analog signals and digital signals. In fact in digital signals it can add time jitters.

Noise is random in its nature, it is not deterministic; most of the noise we are dealing with have an average value equal to 0, so it is no sense to consider the specific value of noise at a specific time instant, but better to speak about noise distribution.

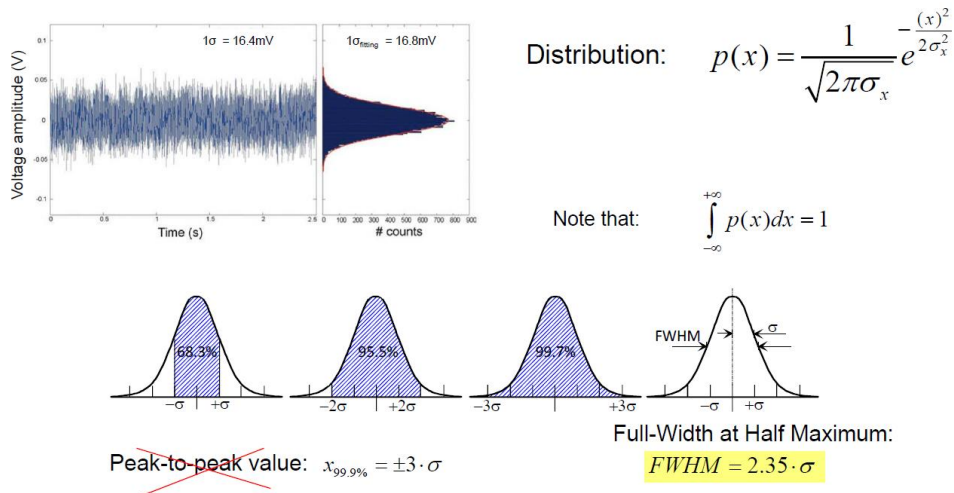Noise often follows a Gaussian distribution. The full area of the Gaussian is equal to 1.



Hence the random event has a probability to have a given number and the sum of all the probabilities is equal to 1. However, often the noise is concentrated within a specific range. This is according to the bottom image. In a gaussian it is no sense to speak about a peak-to-peak value, but whenever we have a random noise that can be described as a gaussian, we can consider the FWHM. Almost all the noise will be within $\pm 3 \cdot \sigma$. The peak-to-peak value is in within this range. So given the sigma, we can define the FWHM of a gaussian is $2.35 \cdot \sigma$.

Noise can be described in the time domain or in the frequency domain.


Instantaneous value is nonsense, better to measure the power: $Power = \frac{1}{T} \cdot \int_0^T |x(t)|^2 dt$

“Ergodic” process (time average = samples average), Gaussian, with nil mean value


Variance, “power”, mean squared value: $\langle x^2(t) \rangle = \sigma^2$

Parseval's theorem:
 
$$\sigma^2 = \langle x^2(t) \rangle = \int_0^\infty S(f) df$$



 Root mean square, rms: $x_{rms} = \sqrt{\sigma^2}$




The power of a signal can be computed in two ways. We can integrate the value of the voltage measured between 0 and time T in dt and divide by T to get the voltage average value. For a noisy signal, the average value is 0. If we have a gaussian centered around a value, e.g. 800mV, the average value is 800mV.

If we compute the integral of the square of the voltage between 0 and T and then we divided by T, we don't get the average voltage but the average in the time domain of our signal. This is also called variance of the signal, **average power** of the signal.

$$\langle V^2 \rangle = \frac{1}{T} \int_0^T |v(t)|^2 dt$$

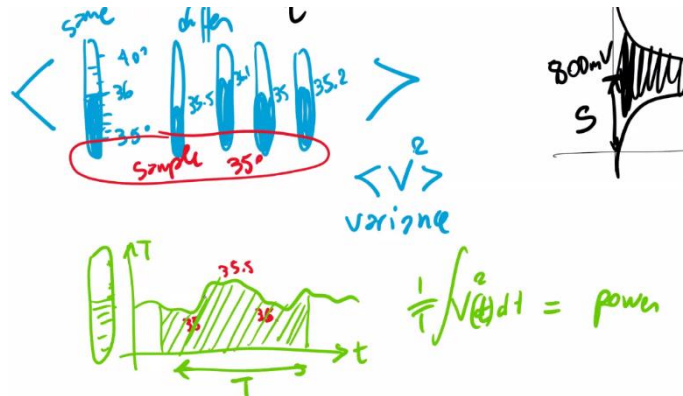Variance is a value related to a set of values. Imagine we have a thermometer with a possible measured value between, 35° and 40°, and we take the measurement with different (or the same several time) thermometers of the same quantity, and then we average them, we get the variance of the experiment.



Conversely, we can take one thermometer and see how the temperature varies over time. If we compute the area and we divide by T, we get the power of that signal.

If we consider **ergodic processes**, the time average is equal to the samples average, so the two previous quantities in the examples are the same. Moreover, the **Parseval's theorem** says that if we have a signal, if we have the time dependent waveform of the noise and the spectrum of the noise, if we compute the power in the time domain, that is the variance, is equal to the integral of the spectral density of the system.

If we compute the square root of the power we are computing the **root mean square**. Sigma is the quantity that if we take 3 sigmas on the right and on the left of the gaussian curve and we compute the area, we get the 99.7% of finding the signal in that range. In fact, the peak to peak amplitude of the signal is more or less 6 times sigma.

Two noise sources: $v_t(t) = v_1(t) + v_2(t)$ **x**

Mean total value: $\langle v_t(t) \rangle = 0$

Total variance: $\langle v_t^2(t) \rangle = \langle [v_1(t) + v_2(t)]^2 \rangle = \langle v_1^2(t) \rangle + \langle v_2^2(t) \rangle + 2 \langle v_1(t)v_2(t) \rangle$

... in case of NO correlation : $\langle v_t^2(t) \rangle = \langle v_1^2(t) \rangle + \langle v_2^2(t) \rangle$ Such as the effect overposition principle

... in case of TOTAL correlation $v_1(t) = v_2(t)$: $\langle v_t^2(t) \rangle = 4 \langle v_1^2(t) \rangle$

100% ERROR ! but ... NEGLIGIBLE ! ("only" 41% on rms value)
Therefore... let's consider all noise sources as uncorrelated

CORRELATION AMONG NOISE SOURCES

Let's suppose we have a resistor. The resistor is noisy, with a spectral density that is a number, that in the case of 1 kOhm resistor at RT is 4nV/sqrt(Hz).

If then we take another resistor that is noisy and we put it in series, the equivalent resistor has a value of 2k, but the noise is not 8 nV/sqrt(Hz), we don't get the sum, because it is the power and variances that sum up.

$$\sigma_{\text{tot}} = \sqrt{\sigma^2 + \sigma^2} = 5.6 \text{ nV}$$


We might have another issue. If we study a circuit, in the circuit we may have different components, resistors, opamps, capacitors and so on. Each component (except for capacitors) will have its own noise, and we should consider the sum of all the noise contribution. But how to do so? Should we sum the amplitude or the power?

If we have a signal that is the sum of two signals, like in x. Mean total value is 0, because both the integrals are zero, since the two processes are random noises. But then when we compute the variance, we have to compute the power 2, that is not just the sum of the power of the two signals, because there is also the third contribution. **In case of no correlation**, the third contribution is negligible, so **we can apply the principle of the superposition of effect in the powers, not on the individual noise**.

If signals are correlated, the sigma of the two signals is the same, and the overall sigma_tot is two times the sigma of the signal. Even if we had, by chance, considered the two signals uncorrelated, the error committed in doing this is not so big, so in principle we can consider all the noise sources uncorrelated.

SHOT NOISE

 It is due to the granular nature of charge crossing the junction. The charges passing across the channel varies depending on the time instant at which we are looking the situation. We would see several deltas related to the passage of the electrons, and in the frequency domain this still remains with a comb shape.



Electrons are random in movement due to Brownian motion of charge, so the real spectrum in the frequency domain will be similar to a cardinal sin of events, which has a zero crossing in the thousands and thousands of GHz → where we study the noise we can consider the shot noise to be flat.

Due to the "granularity" of charge crossing a junction (like rolling marbles instead of a "liquid" flow)

- shows up only if there is a current flow
- the rms value increases with \sqrt{I}
- depends on f... but... almost "white" noise


$$\sigma^2 = \langle i^2 \rangle = 2 \cdot q \cdot I \cdot \Delta f$$

"Like a rain on a thin roof"

This noise increases with the amount of current. If the current is low, the noise is low. If the current increases, then even the noise increases. The proportionality factor of increase is $2 \cdot q$.

The shot noise $2qI$ is not depending on frequency, nor on a resistor value, it depends just on current. Of course, it is proportional to the bandwidth, we need to multiply by Δf of the instrument that is measuring noise to get the sigma square. But the noise contribution is just $2qI$.

So e.g. we have a diode through which an average current is flowing, but we measure the current with two instruments; the first one could be an amperemeter, and the second one could be an oscilloscope. The oscilloscope input has a much higher bandwidth with respect to the amperemeter (e.g. 10MHz vs 10Hz of the latter). So if we look at the same noise on the oscilloscope we would see a much broader noise, a peak to peak equal to 0.6V.

 

Hence depending on the bandwidth of my instrument we will have the total power of our noise. Hence **if the average value of the current increases, also the noise will increase**, but if I consider signal over noise (SNR), this increases with \sqrt{I} .




NB: let's remember that for a 50uA current the corresponding shot noise is 4 pA/sqrt(Hz).

THERMAL (JOHNSON) NOISE

Let's consider a resistor and no current in it. I should see 0V across the resistor, but instead I see some voltage fluctuations across it due to the Brownian motion of electrons. This noise increases with temperature and value of resistance.


 
Due to the granular and never fixed nature of charge



- independent of current flow
- rms value depends on \sqrt{T} and \sqrt{R}
- independent of frequency ("white" noise)

$$\langle v^2 \rangle = 4kT \cdot R \cdot \Delta f$$
  
$$\langle i^2 \rangle = \frac{4kT}{R} \cdot \Delta f$$



$$4kT = 1.66 \cdot 10^{-20} \frac{V^2}{Hz \cdot \Omega}$$


$4kTR$ is the intrinsic noise of the resistor. $4kT = 1.66 \cdot 10^{-20}$ (at RT), and it is similar to q , that is the electron charge. Then we have also to consider the bandwidth.

Again, if we increase R the power increases linearly but the rms value increases by the sqrt(R) (this is in terms of voltage noise).

But if we look at the noise in terms of current, it seems to decrease with an increase of R. But since the power (v^2) increases by R, it makes sense that the current decreases with R.

NB: for a 1k resistor the noise is 4 nV/sqrt(Hz).


FLICKER NOISE (1/f)

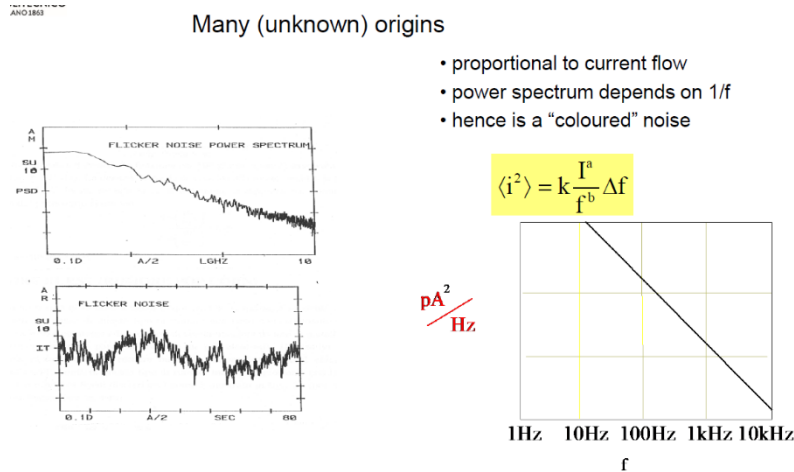

It has many unknown origin and it is proportional to the current flow. Its power spectrum is not constant, it is not white because it decreases with frequency. Usually coefficients a and b are 1, but they can change a bit depending on the real physical mechanism.

The important thing to compute is the **power within one decade**. If we compute the power within one decade of that spectral density, that is kI/f , k and I are constant so what remains is the integral of 1/f that is the logarithm. The flicker noise is not constant, we have not to multiply it for Δf as in thermal or shot noise.

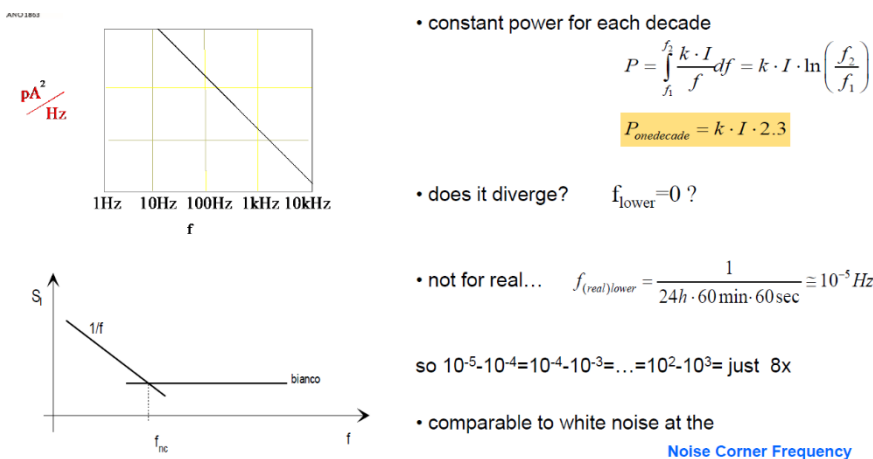Once we found k and the current in the device, then the power within a decade is $P = k \cdot I^2 \cdot 2.3$.




Does this noise diverge?

In theory yes, because if the lower frequency is 0, the logarithm will diverge, even though practically it doesn't. In fact it doesn't make any sense to set f_{low} to be 0, we will have never 0. Then once we have also set the upper frequency, we count the number of decades that we have in between the two frequencies and then we are done, we multiply the P value for that number and we have the flicker noise.

So we have a contribution that varies with frequency due to flicker noise and another that is constant, the thermal and shot noise (white noises). Hence to compare which noise is dominating, instead of


computing the coefficients of the 1/f noise and the level of the white noise, we can quote the **corner frequency** at which the two noise spectral densities are equal.

BURST NOISE

 

It is a noise that keeps moving up and down, usually between two levels or more. If we plot the probabilistic density of this noise it's not one gaussian so there are also a secondary gaussian and so on. Hence it is a more complex noise that can be modelled as a constant contribution for low frequencies and then at HF the noise drops as $(1/f)^2$. It is not like flicker noise because it doesn't go down as $1/f$ and, compared to flicker noise, it is constant at LF.

NOISE I/O TRANSFER FUNCTION

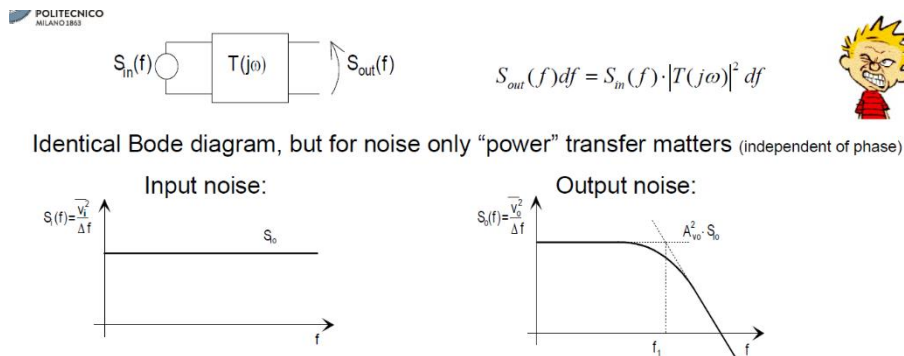

The total output noise power is $\langle v_{oT}^2 \rangle = \int_0^\infty S_o(f) df = \int_0^\infty |A_v(f)|^2 \cdot S_{io} df = S_{io} \cdot \int_0^\infty |A_v(f)|^2 df$

... that's a pity we cannot compute the area (power) as "base x height" ...

We have a noisy source with its noise spectral density and an amplifier with its amplification gain. If the input is a voltage source, the out is the input multiplied by the gain. But since we are considering noise, we have to multiply by the square modulus of the gain (power gain), because we are considering power.


If the input noise is white, the output noise is white if the amplifier has no poles. But if the amplifier has a pole, the output spectral density will show the typical drop due to the pole of the amplifier. The pole causes the voltage gain to drop by -20dB, but since we are in power gain we have -40dB.

Eventually, if the input sigma is constant, the output sigma may not be constant, because the typical Bode diagram of the amplifier will have a pole. Since soon or later we will need to compute sigma_out, it means that we need to compute the square root of the output power, which depends on the input power that is frequency dependent and that should be multiplied by the transfer function of the amplifier to the power of 2, everything then under the integral.



This is equivalent to computing the area of the right image. In computing the area, if the amplifier has 1 pole and we integrate from 0 to inf, we end up with $1,57 \cdot f_{pole}$. This means that if we have an amplifier whose gain is 1 and has a pole, we can compute the integral that is equal to the height of the gain multiplied by a base that is at a frequency given by $f_n = 1,57 \cdot f_{pole}$. This is the **noise equivalent bandwidth** for a single pole amplifier.

NOISE EQUIVALENT BANDWIDTH


 


The pole is NOT the noise bandwidth $f_N = \Delta f$ to consider !

Noise Equivalent Bandwidth: $f_N = \frac{1}{A_{vo}^2} \int_0^\infty |A_v(f)|^2 df$

Very simple cases: 1 pole: $f_N = \int_0^\infty \frac{df}{1 + (\frac{f}{f_1})^2} = \pi \cdot \frac{f_1}{2} = 1,57 \cdot f_1$

2 poles: $f_N = 1,22 \cdot f_1$

  

OK then, the rms value is **SQRT("base x height")** of such an equivalent rectangle


Hence to compute σ_{out} we can consider the σ_{in} at 0Hz, the gain at 0Hz and then multiplied by the noise equivalent bandwidth.

So we just need to consider the input noise, the power gain at DC and the noise equivalent bandwidth.

If we consider infinite poles happening at f_{pole} , then $f_n = f_{pole}$, because the decay slope is $-\infty$ dB/dec, so we have a rectangle.


If instead the poles of the amplifier are at different frequencies, we should overestimate the noise, considering the bandwidth limited just by one pole, that is the dominant pole at the lower frequency.

 In some circuits we may have an amplifier with a capacitor, like below.




In this case I also have a zero. In this case we consider the Bode diagram as composed by two different Bode diagrams.

 One that is the pink one and one that is the blue one.



 Hence we will have like two poles and again σ_{out} will depend on the two contributions.



So the first contribution has a large gain but low noise equivalent bandwidth, vice versa for the second contribution. Eventually, instead of computing the power two of the members, we can take the, as power 1 and then the square root of the bandwidth.


$$\sigma_{out} = \sqrt{\left(\frac{4nV}{VHz}\right)^2 \cdot 11^2 \cdot \frac{\pi}{2} \cdot f_1 + \left(\frac{4nV}{VHz}\right)^2 \cdot 1^2 \cdot \frac{\pi}{2} \cdot f_2} =$$

$$= \sqrt{4n \cdot 11 \cdot \sqrt{1570} + 4n \cdot 1 \cdot \sqrt{15.7M}} \quad \begin{matrix} f_1 = 1kHz \\ f_2 = 10MHz \end{matrix}$$

One of the two contributions may prevail and the other one could be negligible.

 
Example

Let's apply the noise equivalent BW concept to a very simple amplifier. Let's consider a noisy resistor and we want to measure it with an instrument, e.g. a voltmeter. The voltmeter will have its BW due to the parasitic capacitance C. Let's compute the output rms noise, but to do so we need to compute the noise equivalent BW of the circuit. To do so, it will be $\pi/2$ divided by the pole, which is $1/(2 \cdot \pi \cdot R \cdot C)$. The result is the one below.



Hence the noise in output of the instrument will be proportional to C and no longer proportional to R. This doesn't mean that the C is the noisy component, it is the fact that the rms noise depends on the BW that introduces the C in the noise computation, because the noise increases with R and the BW reduces with R, so the product is independent on R.

Simple RC network:

 

Full computation:

$$T(j\omega) = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{1 + sCR}$$

$$S_o(f) = \frac{4kT}{R} \cdot |T(j\omega)|^2 = \frac{4kT}{R} \cdot \frac{R^2}{1 + \omega^2 C^2 R^2}$$

$$\langle v_{or}^2 \rangle = \int_0^\infty S_o(f) Hf = \frac{4kT}{R} \cdot \int_0^\infty \frac{R^2}{1 + \omega^2 C^2 R^2} df =$$

$$= 4kTR \cdot \left[\frac{\arctg(\omega CR)}{2\pi RC} \right]_0^\infty = \frac{4kTR}{2\pi RC} \cdot \left(\frac{\pi}{2} \right) = \frac{kT}{C}$$

"Equivalent" computation:

$$\langle v_{or}^2 \rangle = 4kTR\Delta f = 4kTR \cdot \frac{1}{4RC} = \frac{kT}{C}$$


for C=1pF we get 65µV_{rms}

So what? Does rms noise depends only on C? Is C noisy instead of R?


Hence the larger the C the lower the noise, because if C increases the BW decreases.

NOISE EQUIVALENT GENERATORS

Real circuit:

 

Equivalent circuit:

 


Total input-referred noise (no R_{in}):

$$S_m(f) = 4kTR_s + e_v^2 + i_1^2 \cdot R_s^2$$


Total output noise:

$$S_{out}(f) = |T(j\omega)|^2 \cdot \left\{ S_m(f) \cdot \frac{R_n^2}{(R_s + R_n)^2} + S_1(f) \cdot \frac{R_n^2 R_s^2}{(R_s + R_n)^2} \right\}$$

 No need to compute the output noise... let's stop at the input!



 
Instead of using the individual noisy sources in a schematic, it is a great advantage to consider the noise equivalent generators. For instance, we may have an inverting stage with all the noises related to the resistances, and current noises in the amplifier. The output total noise is due to the contribution of all of them. We can compute the contribution of all the noise sources to the output.




If we change the value of resistances, but keeping the same gain, what will change is the contribution of V3 and V4. If we change Rin, then the input contribution will change.

So if we leave the noise sources spread along the circuit is very difficult to decide how to optimize the signal and the circuit.

 The best solution is to consider the stage to be ideal, noiseless, and we consider the noise sources to be applied at the input. So we have a voltage input equivalent noise source and a current equivalent noise source. Then we connect our source.




Modelling all the noise sources with just a voltage or current equivalent noise generator is not enough, because if for instance at the input I place a very large input resistance, if R increases up to infinity, the noise generator would have no effect because at the output I'm not finding any value because the node to which the voltage noise generator is attached is floating, so at the output I find no noise. Of course this is not true because the circuit has noise.

 

So the other possibility is to use just a current generator for the equivalent noise. But this is still a problem if we have a source with a very low R, because noise current recirculates in the shortcircuit and no noise is presented at the output. So we need to use both the generators.

Voltage equivalent generator

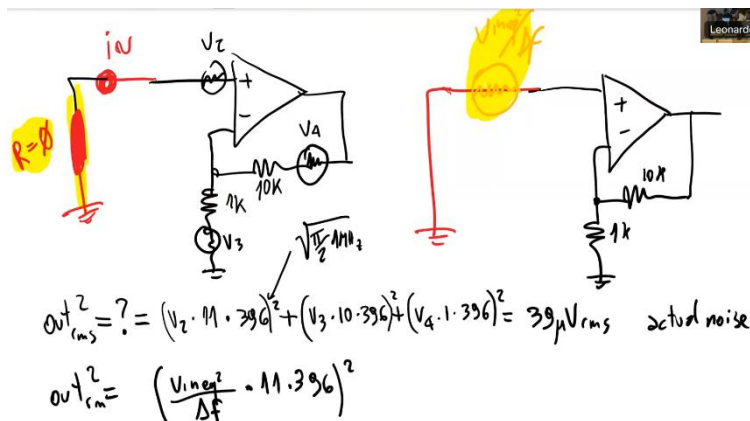To compute it, we choose a R of the source equal to 0. If so, the current noise generator dies thanks to the short and it has no effect on the circuit. So we need to shortcircuit the input to compute the voltage equivalent generator. Then we compute the total output rms noise in the real circuit; then we shift to the model circuit and the output noise for the model circuit is the second line.



Now, if we want the model circuit to be equal to the real circuit, we have to equate the two expressions.


$$\frac{V_{in} \cdot \Delta f}{\Delta f} = \frac{(39 \mu V_{rms})^2}{(11 \cdot 396)^2}$$

The unit of measure is (nV/sqrt(Hz))^2.

Current equivalent generator

In this case, the input is floating, so that the voltage noise equivalent generator has no effect. Then the computations are the same than in the case of the voltage generator.

 However, there may be situation where the circuit is "bad", like in the image below. In fact, Iin pumps into a high impedance node, infinite impedance, so that node moves to infinite voltages, so the contribution is really dramatic. So we introduce a high value resistance, we don't consider it infinite.




Of course, only in this case the equation could diverge and we need to introduce the resistance R^* . Then we have to compute the limit.

$$\begin{aligned} \text{Out } p_{rms} &= (V_2 \cdot 11 \cdot 396)^2 + (V_3 \cdot 10 \cdot 396)^2 + (V_4 \cdot 1 \cdot 396)^2 = 50 \mu\text{W} \\ \text{Out } p_{rms} &= \frac{i_n^2}{\Delta f} \cdot R^2 \cdot 11 \cdot 396^2 \\ \lim_{R^* \rightarrow \infty} i_n^2 / \Delta f &= \left(\frac{50 \mu\text{W}}{R^* \cdot 11 \cdot 396} \right)^2 = \emptyset \end{aligned}$$

We see that in this circuit, just by chance, the current equivalent noise generator has no effect. Hence this specific circuit can be modelled with just one noise equivalent generator, but this is just by chance. In fact, if we had considered the noise bias current of the opamp, the limit would be different from 0.

Once we have the two noise current generators we can compare them to our source. The source will have its resistance R with its noise and the input generator; I can forget about the rest of the circuit and consider just the following.

 We want to compute the Thevenin equivalent of this circuit; in this way we achieve the equivalent input source, the one in red, where the total noise is not just the noise of the source itself, but we have also the contribution due to the current and voltage noise equivalent generators.



The new equivalent noise generator will be the following.

$$\frac{V_{in, tot}^2}{\Delta f} = 4kTR + \frac{V_n^2}{\Delta f} + \frac{i_n^2}{\Delta f} \cdot R$$


SIGNAL-TO-NOISE RATIO AND NOISE FACTOR

MILANO 1803



Signal-to-Noise Ratio: $\frac{S}{N} = \text{SNR} = 10 \log_{10} \left(\frac{V_{in}^2}{V_{n,i}^2} \right) = 10 \log_{10} \left(\frac{V_{in}^2}{(4kTR_s + e_v^2 + i_n^2 R_s^2) \cdot \Delta f} \right)$

 Noise Factor: $F = \frac{\text{SNR}_{in}}{\text{SNR}_{out}} = \frac{S_i}{N_i} \cdot \frac{N_o}{S_o} = \frac{N_o}{G \cdot N_i} = \frac{\text{Total output noise}}{\text{Total output noise just due to } R_s} = \frac{\text{Total input noise}}{4kTR_s}$




Noise Equivalent Temperature: $T_{eq} = (F - 1) \cdot T_0$ just to tell how "hot" the noise is

The noise factor is given by the ratio between the total noise of the real circuit divided by the noise of just the source. Hence the noise figure is a mathematical number that compares the total noise of the circuit with the noise of the source. NF tells how bad the amplifier was in increasing the noise of the source. The extra noise added by the amplifier is a NF quantity higher than the source noise.

Recap

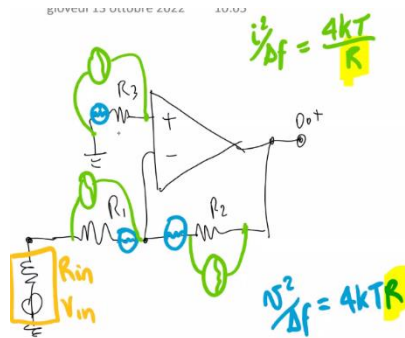
Given a real circuit, e.g. the one in the image, all the components are noisy and they can be described with their noise generator (either voltage or current noise). The PSD $i^2/\Delta f = 4kT/R$ for the current generator.




We can move from this circuit to another one, not considering all the components. As soon as I discover the output to be noisy, I want to change something to reduce the extra noise. But if I study all the individual components it is different to understand which components gives the noise \rightarrow let's move to the noise equivalent.

I want to consider the circuit to be noiseless because I computed the equivalent noise for all the noise source, and I get a voltage and current noise equivalent spectral densities. Then I attach the input (e.g. microphone) and I have to consider also the intrinsic noise of the source.

 
This second circuit is identical to the previous one.



If they are equivalent, we can stop at the input stage and avoid the opamp, considering only the source and the input stage. In studying this circuit I'm not committing any error, because the output noise is not needed to be computed, because if I want to compute the importance of the intrinsic noise of the source compared to the noise added by the amplifier it is enough to stay at the input stage \rightarrow we can forget what happens in the rest of the network (red part, R_1 is the input impedance).

 

 If we stop at the input we can compute the total input noise, considering the Thevenin equivalent of the circuit (not considering the rest of the network).



The one on the left is the total noise at the input, and it is mathematical, we cannot measure it, it is the one used to have the equivalent circuit to behave like the real one with all the noisy components inside. In fact, the equivalent input noise generators are a mathematical modelling, we have indeed the same output noise, but the noise I find at the input of the model circuit is higher than the one in the real circuit. So the noise we compute thanks to the equivalent is not real, it is just a modelling, the upper result is a model, we will never measure it in input of the stage.


This modelling is useful because it let us define some figures of merits, to understand if the amplifier is good for the application I want. I can define for instance the S/N.

SIGNAL TO NOISE RATIO

We cannot compute directly the ratio between the signal in V and the noise that is a spectral density, so we have to consider power both at the numerator and denominator.

What is the power of a sinusoidal signal whose peak is V_p ?

 If we compute the integral between 0 and T of the square, we get the rms value of the signal and to get the PSD we need to take the square root. So the power of the sinusoidal is equal to the peak value divided by sqrt of 2. It is an equivalent DC voltage with this value, it dissipates the same power of the sinusoidal with a V_p value.



$$S/N = (V_p/\sqrt{2})^2 / [(V_{total}^2)/\Delta(f)] * \Delta(f)$$


Once we find the input σ^2 we can compute the ratio.

So every time we have to compute the SNR we have to compute the $10 \cdot \log$ of the ratio between powers (to express it in dB). At the denominator I have the σ_{rms}^2 of the noise to the power of 2.

$$SNR = 10 \cdot \log_{10} \frac{(V_{in,peak}/\sqrt{2})^2}{\sigma_{rms}^2}$$

If instead of considering powers as above, we prefer to consider peaks or rms values of the input, we can do it, we can compare the input rms value with the noise rms value (green), that is sigma. In this case we have to consider $20 \cdot \log$, and I will get the same number.

27dB, for instance, means that at the input the signal is the black one and the noise is 3 mV rms, a factor 27dB lower than the signal.
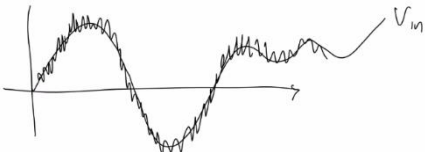
$$\begin{aligned}
 \text{SNR} &= 10 \cdot \log_{10} \frac{\left(\frac{V_{\text{inpeak}}}{\sqrt{2}}\right)^2}{\sigma_{\text{rms}}^2} = 10 \cdot \log_{10} \frac{(100\text{mV}/\sqrt{2})^2}{(3\text{mVrms})^2} = 27\text{dB} \\
 &= 20 \log_{10} \frac{V_{\text{inpeak}}/\sqrt{2}}{\sigma_{\text{rms}}} = 27\text{dB}
 \end{aligned}$$


However, the SNR considers the full noise, so it doesn't tell me how much the signal is bad, since it considers the source noise and the amplifier together. So it is better to define the noise factor, which compares the intrinsic noise of the source with the one of the amplifier.

NOISE FACTOR

It can be computed at the output or at the input, it is the same. It is the total noise at the numerator divided by just the noise of R_s .

$$\begin{aligned}
 \text{NF} &= \frac{\text{total noise}}{\text{noise of just } R_s} = \frac{4kTR_s + \frac{v_n^2}{\Delta f} + \frac{i_n^2}{\Delta f} \cdot R_s^2}{4kTR_s} \\
 \text{NF} &= 10 \log_{10} \left(1 + \frac{v_n^2/\Delta f}{4kTR_s} + \frac{i_n^2/\Delta f}{\frac{4kT}{R_s}} \right)
 \end{aligned}$$

Then we have the **Noise Figure**, that is the dB version of the noise factor.

If we buy an amplifier with no noise, $\text{NF}_{\text{ideal}} = 1 = 0 \text{ dB}$. It means that the amplifier is not introducing any noise.

Instead, $\text{NF} = 4 = 6 \text{ dB}$ means that $10^{(6 \text{ dB}/10)} = 10^{0.6} = 4$ it means that the number in the parenthesis is 4, so the amplifier introduces a noise equal to a factor 3x compared to the noise of the source (microphone).

So if e.g. $R_{\text{in}} = 1\text{k}$, the intrinsic noise is $4kTR = (4 \text{ nV}/\sqrt{\text{Hz}})^2$, but the total noise will be the intrinsic noise multiplied by 3 due to the amplifier plus the intrinsic noise of the resistor, that is in the end the intrinsic noise multiplied by 4.

So the noise figure defines how good is the input with respect to the amplifier.

The noise figure relies on R_s , that is a real number, T that is the temperature and on noise spectral density that are mathematical values obtained studying the ideal circuit. So the NF can never be measured, it can

just be calculated. In reality, despite being the passage just mathematical, the noise figure can be measured.

We have a real circuit, and all the resistances are noise. Let's measure the SNR_{in}, that is equal to the signal divided by the noise, and the SNR_{out}.

If everything were ideal, the output noise should be equal to the input noise, but it is higher because the amplifier adds a contribution.

We can compute SNR_{in}/SNR_{out} = S_{in}*N_{out}/N_{in}*S_{out} = N_{out}/(N_{in}*G), where N is the noise.


N_{out} is the total output noise, and N_{in}*G is the output noise just due to R_{in}, so we are getting NF.

So NF has a mathematical equation but we can also measure it measuring SNR_{in} at the input, SNR_{out} at the output and then performing the ratio.

NOISE EQUIVALENT TEMPERATURE

Moreover, the input microphone (source) has its R_{in} and related noise, but instead of the noise 4kTR related to R_{in}, let's consider the total noise adding also the amplifier contribution. Now the resistor is noisier wrt the simple resistor.

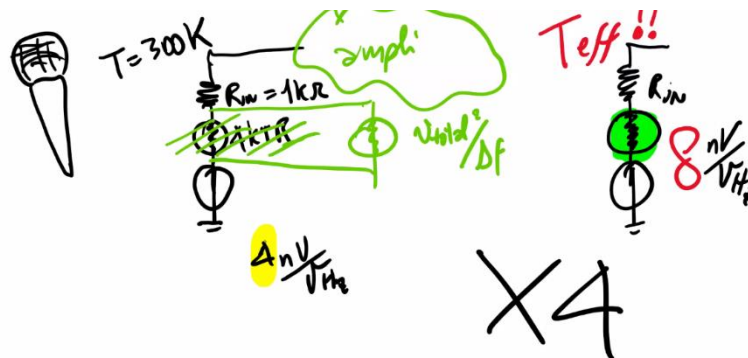
This means that my resistor has a higher noise, so the resistor is not like at T = 300 K as it was alone, but it is at a higher T_{effective} (T_{eff}). If previously it was at 4 nV/sqrt(Hz), since we are a factor 4 (in terms of power) of improvement and since the rms is the sqrt of power, we get 8.



So the amplifier at 300K is so noise when connected to the amplifier as if it was alone at 900K.

NOISE FIGURE - Computations

 Noise Figure:
$$NF = 10 \log_{10} \left(\frac{4kTR_s \Delta f + \langle v_i^2 \rangle + \langle i_i^2 \rangle R_s^2}{4kTR_s \Delta f} \right) = 10 \log_{10} \left(1 + \frac{\langle v_i^2 \rangle}{4kT \Delta f} \cdot \frac{1}{R_s} + \frac{\langle i_i^2 \rangle}{4kT \Delta f} \cdot R_s \right)$$



Minimum at:

$$R_{s, opt} = \sqrt{\frac{\langle v_i^2 \rangle}{\langle i_i^2 \rangle}}$$

$$NF_{opt} = 10 \log_{10} \left(1 + \frac{\langle v_i^2 \rangle}{4kTR_{s, opt} \Delta f} + \frac{\langle i_i^2 \rangle R_{s, opt}}{4kT \Delta f} \right) = 10 \log_{10} \left(1 + 2 \cdot \frac{\sqrt{\langle v_i^2 \rangle \cdot \langle i_i^2 \rangle}}{4kT \Delta f} \right)$$

Let's draw the noise figure, that is the one enlightened in yellow. The first term decreases with R_s , while the second one increases with R_s . When the first term prevails and it's much higher than the other, 1 is negligible and also the last one, and this happens for low value of R_s .

For low values of R_s , we have a high number in the parenthesis related to, so the equivalent voltage noise of the amplifier gives the major contribution, whereas for high values of R_s the other terms becomes dominant. At low R_s , NF decreases as 45° , at high R_s it increases with 45° (factor 10 dB).


The optimal R_s can be found by computing the derivative. If we do the ratio of the equivalent voltage and noise generator and we take the square root we get the optimal R_s . Then we can also find NF optimal, in which contribution x and x will be the same.

In the end, the amplifier itself with all its noise is equivalent with a voltage equivalent and a current equivalent and I attach them to the input where I attach also the microphone (source). Let's suppose current equivalent is $10\text{pA}/\sqrt{\text{Hz}}$ and voltage is $5\text{ nV}/\sqrt{\text{Hz}}$, and if $R_s = 1\text{k}$, noise of it is $4\text{nV}/\sqrt{\text{Hz}}$.

Let's plot the noise figure.


$$NF = 10 \cdot \log_n \left(1 + \frac{(5\text{nV}/\sqrt{\text{Hz}})^2}{4kTR} + \left(\frac{10\text{pA}}{\sqrt{\text{Hz}}} \right)^2 \cdot \frac{R}{4kT} \right)$$

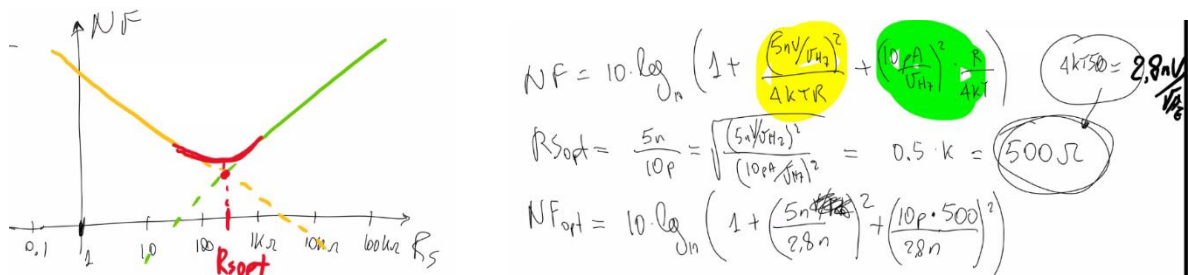At low values of R_s the second contribution is the most important one, whereas for high values it is the last one.




We discovered that the NF has the trend in the left image.

 
If for instance we use a resistor smaller or greater than the $R_s = 500\text{ Ohm}$ optimal. Nevertheless, the amplifier gives $5\text{nV}/\sqrt{\text{Hz}}$ and $10\text{pA}/\sqrt{\text{Hz}}$. Without the amplifier



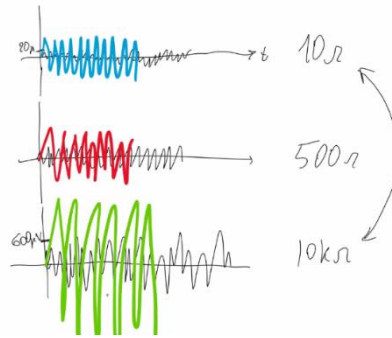If then we connect the amplifier, the real noises are:




The ratio between the real value and the ideal value is in the R_{opt} case. If we choose a resistor too low, the problem is that we have a high noise, we are not decreasing it. The same if the resistor is too high. At $R_{s,opt}$ we can pretend the noise to increase by a factor 2, whereas in the case of too low R , the ratio between ideal and real is $\times 10$, and $\times 12$ with a too high resistor.

 

TOTAL INPUT NOISE

Total input noise (no R_{in}):
 
$$S_{in}(f) = 4kTR_s + e_v^2 + i_i^2 \cdot R_s^2$$



**NF shows how electronics worsens the intrinsic noise of the source
NF is NOT a signature of the total noise !**

The minimization of the noise factor does correspond to the minimization of the noise? No, because the total input noise is equation x. If we plot it, the total input noise is the noise of the resistor plus the noise of the amplifier plus the current equivalent noise of the amplifier multiplied by R_s^2 . e_v is not depending on r , so it is constant, then the resistor contribution that increases with R_s and the current contribution that increases as R_s^2 .


When the two contributions touch, we get the $R_{s,optimal}$, and where the total noise gets as close as possible to the ideal noise. The minimum noise is towards $R_s = 0$ because we have only the equivalent

voltage generator, and the current generator gets killed by the shortcircuit, and it remains only the voltage noise generator. If instead we move toward very high values of R_s , then the contribution that dominates is the current noise generator, the other two are negligible.

The minimization of the noise figure is to choose the source R as similar as possible to $R_{s,opt}$ if we have to choose the amplifier. Conversely, if the input is already defined, choose the amplifier so that its noises (current and voltage) in ratio are in the order of R_s of the source. If so, the total output noise from the system has an extra contribution from the amplifier is minimum with respect to the one from the source.

Instead, to reduce the noise in output from the amplifier, choose an R_s that is very very low. The lower R_s gets, the lower the noise becomes, saturating to the equivalent input voltage noise of the amplifier.


Example 1

 

MOS (dashed lines) and BJT (solid lines) transistors at $I_C=I_D=1\text{mA}$

 
- a) Draw the NF plots vs. $R_s=10\Omega\text{--}10\text{M}\Omega$, at 10, 100, 1k, 10k and 100kHz
- b) Select the lowest noise transistor for $R_s=10\text{k}\Omega$

We have two transistors; solid lines are voltage generator and current generator for BJT, dashed for MOSFET. The voltage noise generator for the BJT is lower than the one for the MOSFET and white. Instead, for a MOSFET transistor, since the gate current is low, the current noise generator is lower. The current generator for the BJT is higher, I can see some flicker noise. As for the MOS, since the gate current is ideally 0, the shot noise should be lower but as for the voltage noise at the input it is higher. Moreover, MOS transistors have a higher Flicker noise in terms of voltage.



 - a) If we consider the BJT transistor, I can see that we have 1nV and 1pA, with 10pA of flicker noise in current. The value in the middle part is half of a decade, since we are in a log-log plot, so it is $\sqrt{10}$. Now let's draw the noise figure; we have to compute $R_{s,opt}$ and NF_{opt} . $R_{s,opt}$ depends on V_{in} and i_{in} , as seen before. Let's consider the point at 10 Hz; it is 1nV/10p, so 100Ohm.


Then the noise figure in the green points for the current noise is always the same, and there $R_{s,opt} = 1k\Omega$.



Then we can compute the NF_{opt} . $NF_{opt} = 10 \lg \left(1 + 2 \left(\frac{A_n \cdot L_n}{4kT} \right) \right)$

$NF_{opt} = 1.2dB$, and $R_{s,opt} = 100\Omega$.

 The last ratio in the parenthesis has a different value depending on the chosen point. For high values of R_s , we can find a point, the same for low value of R_s and then knowing the trend of the curves we can plot the value of NF .




So we compute $R_{s,opt}$ and NF_{opt} and then we choose values of R_s smaller and bigger than $R_{s,opt}$, we compute the NF value. E.g., in the case of $R_s = 100k\Omega$ it is the following.

$$NF = 10 \lg \left(1 + \left(\frac{1n}{40n} \right)^2 + \left(\frac{10p \cdot 100k}{40n} \right)^2 \right) \approx 28dB$$


Then we repeat the same procedure but with a lower value of R_s , e.g. 1Ω , and we put another point in the NF vs R_s plot. Then we go down by 45° and the two trends will cross in correspondence of $R_{s,opt}$.

 The yellow portion depends on the current, while the pink portion depends on the voltage.




When we move alongside a plot of the noise current where it is the current that changes, the right shoulder of the NF plot decreases and it is shifted downward if the noise current is decreasing (e.g. in the case of the BJT from the black to the green points). Hence if we increase i_{in} noise, the $R_{s,opt}$ decreases.

If we want to compute the total noise, we may be in the case where v_{in} is constant, then we have the effect of $i_{in} \cdot R_s$ and then $4kTR_s$ (upper image). Otherwise, we can have also the case in the bottom image, is i_{in} is very low. In the first case the total noise is almost given by v_{in} and i_{in} , in the bottom case $4kTR_s$ appears in a certain region, so the position where we have the minimum distance between noise and R_s is different. So the noise figure (pink) is different, and the minimum noise figure is lower.

 


If we plot the NF in the two cases, V_{in} is the same, so the left shoulder is the same. What changes between the two is the right shoulder.

 I can confirm that the NF in case 2 is lower than NF optimum in case 1, simply because i_{in} decreased.




Better to change the amplifier or the source?

 
Now, I bought an amplifier, the microphone with 1k resistance (not the ideal 500 Ohm). Due to the V_{in} and I_{in} of the amplifier I discover that the curve is the yellow one, but R_{in} is not the optimal one. We can hence change the amplifier so that we center V_{in} and I_{in} to have R_{opt} in correspondence of R_{in} or we can change R_{in} .



 Since we are on the right part of the plot, is I_{in} to be reduced so that R_{in} eventually is in correspondence to R_f . However, we will never be able to go to negative values of NF, the limit is 0 dB (we have $1 + \dots$ in the parenthesis).



NOISE IN DIODES

 

$$\langle v_s^2 \rangle = 4kTr_s\Delta f \quad \langle i^2 \rangle = 2qI_D\Delta f + K' \frac{I_D^a}{f} \Delta f$$




$$S_{out} = 2qI \cdot \frac{(1/g_m)^2}{(1/g_m + R)^2} + \frac{4kT}{R} \cdot \frac{R^2}{(1/g_m + R)^2}$$


$r_D = 1/g_m$ is NOT noisy... but it seems so: $\langle i_s^2 \rangle = 2qI_D\Delta f = 2q \frac{kT}{kT} I_D\Delta f = 4kT \left(\frac{1}{2g_m} \right) \Delta f$

Equivalent Noise Resistors: $R_{eq,I} = 2 \cdot \frac{1}{g_m} \quad R_{eq,V} = \frac{1}{2} \cdot \frac{1}{g_m}$

 I may have a situation where I pump a current in a diode. The diode has a drop of 0.6V across it and I know the typical V-I curve of a diode. But if the temperature changes of light, the current voltage characteristic may drift.



 
When we operate a diode, we operate in a specific working point, and then we perform the small signal analysis around that point. And the resistance of the diode is the tangent of the curve in the w.p..



Hence a diode can be model with its $1/g_m$ but also a parasitic real resistance r_d . r_d is a real resistor, while $1/g_m$ is a small signal parameter.


There is a current generator in the diode model due to the current that flows in the junction and it is a shot noise $2qI$, where I is the polarization current. Then there is also the thermal current noise due to the r_d component (or we can also consider its voltage noise). More precisely, the I of the shot noise considers also the Flicker noise, but we can neglect it by now and consider only the two white noises.

 Let's compute the noise of the diode that enters in the amplifier. The amplifier has its internal R and I want to know the current that enters in the amplifier, to then retrieve the noise. We apply the principle of superposition of effects.




The total noise that enters in the amplifier is given by the yellow formula. The I and r_d to be used in the diode as to be chosen carefully. It is not true that if I and r_d both increase the noise increases. In fact,

 These are the golden rules if we are measuring the diode with a transimpedance amplifier (left case). Instead, in the right case it is important to increase I and decrease r_d .




The left case is called **photocurrent mode** (we set the voltage to be constant), while the one on the right is called **photovoltaic mode** (we set the current to be constant).

 We can also use another approach, operating the diode in the reverse bias regime (left) or in a circuit where the current I is equal to 0 (forward bias and no current at all).



Shot noise remark

 
Shot noise is $2qI$, but if I multiply and divide by kT , $kT/q = V_{th}$ and $V_{th}/I = 1/g_m$.



So it seems that the shot noise is equivalent to the noise of a real actual resistor whose R should be equal to $2 \cdot (1/g_m)$. This is, however, from a mathematical standpoint \rightarrow shot noise can be modelled as a thermal noise.

Example 2

MILANO 2893

 

OpAmp: $A_0=100\text{dB}$, $\text{GBWP}=10\text{MHz}$, $4\text{nV}/\sqrt{\text{Hz}}$ and $5\text{pA}/\sqrt{\text{Hz}}$ noise

- a) Compute output rms noise, with trimmer's cursor at the two ends
- b) Discuss the role of the $1\text{k}\Omega$ resistor


Resolution

The potentiometer can be either to 0% or 100%.

0%


In this case we have that with 0.6V across the diode we will have 4.4V across the 470Ohm resistance and so a current of 9.4 mA in the diode.

 Now let's introduce the diode, that can be modelled with its r_d in series with its noise generator, then $1/g_m$ and the corresponding shot noise in parallel to it. $1/g_m = V_{th}/I_d = 25mV/9.4mA = 2.7 \text{ Ohm}$



If $r_d = 10 \text{ Ohms}$, $4kTr_d = 0.4 \text{ nV}/\sqrt{\text{Hz}}$.

 
Then we go straight into the opamp and then we have the cursor, so let's consider the case where it is at $x = 0$. We can write the noise for these resistors.



We know the opamp will be compensated, so the second pole will be after the GBWP. The beta of this configuration is $1/4.7$, so the $1/\beta$ is 4.7.


So the circuit has a bandwidth set by f^* . So if in this configuration (non inverting), the gain will be 5.7 and then at f^* I die as Gloop dies. From user standpoint the circuit has a pole at f^* and one where the second pole of the opamp is.

 - a) We have 5 contributions to the noise, let's consider them all. Let's consider the power two of the output rms, that is the sigma squared out. When we study 2.8nV contribution noise, it won't go directly to V+, because it is in series with the resistors (not other generators, they are not active), so we need a voltage partition. Then I multiply by 5.7^2 that is the gain of the stage.




To be coherent, I know that we have all squared, and we have a noise spectral density, so we should multiply for the noise equivalent bandwidth. Which has to be computed. In the case of one single pole, the noise equivalent BW is the pole of the real circuit multiplied by pi/2. This is the first contribution of the first noise source. Then I have to consider the 0.4nV generator, then I multiply by the gain and the equivalent bandwidth.

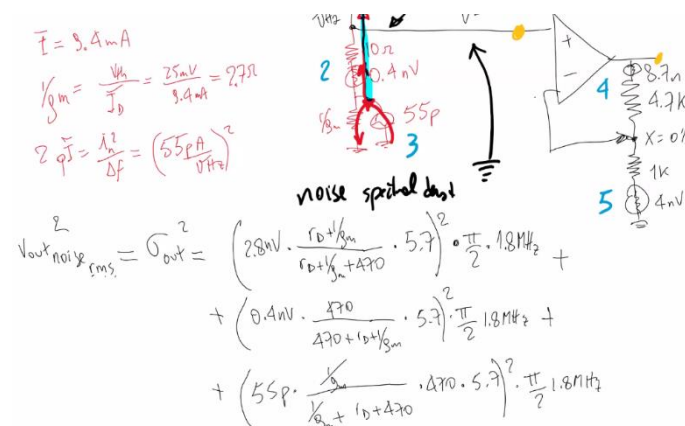
Then we have the current partition for the last generator, 2qI.



For the 4th contribution, the other noises are off, so V* (V+) is 0, so no current flows in the branch where we have 1k, so the 8.7nV appear straight at the output of my stage. The I have to multiply by the bandwidth. For this, we have to consider the behaviour of the circuit when the input is not the classical input, but the input is the 8.7nV generator. F* is the same as before, and for generator 4 the real gain is 1 up to f*, firstly with 20db. So for the user the pole is at f* again (1 is the ideal gain of this generator to the output).

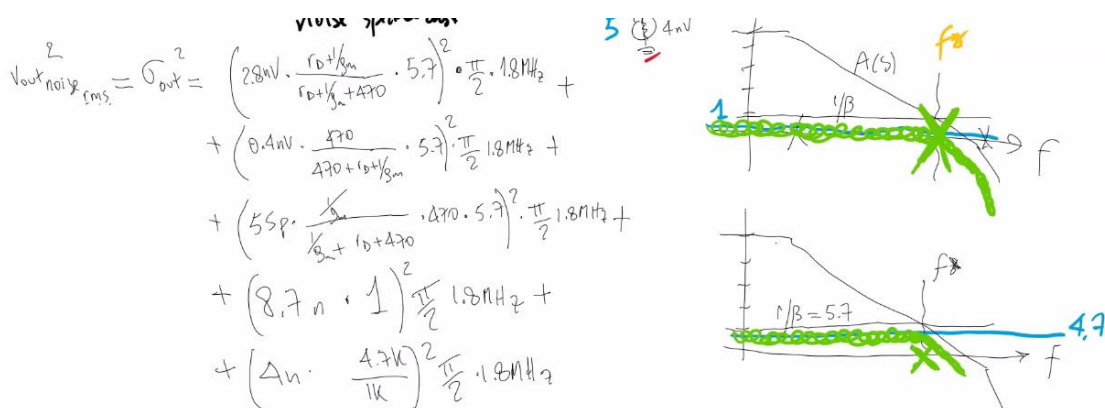

 As for the 5th generator, it is an inverting gain stage. Then the equivalent bandwidth, even for this generator is at f^* (ideal gain is 4.7, then we plot $A(s)$ and $1/\beta$ that is 5.7. Again, the pole is still f^*).



To complete the calculations, let's put numbers paying attention to what is negligible with respect to something other.

$$V_{out\ noise\ rms}^2 = \sigma_{out}^2 = \bullet \left(2.8nV \cdot \frac{4.7k}{4.7k + 470} \cdot 5.7 \right)^2 \cdot \frac{\pi}{2} \cdot 1.8MHz = (431n \cdot 168)^2 = 725 \mu V_{rms}$$

$$\bullet \left(0.4nV \cdot \frac{470}{470 + 168} \cdot 5.7 \right)^2 \cdot \frac{\pi}{2} \cdot 1.8MHz = (2.3n \cdot 168)^2 = 3.8 \mu V_{rms}$$

$$\bullet \left(55p \cdot \frac{4.7k}{4.7k + 470} \cdot 5.7 \right)^2 \cdot \frac{\pi}{2} \cdot 1.8MHz = (0.8n \cdot 168)^2 = 1.4 \mu V_{rms}$$

$$\bullet \left(8.7n \cdot 1 \right)^2 \cdot \frac{\pi}{2} \cdot 1.8MHz = (8.7n \cdot 168)^2 = 14.6 \mu V_{rms}$$

$$\bullet \left(4n \cdot \frac{4.7k}{1k} \right)^2 \cdot \frac{\pi}{2} \cdot 1.8MHz = (18n \cdot 168)^2 = 31.6 \mu V_{rms}$$

So the final remaining contribution is slightly higher than the dominant one (725).


$$\sigma_{out\ noise} = \sqrt{(725 \mu V)^2 + (3.8 \mu V)^2 + (1.4 \mu V)^2 + (14.6 \mu V)^2 + (31.6 \mu V)^2} \approx 726 \mu V$$

So when $x = 0\%$, Gain = 5.7 and $\sigma_{rms} = 0.7$.


So to reduce the output noise we don't change resistor, noise or current, but we have to change the 470 ohm resistance. If we change it, the current changes. To reduce the contribution of it, I have to reduce the value properly. A possible solution to reduce the value but having the same current is also to reduce the power supply.

Even better, we can change the circuit. Instead of using a resistor to bias the opamp, which has a high thermal noise, we could use a pnp transistor as a current source. If we have a transistor with a beta of 100, it means that $I_b = 9.4m/100$, so we need a base current of $4.4/100 * 9.4m$.

 However, also this current generator has to be modelled with its shot noise of $2qI$. And also the resistor on the base has a noise to be considered.



 
However, 470 ohm was also at the denominator of the voltage partition related to the noisiest generator. This means that probably the reduction of the resistance is not enough. Maybe it is better to increase the 470 resistance instead of decreasing it. Let's see what's better.



If we reduce too much 470, the noise generator reduces, but the other contributions take into account. If we instead increase 470, we can have it still dominating, but at the same time, thanks to the power 2, the increase in 470 reduces the noise.

100%

 
We have to consider a brand-new circuit. The two resistors at the output are in series so they act as a 4.7+1 = 5.7k resistor.



- a) All the contributions to V^* are the same as before. We have just to consider the contribution of the 5.7k resistance. It is zero because if we turn off all the left part, $V^* = 0$ and $V_{out} = 0$, so the resistances are between grounds and their contribution is nihil. The current noise flows inside the opamp and it is the opamp that swallows it. Hence noise is much smaller than before.


$$\begin{aligned}
 X=0\% & \quad G_{an} = 5.7 & \quad \sigma_{rms} = 0,7 \text{ mV}_{rms} \\
 X=100\% & \quad G_{an} = 1 & \quad \sigma_{rms} = 0,050 \text{ mV}_{rms}
 \end{aligned}$$

- b) The role of the 1k resistor is the following. Let's consider a configuration as the following. We run the risk that when the potentiometer is at $x = 0\%$, we are at ground, so the gain is infinite, so we add a resistor at the bottom of the trimmer so that the gain remains finite (REG, change image).

 

Example 4

NICO
13

 

OpAmp with $v_{in}^2/\Delta f = (8nV/\sqrt{Hz})^2$ and $i_{in}^2/\Delta f = (0.5pA/\sqrt{Hz})^2$


- Compute the noise equivalent for input V1
- Compute the output rms noise

Now also the opamp is noisy.

Resolution


Let's redraw the circuit adding the noise sources.

- The opamp has current sources.

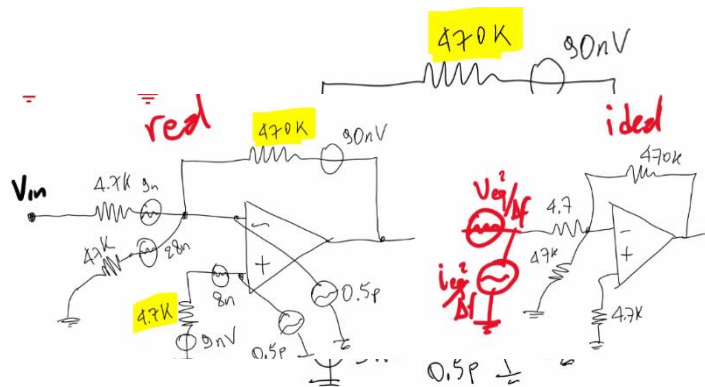


I want to study the real circuit to compute the voltage equivalent and current equivalent generators to be placed at the input and get an ideal net.

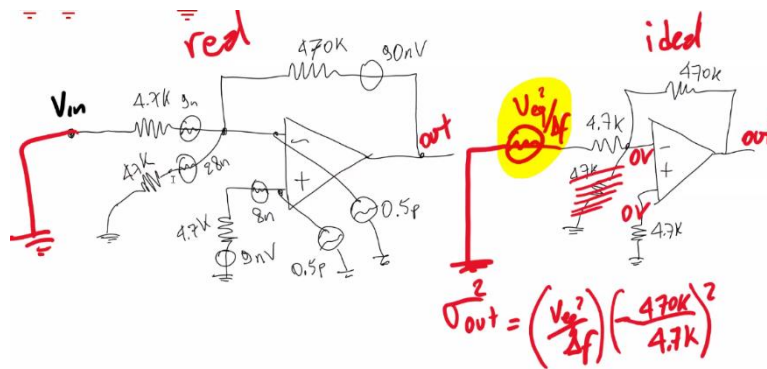To compute V_{eq} , let's connect the input of the two networks (ideal and real) to ground. Thus I can forget the current equivalent generator in the ideal circuit. Then in both circuits I compute the total noise at the output and then I compare the two values.




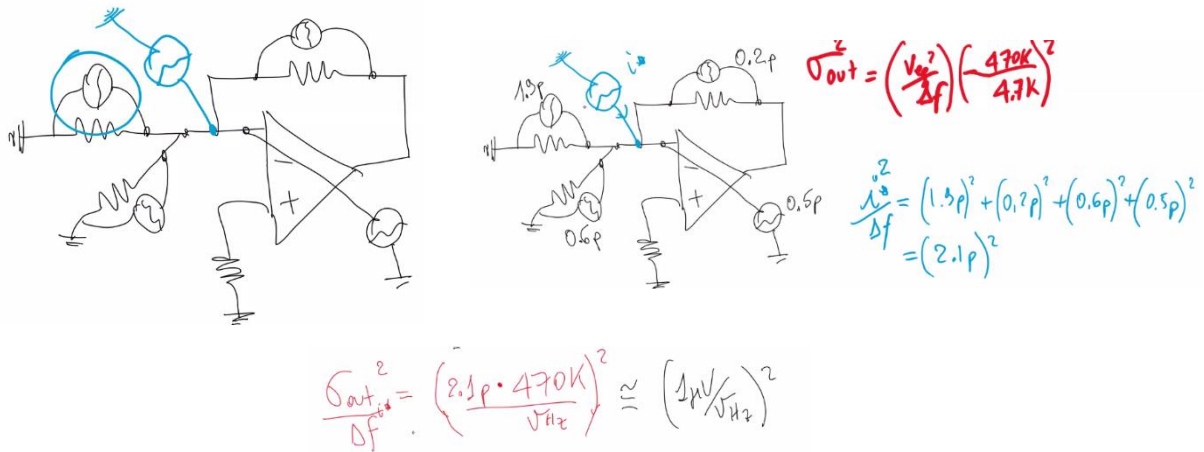Now let's study all the noise sources for the real circuit. Sometimes, it is better to consider the current noise generator instead of the voltage noise generator. Because of how the network is build, I can consider a unique current generator given by the sum of all the power current generators.



Then I compare this last result with the previous result from the ideal circuit, once also the other input is computed.

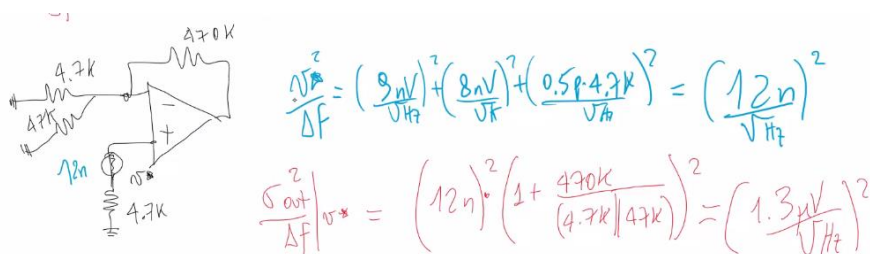Now let's consider the noise sources related to the input +, because so far I've analyzed only the - terminal input. Then I compute the output noise due to V^* .




In total, in the real circuit: $\sigma_{out}^2 / \Delta f = \left(\frac{1.3\mu V}{\sqrt{Hz}}\right)^2 + \left(\frac{1.3\mu V}{\sqrt{Hz}}\right)^2 = \left(\frac{1.6\mu V}{\sqrt{Hz}}\right)^2$

This is the total output spectral density due to the real circuit, and we also have the one in the ideal noiseless model and now we need to equate them.

We have now to compute the current equivalent generator. In the real circuit the reasoning is the same, I put all the noise generators as current and then all in parallel. But in this case the input is floating, so the 4.7k resistor is not playing a role because floating.

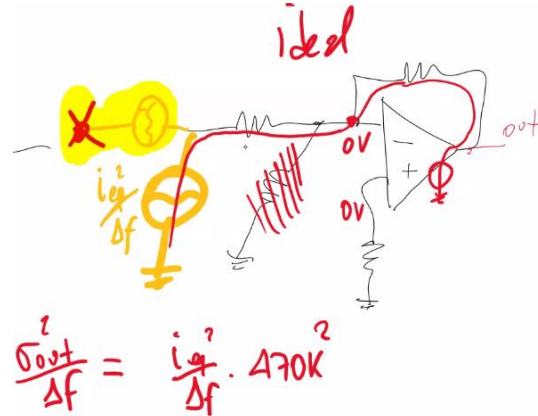Firstly, let's reason on the ideal network.




Now let's compute the real noise. The part related to the + terminal remains the same in terms of noise voltages. Instead, the macro noise current generator cannot be used, because the input is floating and so the related current noise generator must not be considered. Also the gain of the stage changes.


$$\begin{aligned} \frac{i_g^2}{\Delta f} &= \cancel{(0.2p)^2} + (0.6p)^2 + (0.5p)^2 = (0.8p)^2 \\ \frac{\sigma_{out}^2}{\Delta f} &= \frac{i_g^2}{\Delta f} \cdot 470K^2 + (12n)^2 \left(1 + \frac{470K}{47K}\right)^2 = (0.8p \cdot 470K)^2 + (132n)^2 \\ &= \left(400 \frac{nV}{\sqrt{5Hz}}\right)^2 \\ \frac{V_{eq}^2}{\Delta f} &= \left(\frac{400nV}{\frac{V_{Th}}{470K}}\right)^2 = (0.85pA_{V_{Th}})^2 \end{aligned}$$

Now we can compare the noise of what we connect (the source) with the input equivalent noise generators and then we can compute the NF.

 NB: if one of the two inputs, either V1 or V2 is detached, the corresponding resistance will be floating, and the overall noise will be lower.




NOISE IN OPAMPS

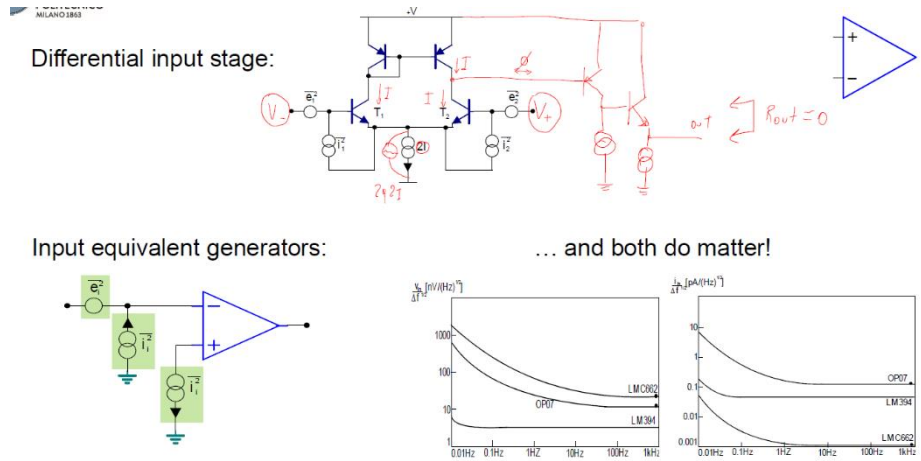

In an opamp we have BJT or MOS transistors, and each component has its noise. This is the reason why we compute the current and noise voltage generators for the opamp. Since we have two inputs, we have two voltage generators and two current generators. Then the two voltage generators are in series, so it reduces to one in the final representation.


The noise of each passive component attached to the opamp is then added to the equivalent noise current or voltage generator at the input of the network. However, in doing so, we are theoretically over-estimating the noise because we consider the same passive components twice for each generator (e.g. for the feedback resistor).

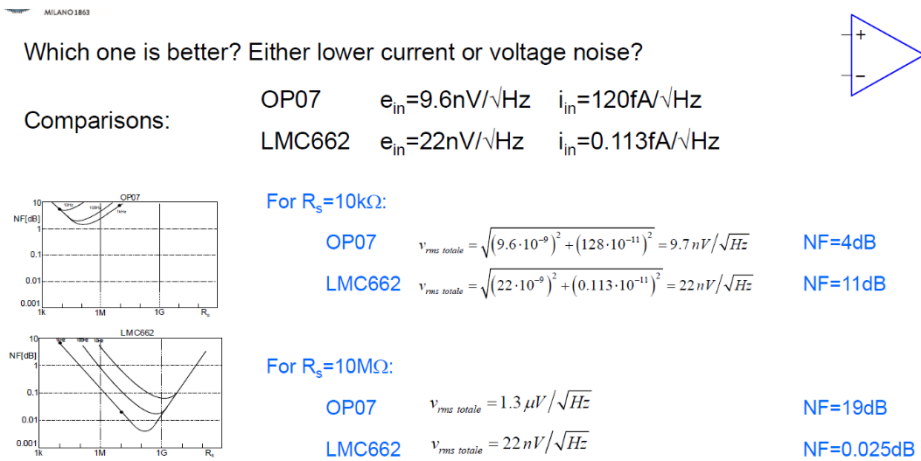On the market, we find different opamps, quoted in terms of equivalent voltage or current noise generators. In general, BJT opamps have a higher current noise with respect to MOS ones, but then the trend is opposite for the voltage noise.



To choose the better, we should place the opamp in the real circuit and then compute all the noise figures. So for low value of R_s the first one is better, whereas for high values the other one is better. So depending on the circuit, the voltage or current noise of the opamp matters more or not.

 Let's consider a simple buffer to which we connect our microphone with V_{in} and R_s . If we study the total noise of the circuit, we realize which R_s is better, and it depends on the noise figure (the red distance). Where we have the minimum distance between the total noise and the R_s noise gives the $R_{s_optimal}$.




If i_{in} increases, its shoulder (right one) will shift upward. The same applies for the left shoulder of NF if V_{in} increases.

INSTRUMENTATION AMPLIFIER – INA

DIFFERENTIAL AMPLIFIER


We have two sources and we want to compute the difference.

 The signal that gets positive amplification is that with R2 to ground and in the + terminal.




The problem of that in this circuit the input impedance is not infinite.

 
Let's consider a LDR. A possible way to amplify a voltage signal is to use an amplifier.




But now the issue is different because in the real circuit the current generator is not where we have the sensor, and the same for the sensor. But in this case there may be a series resistor in series with a wire and so the current generator is giving current not just to the sensor, but also there is a drop on the cable resistances. So instead of seeing 50mV I see 59mV, but this gives an error in reading the temperature.

 

So this two wire configuration is not good. Better to use the 4 wires configuration. One wire is used to pump current in, one is used as ground (I sink current out from this wire) and the other two are used to measure voltage difference. Now we have a voltage drop across the two power wires, but no voltage drop on the wires used to read the voltage of the sensor. This is true if the voltage difference amplifier, with infinite input impedance.

 

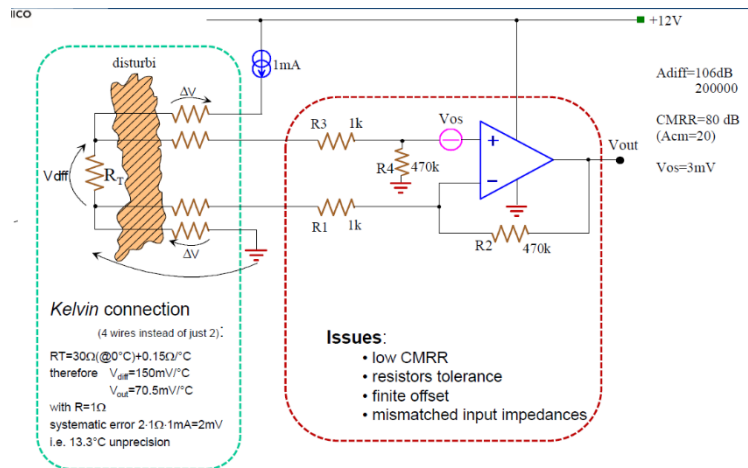
So the classical differential amplifier is not good.



If we have inputs with different source impedances, the problem is that even though the input voltages are the same, also because the input impedance of the amplifier are finite, the output is not 0.

So we could in principle use a buffer between the source and the input terminals of the differential amplifier. However, we have another problem, because the buffer are noisy, so the same noise is also at the output at the buffer, whose gain is 1, and then will be amplified by the next stage.

 
So let's put an amplification instead of a simple buffer.



This is good because if R1 are noisy, thanks to the amplification, the input source noise gets so amplified by the first stage that the noise of R1 becomes negligible.

But then, there is another issue. If the signal has a common mode CM, typically we want to amplify the differential mode and not the common one, but with the upper circuit we amplify both, so if the input signal increases too much, we saturate the first stage.

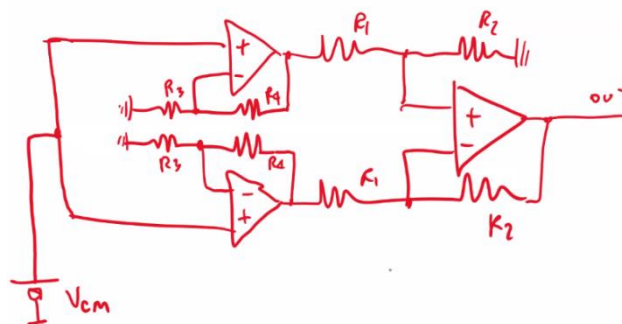Let's apply a common mode signal to the next circuit. The output of the opamps of the first stage will saturate, so the output signal will be random and any differential signal won't be seen because of the saturation.




Hence in this case any differential input won't be seen to the output due to the fact that the V_{cm} saturates the opamp. To avoid the amplification of V_{cm} we connect the two R_3 resistors.

Let's connect the two resistors R_3 to V_{cm} . Now the common mode gain of the first stage is equal to 1, so we don't have saturation anymore. Let's apply now the differential signal. If it is like in the image, also for this case the gain is 1, so it is not good.


Hence the solution is to connect the R_3 resistances to the $-$ terminals of the opposite opamp because I don't want to touch the input to preserve its quality (differential signal). This is the ultimate connection. By doing so, the R_3 resistors are in parallel, and I can simply use one resistor R_g .

Thanks to this connection, the CM signal has a gain 1 in the first stage, and the second stage has a gain equal to R_2/R_1 . But since the two nodes in output of the first stage are equal, now the common mode signal in output is 0.

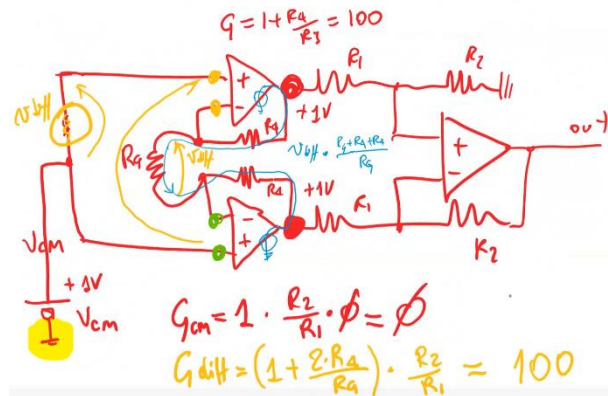As for the differential signal, thanks to V_G we are copying the values on the terminals of the opamps of the first stage, so we have a current in R_g that passes through R_4 and goes to the second stage.



 So we have a perfect rejection of the common mode.



Differential gain: $A = A_1 A_2 = \left(1 + \frac{2 \cdot R_3}{R_G}\right) \cdot \left(\frac{R_2}{R_1}\right)$


Common-mode gain: $A_{cm} \approx 0$

finite, accurate and reliable Gain
 twin extremely high input impedances
 extremely low output impedance
 extremely high CMRR


between 1 and 1'000
 > 10MΩ
 < 100Ω
 > 90dB

REFERENCE PIN

 Let's see how to connect to an external load. Let's imagine the V_{in} at the input is zero and also V_{cm} , because we want to study the gain between V_{ref} and V_{out} .




 Since the input stage is off, we have everywhere 0, so the inputs to R_1 are at ground. We can hence do the calculations. We end up having a gain 1 from V_{ref} to V_{out} .



Whatever we connect to the reference pin, the effect is to have an offset in the output equal to the V_{ref} . We can use the V_{ref} to apply a constant DC value to the output of the INA. Then if V_{diff} moves positive and negative, the amplified V_{diff} in output will be superimposed to the V_{ref} offset.

 A minor issue is that the impedance that we see from the reference pin is $R_1 + R_2$, so usually $R_1 = R_2 = R_f$ by the manufacturer, so the impedance we see is $2R_f$. If $R_f = 100k$, the impedance is $200k$, so we




cannot attach a voltage partition network to the V_{ref} pin without considering the resistance in input. If the impedance of the partition is smaller with respect to the $2R_f$, it goes in series with the $2R_f$ and negligible, but if it is big, to avoid any voltage drop due to different impedance it is better to use another opamp (buffer) to connect.


SENSE PIN

Whenever we apply an input signal V_{diff} , we can compute the V^* value and if sense is connected there, when V_{ref} is grounded, V_{out} is $V_{diff} * G_1 * G_2$.

 This equation holds whenever the sense pin is connected to the output. If the sense wire goes and touches another output, the gain of the stage is still independent on the A0 of the opamp and what we have after the output, because thanks to the feedback what sets the gain is REF.



This is the reason why the sense pin and the output pin are kept separated. So it is important to connect the sense pin to the point of the network where we want our amplified output. Of course, also the sense wire has a certain resistance, but the difference is that in the output wire a huge current flows and the voltage drop across the 10mΩ resistance of the output is high, but on the sense wire I have a small current because we have a 10mΩ in series with the 2Rf resistance seen by the sense pin (hundreds of kΩ), so the wire resistance is negligible.

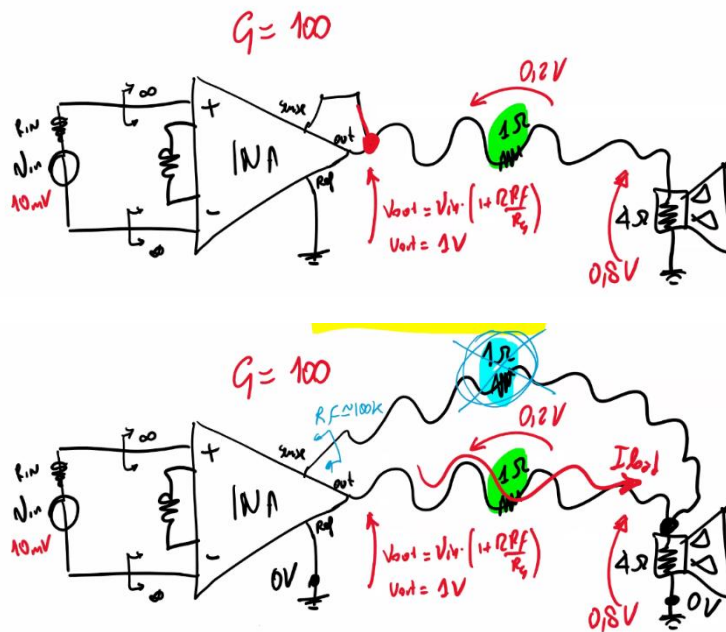


Moreover, if Vref pins are attached to two different ground, they are not exactly the same, so it is better to connect the two grounds also with the reference wire, because of the same problem of the voltage drop on the GND wire resistance.


We use the reference pin to go and touch the load as close as possible to solve this issue. In this way, we have something similar to the 4 wires connection.

Moreover, if we use the shield to reject EMI, for the EMI the output of the buffer used to drive the shield is ground, so we should be ok. The problem is that every time we have a wire connected to ground, the wire acts as an aerial.

 If the wire has a given length it receives all the EMI because it acts as an aerial, so it runs the risk of capturing EMI and the voltage of the source will be affected by disturbances. The best way to kill this disturbance is to connect to ground the source side of the cable but I cannot because I'm driving with V_{cm} from the Guard.



 What we can do is to connect a capacitor to the other side of the shielded cable, so that the other side's HF component are killed by the capacitor.




Quality of the signal has to be preserved because the INA has a huge gain, for signal even in the order of $10\mu V$, so any noise can have a huge effect on the output.

Missing guard pin

If however we have no Guard pin in the INA, we can do something different.

 To create a guard pin we can take the V_+ voltage and V_- that are copied across R_g , so we use two high value resistors in parallel to R_g and take the value in the middle of them, that then is buffered. The resistance must be huge not to change the value of R_g and hence the gain of the INA.




COMMUTATING AUTO-ZEROING

INA is usually used to achieve high gain, so I want the opamps in the INA to be very good opamps with low noise, offset and bias current. How can we buy an opamp with low offset?


There is a solution that is the **auto zeroing**.

We use a standard opamp even with a high offset voltage. We connect some components outside the opamp to measure the offset voltage and then subtract the offset voltage to the opamp itself.

 If the opamp is buffered and it has an offset:



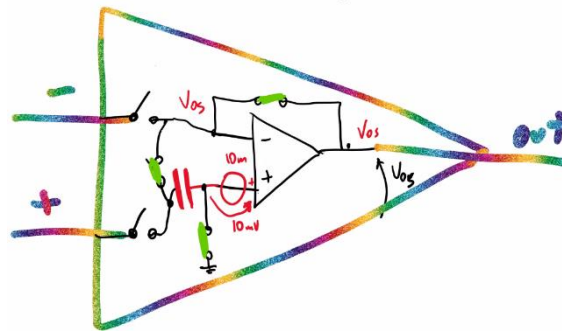
To subtract the offset I introduce switches and capacitors. I detach the input pins from the opamp itself. When they are open, I close the switch to ground and close the switch of the buffer. The output will reach the offset value. Then the Vos value in output that is buffered back is connected to a capacitor → I'm storing the Vos on the capacitor (I've closed the green switches).



After this, I reopen the green switches and close the input path switches. Now I have a capacitor that charges to Vos in series (with opposite sign) with the offset itself and hence the two cancels out. It is an approach used for the opamps in an INA.

EFFECTS OF MISMATCHES IN INPUT PATHS

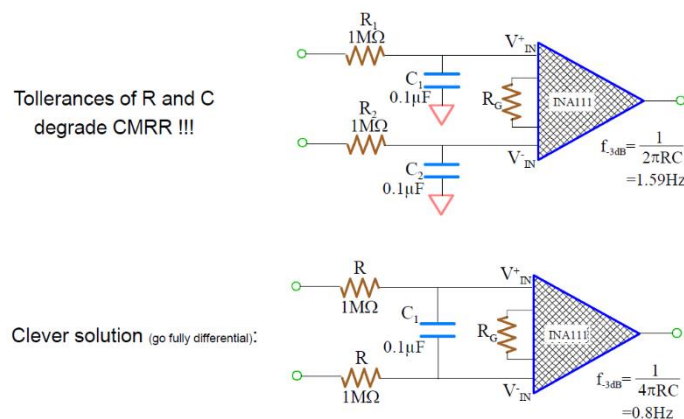In the INA we should also preserve the symmetry of the stages, in particular of the first one. Let's imagine now we want to introduce a LP filter before the INA. The first solution is a bad solution because the circuit is no more perfectly symmetrical.



In fact the resistances R have their tolerances, and in the worst scenario they move in the opposite direction. Moreover, also the capacitors have tolerances and everything. So in the first case one path will have a certain gain, and the other path a different one due to the tolerances of components. Ideally the paths are equal but they have minor differences and the poles move.


If the common mode is not DC and it moves, it is rejected by the INA of course, but if we have mismatches in the case of input the filtering action will be different and so a Vcm signal eventually appears at the input of the INA as if it was a differential signal. But then the INA amplifies this and hence we would see in the output of the INA something related to the Vcm signal.

So either we use very precise components (too expensive) or we change solution, shifting to the second one. The resistors still have some mismatches, but the new situation can kill the signal.

TIME VARYING MISMATCHES

If we buy a very low noise INA, when we assemble it on a PCB, the traces are made of copper, the pins are made of Kovar and then we use lead to solder. Since we are soldering two metal wires, every time we have this, if there is a difference in temperature between one soldering and the other soldering, due to Seebeck effect we generate a $V_{diff} \rightarrow$ thermocouple.

 
Time-varying mismatches (flicker noise, drifts, offsets) sometimes due to unexpected causes:




If the temperature on the pins of the INA is different, we create a differential imbalance in terms of voltage and hence even a small change in temperature on the PCB can cause an output in the INA, because the INA is very sensible.

DATASHEET

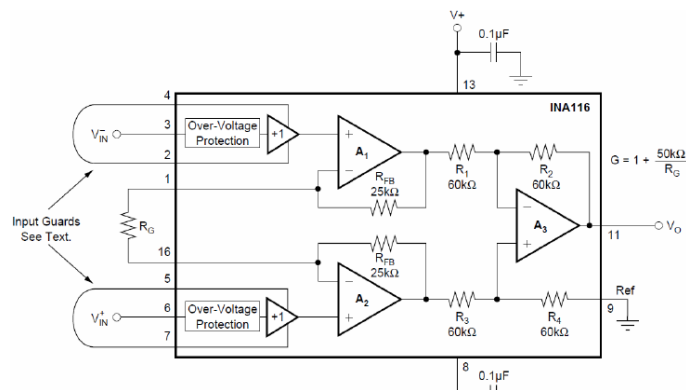We have name, image and suppliers name in it. Then there is a list of important features and a schematic of the inside of the component. Eventually, the manufacturer doesn't provide the sense pin, but sometimes we have an over-voltage protection.



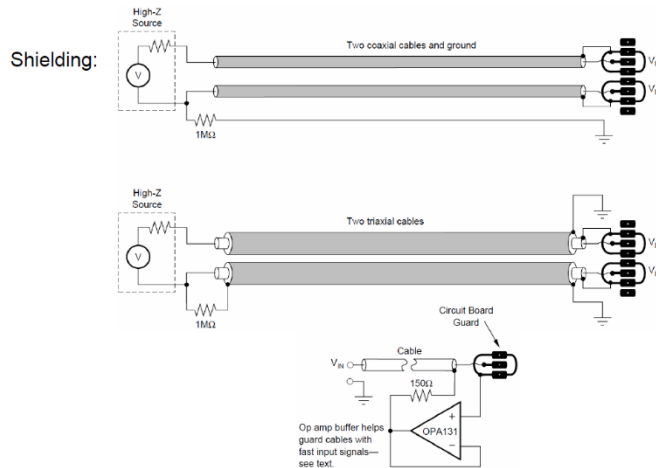We can for instance connect a source with two coaxial cables, one in the - pin and the other in the + pin of the INA, since the two input voltages could differ, the manufacturer can provide two different guards to drive the two different coaxial cables. To further protect the quality of the signal, we could use a triaxial cable (second image) with the final outer shield connected to ground.




Voltage from a solution

INA can be used often to measure voltage generated by two electrodes placed inside a solution. We have also an electrode that is the solution ground, without which nothing would work.


The opamps of the INA are made by transistors, so they will require a bias current in input. This means that if we want the circuit to work, we need to go and touch the signal inputs with the bias. We have to introduce on resistor to ground because in this way if V_{in} is 0, bias currents come from ground and everything works (without the resistance it would be impossible). $V^* = -2V$, which is a common mode voltage that can be removed by the INA, but to reduce it we could reduce the value of R to 100k, or improve the quality of the circuit by introducing symmetry.

 We have also to preserve symmetry, because if we detach the input and we use just a resistor, we provide I_B only on one pin but not on the other, and the output saturates to the value of the input (+ or -) where the output current enters. So we add another resistance to bias the - terminal.



Then, when we connect the source of the signal, the R_s should be smaller than $2 \times 220k$, otherwise the voltage that we have in input to the INA will be affected by the resistive partition. So the resistances to be introduced should be big enough not to have voltage partitions.


 
Coming back to the solution, if I have a solution and give just the metal wires to the INA, the INA as this will never work because it doesn't have I_b . So we need another electrode that touches the water and goes to ground (blue one).



Thus the two I_b can come and flow from it.


PROGRAMMABLE GAIN AMPLIFIER (PGA)

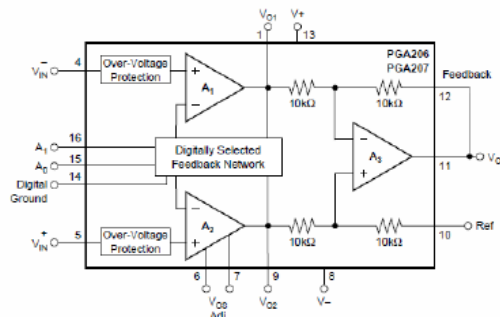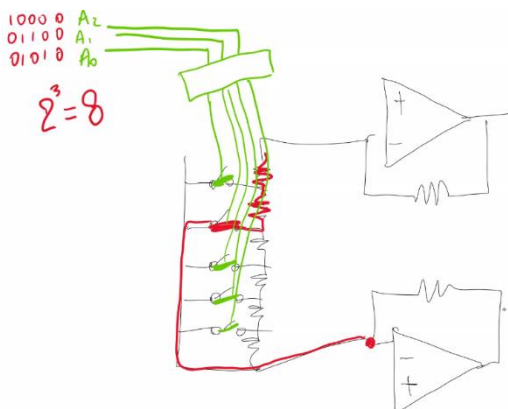It's not just an INA because we have a selectable net of resistance inside. Basically, in place of a single R_g we place a parallel of resistances with switches, we use a decoder with digital inputs and we are done.



We could have used a classical INA and a series of selectable resistances depending on the closure or not of mosfet transistors. However, the problem is that if we have a V_{cm} signal, eventually if we use a μC to control the gate of it, we have to grant on the gate $V_g = V_s + V_t$ to have it closed, but the problem is that in this case we are not sure, because if V_{cm} varies too much, it could be closed anyway.

Example 1

 


$R_{IN1}=100k\Omega$ $R_{IN2}=100k\Omega$ $R_{G1}=10k\Omega$ $R_{G2}=1k\Omega$ $C_G=1.6nF$ $R_1=3.3k\Omega$
 $R_2=2.2k\Omega$ $R_L=1k\Omega$ all resistors inside INA be $100k\Omega$

- Compute V_{out} for $V_{in} = 0V$
- Compute the ideal gain v_{out}/v_{in} at low and high frequency
- Compute poles and zeros


Resolution

- At DC output will be 2V because of the Vref signal.
- $G = 1 + 2Rf/Rg$ but Rg depends on the frequency because we have the capacitor Cg . At DC, $Rg = Rg1$ and $G = 21$, while in AC $Rg = Rg1 || Rg2$ and $G = 221$. This is the gain up to where the sense pin touches. Now I have to compute the gain between V_{in} and V_{diff} (input of INA), but since this gain is 1, $G_{ina} = G_{overall}$.

Let's plot the Bode diagram and compute poles and zeros. As for the pole, the total R is NOT $Rg1 + Rg2$, because inside the INA we have opamps. So terminals of $Rg1$ are at 0 thanks to virtual grounds of the inside opamps (input has to be switched off when we study poles). As for the zero, we do it with the GBWP.

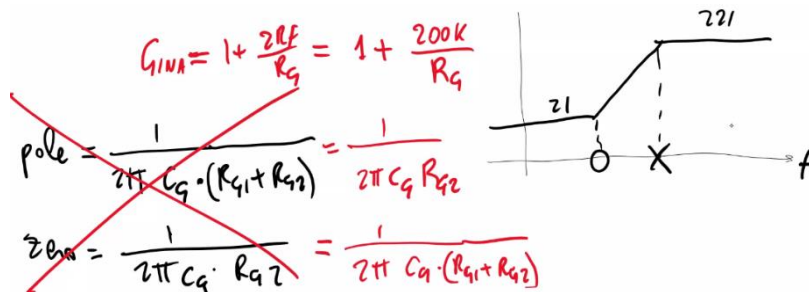

Example 2

 

INA with $R_f=100k\Omega$

- Plot the Bode diagram for the $v_{out}(f)/v_{in}(f)$ ideal gain
- Modify the circuit to provide a DC gain of 1000 and a low-pass filtering action with 2 coincident poles at 100kHz

Resolution

- a) Reference is to ground, so V_{out} is 0 in DC. Let's see where the sense pin touches, and then we have G_{in} . I don't care about the presence of the 1k resistor. Moreover, since I touch the output there the impedance I see looking from the output is 0 because the output is a voltage source, so the output capacitor is not introducing a pole because the output is driven by a voltage generator whose output impedance is 0, so the output voltage is independent on the 1k resistance and the capacitor.


Now let's compute V_{diff} with respect to V_{in} . 1n and 22n are in series $\rightarrow 0.8nF$. Then we have a HP filter with the 100k resistance, with the pole that will be $1/(2\pi \cdot 0.8n \cdot 100k)$.

Then the INA has a certain network as R_g , so again gain will be low at DC and high at AC, so we will have a pole and a zero related to the R_g . $G_{in}|_{DC} = 21$, $G_{in}|_{AC} = 92$.


Pole is $1/(2\pi \cdot 10\mu \cdot 220)$ and zero is $1/(2\pi \cdot 10\mu \cdot 10220)$.

Now I have to combine the three gains.

 
If the pole is at a lower frequency than the zero, the Bode diagram will be the one on the left.



 If instead the pole of the input capacitor is higher than the pole of the other capacitor, we have the following.




Last case, if the pole is in the middle:

 

CURRENT FEEDBACK AMPLIFIERS

VOLTAGE MODE CONFIGURATION

 
The basic idea is to use voltage mode opamps with two high impedance inputs (+ and -) and then the output was a voltage.



Requirements:

- voltage-driven inputs → high impedance inputs
- voltage output → low-impedance output

 In this configuration we can introduce a feedback. If the V_{in} is applied to the +, on the other pin we apply a voltage with the feedback and thanks to the high feedback gain the error becomes 0 and we have V_{in} also on the other pin, and eventually the ideal gain is the one of a non-inverting configuration. Then we can study the frequency response of this structure.



Performances:

- 20dB/dec slope
- constant GBWP (hence trade-off between gain and bandwidth)
- limited SR (tens of V/μs)
- strict relationships among f_0 , I_{tail} , C_{comp} , SR (again trade-off)

Thanks to the feedback, the pole of the opamp is pushed to HF, at $f^* = f_0 \cdot (A_0 / (1 + R_2/R_1))$. Then $G \cdot \text{pole} = f_0 \cdot A_0 = \text{GBWP}$ (gain is the one of a non-inverting configuration).


In the voltage mode configuration, the position of the pole depends on the gain. Than gain multiplied by pole is a constant number called GBWP. If we want a high gain the BW will be low, due to trade-off gain-bandwidth.

But we can change the way to introduce a feedback to reduce this trade off.

CURRENT FEEDBACK (CFA)

We design a brand new opamp where we have a positive input pin, **inside the opamp we have a buffer that reads the voltage on the + and provides it to the other pin, the - pin**. The voltage at this node is equal to V_{in} by design, independently on the feedback.

 If then we connect a resistor R_s , the buffer should provide a current through the resistor R_s . Now **the second trick is to provide a voltage at the output at the opamp that is not proportional to the error voltage but to the current that the buffer has to provide on R_s .**



Requirements:

- one high-impedance input (hence voltage-driven input)
- one low-impedance input (hence input-current, i.e. Acting as an output)
- voltage output (proportional to the input current)

$$G_c = 1 + \frac{R_F}{R_s}$$

It looks identical to VOA, but completely different feedback action


The opamp is no more the voltage mode opamp. If the gain is very high, even if the current is 1mA, the output voltage is high. But if the voltage in out is high, thanks to R_f , there will be a current flowing through it provided by the opamp because the $-$ terminal has to remain to V_{in} . So now the current that should flow through R_s is not just provided by the input buffer but also by the output voltage generator. Eventually, the input buffer has to provide a small current if the output voltage is high.

Eventually, if the gain of the voltage generator that provides a current proportional to the current the buffer should provide is so high, the buffer has to provide a very small current. So in the end in output we will have a reasonable voltage that is the one needed to flow across R_s without the need of any current from the buffer. So it's the output voltage generator of the opamp that provides the current, not the buffer.

V_{out} is given by $V_{in}/R_s * (R_s + R_f)$, the current that must be provided because the buffer sees V_{in} at the input (the current could be provided by the buffer but it is provided by the feedback). In the end, the ideal gain is the same gain we get with the voltage mode non-inverting opamp.


Let's design such a circuit.

CFA DESIGN

 

The buffer has his own output impedance R_b (that ideally is 0). Then let's provide a copy of the current that the buffer provides in output. Then i_2 is converted into voltage using a high value R_{ol} . Then this voltage is buffered and the voltage is provided to the output.


If this is our CFA, we have our opamp and if in input $V_{in} = 2V$, on the - we get 2V. If now $R_b = 1k$, the current of the buffer should be 2mA. But the current should not come from the buffer, but from the opamp power supply. Now we copy this current and feed it to a resistor and we buffer the voltage to the output. If the resistor is huge, e.g. 1M, the output will be 2kV, which is impossible because it will saturate to PS. Now I take this output voltage and use it to help provide the current in R_b through R_g . Current in R_b must be 2mA, but now I have two currents, one from the input buffer and one from the output buffer. So the input buffer can reduce its current provided. Going on, the output voltage reduces because the current in output to the input buffer reduces, up to the point the input buffer is not required to provide any current, because R_f will provide the current thanks to the internal gain of the amplifier.

 

What is the right value of V_{out} ? It's the one such that $V_{out}/(R_f+R_b) = V_{in}/R_b$ (current we need). R_f and R_b are not in series, but since there is the CFA and the opamp that has a smart gain inside such that $V_{out} = i_{in} * R_{ol}$, where i_{in} is the current the buffer input has to provide, then if R_{ol} is infinite is enough for i_{in} to be 0 to have a value.

So i_{in} (current provided by the input buffer) could be something but in reality is 0. Let's make a comparison between the voltage mode amplifier and the CFA. In the first one the current in input to + is 0, but also in the CFA it is. Then it means that there is no voltage drop and + is V_{in} for both. Now, for VOA, node - is 0 at the beginning, so there is an epsilon different from 0, so V_{out} increases a lot towards infinity, so also - increases to a given value V_f and epsilon decreases towards 0. Eventually, V_f goes to become equal to V_{in} so that $V_{out} = V_{in}(1+R_2/R_1)$.

As for CFA, since there is a buffer, we find V_{in} at -. Epsilon is already zero. But then we must provide a current. This current is provided by the input buffer, but this causes the output voltage to increase to very high values. - remains fixed at V_{in} , but the current through R_f (provided by the opamp) increases. Finally, due to the gain, the current through R_f increases so much that I no longer need to have a current fed by the input buffer and if = V_{in}/R_b .

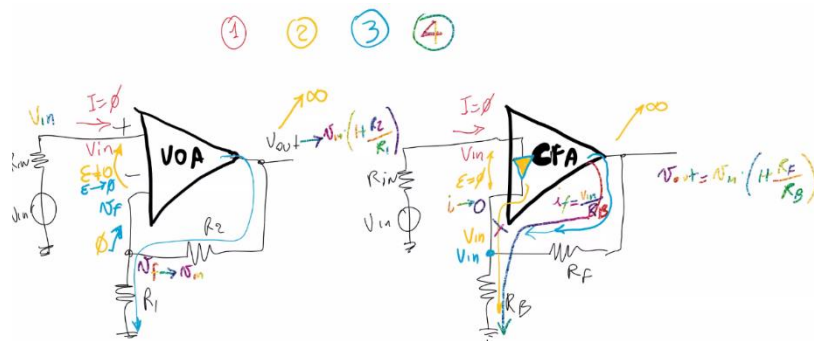

From an external point of view, they both provide the same gain. If we study the beta in the VOA, it is as below.


$$\beta = \frac{R}{R+R_2} = \frac{1}{1+\frac{R_2}{R}} \quad G = 1 + \frac{R_2}{R_1}$$

Hence in VOA the beta is very much related to the gain. If we want to change the gain (by changing R1 or R2) we change also the beta and hence we change also the pole.


As for the CFA, the beta depends only on Rf and not on Rb. Hence if we change the gain by changing Rb, Gloop doesn't change and the position of the pole remains the same.

CFA MODELLING

Let's try to solve the KVL.

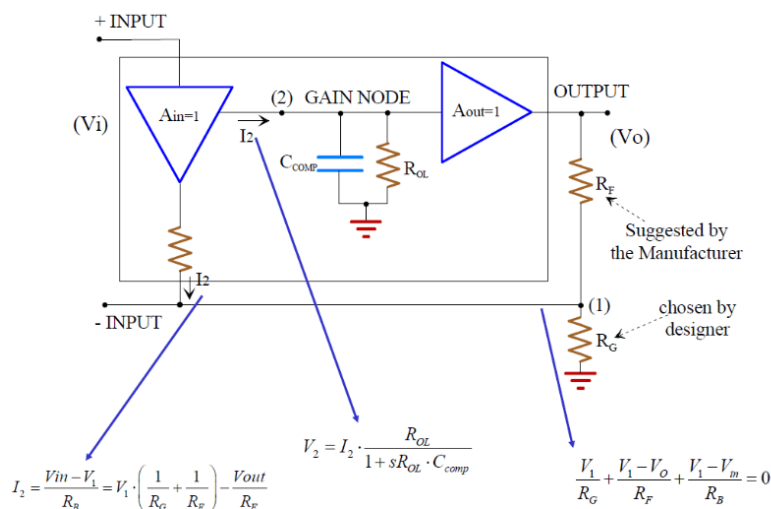

Ccomp introduces a pole, then the voltage on Rol (V2) is buffered at the output. Once we have Vout, (Vout-Vin)/Rf is the current in Rf. Then we can find the current in Rg and the one in Rb. The final equation Vout/Vin is really a mess. But we can understand it. It says that the gain is still 1 + Rf/Rg, but this quantity is divided by a correcting factor. However, if Gloop is very big (hence Rol very high), ideally the denominator is 1. Then there is a pole of the Gloop, due to Ccomp and Rol.

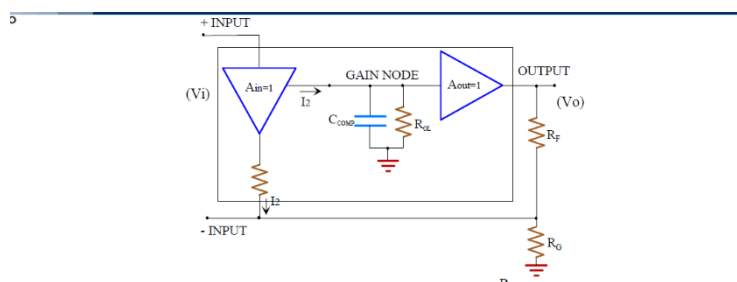

Closed-loop Gain:
$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{R_F}{R_G}}{\left(1 + \frac{R_F + \left(1 + \frac{R_F}{R_G}\right) \cdot R_B}{R_{OL} \cdot A_{out}} \right) \cdot \left[1 + s \frac{\left[R_F + \left(1 + \frac{R_F}{R_G}\right) \cdot R_B \right]}{A_{out} + \frac{R_F + \left(1 + \frac{R_F}{R_G}\right) \cdot R_B}{R_{OL}}} \cdot C_{comp} \right]}$$

The new pole is with a new tau that is not Rol*Ccomp. If we look at the tau, we realize the pole, if Rol is very big, what remains is Aout, that however is a buffer so it is one. So if Rol is big, the real gain is the ideal one and the new pole has a certain dependency on resistances, as below.

Bandwidth:
$$f_{pole} \cong \frac{A_{out}}{2\pi \left[R_F + \left(1 + \frac{R_F}{R_G} \right) \cdot R_B \right] \cdot C_{comp}}$$

For low gain ($R_G \ll \frac{R_F \cdot R_G}{R_F + R_G} = R_F \parallel R_G$) we get $f_{pole} \cong \frac{1}{2\pi \cdot R_F \cdot C_{comp}}$

Bandwidth depends only on R_F , not on R_G , hence **NOT ON GAIN!**

Instead for high gain (>50) we get $GBWP = \frac{A_{out}}{2\pi R_B \cdot C_{comp}}$

As for VOA, again trade-off Gain & Bandwidth (i.e. constant GBWP)

If $R_f \gg$ than the rest inside the [] brackets:


$$R_f \gg \left(1 + \frac{R_f}{R_g} \right) \cdot R_b$$

$$R_f \parallel R_g = \frac{R_f \cdot R_g}{R_g + R_f} \gg R_b$$

$R_f \parallel R_g$ should be in the range of 100 ohms, so we design an input buffer with $R_b \ll 100$ Ohm. If so, what remains in the [] is just R_f . So the pole depends on R_f and C_{comp} . C_{comp} is inside the opamp. If $R_f = 1k$ and $C_{comp} = 1p$, $f_p = 160$ MHz.

Thanks to CFA the bandwidth is huge and set by R_f , and the gain is changed by changing R_g .

 Let's make a Bode plots comparison (colored ones are the gains). In VOA, the higher the pole gets, the smaller the pole, because $GBWP = \text{const}$.



NB: In CFA, we must not change the gain with R_f . However this holds if $R_b \ll R_g \parallel R_f$. But if we want to go to high gains, R_g becomes so low that eventually it is not granted that the previous inequality holds \rightarrow valid for not to high gains.


If the gain is high, then it is not true that R_f prevails in the pole equation, but it is the opposite, so R_f is negligible with respect to the rest.

To know the value of the GBWP, we get (the only parameter is R_b , the others are constant and inside the opamp):

Instead for high gain (>50) we get $GBWP = \frac{A_{out}}{2\pi R_B \cdot C_{comp}}$


As for VOA, again trade-off Gain & Bandwidth (i.e. constant GBWP)

 At high gain, the CFA configuration becomes equal to the VOA, so we are in a condition where the GBWP remains constant as the VOA, but I want to remain in the region where I can change the gain while the pole remains constant.



CFA BANDWIDTH

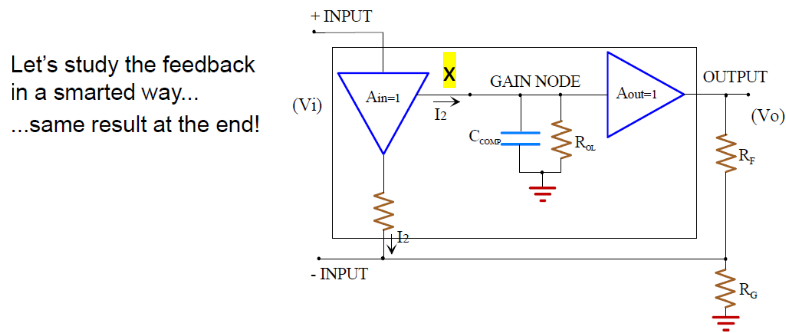We can also study the CFA in a standard way we have always studied them.



With open-loop: $pole_{openloop} \approx \frac{-1}{C_{comp} \cdot R_{OL}}$ $G_{loop} \approx -R_{OL} \cdot A_{out} \cdot \frac{1}{R_B + R_F} \approx -\frac{R_{OL}}{R_F}$

... hence, when loop is closed:


$$pole_{closedloop} = pole_{openloop} \cdot (1 - G_{loop}) \approx \frac{-1}{C_{comp} \cdot R_{OL}} \cdot \frac{R_{OL}}{R_F} = \frac{-1}{C_{comp} \cdot R_F}$$

NB: Vout must not to be partitioned on Rf and Rg because it is not Vout that dominates and determines the Vf to be fed back. Here the middle of the voltage partition is already set to Vin.

Let's study the circuit and get the CL pole of the configuration. The OL pole is Ccomp*Rol (on the two links connected we have high impedances).

The root locus is a plot where we plot where the poles are in the S plane, being S the complex frequency and real part.

 If we know where the OL pole is, if we close the loop the CL gain pole can be somewhere on the left. In fact, the possible poles on the CL config lie down on the left. The higher Gloop gets, the far away the CL pole is. The CL pole will depend on Rf.




As for Gloop, let's cut at the output i2 (x). I pump i_test and we are in DC, so Ccomp is open. we can get the voltage Vout that is i_test*Rol*Aout. If Rg is larger than Rb, when we study Gloop, we have

$R_g \parallel R_b$, but R_b wins the parallel and so we can say $R_f + R_b$ (R_b wins in the parallel with R_g). Then we have that the current generated on this series of resistance is equal to i_2 . So we can make the KCL and get the Gloop. Then $R_b + R_f$ is almost R_f because R_b is very small.


So the CL pole is equal to OL pole multiplied by $1 - \text{Gloop}$. **Pole_CL = Pole_OL*(1 - Gloop)**. Gloop is negative in general.

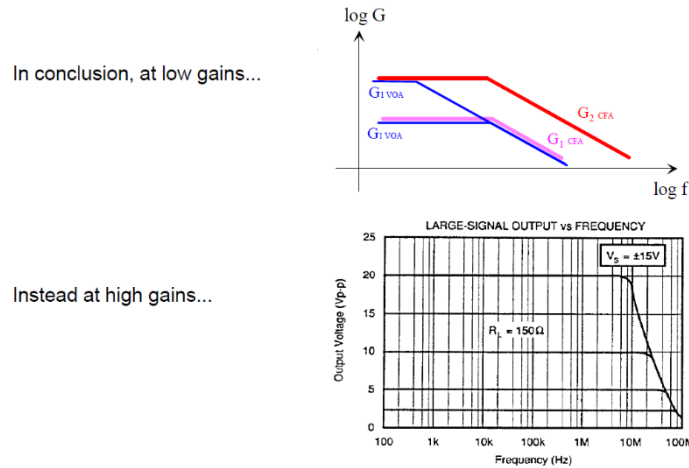So the closed loop pole is given by $C_{comp} * R_f$, when the loop is active (not when the loop is open). so the previous result is valid, always remembering the assumption on R_b .



REAL CFA ARCHITECTURE (to be known)

 I want a buffer with a gain 1, and I take a BJT where I enter with V_{in} at the base and I take the signal on the emitter. If R_e is very high, much higher than the $1/g_m$ of the BJT, gain is 1.




But if R_e is excessively high, we have not to use a resistance, otherwise even with a small current we get too much voltage drop on R_e . So we use as a resistor a current generator. In small signal analysis it's a buffer, but in big signal analysis, $V_{out} = V_{in} - 0.7V$, but I need a buffer, I cannot loose 0.7V.


To regain the 0.7V we use another buffer but we loose 0.7V in the opposite way.

But there is an issue, if V_{in} goes positive, V_{in} increases in output, but if V_{in} decreases the output decreases but a NPN configuration is happy if the base increase, because the emitter increase (first buffer), since we have a parasitic capacitance that takes the charge. However, if we decrease the base of the first buffer, e.g. we go down from $V_{in} = 2V$, the capacitor is still at 2V and the capacitor discharges slowly thanks to the current generator that drinks the current. So if V_{in} drastically increase, V^* copies, but if V_{in} drastically decreases, V^* goes down and reaches the 0.7V gap after a long time because there is a slow discharge of the capacitor because the BJT goes off.

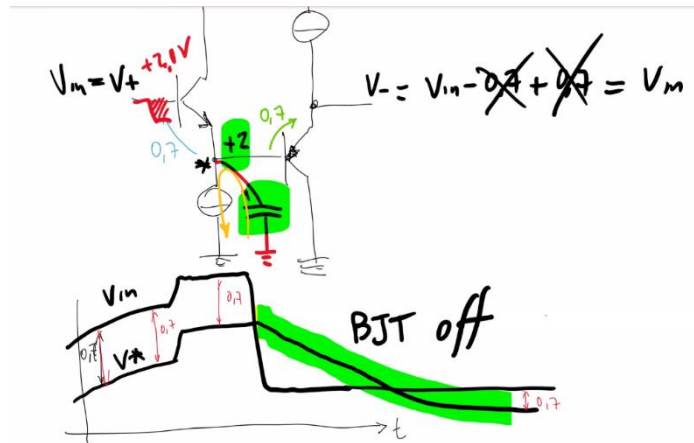
Hence the transistor is smart in going up but not in going down. To have symmetry in the circuit, let's duplicate the input stage.



 Let's introduce a P-channel with a current generator and another buffer.



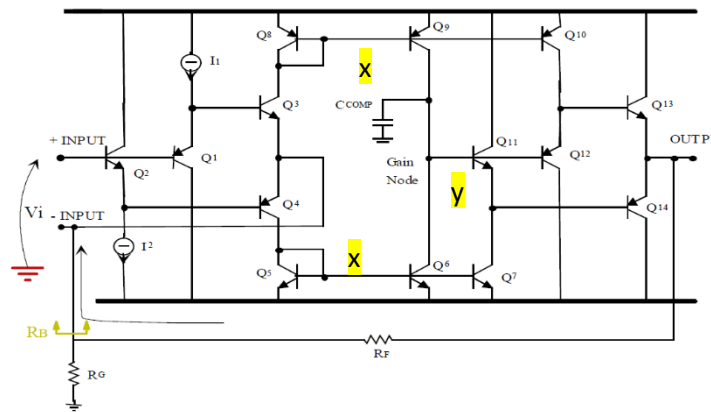So input required current is 0, and the output current is the one that flows out in R_g . Then I need a copy of this current to be provided to R_o . So the i_{in} current comes either from the top or bottom branch of the output BJT couples. So we place current mirrors (black, x) to copy the currents.



Complementary npn+pnp darlington configurations, hence better SR...
 but problems of matching, hence higher offset voltage


Q_2 and Q_4 is the first couple of followers, the other one is Q_1 and Q_3 . The collector of Q_3 should go to PS, and the collector of Q_4 to ground, but instead I use current mirrors.

So the first input buffer is created. Now I have to add R_{ol} and the buffer output. As an output buffer I copy the output buffer, but there is a difference. I use a current that is the current proportional to the one that we have in the mirror. The impedance we see from y is $\beta \cdot 1/g_m$ parallel to something both in Q_{11} and Q_{12} . Since we want the highest possible R_{ol} , the only R_{ol} that suits the work is the parasitic R_{ol} . $r_{o9} || r_{o6} || (r_{in} \text{ of the output buffer})$ is the R_{ol} . R_{ol} will be in the range of kOhms at the most. To increase it I can increase the mirroring factor if the x mirrors, increasing the area of the Q_9 transistor. So we will have a lower R_{ol} but a higher current that is like having a higher R_{ol} in the end.

CFA SLEW RATE

In the differential pair VOA we pump a constant current ($2I$) that is splitted evenly but then we have the capacitor C and so the pole of the configuration is set by the Miller effect with the capacitor C . The SR of a VOA depends on the current $2I$, and also the bandwidth depends on it.

Voltage Mode (VOA)

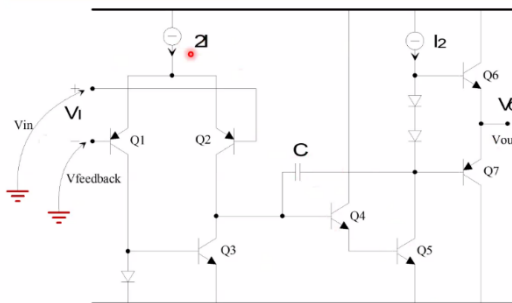


Requirements:

- voltage-driven inputs → high impedance inputs
- voltage output → low-impedance output

Instead, in a CFA imagine we apply a big step in input. This step is applied to the other pin; since I apply a big step in voltage, the current that flows is the step we gave divided by R_f . But this current is suddenly mirrored by the mirror and flows in C_{comp} giving a $dV/dt = SR$.

So the Slew Rate that is dV_{out}/dt depends on a current that is not constant, because it gets higher if it's high the step we apply, it is not constant as it was in the VOA that is constant.

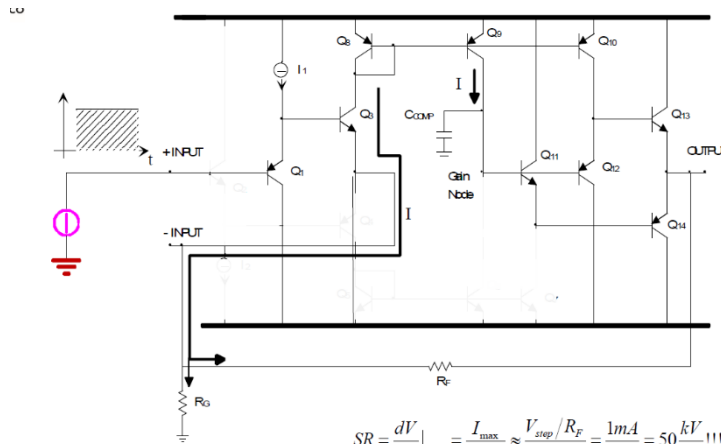
So the CFA is good because it has a high slew rate.



$$SR = \left. \frac{dV}{dt} \right|_{\max} = \frac{I_{\max}}{C_{\text{comp}}} \approx \frac{V_{\text{step}}/R_f}{C_{\text{comp}}} = \frac{1\text{mA}}{1\text{pF}} = 50 \frac{\text{kV}}{\mu\text{s}} !!!$$


CFA TRANSIENT RESPONSE

 Indeed there are second-order effects, which degrade SR



This is the real circuit. We apply a big step (e.g. from 0 to 2V) and we have a npn transistor, which is good, because if we increase the base, we have 0.7V across base and emitter. Then if we increase further the voltage (up to 3V) at the base, also the 0.7V wants to increase, and the current in the transistor Q1 increases too much, because we have the characteristic of a diode, and above 0.7V if we increase the voltage a bit, we increase also the current but a lot more, so we quickly charge the capacitor C2, so base of Q4 rises rapidly and the emitter goes to 2.3V (from 1.3V previously). Unfortunately, now Q4 is slow, because we have -0.3V across Q4, because the output previously was 2V, so Q4 is off. So to move up the output, we have the Q3, which is fast. In fact, npn transistors are fast in the rising edge transition, pnp not (due to parasitisms), but they are in the falling edge.

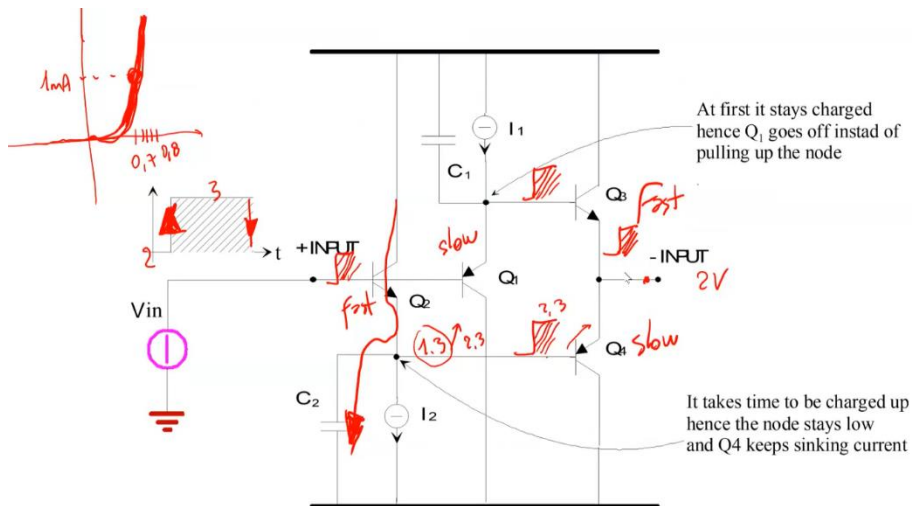
In this case we have the parallel combinations of two paths, fast and slow and slow and fast. So I don't have a fast-fast path to provide a SR.



ISSUES

The input buffer is ideal, but this is not perfectly true.

 
If we consider just one path, the one below, we have 0.7V on both. But this is not true, because pnp and npn transistors are made with different doping, so there might be a mismatch between the two values. If so, there is an offset equal to 100mV between input and output. I can compensate this mismatch by changing the current in the two BJTs, so we reduce the current in the second BJT.



But again, this is not true because the I-V characteristic for a pnp or npn transistor changes if the temperature varies. So even if I find the perfect matching with currents to cancel out the offset, temperature changes create a problem.

We have to avoid this offset due to the mismatch between npn and pnp transistors. So we can try to improve by using not just two transistors but more.

The idea is that, since one transistor needs 0.7V and the other one needs 0.8V (in our example), instead of using just a current generator let's use a diode, and for the second stage we use the pnp transistor and we recompensate the drop we introduce with the diode. So the npn needs a voltage of 0.7V, the pnp of 0.8V, why not using diodes to compensate? Yes, I design a diode made by transistors of opposite polarity.

 


Now V_{os} is ideally 0, the transistors are all bad but they compensate each other. So both on the bottom side and top side we use a diode. The red improvement of the next image is very good. And we added it also at the bottom.


Then we have another issue, let's forget about diodes for now. Imagine now I increase the + voltage node (we have also the twin path). Usually the PS is dual, so at the bottom top we have +/- 12V. Externally then we connect R_g and R_f .

When input is 0 (black values), we have some parasitic capacitances, but no current at all. If we increase to +2V, some BJTs are fast, and some are slow.

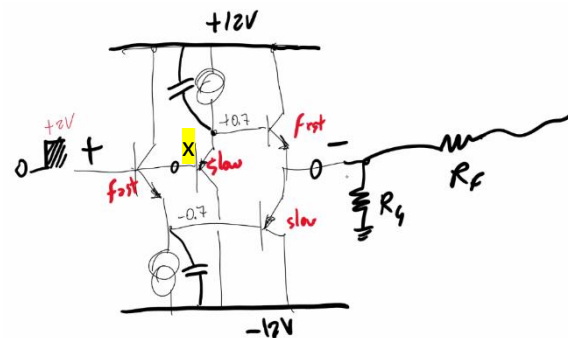
When we move from 0 to 2V, the x BJT goes off and the upper capacitor is discharged through the current generator.



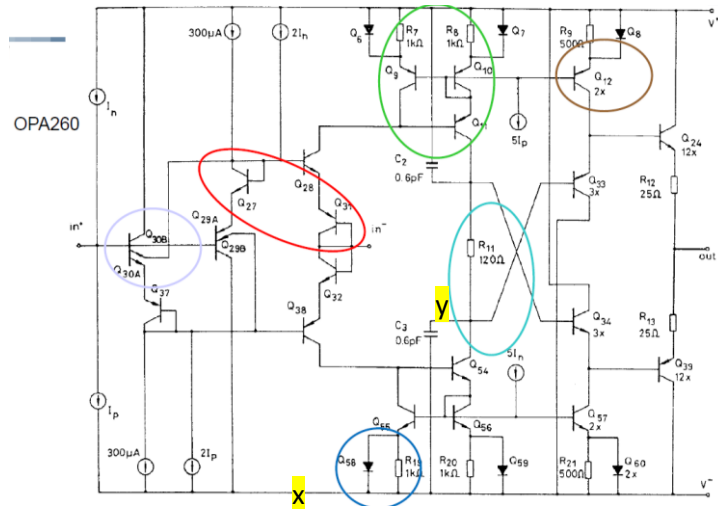To speed up the circuit, if we go to 2V suddenly, we face immediately a slow transistor after the fast one. So we can use a **double emitter transistor**.




Double emitter transistor (npn)

 

We use the second emitter and we connect it to the emitter of transistor x of the previous image. In the schematic is the purple circle. If the input voltage increases too much, the second emitter activates and we pump current into the node of Q28 speeding up the circuit. Thus we drastically increase the SR.

Now I want to mirror, in the previous configuration we relied on it, and we want also to improve the value of RoI that was in the order of kOhms.

 We can use different mirrors, like the classical one or an improved one placing a Re.




By improving the output impedance we improve RoI, the impedance of the gain node. In the schematic it is the green circle (Wilson), where the diodes further improve performances. In fact, if we increase the voltage at the base, we have the $1/g_m$ and a resistor, and if the base is increased to very high values, some portions of the voltage drops across the base-emitter and a portion across the resistor. But if the base is increased very much, soon or later we would love the voltage we apply to fall totally as V_{be} . For this reason we introduce a clipping diode. Hence for low values of V_{be} (0.7 – 0.8V) we are ok, but then when the voltage is high the diode clips the voltage at the maximum value of 0.7V, so the emitter is clipped at 0.7V, the V_{be} has a maximum value of 0.7V and hence the vase cannot go above 1.4V compared to the bottom level x, otherwise the transistor starts drinking a huge amount of current that it is okay that because it helps in pumping a huge amount of current from the gain node and then get the amplification.

Finally, the light blue circle. We would like to have the transistor always on, no output current but on to have a low parasitism. To achieve so, the pnp has to be connected to a slightly lower voltage (y) and the npn at a slightly higher one. To do the splitting I use a low value of resistance, R11.

CFA OTHER ARCHITECTURES


It is the same configuration as before. The buffer with Q3,4,5,6 is the same, then we have a buffer Q9,10 and they introduce R_f inside the opamp, we cannot choose it. This is ok because R_f has to be kept constant to get the pole we want, then we change R_g .

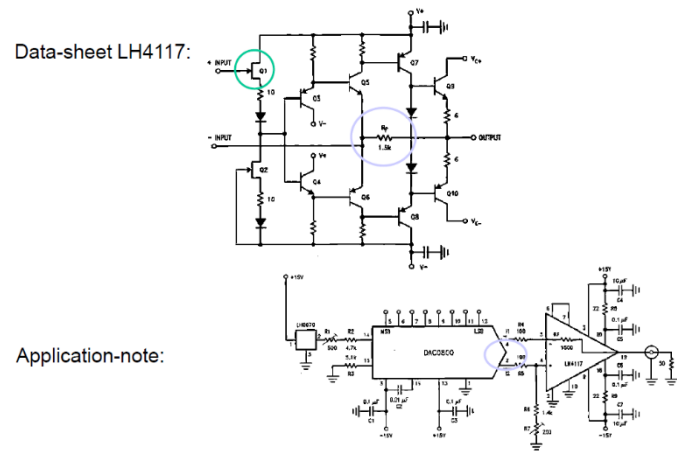In our initial modelling we considered just C_{comp} , so there will be for sure some parasitism due to the buffers, and because of this there will be other poles that limit the bandwidth and the manufacturer knows that eventually if we shift the pole due to R_f , eventually the BW is limited by the other poles due to parasitics. So the manufacturer directly places R_f in the CFA.




OPERATIONAL TRANSCONDUCTANCE AMPLIFIER – OTA

 It is neither the VOA, nor the CFA. The VOA has volts in input and provides volts at the output. The CFA has voltage in input an output is again a V. Now we apply a V_{in} in two positions and we want a current in output. Then there will be the amplifier where the inputs are currents and the output is a current as well.




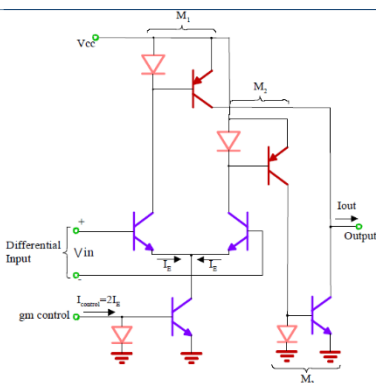OTA is a differential pair with a tail current that is provided with a current mirror, and the diode is the current mirror.



$$g_m = \frac{dI_{OUT}}{dV_{diff}} = \frac{dI_{OUT}}{d(V_+ - V_-)} = \frac{I_E}{kT/q}$$

 - both inputs be high impedance (like VOA)
- output be current (like Norton)
- transconductance gain (I_{out}/V_{diff}) adjustable through a pin!




We can redraw the circuit as above (using active loads). We need to properly subtract the black and green currents. If I pump $I_{control}$, then due to mirroring ratio I have $2I_{control}$, and the output current should be I_1 (black) – I_2 (green). To compute the difference we use another current source mirror at the bottom.


If no input is applied, the output current is 0, but if we have an imbalance in input we have output current. To compute the value of the output current, we shift to small signal analysis and the input pair will have a $1/g_m = V_{th}/I_{control}$ (all in DC the $I_{control}$) and $V_{th} = kT/q$.

SMALL SIGNAL ANALYSIS

 Current generator $2I_{control}$ will be open in AC signal analysis. The signal current that we have, thanks to the mirror, is doubled and we have the output.




 
gm is set by the I_control, so we can change the gain by changing the I_control. The output pin is the one with which I select I_control.



Ideally, if we enter in the circuit above with 2V on the + and 2.3V on the minus, the voltage difference is 0.3V that, multiplied by that value of Gm will give a $i_{out} = Gm \cdot v_{diff}$. It is like a voltage mode amplifier cut in half, because a voltage mode amplifier has another stage after that converts the current into a voltage.

All the internal nodes of an OTA are low impedance, the only high impedance node is the output, that shows an impedance that is the r_o of the two transistors in parallel.

  Hence in an ota we have a very high input and output impedances. We have also another pin, the control pin (I_control, also called I_ABC).



$$i_{out} = G_m(I_{control}) \cdot v_{diff} = \frac{I_{control}}{kT/q} \cdot v_{diff} = \frac{I_{control}}{25mV} \cdot v_{diff}$$

Advantages:
 all low-impedance nodes
 wide bandwidth
 $f_{pole} = 1/2\pi C_{LOAD} R_{LOAD}$

Disadvantages:
 no infinite gain
 no "VIRTUAL GROUND"
 it is used open-loop

Gain of the OTA


It is based on the differential pair. We apply a differential signal between the two input transistors, and since they are biased with certain currents, if we measure the two collectors' currents, I_+ and I_- , if v_{diff} is 0, the two collector currents are just the biasing currents, so the tail current $I_{control}$ is split in half in the two sides (left).

If we apply a v_{diff} , the two transistors are slightly modified, we bias them with different voltages. We can study the circuit by linearizing the behaviour of the transistors, using the small signal equivalent. But this is a wrong assumption with a v_{diff} of 1V. anyhow, let's try to do this. The transistors are modelled with the $1/gm$. A differential current will be generated with the value in the following image.

However, in an OTA we don't simply use a resistive load but a current mirror, so that the current is mirrored and the $i_{out} = 2 \cdot i_{diff} = Gm \cdot v_{diff}$.
 In the OTA, the $Gm = gm = (I_{control}/2)/25mV$.

The $I_{control}/2$ depends on the design of the OTA. If the mirroring factor of the mirror is 1:1, if the tail current is $I_{control}$ we will have half it in each branch.

 In the linearized analysis we found that the output current is proportional to v_{diff} and the transconductance of the OTA. However this is not true if the input signal is too high.




Advantages and disadvantages

The OTA has all the input nodes at low impedance, so even if we have parasitic capacitances, the poles they introduce are at very HF, and this is an advantage. Who sets the pole in the OTA is the capacitor C_I at the output stage.

The disadvantage is that the voltage mode opamp has a A_0 very huge, whereas the G_m (tens of mA/V) here has a very low value, so the gain of the OTA is limited, so we cannot use it to perform a feedback in this configuration, because the G_{loop} of the stage is not infinite and very very limited.

If we want to use it like this, we can but we have to increase the gain of the OTA for example with a Darlington couple to improve the gain of the overall stage as below. i_{out} gets amplified by the $\beta + 1$ of the two components.

 If then we place another resistance we can have a gain we want. But the message is that with just the OTA we cannot achieve a feedback loop.



However the big issue is the **strong nonlinearity**. The $I_{control}$ that we pump is constant, and $I_{C-} + I_{C+}$ must be equal to $I_{control}$. Then we know the transistor has 0.7V across its V_{be} , so $V_{in-} - V_{in+}$ cannot be high as 1V, because it is impossible to have 0.7V on one V_{be} and on the other. In fact, the v_{diff} should be 0.7V - 0.7V, so it should be limited to few hundreds of mV at the most.

Real gain


We have to study the circuit using the correct equation for the BJT transistor, the exponential one for I_c . We wrote the value of v_{diff} and we compute I_+ and I_- . We end up with a I_{out} that doesn't depend linearly on v_{diff} . There is an hyperbolic tangent that links the v_{diff} with the I_{out} .

So the real input output characteristic of a differential pair has an hyperbolic tangent behaviour, meaning that if $v_{diff} = 2 * V_{th}$, so 50mV, then one input transistor is carrying more current than the other, but


since their sum must be equal to $I_{control}$ it means that, compared to $I_{control}/2$, one transistor is carrying more current and the other one less.

Eventually, in order to operate as a differential pair the differential signal must be in the range of few tens of mV, because the trend is linear only in this case. If we apply e.g. 1V, we are outside the linear range and one transistor carries the full $I_{control}$ and the other is completely off. Hence we have a saturation of the differential pair when the full $I_{control}$ flows in one transistor or the other.

 If we compute the slope of the curve, it is maximal for small v_{diff} . $dI_C/dv_{diff} = g_m$ that is the slope of the curve and the transconductance of the stage. So we can use this differential pair in the range of few thermal voltages.



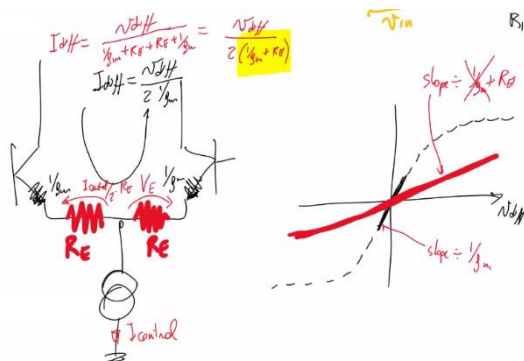
To increase the linearity region, we can start from the differential pair (with the small signal $1/g_m$ for each input transistor, which is very steep when $v_{diff} = 0$ but then saturates) is to add a degeneration resistance R_e . Given then $I_{control}$, we have voltages drop on the R_e (V_e) and the differential signal is now given by the following.



With R_e the gain drastically reduces (slope is less pendent) but we have a more extended linear region. So we can apply even higher differential voltages in input, but soon or later we will reach anyhow the saturation. So we have a trade-off between dynamics and linearity.

IMPROVED DYNAMICS AND LINEARITY

 A much better approach is by adding two diodes and forcing a current through the diodes, and then we remove the current (I_D). If so, the two current compensate. But we introduce a close loop.



$$I_{in} = I_{D-} - I_{D+} = -(I_{D-} - I_{D+})$$

Now there is an input current !!!

$$I_{in} = I_{D-} - I_{D+} = I_{T+} - I_{T-}$$

But the out/in relationship is linear!!!

$$I_{out} = I_{C+} - I_{C-} = \frac{I_{control}}{I_d} \cdot I_{in}$$



where $|I_{in}| < I_d$

Translinear principle: $I_{D+} \cdot I_{T+} = I_{D-} \cdot I_{T-}$

Node currents: $I_{D+} = I_D - I_{in}$ $I_{D-} = I_D + I_{in}$

Output signal current: $I_{out} = I_{T+} - I_{C-} = I_{control} - I_{T-}$

We take the differential pair, we put diodes and we use current generators to remove the currents. Then the two diodes are connected together and we pump $2 \cdot I_D$ and we remove them separately. If $v_{diff} = 0$, the stage is fully symmetric but if we apply some v_{diff} , one input will be higher than the other. But at the same time also the voltage across the two diodes will be different. We can write a KVL. V_{be+} causes I_{c+} and V_{be-} causes I_{c-} .

 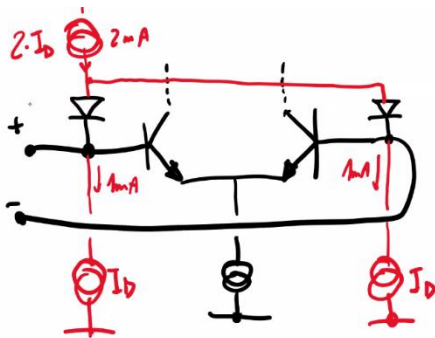

$$V_{D+} + V_{BE+} = V_{D-} + V_{BE-}$$

\downarrow \downarrow
 I_{c+} I_{c-}

Every time we have a circuit that has a diode, pn junction, diode, pn junction and so on and then is closed, every we have a loop where there are just pn junctions connected in series, we can apply the **translinear principle**. It applies every time we have a loop of transistors or diodes.

According to Kirchhoff, the sum of the voltages in a resistive network should be equal to 0.




$$\sum V_i = 0$$

$$V_1 + V_2 - V_3 - V_4 = 0$$

$$V_1 + V_2 = V_3 + V_4$$

 If now we consider diodes or transistors, given the V across the transistor, which is the current that flows? It is more or less the $I_{collector}$.




$$I_c \approx I_{sat} = I_s \cdot e^{V/V_T}$$

$$V = \frac{kT}{q} \cdot \ln \left(\frac{I_c}{I_s} \right)$$

Now we can find out the value of V. Hence the voltage across a transistor is proportional to $I_{\text{collector}}$ (I_c). So the voltage across a pn junction is given by a constant coefficient ($K = kT/q$) multiplied by the logarithmic.

Now, let's apply KVL but with this expression for voltages.
 
$$k \cdot \ln\left(\frac{I_{c1}}{I_{s1}}\right) + k \ln\left(\frac{I_{c2}}{I_{s2}}\right) = k \ln\left(\frac{I_{c3}}{I_{s3}}\right) + k \ln\left(\frac{I_{c4}}{I_{s4}}\right)$$



If all transistors are equal and belong to the same Si chip and are equal in terms of area and processing, all I_{s1} , I_{s2} , I_{s3} , I_{s4} are equal. Then, if the transistors are at the same temperature, also the K coefficient is the same. So we can write the following.

$$\begin{aligned} \ln I_{c1} + \ln I_{c2} &= \ln I_{c3} + \ln I_{c4} \\ \ln (I_{c1} \cdot I_{c2}) &= \ln (I_{c3} \cdot I_{c4}) \\ \prod I_{cc} &= \prod I_c \end{aligned}$$


Hence the product of all current in the clockwise direction must be equal to the one in the counterclockwise direction (it applies just for only BJTs or diodes, not mixed).

Given a loop of closed-connected branches, Kirchoff's law says: $0 = \sum_{j \in \{CW\}} V_{e_j} - \sum_{l \in \{CCW\}} V_{e_l}$


$$V_e = K \ln\left(\frac{I}{I_d}\right)$$

$$\prod_{j \in \{CW\}} I_j = \prod_{l \in \{CCW\}} I_l$$

For loops with just BJTs, $K=kT/q$

 


For loops with just MOSFETs, $K=nV_T$

 

Every time we find a loop where we have just base-emitter, base-emitter junctions, if we know the currents flowing in each transistor, then the Kirchoff law, that is the sum of all the V_{be} that must be equal to 0 results in the equation with the products of the currents.

 Coming back to the circuit, we have introduced diodes and current generators. We have I_{d+} and then we remove I_d . If I_{d+} is different from I_d , the difference must flow out through the + pin, and the same for the minus terminal (I'm assuming the base currents to be negligible). So we have an input differential current i_{in} .



$I_+ = I_D - I_{D+}$ and $I_- = I_D - I_{D-}$
 They can differ,
 so an input differential current exists!

$$I_{in} = I_+ - I_- = I_{D-} - I_{D+}$$

But the out/in relationship is linear!!!

$$I_{out} = I_{C+} - I_{C-} = \frac{I_{control}}{I_D} \cdot I_{in}$$

when $|I_{in}| < I_D$

Translinear principle: $I_{D+} \cdot I_{T+} = I_{D-} \cdot I_{T-}$

Node currents: $I_{D+} = I_D - I_{in}$ $I_{D-} = I_D + I_{in}$

Output signal current: $I_{out} = I_{T+} - I_{control} = I_{control} - I_{T-} = I_{T+} - I_{T-}$


Let's now use the translinear principle (bottom equations). I'm interested in i_{out} , that is $I_{T+} - I_{T-}$. We end up with an equation that tells us that the current output is proportional to the input differential current multiplied by a gain that is $I_{control}/I_D$. With a minor v_{diff} , I_{D+} and I_{D-} differ but we remove the same I_D , so i_{out} is created as a consequence of i_{in} (with no input signal there is complete balance and $i_{in} = 0$). The gain of the stage is now $I_{control}/I_D$.

NB: i_{in} must be smaller than I_D , because otherwise it means that one diode is completely off. But I want the translinear principle to operate, so I want some current I_{D+} and some current I_{D-} and some I_{T+} and I_{T-} .

We started from a circuit with infinite input impedance in input on + and - terminals, so we can apply a V_{diff} but input current is 0, but we ended up with a configuration with a low V_{diff} but a i_{in} .

We ended up with a configuration with a differential input current, so it seems that we have a brand new configuration.

 In the left mode we have a differential pair and $I_{control}$ and that's all, input current is 0 at + and - terminal. We just can apply V_{in} and we get a certain I_{out} . However, this solution is strongly nonlinear, so the OTA can be used only with a V_{in} within few V_{th} .




When I_D is not used, the linearization is **off** and:

$$I_{out} = \frac{I_{control}}{kT/q} \cdot V_{in}$$

when $|V_{in}| < kT/q$

Transconductance amplifier

 

When I_D is set, the linearization is **on** and:

$$I_{out} = \frac{I_{control}}{I_D} \cdot I_{in}$$

when $|I_{in}| < I_D$

Current amplifier


If we use the right new solution, now V_{in} (of the amplifier, not v_{diff}) is almost equal to 0 (not equal to 0 otherwise the input transistors won't be on) and there exist a I_{in} differential input current. Now the

output current is proportional to the input current through a gain set by $I_{control}/I_D$, and this holds just if $i_{in} < I_D$, because I want the input transistors to be on.

So the OTA can be use in the standard left mode or as a current amplifier with a linearization network, if we can pump current into the stage.

OTA DATASHEET

POLITECNICO MILANO 1863

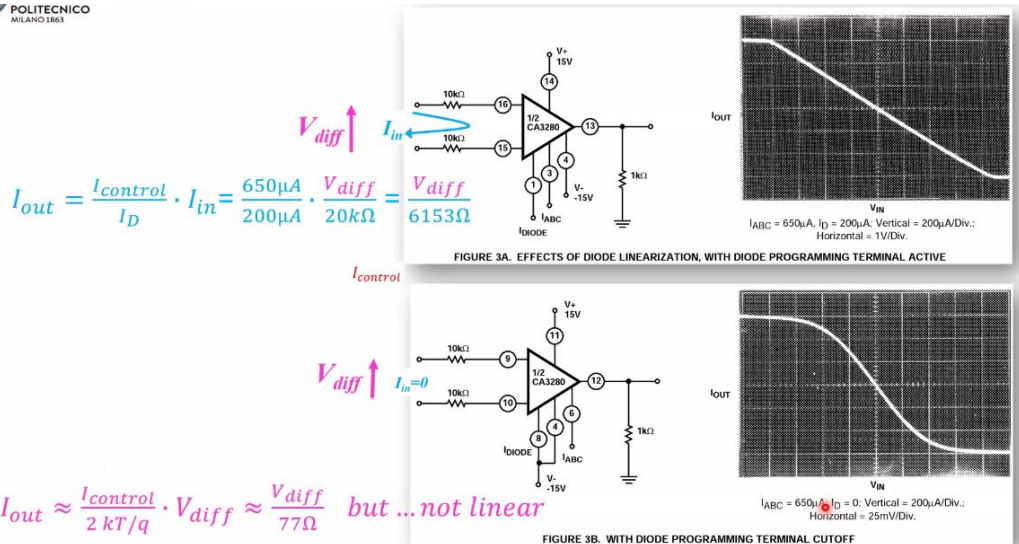

With the standard mode we have a high gain but a strong distortion and saturation (bottom). In the top improved situation, we have a smaller gain and thanks to I_{diode} , 16 and 17 pins become a shortcircuit almost, because V_{in} at the input of the OTA is almost 0 due to the translinear principle (v_{diff} is not 0, we have the 10 kOhm resistances to separate the two). So the classical OTA can be used with small v_{diff} .

In the brand new configuration there may be saturation if V_{in} gets so high that $I_{in} = I_D$ and one of the two transistors or diodes are off, so the stage is no more operating. However, the linear range is still larger than in the standard case.

Moreover, the transconductance changes with $I_{control}$, since it is $I_{control}/25mV$. So the higher $I_{control}$ the higher the G_m .

The frequency of the OTA is very high, so G_m remains constant for frequencies up to hundreds of MHz.

 


FIGURE 11. AMPLIFIER GAIN vs FREQUENCY

Why if we increase the $I_{control}$ there is also an increase in the pole?

It's a secondary effect of the differential stage. Inside the OTA we have some parasitic capacitances, the one of the base-emitter junction of the transistors, which changes with the transconductance g_m . g_m changes with current and so if we increase the current, then $1/g_m$ increases and also the parasitism decrease and the pole improves and gets better.

Function generator

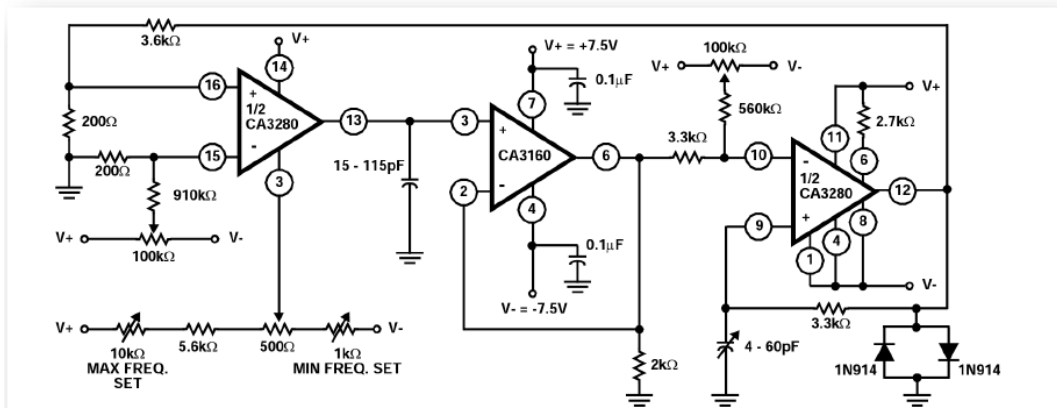


FIGURE 9. CA3280 USED IN CONJUNCTION WITH A CA3160 TO PROVIDE A FUNCTION GENERATOR WITH A TUNABLE RANGE OF 2Hz TO 1MHz

We have a CFA at the beginning whose output current depends on the differential input signal (16 and 15) multiplied by the G_m of the CFA. But the G_m depends on the $I_{control}$ current. So in output of the CFA I have a constant current proportional to the potentiometers positions. The current flows in the capacitor, the voltage on the capacitor increases linearly and then we go to another amplifier and a positive feedback opamp, that a Schmitt trigger. So we have a constant current in output of the CFA flowing into a capacitor, the voltage gets amplified, then I reach a Schmitt trigger and when I cross the threshold the trigger commutes. Once the commutation is done, the voltage in input to the CFA reverts, so the current direction in the CFA reverts and so also the ramp on the capacitor goes down and so on.

Triangle wave-to-sine converter

 


FIGURE 10. TRIANGLE WAVE-TO-SINE WAVE CONVERTER


We enter with a triangular signal and the output is a sinusoid. So this stage performs a sort of non-linear input-output characteristic.

Moreover, sometimes the OTA is represented with the input diodes displayed, to highlight the input diodes used for linearization.

Advantages of the OTA

The OTA is important because it can be used as a voltage reader (infinite input impedance) and the output is a current or we can exploit the linearization current, pump it through a pin in diodes and now the input

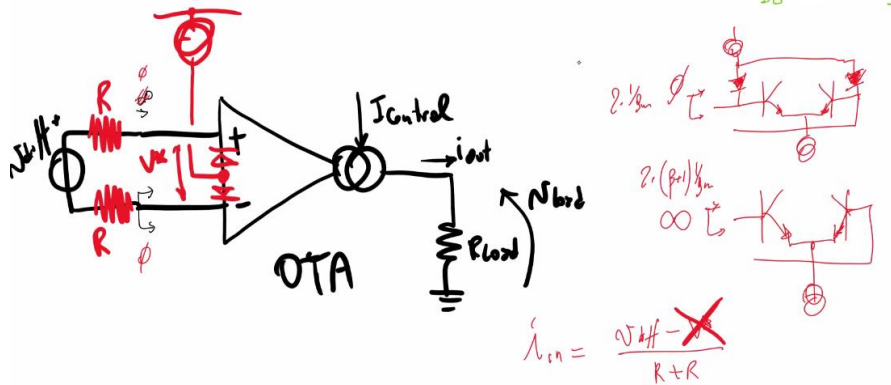impedance is almost zero because the V_{in} at the input of the amplifier is 0. With the diodes that are permanently on I see the impedance $1/g_m$ of the two diodes, no more $(\beta+1) \cdot (1/g_m)$. Hence to use this circuit I must introduce two resistances otherwise I cannot apply a v_{diff} .




The advantage of an OTA with a linearization network that is actually behaving as a Norton amplifier (we will see this) is that the OTA has $I_{control}$, so we can change the gain of the OTA by changing it, in both the standard case or in the linear one. Conversely, in the Norton is fixed.


Example – Voltage controlled LP filter

We have a component at the output to increase the gain. If G_{loop} is very high and we apply something positive at +, a current is pumped out and it causes a voltage over the Darlington network (which has a very high impedance). The Darlington is a follower, so V_{out} increases and also the - terminal, where we will get V_{in} . But if I have V_{in} at - terminal, what is V_{out} ? It is not $V_{in} \cdot R_1 / (R_1 + R_2)$, no! The signal propagates in the clockwise direction, it is the voltage at x that gives the voltage at the - terminal, so $V_{in} = V_{out} \cdot R_1 / (R_1 + R_2)$.

i.e. $f_{pole}(V_c)$

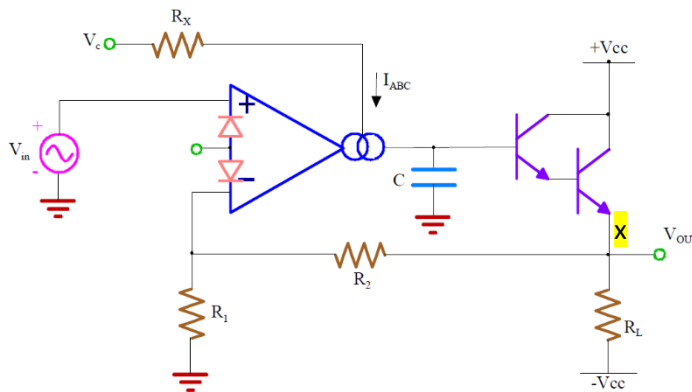

 If we change $I_{control}$ the gain is always $1 + R_1/R_2$. so what is $I_{control}$ doing? Let's compute the G_{loop} by cutting the circuit.



If we pump i_{test} , R_{ol} (in parallel with the output capacitor) is so high that the transistor is pumped in the Darlington couple. Then we have the current that flows in R_2 and R_1 . Then I get v_f , but then since I'm studying Gloop I multiply by G_m (open loop gain of the OTA). Since Gloop is very high, we can assume the stage to be ideal.

Real gain


Let's now study the real gain of the circuit. The open loop pole is due to C multiplied by the total equivalent resistance.

$$pole_{open-loop} = \frac{1}{2\pi C \cdot \beta^2 \cdot \left(\frac{R_2}{R_1} + R_2\right)}$$

$$\approx \frac{1}{2\pi C \cdot \beta^2 \cdot R_C}$$

$R \cdot G_m$

 We can see that the pole is constant. Let's now write the Bode plot. The gain is constant and given by $1 + R_2/R_1$, and we have a pole in the circuit (no zeros) that is the open loop pole multiplied by $1 - Gloop$. We can see that the pole varies with $I_{control}$.



In this configuration the gain is fixed but we can change the pole of the circuit.

ISOLATION AMPLIFIER – ISO

We want the power supply of the output stage to be separated wrt the one of the input stage, so that the we don't have damages on both sides.

- Requirements:**
- isolated input and output stages
 - double power supply
 - galvanic isolation



 



Figure of Merit: **Isolation Mode Rejection Ratio**

 

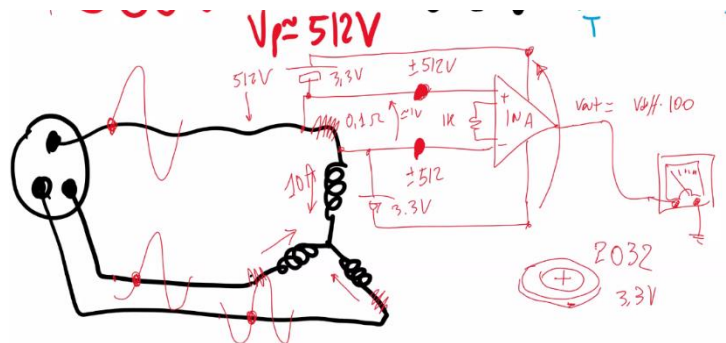A possible application is the following, where we don't have defined a ground.



 
So we need to define a ground, that is not 0V but it moves up and down by 500V. So it is not easy to connect a low voltage opamp with a high voltage source.



To connect the electronics to a tri-phase power supply we put a resistor at the center of the tri-phase, not on the outside. Thanks to this the center is at 0, and to be sure I can connect it to earth (literally ground). Now we can attach the amplifiers to the small power supply and the electronics work.

But if the ground disconnects, we broke everything and we kill all, destroying the opamps, having hence shock hazards.

 So I want an amplifier that is capable to introduce **galvanic isolation**, because I don't want the shock hazard to propagate.




Galvanic isolation means that we can bias the two stages independently inside the same amplifier. We can define the **Isolation Mode Rejection Ratio (IMRR)**. An ideal ISO has output 0 if input is 0 whatever is the difference between the two power supply. The better the isolation, the higher the IMRR.

EXAMPLE OF APPLICATION

Not just to measure high current and voltage, but also low voltage if we want for instance to measure the ECG of a patient and we want to prevent any short in the equipment to kill the patient.


Right-leg driven ECG amplifier

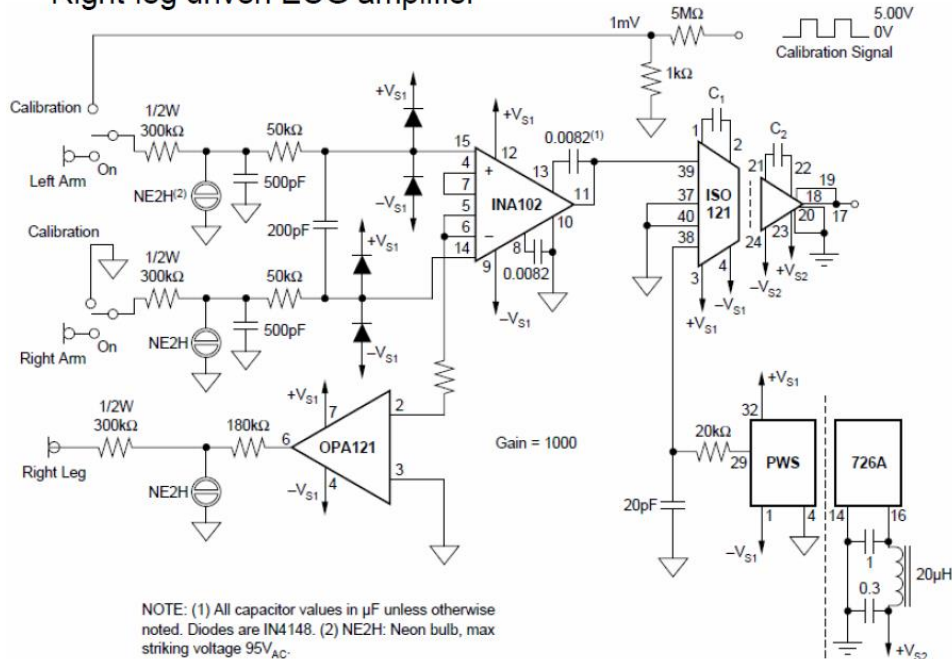

Example of IMRR response

The IMRR can be very high, over 60dB, but if we increase the frequency at which the two grounds move, the isolation mode becomes less effective.

IMRR frequency dependence

 

Transient Immunity: ISO122 TI < 1000V/ms


Isolation techniques: Optical
Magnetic
Capacitive

OPTICAL COUPLING FOR THE ISOLATION


Based between an emitter and a receiver. We can use a LED and a transistor; if we have current through the LED we will also have it through the transistor, so it is for instance for digital circuits (upper circuit, **optocoupler**). Typically LEDs require 1V across them to be on. Thanks to the pull up resistance, if there is a current flowing there is a voltage drop across the resistance of the second stage and the output is high.

Advantages:

 - “light” breaks the “electrical” loop
- high EMI
- trivial for digital signals
- problematic for analog signals



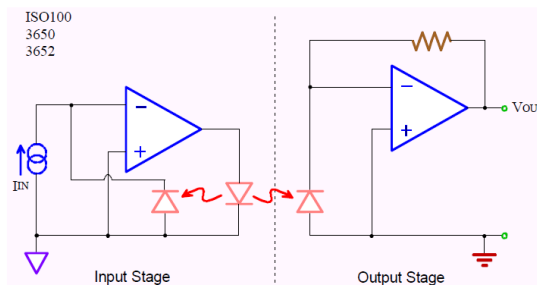Example of optical coupling for analog signals:




For an analog information we need something smarter, because we have a certain signal and we want an analog output.

Optocoupler for analog signals


LED and phototransistor are not made on the same substrate because if something happens on one side we destroy both sides of the chip, so the real optocouplers are made with two different chips.

Then somehow they are coupled in some way optically. Usually, given i_{led} and i_{ph} , the relationship between the two can be linear. So if we pump a given current in the LED, the current in the PD will be of a certain value depending on the coupling. If the coupling is not perfect, we run the risk that there are some mismatches, because if we pump a given input current, we don't know the value of the output current.

 


So we cannot use an optocoupler applying a V_{in} and using a resistor and an optocoupler to transfer an analog signal, because it doesn't work. In fact, the input current i_{led} is as below, but the relationship between i_{led} and v_{led} is not constant, but exponential. So the light we create generates a current in the phototransistor depending on β_{opt} , which is eventually varies too much.

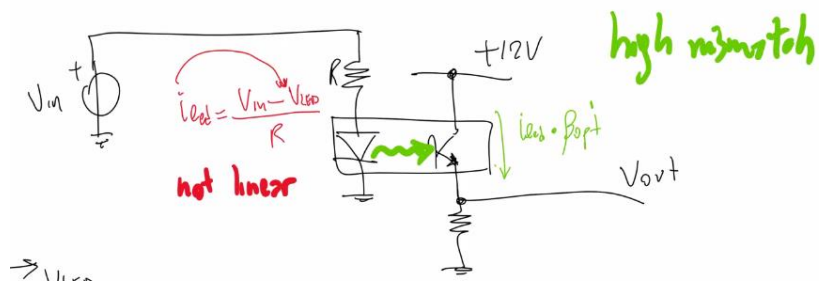So in the end $v_{out} = i_{led} * \beta_{opt} * R_{out}$ is not linearly related with v_{in} .



 A drastic improvement is the following. Now i_{led} is $v_{in}/1k$. For the second stage we use another bias voltage but instead of using just a buffer as in the circuit above, let's use a transimpedance amplifier and the transistor is biased at high reverse voltage. Now $V_{out} = V_{in}/1k * \beta_{optical} * 10k$.




$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1} \cdot \beta_{opt}$$

$$V_{out} = \frac{V_{in}}{1k} \cdot \beta_{opt} \cdot 10k$$


The drawback of this configuration is the $\beta_{optical}$, which is a factor that changes a lot. It is not fixed, but it has a very high variability.

So if we have a component that is really bad because it has a high tolerance, instead of putting something that has a low tolerance, let's use this component (the optocoupler) twice to compensate the error introduced by one.

 Since the beta varies, one optocoupler will be used to move the signal in one direction, and the other to check what the cross-signal is. In this way I_{pt} will be the same on the two branches. This current I_{pt} can be used to properly drive the LED.




We must use the input signal V_{in} to drive the LED, but then I cross-check with the phototransistor to regulate the i_{led} . We can hence let the current V_{in}/R_1 to flow through the transistor of the second optocoupler (but we cannot do this because we have the collector of a transistor), so I use an opamp to drive the LED, and the opamp is happy if the voltage it sees is 0 at the + terminal. So we have the negative feedback loop, because the current in the optotransistor increases if the light from the LED increases. If the loop is strong, we have the following. The current flows through the transistor because we are pumping it.

 

Since beta optical is very much variable, also i_{led} will be but I don't care because what I care is the current I_{pt} , which is a twin brother of the current x . But **we must assume that both optocouplers are identical**, they cannot mismatch, but they can be both 'bad'. Thus we can conclude that $V_{out} = V_{in} * (R_2/R_1)$.

Example of an optocoupler

Example of isolated front-end:

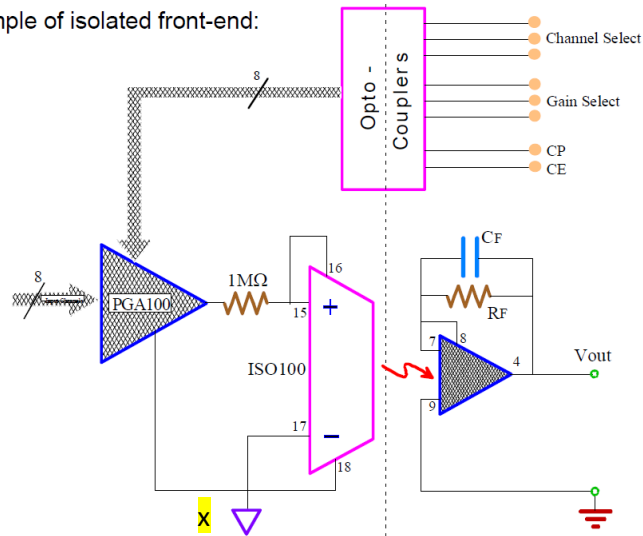


One pin is to ground (x), in another pin we enter with a resistor (1 MOhm) and it is used for the feedback and the output need an external Rf and capacitor Cf to introduce the low pass filtering action. Then we can also use individual optocouplers (top of the image) to apply the signal from the microcontroller back to the PGA. Thus the isolation amplifier guarantees the isolation of the analog part and the 8 optocouplers guarantee the isolation in the digital connection between input and output.

MAGNETIC COUPLING

Another way to isolate input and output is by using transformers, but they are not very much used. But if we apply a constant DC value in input, the output current will be 0 because we are applying a constant value to a transformer. In order to transfer a DC signal and have an output DC signal we have to modulate that value and demodulate it.

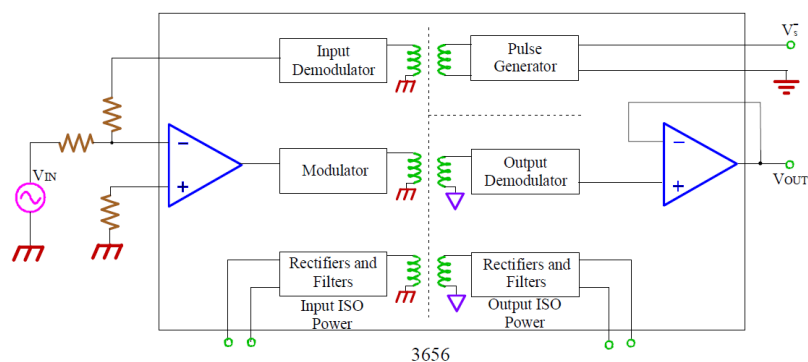Hybrid and compact transformers with modulation/demodulation techniques are needed




To introduce a global feedback we cannot use a resistor to connect the input and the output, we need to use another modulator and demodulator.

CAPACITIVE COUPLING


Another possibility is to use them. We can use an ADC modulator, we enter with a voltage, convert it into a digital information, we charge the capacitor and on the other side we use a DAC that reads the information on the capacitor and converts back to an analog information. Nevertheless, the optical one is the better.

NORTON AMPLIFIER

 Amplifier that reads current and provides a current. So low impedance in input and infinite impedance in output.




To have an infinite input impedance we have used a transistor (BJT, or MOSFET, even better). If we want to have a low input impedance we need to enter into the emitter of a transistor, after the transistor is properly biased. The impedance we see is $R_E || 1/g_m$. The advantage of BJT transistor is that $1/g_m$ is V_{th}/I_c , usually in the order of ohms, while in the MOSFET transistor $1/g_m$ is $1/(2kV_{ov})$.

 

With the Norton amplifier we want an input differential pair, so let's add two inputs. We want the inputs to be very low impedance. The current that is useful is the one that enters into the emitter and exits from the collector, to provide the output signal. If we want that all the current enters in the collector, R_E must be maximized \rightarrow better to use a current generator in place of R_E so that I'm sure that I will see $1/g_m$ and the current will all flow in the transistor.

To then perform the difference between the two currents I need to introduce a current mirror. If the two currents are equal, then the output current is 0 due to the mirror.


So if we read no current from the output pin, the bias currents flow in the transistor. We can also have currents moving out from the transistor but I cannot pump to much current in this configuration because it is at the most equal to $2mA$, the current of the current generator, otherwise I push the current in the current generator and not in the transistor and the transistor is off. So this configuration is good if I want to sink current but not if I want to pump it.

 

So I need to add other two BJTs. Of course I need to bias the two branches. A possible solution is to apply the same bias on the two bases of the two couples of BJTs.

But it is better to use, instead of resistances, diodes, which will be the exact copy of the pnp and npn transistors, so I connect them in transdiode configuration. I need to keep those transistors on so I pump current and also sink it. Hence I use two current generators I_0 .
 If I pump I_0 , the two diodes force the voltages across them to be 1.3V, but we don't know the voltages at the sides.


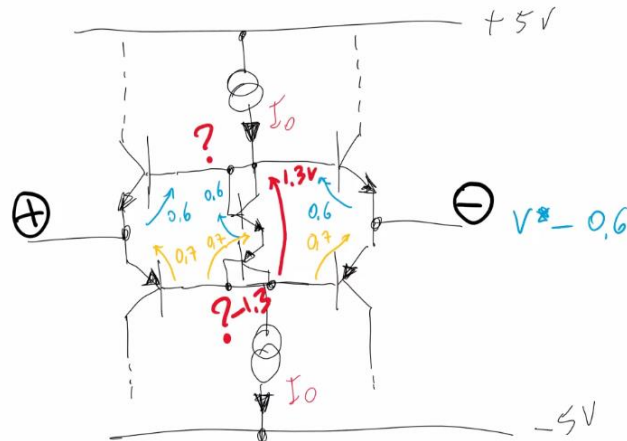
To fix the voltage, I can use the intermediate point, put it outside the circuit and depending on what I attach to that pin I will have the upper and lower voltages.



So the Norton amplifier has a Z pin that determines the voltage I want to apply to the Norton amplifier. Once the voltage applied to the intermediate point is selected, the two terminals will be at a fixed voltage.

Requirements:

  
- both inputs be at LOW impedance
hence current-driven
- output be at HIGH impedance
hence current source




We can use the intermediate point x, bring it outside the circuit and, depending on what we connect at that point, we are fixing the voltage at the input. If for instance we connect it at ground, the two inputs will be at 0V. Hence the Norton amplifier has another input pin that is used to set the voltage we want to apply on the two inputs of the opamp. Because of this we cannot apply a voltage on the terminals of the Norton, it is set by the amplifier, we apply currents.

Then I want the output to be a current proportional to the current difference at the input and so I need current mirrors to subtract signals in input in the proper way.

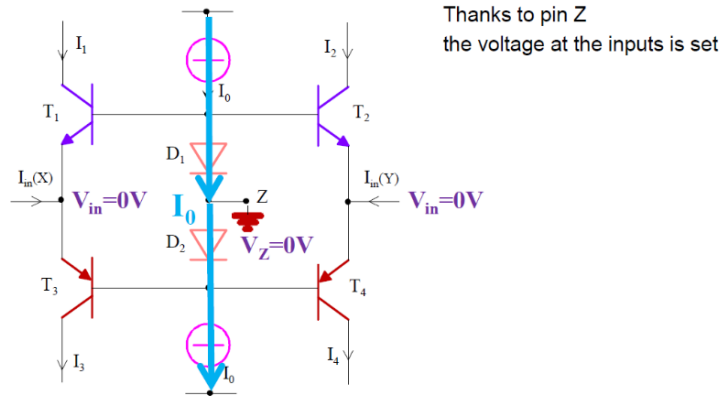So we are forcing current in the middle branch, so the two diodes are on (light blue path). We set node Z to 0V. If the purple npn transistors are matched, and if the pnp red ones are matched, if the input current is 0, the output current is 0.




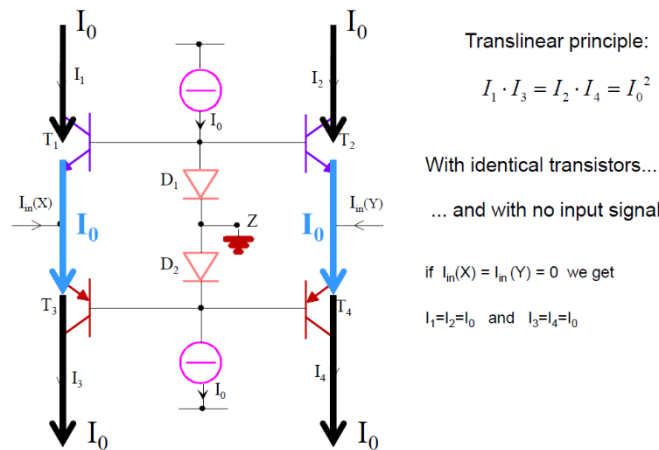Now I want to compute which is the current that flows through the right branch. We can use the translinear principle. Given a network of transistors, the sum of the Vbe voltages in clockwise and counterclockwise directions must be 0. Then according to the translinear principle this concept extends to the currents, but in terms of product.




If the pnp transistors and npn transistors have the same area, the I_0 are the same.

If then I apply a common mode input current, e.g. 1mA, so the currents are the same on the two input terminals, I'm pumping a current that is adding to the biasing current. I_0 is 2mA if the diodes are biased with 2mA, so the current will be 2.5mA below and 1.5mA above to maintain the KCL at x and y nodes. So the common mode signal splits in two if the two $1/g_m$ of the transistors in input are the same. So the CM signal increases the two downward currents and decreases the top currents if the signals are inward and coherent. Instead, if we consider a differential signal (right), we have a different situation.

 


Now we can use current mirrors.

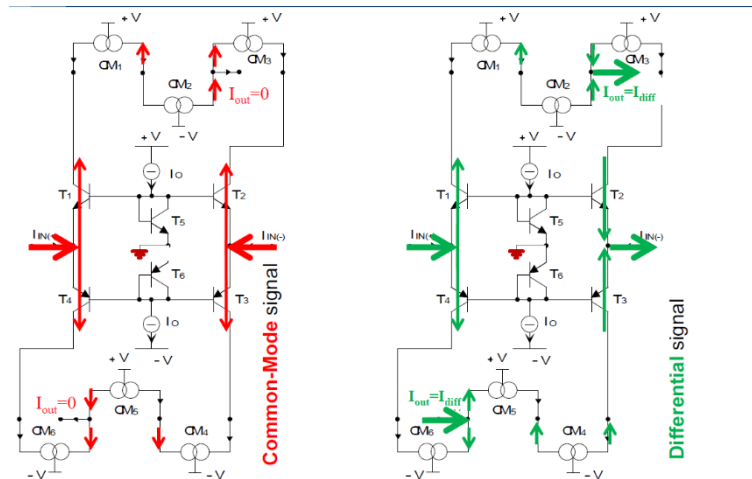


The output is in the branch of the mirror where the transistor part of the mirror is not present (we have two high-impedance nodes touching together, so two collectors). This applies both to the top and bottom sides.

We notice that in the case of CM input signal the output is 0. In the case of a differential signal the output is actually a current.

So this is the final Norton configuration we are looking for. The two inputs are low impedance and the only high impedance node is the output, which provides a signal that is the differential signal at the input. The output is half because we have also the bottom part. So in a Norton, the highest gain we can get is 1. If we want a higher amplification we can add amplification to current mirrors. So let's use a current mirror that is not symmetric.

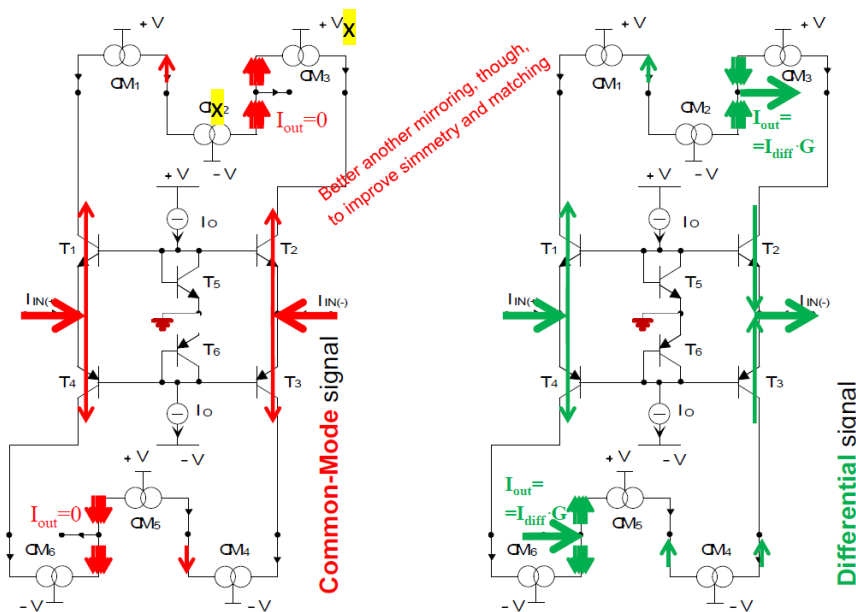


 However, in this analysis we are not considering the base current, in fact the $10\mu A$ in the left transistor has a portion that goes in the base of the two transistors. But if the area of one of the two transistors becomes larger, to increase the mirroring ratio, then also the base current increases, and hence the current that is mirrored is reduced, so the mirroring factor is impaired.



So the Norton amplifier has a A_i amplification but this amplification is limited.

POSSIBLE CONFIGURATION

 

$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_2} + I_o$$

$$I_o = \frac{V_o}{R_F}$$

$$I_o = A_i \cdot I_{diff}$$

$$V_o = \frac{A_i}{1 + A_i} \cdot \left(V_1 \cdot \frac{R_F}{R_1} - V_2 \cdot \frac{R_F}{R_2} \right)$$

Note that A_i is NOT infinite but just few tens!
... hence **NO** "IDEAL GAIN" behaviour

We have the Z pin. If we apply GND there, by design the input terminals of the Norton will be at 0. So if I want to apply a voltage in input, I need to place a resistor to prevent shortcircuits. So the current in R_2 is V_2/R_2 and then it splits in the feedback and in I_2 , and the same for $I_1 = V_1/R_1$. I_{out} flowing through R_f generates a V_{out} . Moreover, $I_{out} = A_i \cdot (I_1 - I_2)$.


So we have a voltage difference amplifier. If A_i is infinite, much higher than 1, $A_i/(A_i+1)$ is almost 1. So this configuration cannot be considered an ideal negative feedback configuration because the gain is not infinite and so we have a real gain of the configuration.

NB: R_f must be present, we cannot use a shortcircuit, because otherwise V_{out} will be always equal to 0.

Inside the Norton amplifier, all input nodes are low impedance, so even if there are parasitic capacitances I don't care, because all the internal nodes are $1/g_m$ of the transistors. If we want to decrease the bandwidth of the amplifier, I can do this externally.


NB: never connect a pin of the Norton amplifier to ground, because it is a voltage source so it wants to stay at the voltage set by the Z, but even if the Z voltage is 0, the voltage on the terminal should be few mV due to mismatches, so if we connect ground to the pin we are creating a short. So we always need to introduce a resistor in the middle. Of course we will have a current across the resistor, but if R is very high, the current will be negligible.

 To set the pole, we put a capacitor in parallel with the output load resistance, so we can set it wherever we want.




If we use the configuration with R_2 in feedback (below), and I put C in parallel to R_1 , now the capacitor sees $R_1 || R_1$, because - terminal of the Norton is grounded. **NO!** This reasoning is wrong because we have a feedback circuit and every time we have a node of the feedback, and we try to move that node,

we are the feedback actioning. So the impedance we have is the 'stupid one', that is $R1 || R2$, but then divided by $1 - \text{Gloop}$, so we need to compute Gloop.

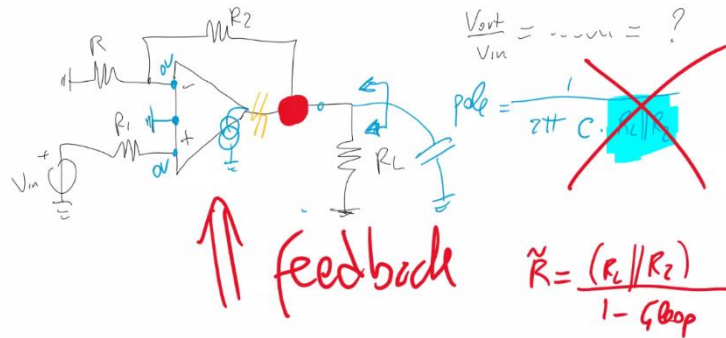

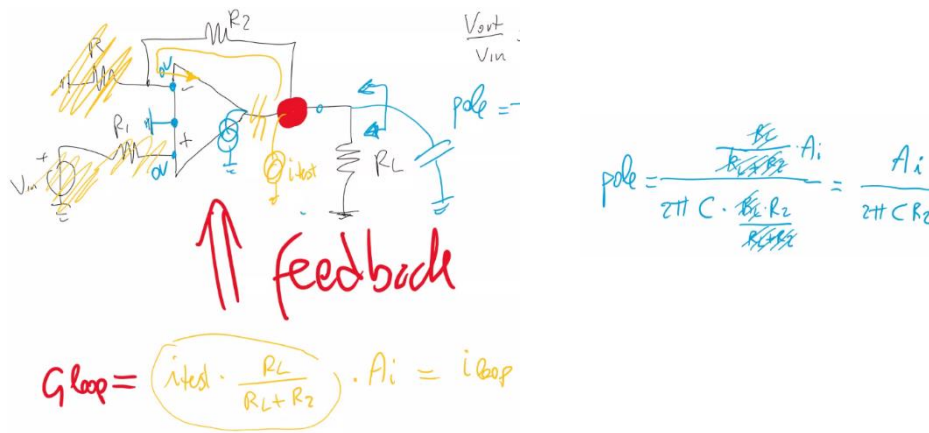To compute Gloop we cut the loop and pump I_{test} . The current in feedback is $I_{test} * (R1 / (R1 + R2))$, that then enters in the ground, there is no need to perform current splitting. So $\text{Gloop} = A_i * (R1 / (R1 + R2))$.






So we have changed the position of the pole with this value of equivalent resistance affected by the loop.

ADVANTAGES AND DISADVANTAGE

We may change the gain and the pole is not changing, because all the internal nodes are low impedance. So the pole of the Norton amplifier as it is is at very high frequency. If we want to shift it to other frequencies we need to add an external capacitor. In particular, is C_{load} equal to C_f since they are at the output and attached to ground? They could differ, but we need to plot the Bode diagram if one of the two is connected.

Advantages:

   
- all nodes have low-impedance ($1/g_m$) hence very low parasitic time constants
- very wide bandwidth
- bandwidth independent of closed-loop gain




SAMPLING

We have to differentiate the time domain and the frequency domain. If we have a DC signal in the time domain and we plot its spectrum, it will be just at 0Hz, where I put its intensity. Sometimes is better not to draw the intensity but the total power. The power of a constant signal from $-\infty$ to $+\infty$ is infinite, so I will have a Dirac delta with infinite height and 0 width.

 
We can then refer to the Laplace transform. A constant spectrum in the frequency domain returns a delta in the time domain. In fact, infinite spectrum it means that the intensity is the same along all the frequencies. If in time domain we sum all the possible frequency, all the sum at a given t collapse at 0, only at the origin $t = 0$ they are summed without disappearing.



Moreover, a periodic signal in the time domain, thanks to the Laplace transform, in frequency it will be the sum of harmonics at replicas of the period of the signal. Not only exists positive frequencies, but also negative ones. **If the signal is real, then the Laplace transform is symmetrical.** Of course, it is true the vice versa. If we have something periodic in the frequency domain, then for sure in the time domain it should be a stack of deltas.

 

 If in time domain I have a comb of deltas, a set of Dirac's delta with height 1 and period T (called T_s , sampling time), since it is periodic, the Laplace transform should be a set of delta, and since it is a set of delta, the Laplace transform should be periodic \rightarrow we still have a comb of deltas.




If we push T_s towards 0, it means that the set of deltas becomes very close one to the other, in the frequency domain the deltas are instead widely spread. If $T_s = 0$, we get a DC signal in the time domain and so in the frequency domain we have a delta at $f = 0$ and the other deltas are at infinity, so they disappear.


SHANNON THEOREM

Shannon theorem, 1949:

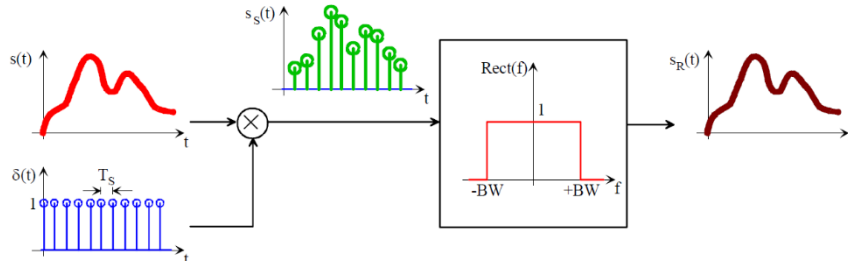
“if a **function $s(t)$** has no frequency components above BW Hz, then it is fully **determined** by its **values**, sampled every $T_S = 1/2BW$ ”



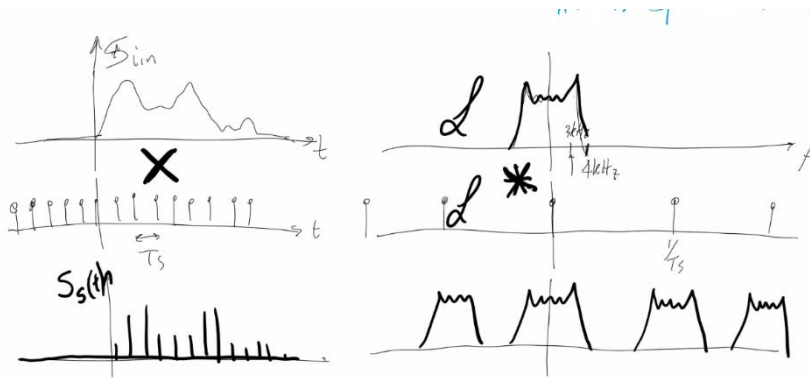The minimum distance between two samples must be at least 1 divided two times the bandwidth of the signal. To reconstruct the signal we can use a LP filter with a width as large as the bandwidth of the original signal.




We have a replica of the original spectrum at multiple of $f_s = 1/T_s$. Then to reconstruct the signal I will use a rectangular filter with a f_{max} slightly higher than the f_{max} of the original signal, but it has to be lower than $f_s - f_{max}$. Thus, when we perform the multiplication in the frequency domain (filtering in time domain equals the multiplication in the time domain) we get in the end a convolution of my samples with the Laplace transform of the filter we use. And we know that the Laplace transform of a pulse is a sinh . So if we multiply the signal spectrum and the filter spectrum we get the original spectra with all the other replicas killed.

 

Eventually the reconstructed spectrum is equal to the original one.

In the time domain we have to convolve the deltas with the sinh of the filter. So we have to draw a sinh for each delta and, given the width $2 \cdot f_{max}$, the sinh cancel each other apart from the positions where we have the zero crossings.

 
In the end we have an analog signal equal to the original one thanks to the Shannon theorem.



This of course happens only if the replicas of the signal in the frequency domain are far from each other, because in this way the filter can kill the replicas.


ALIASING

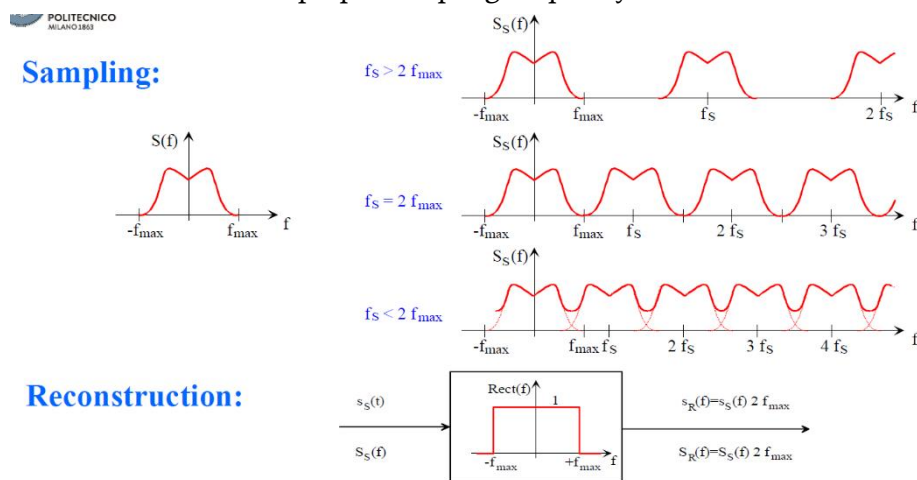It happens when we don't choose the proper sampling frequency.



In the limit case, if $f_s = 2 \cdot f_{max}$, then the replicas touch. If the spectra overlap, we cannot properly reconstruct the signal.

Aliasing in frequency domain

 


We have our signal, a $t_{sampling}$ and in the last row we are obeying the Shannon theorem, so in the frequency domain we will have the original $S(f)$ and some headroom between the replicas.

If Shannon is not respected, either if we filter at f_{in} , we don't simply get our signal but also three replicas, so we have a mis-reconstruction of the original signal.

Anti-aliasing filtering

 Aliasing stems out also from unexpected spurious disturbances with $f_{spur} > f_s/2$




Never trust just on the bandwidth self-limitations of the input welcome signal ...
... anyway, bandpass filtering is a must !


If we know where the frequency content of the signal is, and then eventually we have also spurious disturbances, better not to perform the sampling of the overall signal as it is, but to remove the disturbances.

SPECTRAL DISTORTION AND EQUALIZATION

 
It is easier to employ "rectangular" samples instead of delta-like ones



... but this causes spectral distortion:

 


 Therefore **equalization** is compulsory:



Delta-like samples are difficult to be provided with respect to rectangular samples. Mathematically, the two signals are not the same, but we can say that the rectangular samples is a convolution of the deltas with a rectangular shape whose width is the sampling period.


So we have our original signal made by deltas whose spectrum is composed by replicas of the main spectrum, but now we use a rectangular signal and the spectrum won't be anymore the same as before, because the spectrum of a pulse is a sinc whose zero crossing is equal to $f_s = 1/T_s$. Since in the time domain the rectangular samples are obtained by convolution, it means that in the frequency domain we have to perform the multiplication.

 

The problem is that if now I apply the filter, the spectrum is distorted due to the sinh behaviour. Hence we need to use an **equalization filter**, which is a filter that amplifies the signal with a reconstructing filter that has a gain of 1 in DC and a gain of 1.57 at f_{max} to recover the attenuation.

SIGNAL PROCESSING CHAIN

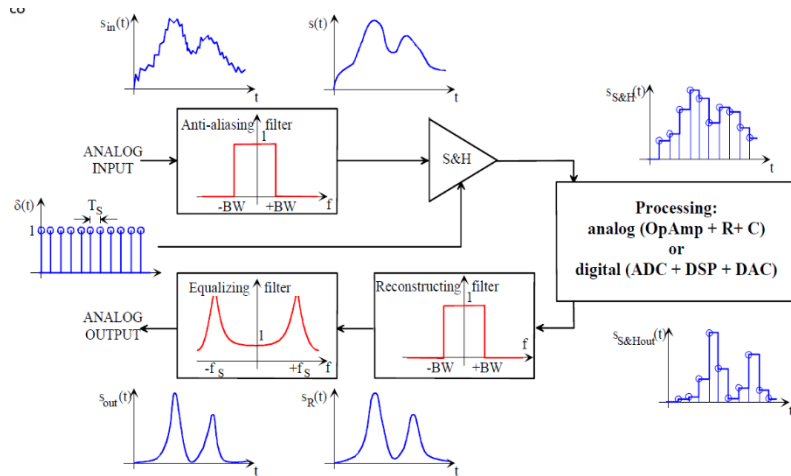In a global signal processing chain we enter with the signal that can be noisy, we use an anti-aliasing filter and we sample it with a proper T_s .



The reconstruction filter can be identical to the anti-aliasing filter and then we should amplify with an equalizing filter due to the distortion introduced by the S&H.

ANALOG FILTERING

To properly reconstruct a sample signal we need filters, either anti-aliasing or reconstructing or equalization ones. We can have different filters, as below.

FIGURE 3-8
The modified Sallen-Key circuit, a building block for active filter design. The circuit shown implements a 2 pole low-pass filter. Higher order filters (more poles) can be formed by cascading stages. Find k_1 and k_2 from Table 3-1, arbitrarily select R_1 and C_1 (try 10k and 0.01µF), and then calculate R_2 and R_3 from the equations in the figure. The parameter, f_c is the cutoff frequency of the filter, in hertz.

$$R = \frac{k_1}{C_1 f_c}$$

$$R_2 = R_1 k_2$$

TABLE 3-1
Parameters for designing Bessel, Butterworth, and Chebyshev (0% ripple) filters.

# poles	Bessel		Butterworth		Chebyshev	
	k_1	k_2	k_1	k_2	k_1	k_2
2 stage 1	0.1251	0.268	0.1592	0.586	0.3666	0.542
4 stage 1	0.1111	0.684	0.1592	1.152	0.1544	0.560
4 stage 2	0.0990	0.640	0.1592	0.668	0.4019	0.537
6 stage 1	0.0941	0.564	0.1592	0.506	0.2072	1.448
6 stage 2	0.0834	1.023	0.1592	1.483	0.1574	1.846
8 stage 1	0.0894	0.624	0.1592	0.638	0.5359	0.522
8 stage 2	0.0867	0.313	0.1592	0.337	0.2657	1.379
8 stage 3	0.0814	0.593	0.1592	0.880	0.1848	1.711
8 stage 4	0.0726	1.184	0.1592	1.610	0.1592	3.013

FIGURE 3-9
A six pole Bessel filter formed by cascading three Sallen-Key circuits. This is a low-pass filter with a cutoff frequency of 1 kHz.

FIGURE 3-11
Frequency response of the three filters on a logarithmic scale. The Chebyshev filter has the sharpest roll-off.

FIGURE 3-12
Frequency response of the three filters on a linear scale. The Butterworth filter provides the flattest passband.

FIGURE 3-13
Step response of the three filters. The times shown on the horizontal axis correspond to a one hertz cutoff frequency. The Bessel is the optimum filter when overshoot and ringing must be minimized.

FIGURE 3-14
Pulse response of the Bessel and Chebyshev filters. A key property of the Bessel filter is that the rising and falling edges in the filter's output look very similar. In the jargon of the field, this is called *linear pulse*. Figure (b) shows the result of passing the pulse waveform in (a) through a 1 pole Bessel filter. Both edges are smoothed in a similar manner. Figure (c) shows the result of passing (a) through a 4 pole Chebyshev filter. The left edge overshoots on the top, while the right edge overshoots on the bottom. Many applications cannot tolerate this distortion.


Stephen W. Smith, www.DSPguide.com
"The Scientist and Engineer's Guide to DSP"

The disadvantage of Chebyshev is that if we look at the time response for a step, the Bessel is smooth but slow. The Butterworth can be faster, but we run the risk of overshoots, that can also be present in the Chebyshev.

HOW TO COMPUTE THE SPECTRUM (FFT)

If we have a signal and the signal lasts for a time T . Then we choose a T_s and we have the samples. If we give the samples to the DFT, the DFT will give us the same number of samples we fed in input, but in the frequency domain. So the number of samples will be T/T_s , and it will be the same number in the frequency spectrum, where the first sample is at $f = 0$, and the last at $f_s = 1/T_s$.

 Moreover, the DFT (and also the FFT) assumes that the signal is periodic. Since after T the DFT doesn't know what there is, it assumes the signal as periodic, retaking the initial value.



The FFT algorithm trusts on the periodicity of the input sequence

... hence FFT spectrum is for the periodic sequence and not the original one!

Since the DFT assumes that the signal is periodic, then a periodic signal has a spectrum made by deltas. But since the spectrum is periodic itself, then it means that the original signal was made by deltas.

Whenever we have a signal, we compute the samples and we apply a DFT or FFT, we get a number of samples in the frequency domain equal to the samples we gave and the spectrum is periodic.

If the original signal was real, then the spectrum is periodic around f_s , and last sample is equal to the first one, so its symmetric. Since the maximum frequency is f_s and we have N samples, the distance between the samples is f_s/N in the frequency domain.

If we sample every T_s , the maximum frequency is $f_s = 1/T_s$. If we sample for a period T of time, the bin width is $1/T$.

Let's imagine we have a sinusoid that is continuous, but we just listen to it for a period T and we take 5 samples every T_s . The DFT will give in output 5 samples with a maximum frequency f_s , and each sample will be separated by the other by $1/T$. However, if we do the same thing but we increase T , the spectrum will be better. f_s will be the same, but we have more samples in the frequency spectrum, because the bin width decreases.



To understand the frequency of a certain sinusoid in time, we compute the spectrum and the smaller the bin width the higher the accuracy with which we detect the frequency.

Moreover, the spectrum may belong to a periodic signal, and this may cause issues, as in the example below.



In the perfect case I see that the spectrum is 0 a part from the 1kHz value, that is the frequency of the sinusoid. But if we add a sample, the last one, that is the same as the first one, now the spectrum is bad, because it is $\neq 0$ in the intermediate points.

In the first case we have stopped before, and since the algorithm for the DFT and FFT considers the signal periodic, we are doing ok. In the other case it's like modifying the signal.

Correct choice:

  


Wrong (unlucky) choice:

  

So increasing the number of samples is something that must be done thoughtfully.

 Due to uneven junction of the input sequence (as assumed by the FFT algorithm)




Therefore, let become independent of the junction...

To solve this problem, we can do windowing.

WINDOWING BEFORE DFT

 The oddness at the junction can be smoothed out through **windowing**



Rectangular (no windowing): $window(n) = 1$ for $-M \leq n \leq M$ and 0 elsewhere

Triangular: $window(n) = 1 - \frac{|n|}{M}$ for $-M \leq n \leq M$ and 0 elsewhere

Hanning (rised cosin): $window(n) = \frac{1}{2} \left(1 + \cos \frac{2\pi \cdot n}{N} \right)$ for $-\frac{N-1}{2} \leq n \leq \frac{N-1}{2}$ and 0 elsewhere

Hamming: $window(n) = 0.54 + 0.46 \cdot \cos \frac{2\pi \cdot n}{N}$ for $-\frac{N-1}{2} \leq n \leq \frac{N-1}{2}$ and 0 elsewhere

Blackman: $window(n) = 0.42 + 0.5 \cdot \cos \frac{2\pi \cdot n}{N} + 0.08 \cdot \cos \frac{4\pi \cdot n}{N}$ for $-\frac{N-1}{2} \leq n \leq \frac{N-1}{2}$ and 0 elsewhere


Given our signal, we window it in the time domain. I can use a rectangular one, that however is like no windowing. After windowing, the signal gets well smooth at the end and it is possible to perform a DFT. The drawback is that the deltas in the frequency domain widens a little, but it is not a huge problem.

SAMPLE AND HOLD CIRCUIT

The idea is that we want to acquire a signal that can be modelled with a voltage generator and it's time and amplitude continuous (fully analog). So we need to reach an ADC and then a microcontroller or microprocessor. Between the signal and the ADC we need to introduce a S&H circuit, which needs to freeze the input signal at specific time instant, so we need to choose a sampling frequency f_s and, once we have selected the sample, since the ADC requires some time for the conversion, we need to keep the signal constant for a certain amount of time, not just providing deltas of signals.

So while the data is constant the microcontroller gives a pulse to perform the conversion. At the end of the conversion the ADC provides the output data and the microcontroller can read it with its input data buffer. We want to design the S&H.

 It can be modelled as a circuit that, when is open, provides a constant information thanks to a charged capacitor. The buffer provides the current without affecting the voltage on the capacitor.



Specs:


Input signal:	-5V ÷ +5V	20kHz bandwidth
maximum admitted error:	< 0.01% FSR = 1mV	
sampling frequency:	100kHz	

Components:

OpAmp:	$A_O=110\text{dB}$	$I_{\text{bias}}=50\text{pA}$
MOSFET:	$V_t=2\text{V}$	$R_{\text{on}}=50\Omega$ $C_{\text{gs}}=0.5\text{pF}$ $C_{\text{ds}}=0.1\text{pF}$

SWITCH

 The switch can be a MOSFET with a proper V_{gs} so that the current that flows through it is given by the following.




The other parameters are depending on the technology of fabrication, except for V_{gs} . We want to provide channel at the source and we don't want it at the drain. So V_{gs} must be higher than the threshold voltage, and V_{gd} should be lower than V_t , not to have channel at the drain. This if we plot I_d vs V_{ds} we have the characteristic on the right. The characteristic increases quadratically with V_{gs} . If $V_{gs} < V_t$ the transistor is off, otherwise it starts to increase the current.

So the transistor can be used as an amplifier if we operate in the saturation region, where the current is proportional just with the input signal and not with the output. This is good because V_{gs} varies depending on V_{in} and V_{out} is not varying depending on itself. So the red and green are the required biasing conditions to have a MOSFET as an amplifier.

Moreover, these two conditions can be put together as $V_{ds} > V_{ov}$.

Instead, in the S&H we need a switch, not an amplifier, we need to connect an input voltage to an output voltage. So the transistor will be used in another configuration. We want to have either no channel both on the source and drain (open switch) or to have channel both in the drain and source. So compared to the amplifier case, we want it to operate in another region, in the ohmic region with sufficiently high V_{gs} or in the completely off condition when $V_{gs} < V_t$.

 


If $V_{gs} \gg V_t$ we have a very low $r_{on} = dV_{ds}/dI_D$, and I want the r_{on} to be very small so that V_{ds} is the smallest possible.

In the amplifier we had to indicate which was the source and the drain, whereas here I have the same behaviour on the source and drain, so I can connect it as I want.

If e.g. I have a nMOS and I want to operate it in triode regime (so channel on both source and drain), given V_{in} and V_{out} (that should be equal to V_{in}), then $V_G > V_{in_max} + V_t$ to have the channel, and if V_{in} moves $+5V$, I must be sure that V_G is higher than the highest V_{in} value and V_t . So I have to apply at least $5.8V$ to have the transistor on. Instead, if I want it off, the worst scenario is when V_{in} reaches the lowest value, so $V_G < V_{in_min} + V_t$ not to have the channel.

CIRCUITAL IMPLEMENTATION

 So the analog signal is applied to the source or drain of the mosfet, accumulated on a capacitor and given to the buffer. The value must be stored and computed without committing an error, so we need to understand which the sources of errors are. The following are the specifications we are considering.



Specs:

Input signal:	-5V÷+5V	20kHz bandwidth
maximum admitted error:	< 0.01% FSR = 1mV	
sampling frequency:	100kHz	

Components: OpAmp: $A_O=110dB$ $I_{bias}=50pA$
MOSFET: $V_t=2V$ $R_{on}=50\Omega$ $C_{gs}=0.5pF$ $C_{ds}=0.1pF$

I'm considering a transistor whose on resistance is limited to 50ohm.


ERRORS

CHARGE INJECTION

Let's compute the V_G value that keeps the MOSFET close. I'm considering V_{in} moving from $+5V$ to $-5V$, if we apply a $V_G = 10V$ to close the switch and $V_G = -7.5V$ to close it.

Having chosen a n-channel transistor we need a V_G high to keep it close and low to keep it open. It's the opposite if we would use a p-channel, so to have it on $V_G < V_{in_min} - V_t$ and in the off configuration $V_G > V_{in_max} - V_t$.
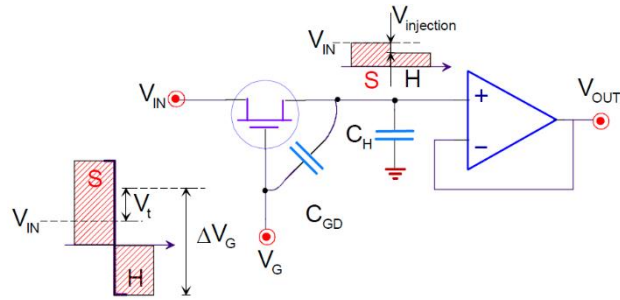
$$V_{injection} = \Delta V_G \cdot \frac{C_{gd}}{C_{gd} + C_H}$$



$$V_{G \text{ SAMPLING}} > V_{in,max} + V_t = +7V$$

$$V_{G \text{ HOLD}} < V_{in,min} + V_t = -3V$$

Let's chose:

$$V_{G \text{ SAMPLING}} = +10V$$


$$V_{G \text{ HOLD}} = -7.5V$$

To guarantee $V_{injection} \leq 1mV$ with $\Delta V_G = \Delta V_{G \text{ max}} = 17.5V$ we chose $C_H \geq 9nF$...

... hence the bandwidth is set to just **354kHz**


If the MOS transistor is fully symmetric, it's difficult to understand which is the source and which is the drain.

 If the MOS transistor has the following cross section, then it is symmetrical (pMOS).




nMOSFETs carry higher current with respect to pMOSFET because of the higher mobility. But then the type of transistor to be chosen depends also on the voltages we are able to apply to the gate of it, if positive or negative.

 In reality, a transistor is not fully symmetric because we have, in the previous example, a floating n-well not connected to anything, and to avoid this (that could change the threshold due to the body effect) another n+ region is created in contact with the well and it is the bulk terminal. So we have 4 terminals in the transistor.



 
If, instead of 4 pins, the transistor has 3 pins, it means that internally the manufacturer has connected the bulk to the source. The fact that we connect the source with the bulk causes, however, an asymmetry. Thus we create a reverse bias diode.




The diode has no effect if I use the transistor as an amplifier, because the drain is usually at higher voltage than the source for a nMOSFET, but it is relevant if I use it as a switch for S&H.

If we have the V_{in} and we buy a discrete component transistor (circled) with 3 pins, if V_{in} is lower than the voltage stored on the capacitor we are ok, the transistor is off and to turn it on we have to apply high V_g . But even if V_g is in the hold phase, so sufficiently low to have the MOS off, still V_{in} moves and if it

 happens that $V_{in} > V_H$ the diode is on, so the transistor is off but the current flows anyhow and we charge the capacitor.



So we have our V_{in} , the S&H signal, and when we sample the transistor is close, so $V_{out} = V_{in}$ and when we open we would like V_{out} to be in hold phase, and when we reclose the switch we want to quickly track V_{in} again. The red one is the ideal operation. But if $V_{in} > V_{hold}$, then the parasitic diode turns on and it causes the transistor to conduct a current, so V_{out} follows V_{in} with a distance equal to $0.7V$, voltage drop across the diode. Then when the voltage decreases below V_{hold} , the capacitor has stored that value and it goes in the hold condition and it stays like there until the signal becomes high and chases it again.

 


The green one is the behaviour we want to avoid, so we cannot use a 3 wires transistor, we have to use a 4 wire transistor, with the bulk contact connected to the most negative PS (if nMOS, positive is pMOS). If the bulk is sufficiently negative, we don't suffer no more of the problem because we sufficiently reverse bias the bulk-source and bulk-drain diodes.



So we cannot use a transistor with the source connected to the bulk.

Every time we open and close the switch, any parasitic capacitance between a node that goes up and down (gate) and the other one that is connected to a floating component (the capacitor), that parasitic capacitance (C_{gd} in the image) causes charge injection. Since the sampling capacitor is connected to anything, we have this problem.

 So we have our V_g that moves from V_{g_hold} to $V_{g_sampling}$ and then again V_{g_hold} .



During the rising edge transition of the V_g , the transistor is on and closed, so there is current and the capacitor charges up to V_{in} . When we have the falling edge transition, soon or later the transistor will be open and the switch will be open, so there should be no variation at V_{hold} , but there is a coupling due to the parasitism of the capacitance. If we change the volage at the V_g , we change the voltage at the series of the two capacitors. If V_g changes, both V_H and V_{gd} changes. How much? We use the partition of voltages.

  

So the higher Ch is, the lower the change in the Vh stored in it. So to reduce this error in the falling edge transition we need to increase the Ch value.

For instance, if delta_Vg total = -17.5 to move from sampling phase to the hold one, we should store the value of Vin, but due to charge injection we see a drop in the voltage stored on the capacitor, delta_Vh, due to charge injection.


It is called charge injection because if we change the voltage delta_Vg, voltage across the capacitor is given by $C = \Delta Q / \Delta V$, so given a capacitor Cgd, if we change the charge across it also the voltage across it will change. The same for Ch. Since Cgd and Ch are in series, the two delta_Q are equal, so if we change delta_Vg we cause the injection of a charge in both, so both Ch and Cgd must discharge.

So charge injection happens every time we open a transistor and from the node of the gate to the high impedance node where there is a capacitor we have a stray capacitance.

We know the value of Cgd and the full jump from Vg up to Vg down, -17.5V, so we know the value of Ch that we can choose.

MULTITECNICO MILANO 1985
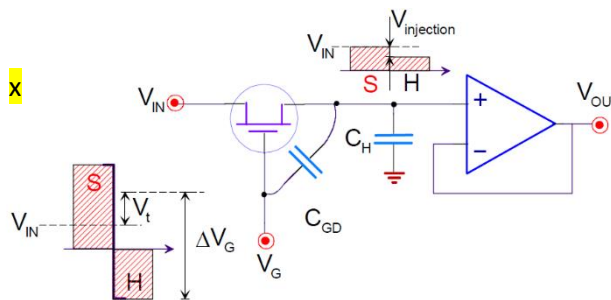
$$V_{\text{injection}} = \Delta V_G \cdot \frac{C_{gd}}{C_{gd} + C_H} \quad \times$$



$$V_{G \text{ SAMPLING}} > V_{in, \text{max}} + V_t = +7V$$

$$V_{G \text{ HOLD}} < V_{in, \text{min}} + V_t = -3V$$

Let's chose:

$$V_{G \text{ SAMPLING}} = +10V$$

$$V_{G \text{ HOLD}} = -7.5V$$


To guarantee $V_{\text{injection}} \leq 1mV$ with $\Delta V_G = \Delta V_{G \text{ max}} = 17.5V$ we chose $C_H \geq 9nF$...

... hence the bandwidth is set to just **354kHz**

The highest capacitance possible is not a good idea because then when we close the switch there will be a given r_on that will go in series with the Ch that cause a tau that gives us the acquisition time of the system.

If we have Vin and the S&H signal, the stored voltage is on the capacitor, and when we close the switch we should quickly reach the new value of Vin but the charge on the capacitor will increase with an

 exponential curve and it depends on the tau. So either we use a lower r_{on} or we choose a low C_H , as low as possible to speed up the acquisition but not too low to have relevant charge injection.




To be more precise, in the equation x we considered ΔV_G as the full transition, from +10V to -7.5V, but when the switch is closed, the voltage on the capacitor is set by V_{in} . The capacitor is then alone when V_G is sufficiently low and given V_{in} , if we apply a $V_G > V_{in} + V_t$ the transistor is on. So the ΔV_G to be used is not the full V_{in} swing, but just the portion where the V_G determines the openness or closure of the transistor. The problem is that ΔV_G , in this way, depends on V_{in} . This also means that $V_{injection}$ changes with V_{in} .

Hence the Charge Injection is not a constant error.

APERTURE-INDUCED NON LINEARITY

POLITECNICO MILANO 1875
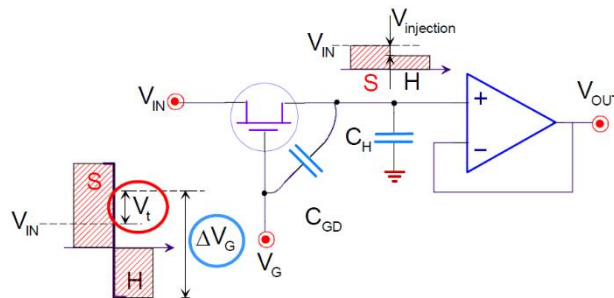
$$V_{injection} = \Delta V_G \cdot \frac{C_{gd}}{C_{gd} + C_H}$$



$$\Delta V_G = V_{IN} + V_t - V_{G\text{HOLD}} = V_{IN} + 7.5V$$

It is not constant, but depends on V_{IN} !

Charge injection error is not constant:

$$\begin{aligned} \Delta V_{G\text{min}} &= V_{IN\text{min}} + V_t - V_{G\text{HOLD}} = -5 + 2 + 7.5 = +4.5V & V_{injection} &= 250\mu V \\ \Delta V_{G\text{max}} &= V_{IN\text{max}} + V_t - V_{G\text{HOLD}} = +5 + 2 + 7.5 = 14.5V & V_{injection} &= 806\mu V \end{aligned}$$

This is not a constant error. If when I take a V_{in} and close and open the switch and the V_{inj} is constant, there is no problem, because I know how to compensate it eventually, because I know the gap between V_{in} and the value of voltage I'm storing on the capacitor. But since V_{inj} changes depending on V_{in} , this is bad.


In the samples I'm acquiring from the microcontroller, we have different errors if the sample has a high or low value. The error gets reducing the more the value sampled becomes low.

So a constant error can be compensated, such as the offset of the opamp, but if it is not constant it is bad.

SIGNAL FEEDTHROUGH

MILANO 1883
 
$$V_{\text{feedthrough}} = \Delta V_{\text{IN}} \cdot \frac{C_{\text{ds}}}{C_{\text{ds}} + C_{\text{H}}}$$



With $\Delta V_{\text{IN max}} = 10\text{V}$ we get $V_{\text{injection}} = 111\mu\text{V}$

... negligible (in this case) compared to the requirements of $<1\text{mV}$

When the switch is open there is a parasitism between source and drain that causes the values across the capacitor C_{H} to change, even if the switch is open.


If we apply $+5\text{V}$ and the switch is close, then I open it and I should have 5V on C_{H} , but if the input drops to -5V I get a V_{inj} on the capacitor of $111\mu\text{V}$, and it's ok because I'm tolerating errors up to 1mV , so we can neglect it.

Of course we cannot neglect it if the C_{ds} is high, the swing in input is high or the C_{H} is low.

DROOP

When the switch is open, the capacitor stays constantly charge in theory, but if there is a leakage, so a current in the transistor or the bias current of the opamp, this leakage current causes a voltage drop.

 
$$\Delta V_{\text{C}} = \frac{I_{\text{leakage}}}{C_{\text{H}}} \cdot t$$



With $I_{\text{leakage}} = 100\text{pA}$ and $C_{\text{H}} = 9\text{nF}$, the stored voltage will droop by 11mV/s

Hence with $f_{\text{s}} = 100\text{kHz}$ we get $\Delta V_{\text{C}} = 0.11\mu\text{V}$ every $10\mu\text{s}$ Hold duration

 
This means that when the transistor gets open, V_{in} can move and the V_{h} should remain constant, but it is not like that, we have a droop that has a slope $dV/dt = I/C$, so the error after a given aperture time is the red one.



If in our case we considering the operation with a sampling frequency $f_{\text{s}} = 100\text{kHz}$, it means that in the worst case scenario the sampling is very short and the hold is very long (not the same duration for both).

If so, the error due to the droop is 0.11 uV, which is still negligible because Ch is sufficiently large and leakage is low. But if we change the opamp, then droop can become an issue.

BUFFER-INDUCED NON LINEARITY

 


To guarantee $\epsilon < 1\text{mV}$ we must have $A_0 > V_{\text{out,max}}/\epsilon = 5,000 = 74\text{dB}$

We know the buffer has a limited A0, so ideally the epsilon is 0, but since A0 is finite, to have a given voltage at the output the epsilon will be Vout/A0. Since I want epsilon < 1 mV, then Vout/epsilon = 5000, meaning that we cannot buy whatever opamp we want, but an opamp whose A0 is higher than this value.

APERTURE DELAY TIME

MILANO 1853


$$\Delta V_{\text{aperture}} = \left. \frac{dV_{in}}{dt} \right|_{\text{max}} \cdot T_{\text{aperture}} = 2\pi \cdot f_{\text{max}} \cdot V_{in,\text{max}} \cdot T_{\text{aperture}}$$

 

With $T_{\text{aperture}} = 1\text{ns}$ we get $\Delta V_{\text{aperture}} = 2\pi \cdot 20\text{kHz} \cdot 5\text{V} \cdot 1\text{ns} = 0.63\text{ mV}$

It's a **dynamic error**, so far we have considered static ones. Data is sampled in the falling edge transition because during sampling the switch is close and when I move from S to H the switch gets open. So the sampling transition is the falling one, because I remain constant in the H phase when I open the switch. But maybe the Vg voltage requires some time to commute from high to low when the microcontroller gives the command.

 The uC commands the ADC and the S&H phases. The typical PS of uC is 3.3V, so the signal to the S&H circuit is e.g. from 0 to 3.3V. But to the gate we need 10V/-7.5V. so we cannot directly connect the uC, we need a voltage amplifier stage between the uC and the S&H circuit.



In the hold phase we apply -12V hence, and in the S phase 12V. This is good because even higher and lower the one requires. But from the time when we apply the command and the swing is done by the transistor some time instants appear. So the aperture delay time causes a sampling error, because we are not sampling the value at the time instant we want.

Let's compute this error. It depends on how fast V_{in} is, so if I don't know V_{in} I cannot quantify it. The highest error occurs when V_{in} changes with the fastest speed. The maximum speed of variation is where we have the maximum frequency f_{max} . So the maximal speed is like having a sinusoid at f_{max} of the signal.


So let's consider a sinusoid at f_{max} : $V_{in} = V_p \cdot \sin(2\pi \cdot f_{max} \cdot t)$

Let's now compute the maximum value of the slope of the signal, so we compute the derivative and we take the maximal value. So the maximal value of a sinusoid is:

$$\frac{d V_p \cdot \sin(2\pi f_{max} t)}{dt} \Big|_{max} = V_{peak} \cdot 2\pi f_{max} \cdot \cos(2\pi f_{max} t) \Big|_{max}$$

$$max \text{ slope of input signal} = V_{p,max} \cdot 2\pi f_{max} = \frac{dV}{dt} \Big|_{max}$$

 If we know this and we multiply this for the maximum aperture delay we get the maximal possible error. Aperture time $T_{aperture}$ depends on the electronics, such as due to the SR of the opamp that drives the gate signal.




This error is pretty high with a $T_{aperture} = 1ns$ even. If the SR is so large, so us, this error can be very huge.

Is this delay really an issue?

It depends on the application. In some ones, like in the audio applications, we just need a sufficient number of samples with a proper spacing coherent with the Shannon theorem. But the Shannon theorem never tells where to start, so the comb with which we sample the signal is different, if the delay is constant along all the samples, then there is no problem at all. So if the aperture delay is constant for all the samples it is not a problem.

However, there are also other applications where it is important to properly sample the signal and measure its intensity to know the position of, for instance, of the peaks starting from a specific time instant. In this case, even if the delay is constant we run the risk of sampling a sub-maximal value, not the maximal one.

APERTURE TIME JITTER

 

In case of a CMOS drive: $\Delta V = 6 \cdot \sigma_{aperture} = 75\mu V_{DD}$ (18bit) trascurabile

The problem is that the aperture delay could be not constant, so it is really a big issue in this case.

Let's consider the following example. Previously, when the uC applies the commutation, we crossed the threshold of the Schmitt trigger, output went low and we had the opening of the switch. And this happens at a precise voltage.

However, there may be some fluctuations on the power supply and so on the threshold. The opamp is noisy as well as the resistors, so the threshold is not constant but noisy.

If the threshold is not constant, apart from the delay to the time the threshold is really crossed, there may be a jitter.

To quantify it we need to know the vertical fluctuation of the threshold, then the slope of the commutation so that we can compute the jitter in amplitude. Given the vertical sigma, the horizontal one depends on the slope of the commutation. Once we have the horizontal jitter, the vertical jitter of the stored value depends on the slope of the Vin signal, and we can use the same equation used for the aperture delay time.


The 13uV value we get is either the sigma or the peak-to-peak value depending on the way in which we quantify the fluctuations in the threshold value.

To understand how big this error is we need to look at the following ADC. Depending on the number of bits of the ADC, the ADC can quantize the analog input signal with a LAB resolution of mV, uV or less.

So depending on the number of bits this error is negligible if bits are few, but if the ADC has a lot of bits, then the error is significant because the ADC resolution is very high.

ACQUISITION TIME

POLITECNICO MILANO 1863

 


Acquisition (Sampling): **linear ramp** $t_{SR} = \frac{10 - \Delta}{SR} = \frac{(10 - 1.25)V}{2.8V/\mu s} = 3.1\mu s$
 and **exponential charge** $t_{lim} = \tau \cdot \ln \frac{\Delta}{\epsilon}$

For example: with $I_{Out,max} = 25mA$ we get $\Delta = 50\Omega \cdot 25mA = 1.25V$

It's still a dynamic error. We are in the sampling phase and we track the signal. Then we move to the hold phase. V_h is fixed and V_{in} moves. Then we move again to sampling; in the worst case scenario we have stored the minimum input signal on C_h and then we need to acquire the maximum input signal. So we need to move e.g. from $-5V$ to $+5V$. The time needed to reach the final value is called acquisition time.

 If the circuit was the following one, when I close the MOSFET it acts as a R_{on} , so I have an exponential increase to $5V$ from $-5V$.



The tangent of the curve in the origin touches the asymptotic value after τ . Hence the following.

$$\left. \frac{dV}{dt} \right|_{max} = \frac{\Delta V}{\tau}$$

From this equation we can compute the time that it takes to reach the final value. Theoretically, the error $\epsilon = 0$ will be reached after an infinite time. Once defined the maximum error we can accept we can define the acquisition time (equations to be remembered).

$$\epsilon_{min} = \Delta V \cdot e^{-t/\tau} = \epsilon$$

$$t_{acq} = \tau \cdot \ln \frac{\Delta V}{\epsilon}$$


In our case we have to perform the following calculation.

$$t_{acq} = R_{on,max} \cdot C_h \cdot \ln \frac{10V}{1mV} = \tau \ln 10000 = \tau \cdot 10$$

Time that the sample and hold takes to move from the previous stored value during the hold phase up the then new value during the sampling phase. It is a transition modelled with an exponential charge.

When the switch is closed, it behaves like a R_{on} , the capacitor has its capacitance and so we have a $\tau = R_{on} \cdot C_H$. Hence if this is the circuit, V_{out} will move from the previous value (-5V in the worst scenario) to the new value (+5V). We need the time for the capacitor to charge to the new value. We will have an exponential increase whose τ is the one previously calculated.

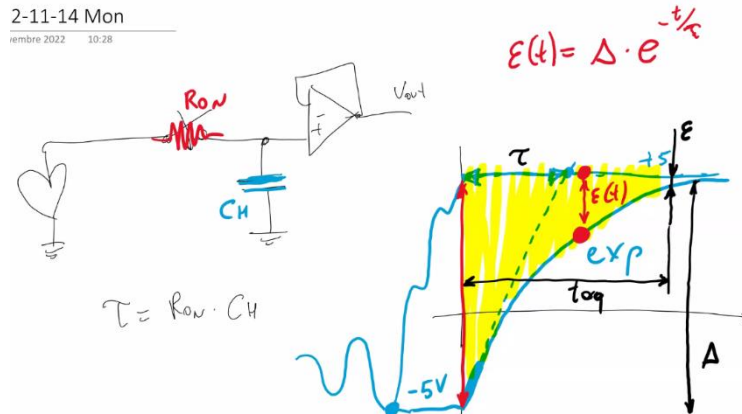The time needed to acquire the proper value depends on the epsilon value we are willing to reach at the end of the transition.




From the equation for epsilon we get the time of acquisition.

Unfortunately, in a real circuit we can have also other limitations. The circuit could be driven from a previous stage, e.g. another opamp, that could introduce a further limitation.

The opamp has two issues: the slew rate and the maximum current the opamp can provide to the external circuit.

 Hence if the load is a resistive one and the input varies too fast, due to SR the output of the opamp will have a transition limited by the SR.



Moreover, if the output of the circuit is not just a resistor but a capacitive load also, the voltage output depends on the current that flows in the capacitor divided by the capacitance itself. If the output is current limited, the maximum variation we can reach by charging the capacitor depends on the maximal current of the opamp.


$$\left. \frac{dV_{out}}{dt} \right|_{max} = \frac{i_c}{C} \Big|_{max} = \frac{I_{out_{max}}}{C} = -$$

Hence the output with a capacitor has a limited slope that can achieve depending on the capacitance value. Hence we have a limitation in the swing from one value to the other that is slower than the one predicted by the external SR of the capacitor, but that is due to the $I_{out,max}$ capability of the opamp. So the voltage swing can be determined by the SR or the $I_{out,max}$ depending on which is the minimum.

If before a S&H stage we put e.g. a buffer, when we close the switch we have the limitation set by the $\tau = R_{on} \cdot C_H$, but also another limitation set by the $I_{out,max}$ of the opamp or the SR of the opamp. We need to understand which between these last two is the lowest (i.e. the more limiting) and we consider it.

If this is the case, in the transition from on value to the other, it is not an exponential curve till the end, because it is given just by $R_{on} \cdot C_H$ (and so Δ/τ initial slope), but the slope at the beginning of the transition may be smaller if the input opamp cannot provide the one we need.

So what happens is that we store a value and once we move from the hold phase to the sampling phase the switch closes and we need to reach the new final value. But the transition is not an exponential curve with an initial slope of Δ/τ if the opamp has a limitation that is smaller. We will have the dV/dt max of the opamp. This limitation of the opamp causes the transition to be slower, and it will stop acting on the circuit when the residual Δ we need to perform will have a new value Δ^* so that it is left just an exponential transition, and this happens when the two slopes are equal, the one of the starting exponential to the one limited by SR.

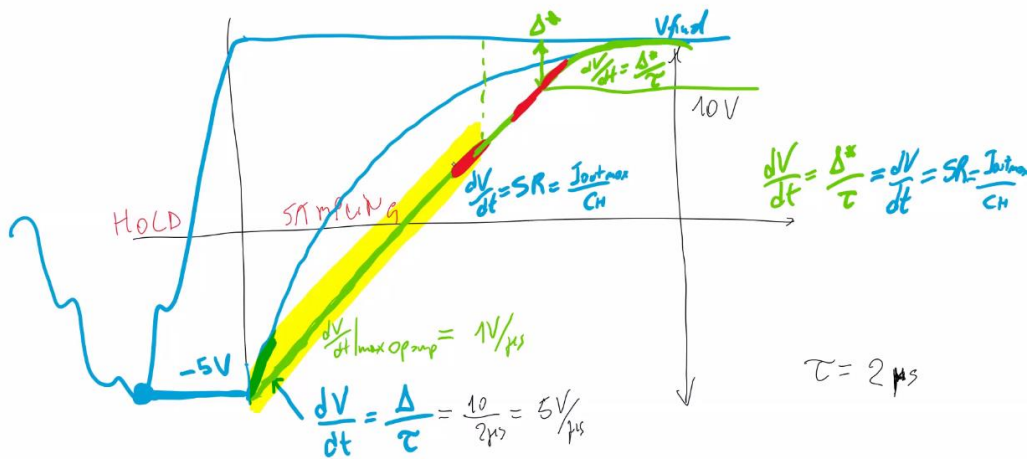


We need to find the value of Δ^* , that is the portion attended with an exponential curve.

$$\Delta^* = \frac{I_{out,max}}{C_H} \cdot R_{on} \cdot C_H$$


So on the top of the transition t_{acq}^* , where the transition is exponential, we need to add a t_{SR} limited transition, where the transition is linear. The total t_{acq} is the sum of these two times (at the written test we can forget about the SR limitations and consider the transition exponential).

Example of SPICE simulations

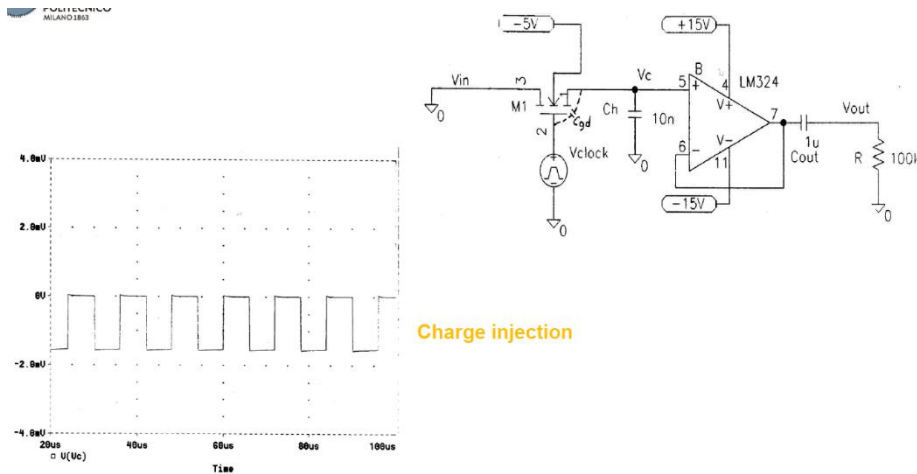

The switch is made by a n-channel transistor. In the + voltages we are in the sampling phase. Then when the gate goes negative there is charge injection that stores charges on the capacitor, and voltage goes down to -2.2mV.

 If we consider a sinusoid and we keep closing and opening the transistor, if the transistor is close we are in the sampling phase. Then we close it and we open it again, but Vout doesn't reach Vin immediately, but later due to t_{acq} . If we open the switch before reaching the input signal we are sampling a wrong value.




If we zoom the region where we have the hold phase, we have a peaking when we open the switch (due to charge injection) and then during the hold phase we are not flat, but increasing or decreasing due to droop.


CHARGE INJECTION COMPENSATION

In order to compensate charge injection we introduce a dummy pair. In fact, in a standard S&H, in theory $V_{ch} = V_{out}$ when the switch is close, but when we open the switch, due to the parasitism and the capacitance C_{gd} , we have the voltage on C_H to change because there is a path through C_{gd} . So value stored on the capacitor is not the ideal value, but we have an injection error.

 Depending on V_{in} we have a certain value of ΔV_g . So this error varies with V_{in} so it cannot be subtracted after the ADC conversion.



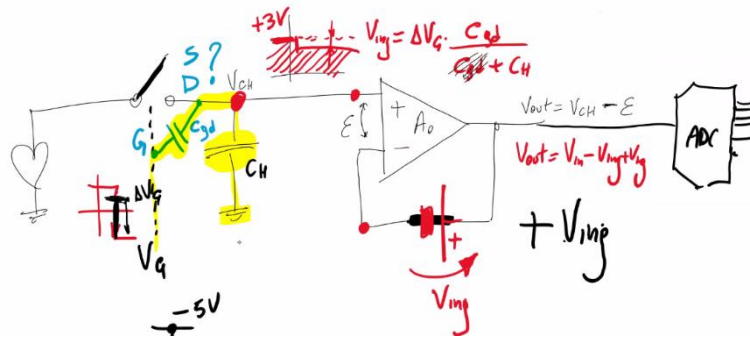
What we can do is trying to compensate the error in another way. If we know the value, we can sum that error in the circuit. Since the value stored on the capacitor decreases by V_{inj} we can place a battery equal to V_{inj} so that the output voltage has this quantity readded to the output.




To put a battery in series to the feedback loop of the opamp we can create a dummy cell. To compensate an error due to a transistor we introduce another transistor. The buffer has in feedback a transistor that closes when the sampling transistor closes (so we have a buffer) but that it opens also when the other transistor is open. So we add also a capacitor in feedback so that when we open the transistor the capacitor acts as a battery and the feedback is connected, so the opamp behaves like a buffer. Of course we shouldn't wait too much or the capacitor decreases.

The advantage of this configuration is that both the two transistors have parasitisms C_{gd} , when V_g is high we charge the capacitor in feedback to 0V. Then, when we apply a transition to V_g , there is a portion of the transition that causes charge injection. But the value of V_g that cause the transistor to move from on to off happens in the same way for both transistors. So the two capacitors will experience the same charge injection. This charge injection through C_{gs} in the input mosfet is of no importance because we are injecting in a voltage generator, so C_{gs} is not impacting on charge injection. The effect is on C_{gd} .

 In the dummy cell, again the C_{gs} is connected to the voltage source of the opamp, so it has no effect, while C_{gd} touches a node that is floating, because the transistor is open (high impedance) and then we have the - terminal (high impedance). So charge injection affects in the same way the two capacitors.



 This applies if the two cells are equal. If the two have some mismatches, the final error at V_{out} will be the $V_{inj,1} - V_{inj,2}$ ($V_{inj,2}$ being the one in the feedback of the opamp). What remains is x.



M2 mimics M1 and eventually inject the same charge, but in opposite direction


Only the residual contribution due to the mismatches remains $V_{injection} = \Delta V_G \cdot \frac{C_{gd}}{C_H} \cdot \left(\frac{\Delta C_{gd}}{C_{gd}} + \frac{\Delta C_H}{C_H} \right)$ X

In this way it is possible to reduce C_H from 9nF down to just 450pF, with the same charge injection.
 So the acquisition time improves (300ns instead of 6.3µs); the signal-feedthrough worsens

In any case, V_{inj} is now lower, so we can use also a C_H that is smaller, which allows to have a shorter acquisition time. The problem is that, if we reduce C_H , there is also the C_{sd} parasitism, and signal-feedthrough increases. If C_H is huge, this latter error is negligible, but if we reduce C_H it becomes relevant.


SIMPLIFY DRIVING

 Let's suppose to have an inverting amplifier with the resistances of the same value, so a gain of -1. We also put a capacitor in feedback to charge it during the sampling phase. Now we want to introduce a switch, and we have to place it like in the image.



Thus we still have a feedback through the capacitor and, even if the input changes when we open the switch, in output we have V_{in} . So the switch must be placed between nodes where the voltage is 0 so that the transistor will be easy to turn on or off. In fact, node x will be 0V in the sampling phase when the transistor is on. Moreover, in this brand new S&H the voltage we need to apply to the mosfet is simply +5V or 0V to keep it open or close.

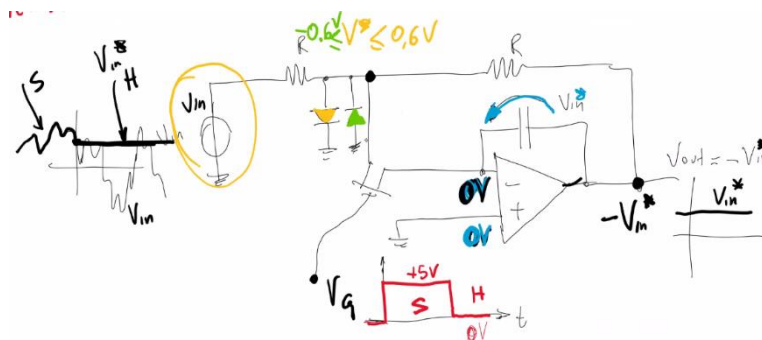However, if the switch is open, node x varies because it is between a varying source (V_{in}) and the output. But this is not a problem because the output voltage is set by the capacitor, so it is not changing. The problem is then to bring node x back to ground, and if it was to a high value, the transistor may have problems. So I don't want node x to be too far away from the V_G value.




So what I can do is to introduce two diodes in counter opposition so that the voltage at node x is less than 0.6V or below -0.6V. Now when we close the switch the t_{acq} is faster.

As a final concept, we have to consider charge injection. Every time we open the switch we change the value stored on the capacitor due to charge injection. Due to the parasitism C_{gd} the voltage V_{ch} changes.

$$V_{inj} = \Delta V_g \cdot \frac{C_{gd}}{C_H}$$


There is no C_{gd} at the denominator because of the virtual ground.

 So if we apply a transition at the gate ΔV_g , we apply it between V_g and ground, so charge variation across C_{gd} is $Q = C_{gd} \Delta V_g$. But this charge must flow into C_H , and C_H touches ground, so its output changes because the Q is the same but the capacitor is different.




Hence every time we open the switch we cause V_{inj} in C_H .

To compensate for V_{inj} we cannot use a dummy cell in feedback because C_H is already in feedback, so we have to play with the other pin. In order to compensate charge injection we have to include a dummy cell by moving the + terminal by the same amount of the - one. The two transistors are driven with the same gate voltage. When we close both switches, the added C_H has 0V stored because of ground. When the switches are open, the added capacitor charges up to V_{inj} and the same the feedback one, and again they cancel out.

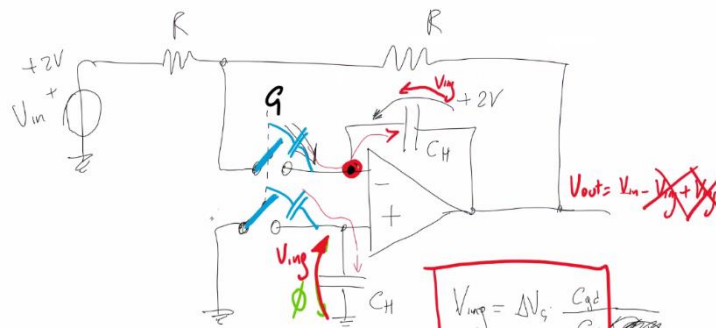

A final issue; opamp requires I_{bias} that flows in the two branches, and they see $R || R$ on the - termina, and GND on the other pin. This will cause an error in the output, so we need to compensate the bias current. To do so, we introduce a resistor equal to the impedance we see on the other path.

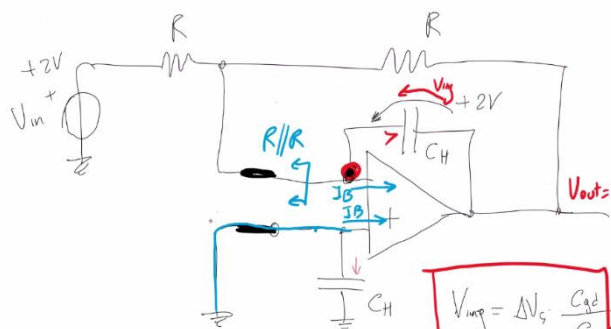


The final implementation is the one below.

What happens in terms of droop?

We have two capacitors, and the two I_{bias} will cause droop on the two capacitors. But does this circuit suffer from a double intensity droop error with respect to the classical S&H configuration? Does droop compensate?


POLITECNICO MILANO 1863

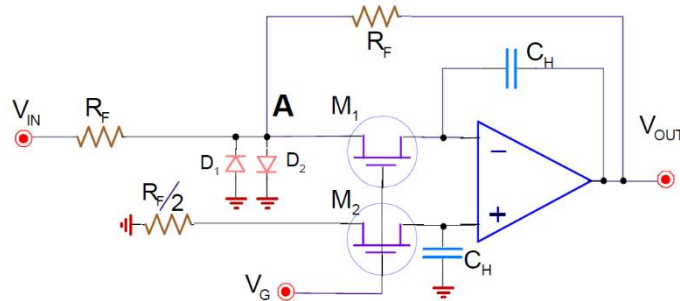

- V_G can have simple low-voltage CMOS levels (0-3.3V), independent of V_{IN}
- the *Aperture-Induced non-linearity* can be drastically reduced

SPEED UP THE SWITCH


POLITECNICO MILANO 1863

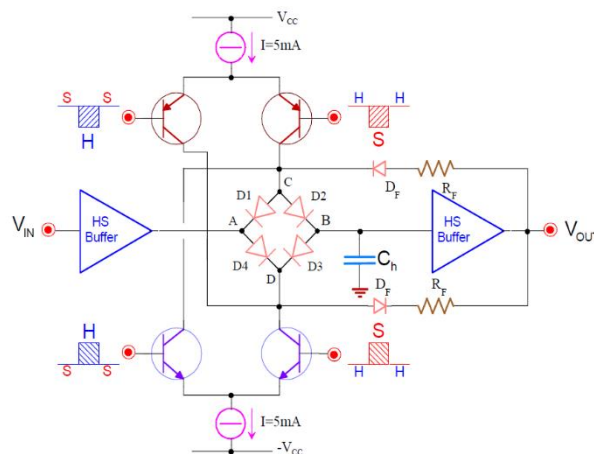

- fast diodes
- criss-cross
- poor accuracy
- timing issues to solve


This is a real schematic. We are designing a new S&H circuit. I want to enter with a signal V_{in} , put a switch and then place the capacitor and the buffer; I want to improve the switch, not using a slow problematic MOS transistor. We could use a BJT transistor, but it is not a good switch because its R_{on} is not symmetric for positive and negative voltages.

 A diode bridge can be used as a switch. This configuration was used after a transformer to convert an AC signal into a DC one. The diode bridge converts the negative peaks into positive one, and then we use a capacitor to have a DC value.




Moreover, if we connect the bridge as in the image, and we pump current in the bridge, it will split and if we have a current source also on the other side and the two currents are matched, the one below drinks the current. So all the diodes are on and hence we have the following voltages. The voltages there (?) will be set by the r_0 of the current generator, but I don't care.

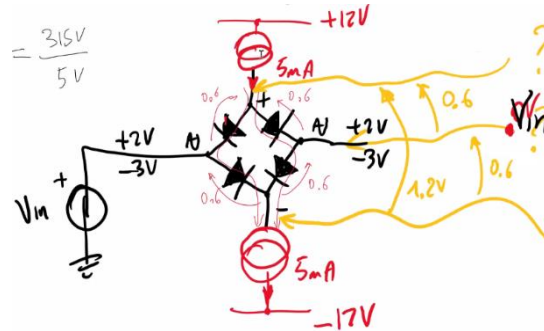
The idea is that if we apply V_{in} to the other node of the diode bridge, the output will be V_{in} . If now we remove the current generators, the diodes cannot stay on.



 If the diodes are open we have no longer control on the output with V_{in} voltage, because diodes are counteracting, so neither I charge the capacitor nor it discharges (red diodes in the image are stopping the current flow).



To stop the current generator to provide a current is to put a switch in parallel to the current generator so that when it is closed the current recirculates, but we have that in this case the PS voltage is put to the upper node of the bridge and we break everything. To stop the current flow we hence may add a transistor. But this is not feasible because if the switch is open, the current it pumped into a node with infinite impedance, which gives infinite voltage at that node, and the switch breaks.

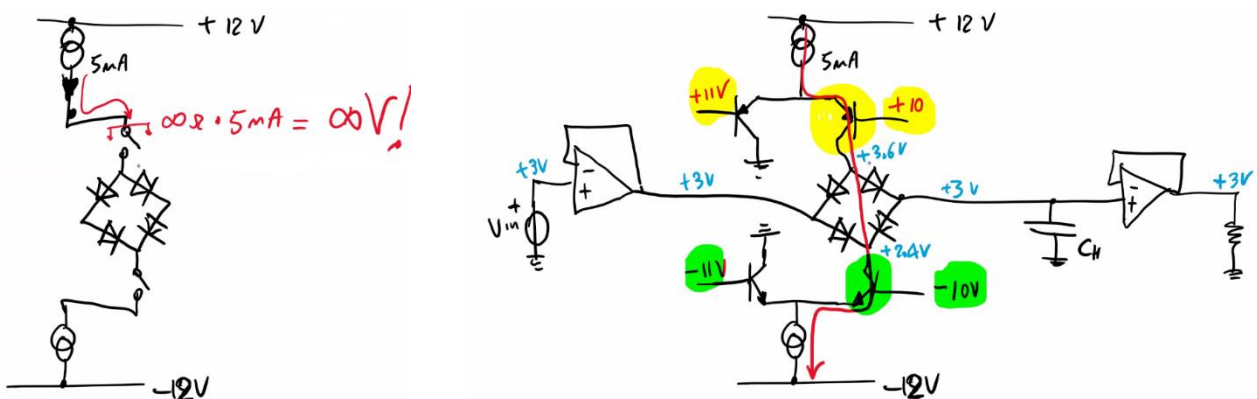


So what we should do is to use a differential pair (pnp and npn transistors). If the bias is the one on the right image, the right transistors are on. So we can use a buffer to apply a V_{in} voltage, and the output goes to a capacitor and eventually an output buffer to provide a current to the load without discharging C_h .

If we invert the bias voltages on the bases of the transistors, the current is in the other branch and the bridge is off.

Of course, the driving of these transistors is not so easy with these high values of voltage. The basic advantage of this configuration is that the diode bridge can be turned on and off very quickly because made just by pn junction, so we don't have to charge a polysilicon gate as in the MOSFET to create the charge in the channel.

This is hence a very fast configuration where we can use high values of current. So we can provide a switch where the r_{on} , impedance from input to the output when the bridge is conducting, is $(1/gm + 1/gm) || (1/gm + 1/gm)$.

A minor disadvantage is the signal feedthrough. In the off configuration, transistors are off but, if V_{in} tries to go positive, e.g. 5V, and the voltage on the capacitor is 3V, one diode is on slightly and the other off, both on the top and bottom paths. If one diode is slightly on, then the voltage drop across is almost 0.3V (not forward bias 0.6V because it is not conducting current). So we have the input/output capacitance of the diodes that is not nihil.

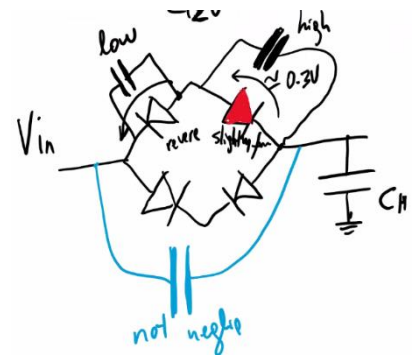


To reduce signal feedthrough across the bridge we need to decrease the parasitic capacitance. To do so, we need to increase the reverse bias. But since V_{in} can be at most 5V in this config, and the voltage across the capacitor -5V, we have at the most 10V of reverse bias on the diode.

In fact, given a diode, if we increase the reverse bias, the capacitance between the anode and the cathode decreases.

In the current configuration, current in the OFF stage is drunk from ground or place to ground. So we change the configuration as below.

FALLENBERG MILANO 1863

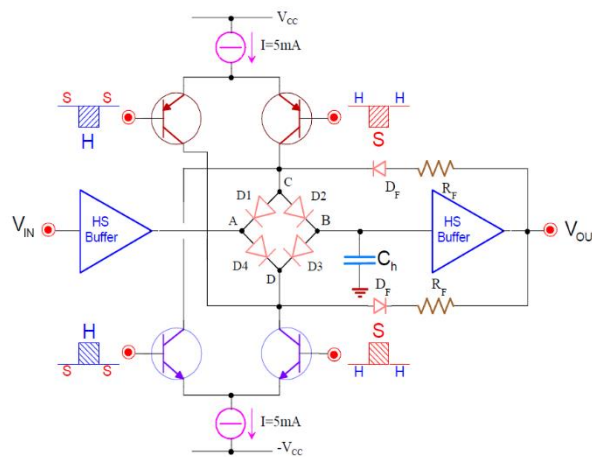

- fast diodes
- criss-cross
- poor accuracy
- timing issues to solve

In the off configuration we don't ground the currents, but I pump them in D in off config, and pump in C. Thus the current cannot go upward in D point or in the BJT at the bottom, and the same for the C point. So I introduce a path, resistor and diode, where the current can come from. The diode is introduced to have only one direction of flow for the current. And the same current that is drunk from the top node is pumped in the bottom node. Hence the two currents compensate and the output buffer has no current to provide.

These currents will generate a voltage across the resistors R_f (5V) and we have node C that goes below (5.6V below 3V) and D goes above (5.6V above 3V).


Hence the reverse bias is so high that the parasitic capacitance is low and the signal feedthrough is drastically decreased.

So far the, in the ON configuration, 5mA are flowing in the red and purple BJT, so there is no current in the buffer and no current in the capacitor Ch. What happens if there is a mismatch between the two current generators? A possible answer is that the capacitor keeps charging up until it saturates. Another possibility is that the current flows in the left buffer. Or, the right answer, is that there is the loop of diodes and thanks to the translinear principle we know the current in the diode bridge and for sure the difference will flow in the left buffer. But if so, voltages of the diodes will mismatch, so the voltage on Ch won't be V_{in} , but with an error due to the mismatch. So the mismatch in the current values causes a offset.


The other possibility is that there is a mismatch in the timing of the transistor, for instance when we turn on the red BJT and off the purple one.

FEEDBACK S&H CONFIGURATION

 
So far we have seen configuration without a feedback. But since we have introduced buffers, we have the Vos error and the epsilon error. Hence we have an error between the input and the output.



 We want V_{out} to be V_{in} , so we have a global feedback. Thanks to this connection, V_{os1} and ϵ_1 are reduced by A_0 , so negligible.



 Moreover, if we want r_{on} to be low, we can put a buffer in series with the switch to have a reduced impedance, as in the configuration below.



The buffer is just a follower, no need to introduce an opamp. Of course, the follower has a voltage drop of 0.6V across it, but thanks to the feedback, the output is still V_{in} . Pnp transistor and npn transistor are needed to provide both the directions for the current, otherwise the capacitor will just charge or discharge.


The resistor is needed because if the switch is close, without it, the loop is ok. If the switch is open, now the base of the transistors is floating, so we run the risk that one of the two transistor is on and we charge or discharge the capacitor, corrupting the output voltage.

Now the R_{on} I see is not the R_{on} of the MOSFET, but it is the $1/g_m$ of the BJT that is on plus R_{on} of the mosfet divided by beta of the BJT. So I also reduce the impedance.

Unfortunately, however, this circuit can be unstable. The first opamp is compensated; then we study the beta network. The beta has a pole due to C_H and $1/g_m$. As $A(s)$ we are considering the forward path, so opamp, follower and opamp, that is the forward gain (s). We notice that the closure angle between $1/\beta$ and forward gain (s) is 40-40, so the circuit is unstable.


In fact, every time we close the switch, if the circuit is unstable, we have some ringing when approaching the V_{in} signal during the sampling phase, so we need a higher settling time.

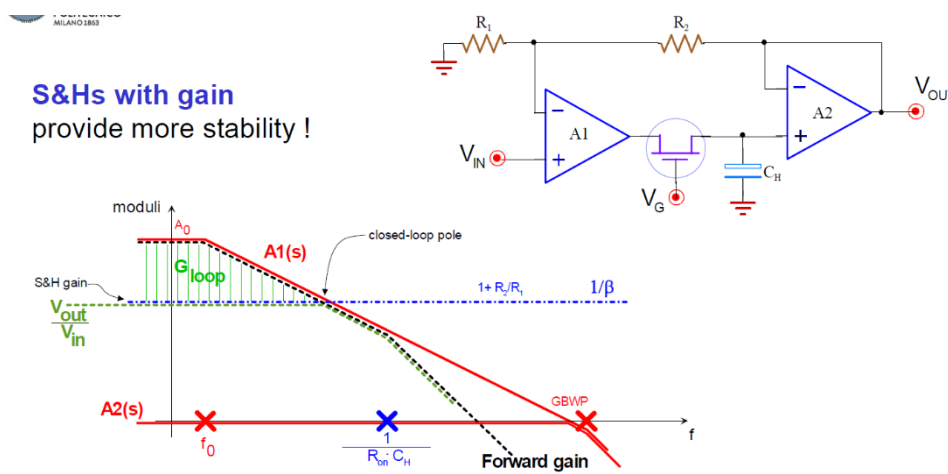To regain stability we cannot add a capacitor in the global feedback, because we don't have a resistor, so what we can do is to introduce resistors as below.




In this case we have the same stage as before, but now the beta is lower and so $1/\beta$ is higher. This S&H is stable and it introduces also amplification. However, the issue here is that if we want to store the full voltage on C_H (e.g. 5V), V_G should be very high, even 10V. Instead, the simplify driving configuration seen previously was lovely because we can drive the transistors with the logic voltages, because of V_G .

 So better to use another configuration. Better not to use a buffer as a final stage but something like below. It's not an integrator.





When the switch is closed, the gain is 1 and capacitor charges to 3V. If then the switch gets open, the capacitor provides 3V to the output even if V_{in} changes.

 The problem is that if the first amplifier is a VOA and we have e.g. $V_{in} = 4V$, the output is at 3V, so the epsilon in input is 1V and the output of the VOA saturates to the PS, that is e.g. 12V. Now the switch is between 12V and 0V (V_G), so even if we apply 12V on the gate we need a huge amount of time to close the switch.




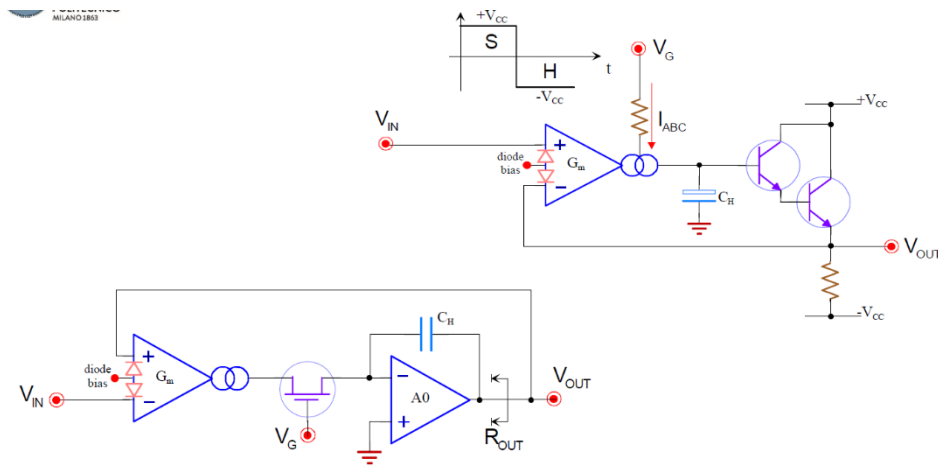 Hence is better not to use a VOA but an OTA followed by an opamp connected as an integrator.



Many opamp manufacture developed an IC with the OTA, the switch, the second opamp, the capacitor.


Example of IC connections

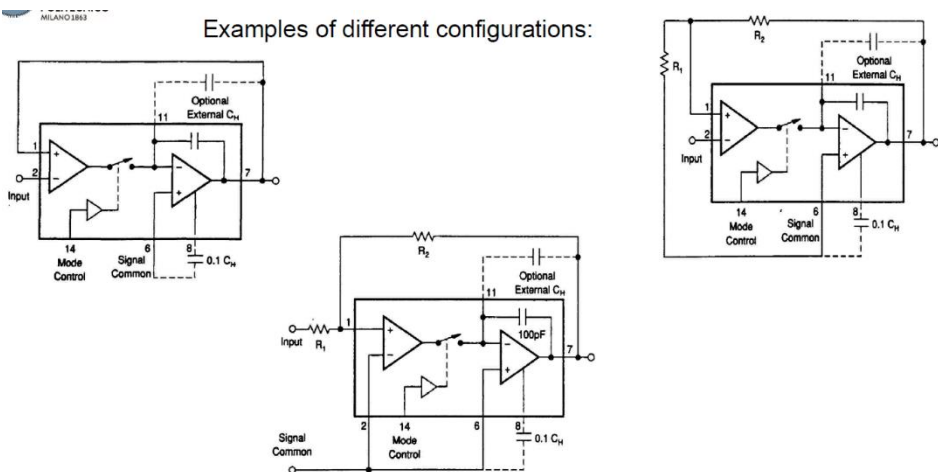

C_H is very important in S&H and it must be very large to hold the voltage for a long period, but if it is big, the t_{acq} is high. So we want a C_H that is high value when we need it and low value when we don't need it.

During the sampling phase I want C_H to be low value, so that we are fast in tracking the signal. Vice versa, in the hold phase I want C_H to be very large so that the voltage stored on the capacitor doesn't discharge due to droop.

 To do so, for sampling when the switch is close I want a small C_H , so I could include a very big capacitor that I leave open during the sample phase and I use another one that is smaller. The two switches are connected one with the other.




Then when I open the switch, the bigger capacitor is attached and the two capacitors are in parallel. But this configuration is not working, because when the switch is closed we store the voltage on the tiny capacitor, but the other one is discharged. Then when we connect it, we place two capacitors in parallel, and the big capacitance was charged to 0V. Hence we need to equalize the charge between the two, so the voltage across the bigger capacitor will be like below (assuming 3V stored on the small capacitance).

$$\begin{aligned}
 & \left\{ \begin{aligned} Q &= 0,1n \cdot 3V \\ Q &= 10n \cdot V^* \end{aligned} \right. \quad C = \frac{Q}{V} \\
 & V^* = 3V \cdot \frac{0,1n}{10n} = 30mV
 \end{aligned}$$

We could introduce an amplification in the following opamp, but in doing so also the offset, error and noise get amplified, so it is not a good solution.


The proper configuration to be exploited is the following.

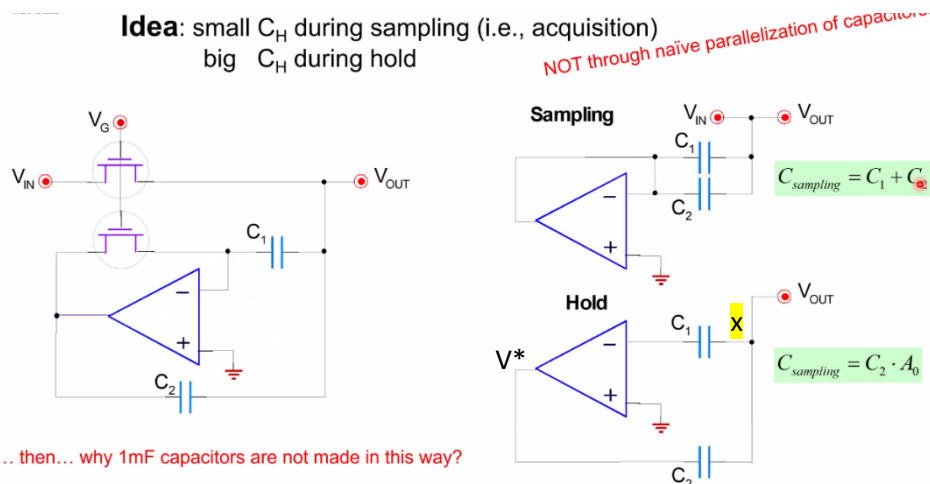C_1 goes to V_G , and when the switches are closed, the capacitances are in parallel during sampling, and during hold phase the opamp is an open loop opamp, not a buffer. The overall capacitance we see is not C_1 , because in series with infinite (terminal), so we see C_2 multiplied by the internal gain of the amplifier.




If C_2 discharges because e.g. an ADC drinks the current, then node x decreases, but if so, - terminal decreases and output increases, so the loop keeps the voltage fixed. C_1 is not acting because no current flows in it, it was charged and it remains charged as a battery.

 
The impedance we see in one node of the loop is then the stupid impedance divided by $1 - \text{Gloop}$, and at node x we see, in the case of resistors, is:



 In case of capacitors we have the following.



 When the switch is closed, V^* is at VG, so 0V, but as soon as the switch is open the voltage across the capacitor discharges, but V^* increases so that the V_{out} is almost flat during the hold phase. Of course there will be a droop, but it is reduced by the feedback.




This configuration works because during sampling we charge both capacitors to 3V. So when we open the switch we don't have a capacitor charged and the other one not so we have to wait for the other capacitor to charge due to redistribution of charge, because now both are charged.

Since in many applications we need large capacitors, why don't we place C_2 big, e.g. 1uF and $A_0 = 1000$ to have an equivalent huge capacitor?

The discharge of V_{out} is very small, but there is something in this circuit that at a certain point makes the circuit not working.

If we look at node x, it is not discharging, and if the V^* reaches the power supply value, the configuration stops working.

 Let's see what happens. We have V_{in} and the S&H signal; when V^* reaches 12V (PS) and saturates, the capacitor discharges (red area) and then it charges in the opposite way and in the end the capacitor keeps discharging. So the V_{out} after some time collapses, so we have a very fast droop.




Hence at a certain time we need to close the switch and **reapply sampling before we reach saturation of V^*** . Otherwise, C_2 discharges very quickly.

MUX AND DIGPOT

ANALOG MULTIPLEXER

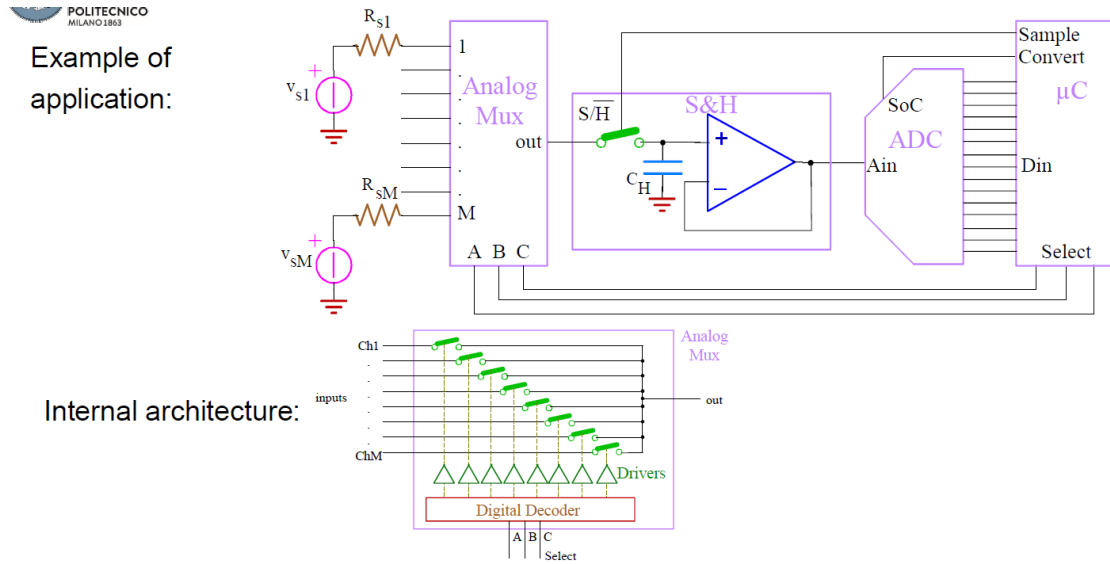An analog mux is a multiswitch. We have different input signals and we want to choose which signal to send to the S&H. We use a digital decoder to select which is the channel to sample.




Pass transistor

Switches must be analog switches, so transistors, but one transistor is not enough, because the input is analog and it can be positive or negative, so we should use very high voltages to drive the switch if we are controlling the MUX with digital levels, so we need charge pump and voltage translator. Hence the best solution is to use a pair of n-channel and p-channel transistors driven with opposite phase. A 0 signal keeps off the n-channel and on the p-channel if V_{in} is sufficiently high.

In the n-channel transistor, if V_{in} is high R_{on} increases. If V_{in} increases and we keep V_{gate} fixed, the n-channel transistor is less closed and R_{on} increases.

If V_{in} reaches $5V$ (gate voltage) $- V_t$, the R_{on} becomes infinite. Vice versa, if we apply $0V$ to the p-mos, while V_{in} is low the transistor is off, but if it increases the V_{in} the R_{on} decreases.

Analog switch implementation:

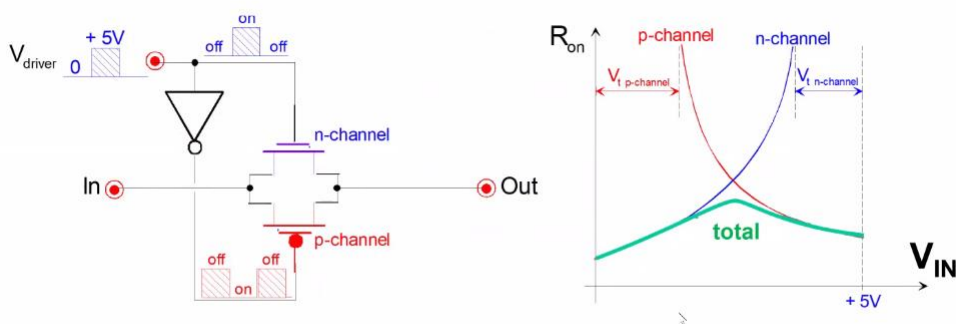

Also useful to compensate **charge injection!**

If we put them in parallel, we have to compute the parallel between the two R_{on} , and we get a value that is almost constant. Moreover, this configuration allows to compensate the charge injection, since we have the C_{gd} of the two transistors. But when we apply a swing to turn the nMOS from off to on, we have charge injection. But we apply a falling edge to have the nMOS off and a rising edge to have the pMOS


off, so the falling edge at the gate of the n channel and the rising edge at the gate of the p channel cause opposite charge injection to the output node, so they compensate each other.

Analog multiplexer's errors



Sources of errors:

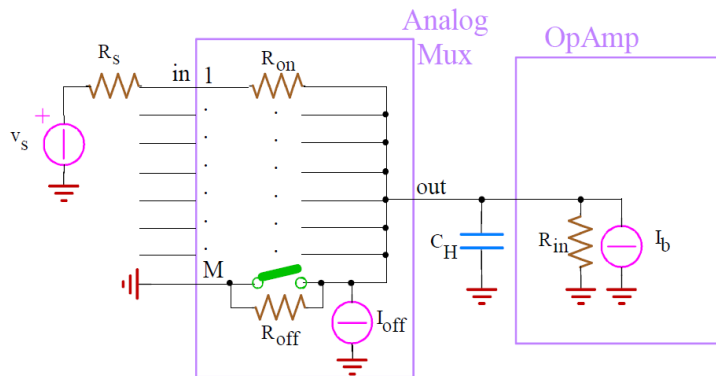- R_{on} $10\Omega \div 10k\Omega$
- R_{off} $>10M\Omega$
- I_{off} $<100nA$
- T_{on} T_{off} $<100ns$



$$\Delta V = \pm v_s \cdot \frac{R_s + R_{on}}{R_s + R_{on} + \left\{ R_{in} \parallel \left[\frac{R_{off}}{(M-1)} \right] \right\}} \pm (I_{off} \cdot (M+1) + I_B) \cdot \left\{ (R_s + R_{on}) \parallel R_{in} \parallel \left[\frac{R_{off}}{(M-1)} \right] \right\}$$

When the transistor is closed, it will show its R_{on} , that usually its hundreds of ohms. If the PS of the chip is very low or the temperature is too high or too low, maybe R_{on} can increase. Similarly for R_{off} , which should be infinite, but it is in the range of MOhms, so eventually also R_{off} can decrease.

Hence **each pass transistor has a leakage current from drain to the bulk**, so from the drain towards the ground, for each switch, and this in both sides of the transistor. But one side is attached to the source, and the right side we have the S&H, so we care about the leakages in the S&H part (they act on C_H), because the leakages on the left causes something in the source, that is not relevant when the switch is open.

Moreover, after the S&H circuit we have an opamp or the ADC.

Let's compute the error and to consider one switch close and all the other opens, at the output of the MUX. I see R_s in series with R_{on} and then a parallel of R_{off} to ground. In fact, if a pin is not connected, it is connected to ground, or to another source, so eventually I would see $R_s + R_{off}$ towards ground, that is still R_{off} because it is much bigger than R_s . I expect the voltage drop across the MUX to be 0, but it won't be zero.

In the equation I should put the highest possible R_s and R_{on} , and at the denominator the lowest R_{off} , R_{in} , R_{on} and R_s .

The second contribution is the one related to I_{off} , because when we open the switches I_{off} drinks current from the resistances. There are M I_{off} and also the I_b bias current. Of course I don't care about the I_{off} on the left of the switches because they die toward ground if the switches are open, but if it is closed I have to consider it, hence the $M+1$. Then the impedance I see from the node of the capacitor is a parallel

Example: ADG508A mux, Analog Devices

- $M=8$ channels
- $R_{on}=400\Omega$
- $R_{off}=10M\Omega$
- $I_{off}=100nA$ (@ 125°C)
- $v_s=\pm 15V$
- $R_s=1k\Omega$
- OpAmp
- $R_{in}=500k\Omega$
- $I_b=0.5\mu A$

we get a maximum error of $\Delta V = \pm 56mV \pm 0.98mV \pm 0.7mV$

the first term is equal to $\frac{1}{2}LSB$ for a 10bit ADC

the sum of the other two contributions is equal to $\frac{1}{2}LSB$ for a 15bit ADC

between all the resistances. In the worst case all the resistances must be the highest possible value, as well as for I_{off} .


If the error is less than $\frac{1}{2}$ LSB we are ok, but if not, we are converting the value in the next bit interval. Hence the error of the MUX is large or not depending on the following ADC.

Timings

Let's suppose to have 16 channels to acquire, and some inputs are high BW, other low BW, and we have just one ADC, uC and S&H.

We select a channel to sample, e.g. the first one. We acquire the first input, we store the value on the capacitor, we close the switch, we wait to track the signal and then we open it in the hold phase, we convert it, we wait for the ADC result. After this the uC reads the digital bus and changes the channel. In order to acquire 16 channels we need to dedicate one slot per channel. The uC decides when to change the channel, apply a pulse to the S&H and to the ADC. Or we can have a master clock that commands the S&H and the ADC, that then tells to the uC if the data is ready or not.

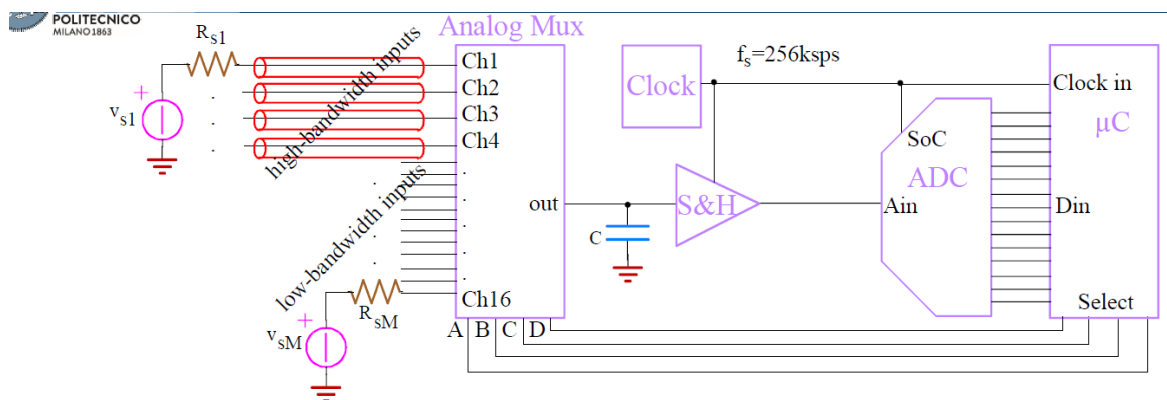Of course, the master clock must be correctly chosen according also to the conversion frequency of the ADC (sps = samples per seconds). A 256 ksp/s corresponds to 3.9 μ s, so the uC will read the data and provide a new selection every 4 μ s.



Example: ADC with $f_s=256$ ksp/s
 every channel scanned at 16 ksp/s ($1/f_s=3.9 \mu$ s and not 1/16 ksp/s!)
 therefore the maximum admitted bandwidth of each channel is less than 8 kHz

What about if $M=16$, but only the first four channels with a 20 kHz bandwidth? Here is the solution:

Ch1, Ch2, Ch3, Ch4, Ch5, Ch1, Ch2, Ch3, Ch4, Ch6, Ch1, Ch2, Ch3, Ch4, Ch7...

for the first 4 channels, the sampling becomes $f_s/5=51.2$ ksp/s, while the other 12 have $f_s/60=4.2$ ksp/s


If we want to acquire 16 channels it requires $16 \cdot 3.9 \mu$ s, that is $1/16 \cdot 256$ ksp/s. So every channel is sampled at 16 ksp/s. But then it means that f_{max} for each channel should be lower than half that value, not 256 ksp/s.

But this approach is not good because it is too slow for the channel attached to high BW signals and too fast for channels attached to low BW signals.

So we should choose another timing. What we could do is to read channels 1, 2, 3, 4, 5 \rightarrow 1, 2, 3, 4, 5, 6 \rightarrow 1, 2, 3, 4, 5, 6, 7 so that we scan the first four channels more often, and the other less often.

It takes 5 readings for channels from 1 to 4 and then 12 conversions to read channel 5 again. It takes 12 times 5 times 4 μ s, so once every 60 conversions for the last 4 channels.

Of course, as for the S&H I relaxed the BW of the signal, but since the S&H is running at 256 ksp/s, every 4 us the S&H must close and open. So since $f_s = 256$ ksp/s, it means that in my signal I need to open and close the switch every $T_s = 3.9$ us. When the switch is close in the sampling phase, the duration to be provided has to be at least the t_{acq} , sufficiently long, and in the hold phase I should have at least the t_{conv} of the ADC (conversion time of the ADC).

 


So $t_{sampler, min} > t_{acq, min}$. $t_{acq, min}$ is tau multiplied by the logarithm above. The error epsilon is half the LSB, so $FSR / (2 * 2^n)$. tau is $R_{on} * C$. The R_{on} is not the R_{on} of just the MUX, but the total R_{on} , so $R_s + R_{on, mux}$.

We have to compute $t_{acq, min}$ in the worst case scenario, when tau is maximum. In fact, by minimum value of t_{acq} we refer to the minimum reliable one, so the longer worst acquisition time.

Another consideration. The minimum duration of t_{hold} should be longer than t_{conv} of the ADC, and the worst case scenario of t_{conv} is when it is maximum, at it can be 10ns in the case of flash ADC, 10us in case of SAR ADC, 10ms for dual-slope ADC and so on.

Moreover, $t_{sample} + t_{hold} = T_s$.

 So depending on the S&H circuit and on the ADC, we could use a very fast S&H so that t_{sample} is very short, because maybe the ADC is slow and t_{conv} is very long, or we can have the opposite.




Coming back to the circuit of the slide, the S&H must be able to close and open within 4us. So at least the ADC should convert within 4us, but if the ADC converts in 3us, we have only 0.9us left for S&H. so better to use a flash ADC that converts in 10ns so that we have 4 us for S&H.

The τ_{max} we have to achieve can be computed from equation x.

$$\begin{aligned} \rightarrow t_{3.9\mu s} > t_s > 0.7 \cdot (n+1) \cdot \tau_{max} \\ n &= 8 \text{ bit} \\ R_{on} \cdot C &= \tau_{max} \leq \frac{3.9\mu s}{0.7 \cdot 9} = 6 \mu s \end{aligned}$$

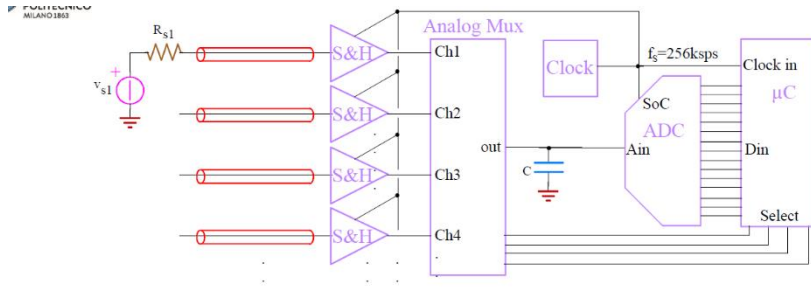There are some applications where we cannot use this technique, because in this technique we have many different signals and we perform multiplexing before the S&H. Instead, there may be other applications where the signals must be acquired on the same time instant. In this case, we need to have a S&H for each signal, and then we multiplex them to the ADC.




Example: ADC with $f_s=256\text{kps}$
4 "fast" and 12 "slow" input channels

With just one S&H after the mux, each "fast" channel should have available a time of $5/f_s=19.5\mu\text{s}$
With one S&H at each channel input, each channel should have $16/f_s=62.5\mu\text{s}$


The master clock should open all the switches of the S&H and open them synchronously. Then it opens and closes the switches of the MUX alternatively.

Improvements

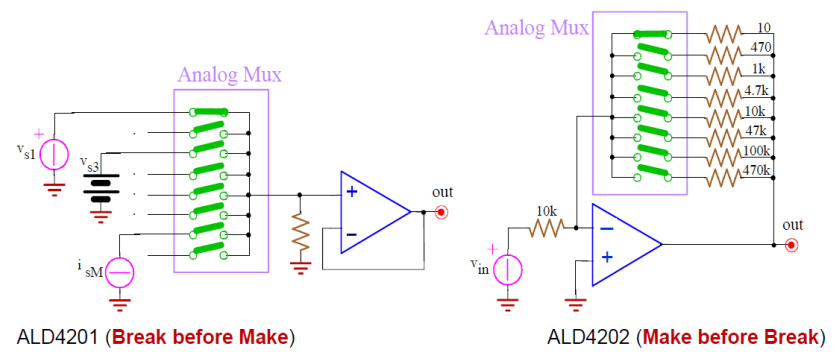

ALD4201 (Break before Make)

ALD4202 (Make before Break)

 


Make before break is needed when the MUX is in feedback, otherwise the output may saturate.


DIGIPOT



Block diagram:

 

Example:

 


Model	Steps	Resistance (kΩ)	Configuration	Non-volatile	Packages	Interface	Operating power	Features	Price (1000)
AD8402	256	10, 50, 100	Dual	No	DIP-14, SO-14	Three-wire	2.7 to 5.5V, 5µA	Full ac specs, nA shutdown current	\$1.66
AD8403	256	10, 50, 100	Quad	No	SOL-24	Three-wire	2.7 to 5.5V, 5µA	Full ac specs, nA shutdown current	\$2.51
DS1267	256	10, 50, 100	Dual	No	DIP-14, SO-16, TSSOP-20	Three-wire	5 or ±5V, 650µA	Stackable wipers for 512-step resolution	\$2.45
DS1867	256	10, 50, 100	Dual	Yes	DIP-14, SO-16, TSSOP-20	Three-wire	5 or ±5V, 650µA	Nonvolatile version of DS1267	\$3.14
DS1802	64	50	Dual	No	DIP-20, SO-20, TSSOP-20	Three-wire and pushbutton	3 or 5V, 2 mA	Log taper, mute, audio specs	\$2.56

The value of the potentiometer is changed by providing pulses to the component. It is a set of resistors one in series with the other, then we have an analog mux that can be modelled as a set of switches. To change the switch we provide the digital address of the switch or, to simplify the connections, we can use 2 or 3 pins, and inside the digipot there is a counter and we decide if to count up or down.


Some digipot can be non-volatile, which means that if we switch off the PS the component remembers the position of the cursor.

If we provide a pulse, the component increments, after having chosen the direction of the counter. One push button can be used to select the direction of the counting, the other to give the pulses. We would like one push button to go up and one to go down.

 
To do so, when I push the down counting button I also want to change the INC pin. So I can introduce a certain delay, but we cannot simply attach the output of a RC circuit, because we could cause a shortcircuit with the up counting button. So we can use a transistor.



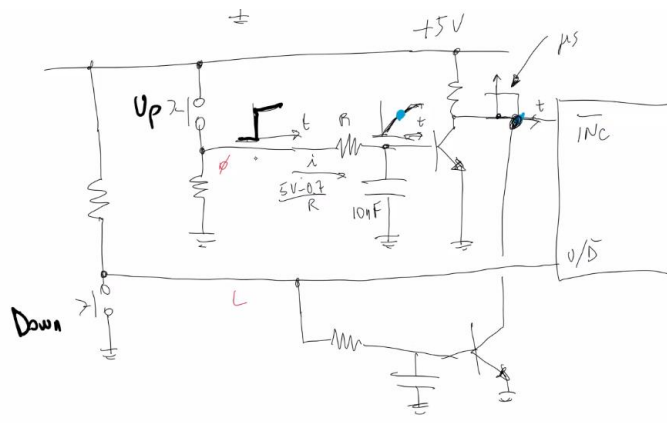
We need then to perform an OR connection to the INC pin to have the up and down push buttons.




Let's consider the following circuit.

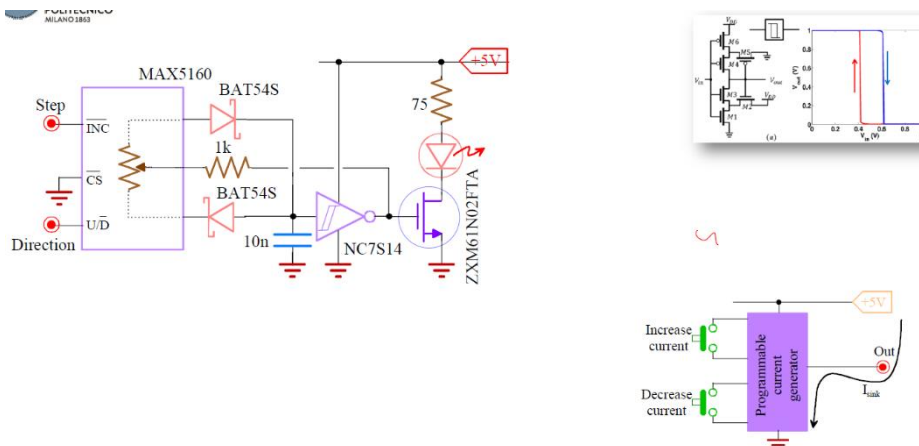

 
We have a NOT port that is a Schmitt trigger gate, with an hysterical behaviour (upper right image). The inverter has two logic levels, 2V and 3V if it is biased at 5V. Above 3V we have the commutation to the high level. So we have an inverter whose output feeds the input with a capacitor to ground. It is hence a digital oscillator.



 We can use a similar equation used during the S&H studying, the one on t_{acq} .



 We can use it because we have an exponential curve also in the oscillator, and the delta we need to reach in the increasing exponential is $\Delta = 5V - 2V$, and epsilon is $5 - 3 = 2V$. So we can properly compute T_{on} . The same for T_{off} , but it changes delta and epsilon.



$$T_{on} = \tau \cdot \ln \frac{V_{oh} - V_{L}}{V_{oh} - V_{H}} = \tau \cdot \ln \frac{3}{2} = \tau \cdot 40\%$$


$$T_{off} = \tau \cdot \ln \frac{V_{H} - V_{L}}{V_{L}} = \tau \cdot \ln \frac{3}{2} = \tau \cdot 40\%$$

$$T_{ox} = 2 \cdot 40\% \tau = 0,8 \tau$$

$$f_{ox} \approx \frac{1}{\tau} \cdot 1,25$$

If now we look at the circuit, we have the NOT gate whose output feeds a resistor that then feeds a digpot, which feeds then two diodes and the input of the NOT gate through a capacitor. To reduce as much as possible the voltage drop across the diodes, we are using Schottky diodes, not standard ones. Its voltage drop is 0.2V

 If at the beginning the C is full discharged, the output of the NOT will be high, and the path that charges the capacitor is the yellow one. Once the capacitor has been charged, the output will move to the low level, and the discharge will be through the blue path.



$$R_{charge} = 1k + 50k(1-x)$$

$$R_{discharge} = 1k + 50k \cdot x$$

$$T_{on} = \tau_{charge} \cdot \ln \left(\frac{1.25 - 0.2}{1.25 - 3} \right)$$

$$= C \cdot R_{charge} \cdot \ln \left(\frac{2.8}{2} \right) \cdot 34\%$$

$$T_{off} = C \cdot R_{discharge} \cdot \ln \left(\frac{2.8}{2} \right)$$


The total $T_{osc} = T_{on} + T_{off}$ is a constant value. Hence oscillation frequency won't depend on the position of the cursor but on the total value of the potentiometer.

$$T_{osc} = T_{on} + T_{off} = 34\% \cdot C \cdot [R_{charge} + R_{discharge}]$$

$$= 34\% C [1k + 50k]$$

By changing the cursor position, T_{osc} remain constant but I'm changing the duty cycle.

Exercise 1

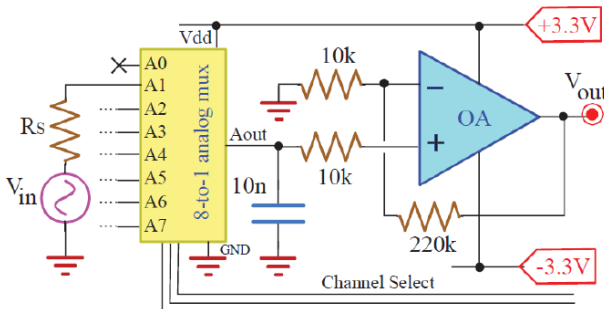

Seven inputs with $R_s=100\Omega-1k\Omega$. OpAmp with sourcing $I_B=1nA$ and $V_{OS}=0.2mV$. Mux with $R_{on}=5-50\Omega$, $R_{off}=2M\Omega-20M\Omega$ and $I_{leak}=5nA$.

- Compute **sampling** and **hold** times for 12 bit resolution and $V_{in,max}=\pm 50mV$ and specify if they are max or min values.
- Compute all static errors and properly add them to compute the total output error in LSBs.

The capacitor acts as a S&H circuit, so we need a configuration where the analog MUX can be connected to one input but eventually to have also all the switches open. Because of this, pin A0 is left floating because we can never have all the pins of the MUX open, one must always be closed (even 0000 is the bits code for a channel to be closed).

Point a)


Once we have acquired the signal, the signal gets stored on C and then goes in the OA that is connected as a standard non-inverting configuration, so the $G = 1 + R_2/R_1 = +23$. $V_{out,max} = V_{in,max} * G = 50mV * 23 = 1.15V$.

The input signal can be either positive or negative, the FSR of the opamp is 6.6V and V_{out} can be both positive and negative, so $V_{out} = \pm 1.15V$.

As for the LSB of the ADC: $LSB = 6.6V/2^{12} = 1.6mV$.

When we want to acquire a signal we need to wait the sampling time, when the switch is close and it will show its R_{on} . The switch is connected to a source and the signal of the source goes to the 10nF capacitor. To quote t_{acq} we need to think at the worst scenario, so when it is maximal.


$t_{acq,max}$ is the minimum acquisition time I need to wait. Of course, also the capacitor must be considered with its own tolerance to have the maximal value. Moreover, in the equation all the other R_{off} are not considered, and these R_{off} are in series with the R_s of different sources, so the $R_{s,max} + R_{on,max}$ should go in parallel with the $R_s + R_{off}$, but since this parallel would decrease the overall

 

resistance, let's neglect the R_{off} . The Δ_{max} to be considered is the maximum swing the output can experience, so the FSR (if not indicated otherwise). Instead, the epsilon is $\frac{1}{2}$ LSB of the following ADC.


If we want to be less conservative, the maximum possible output swing will be due to the maximal V_{in} the user will use, so it can be reduced the Δ_{max} term. In this case $\Delta_{max} = 2.3V$
 In the end, $t_{acq,min} = 100 \mu s$.

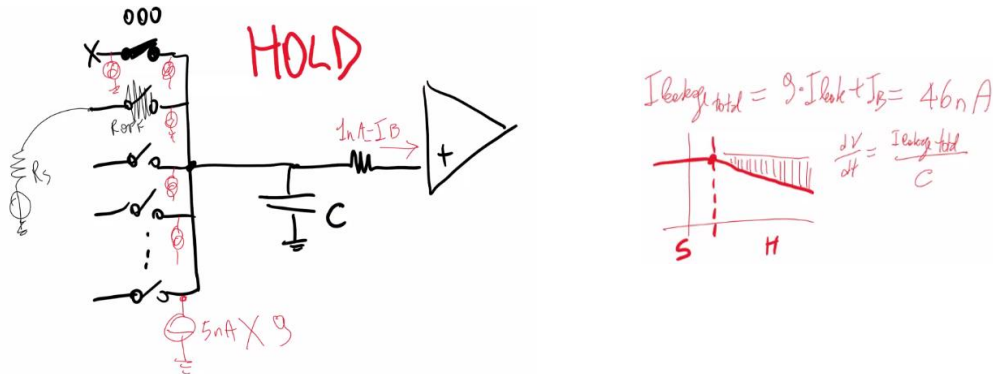Now we have to compute the hold time. I've already acquired the signal so I can leave the switch open, switch A0 is closed but all the other switches are open. We will have the I_{bias} of the opamp and all the leakages currents of the MUX ($5 nA * 9$, because we have 8 switches + 1 switch closed). Then each switch will have its own R_{off} and R_s .



Due to the leakage current the total voltage store on the capacitor will decrease with a constant slope, with a droop that is I_{leak}/C .

 The second source of error is due to the resistors. Even if there were no leakages, due to the R_{off} , the capacitor will discharge due to the RC network. The minimum R_{off} is due to the parallel of all the resistances. The $R_{off,min}$ causes a discharge in the time domain that will be exponential from the sampling phase to the hold phase, while previously it was a linear ramp.




To simplify the computation, let's consider only the first part of the discharge and suppose it linear. The worst case scenario is when the discharge current is due to V_{max} stored divided by $R_{off,min}$. $V_{max} = 1.15V$.

This discharge must be compared with the previous one to see which one prevails. This last one is the dominant, because bigger.

We can hence compute the droop rate.

$$d_{droop} = \frac{dV}{dt} \Big|_{max} = \frac{I_{off}}{C_{min}} = \frac{4 \mu A}{10 nF \cdot (1-t_{hold})} = \frac{4 \mu A}{8 nF} = 500 \frac{V}{s}$$

As for the hold time, during sampling we track V_{in} and then when we move from sampling phase to hold phase V_{in} can vary but V_h on the capacitor should remain constant. Due to the droop, the actual voltage on C_h decreases, and now we want the maximum t_{hold} that causes the voltage to decrease until we reach the maximum error we can stand. The maximum error we can stand is $\frac{1}{2}$ LSB.

 


If the ADC has a conversion time of a given amount, we need to be sure that the conversion time is lower than $t_{hold,max}$, otherwise the voltage across the capacitor may change too much and we convert the wrong value.

ΔV is the maximum one we can stand, that is the error epsilon. This is the time we need to wait at the most when we open the switch.

$$t_{H,max} = \frac{\Delta V}{I_{off}/C} = \frac{0.8mV}{500\frac{V}{s}} = 1.6\mu s$$

 We must keep the switch close for a very long duration and open for a very short time duration. This is the working operation of this S&H circuit, because the circuit has a $t_{acq,min} = 100\mu s$, so $T_s > t_{acq,min}$ and instead t_{hold} should be smaller than $t_{hold,max}$. $t_{conv,max}$ of the ADC should be shorter than $t_{conv,max}$.



So this S&H is pretty bad, because we need a lot of time to acquire the signal (100us) and we also need an ADC able to convert in less than 1.6us.

The f_s of this sample and hold is $f_s = 1/(T_s + T_h) = 1/(102\mu s + 1\mu s) = 9.7$ ksp/s.

This means that the maximum frequency of the input signal, according to Shannon, has to be smaller than 4.7 kHz

Point b)

When we acquire a signal we close a switch, which has its own R_{on} . Then we have the R_s of the source, so the overall voltage drop is $V_{in} * (R_s + R_{on}) / (R_s + R_{on} + (R_{off} + R_s)/6)$. This is the voltage drop between V_{in} and the voltage stored on the capacitor. This is the first error in the circuit; its highest value can be computed considering the highest possible V_{in} , $R_s + R_{on}$ maximal and the $R_{off} + R_s$ minimum.

Then, there is another contribution. If we have a given amount of voltage stored on the capacitor, due to the bias current in the opamp, we have a voltage drop on the 10k resistor, that introduces the error ϵ_{2} . This error is always negative or positive depending on the direction of the bias current. This error has to be multiplied by the gain of the stage to refer it to the output (missing in the bottom image).

Even when the channel is closed, so we have R_{on} , the I_{bias} causes another issue. We have in fact 8 + 1 leakages currents in the MUX, and the 9 I_{leak} plus the I_{bias} flow in the R_{on} , causing an error in the voltage drop stored on the capacitor. This is error ϵ_{3} . In the worst case scenario, if all the inputs are unconnected, the R_{off} are in series with infinite, so it is better to consider only the $R_s + R_{on}$ in ϵ_{3} . Also this error must be multiplied by the gain (missing in the bottom image).

Then there is the final error due to the I_{bias-} of the opamp. When we consider it all the inputs are at 0, so $V+$ of the opamp is 0 because voltage on the capacitor is 0, so also $V-$ is 0, hence I_{bias-} flows just in the 220k resistor. Since I_{bias-} is inward going, we have a positive contribution. This error ϵ_{4} is already at the output, so no need to multiply by the gain

The last final error is due to the offset of the opamp, that is 0.2mV. When we turn off all the other sources, Vos is applied straight to the opamp which has a gain of G.


$$\begin{aligned} \epsilon_1 &= A_{im} \cdot \frac{(R_s + R_{ou})_{max}}{R_s + R_{ou} + \left(\frac{R_{OPF} + R_s}{6}\right)_{min}} = +50mV \cdot \frac{1050}{1050 + \frac{27}{6}} = +158 \mu V \\ \epsilon_2 &= -I_{B+} \cdot 10k = -1n \cdot 10k = -10 \mu V \\ \epsilon_3 &= (9 I_{leak} + I_B) \cdot (R_s + R_{ou}) \cdot \left(\frac{R_{OPF} + R_s}{6}\right) = 46nA \cdot 1050 = 47 \mu V \\ \epsilon_4 &= +I_{B-} \cdot 270k = + 220 \mu V \\ \epsilon_5 &= \pm V_{os} \cdot G = \pm 0.2mV \cdot 23 = 4.6 mV \end{aligned}$$

The total error at the output at the output is the sum of all these errors. Usually I_{leak} has a not known sign.

The non-negligible contributions are the epsilon₁, and can be reduced by reducing R_s, then the one due to the leakages, that can be minimized by reducing R_s or the leakage currents and the epsilon₅ due to the offset. Eventually, the total error is +/- 9.3 mV. To see how much the error is big, we need to compare this value with the LSB of the ADC by doing 9.3/LSB to get the digits that deviates our conversion.


In the computations there is an error. In fact, when we study the errors, sometimes we find the error on the capacitor and some other times we compute it at the output. Of course we cannot sum the errors as they are, but we need to move them in the proper position, so if I find it at the input node I need to multiply it by the gain of the stage to have it comparable with the one in the output. For instance, epsilon₁ should be multiplied by the gain to find the error at the output of the stage. The same for epsilon₂ and epsilon₃.

Exercise 2

 

OpAmps: A₀=100dB, GBWP=100MHz.
MOS: R_{on}<100Ω, V_T=0.8V. ADC: 12bit.
a) Compute the acquisition time.
b) Compute static error on A_{in} in LSB, due to I_B=5nA (sink) and V_{OS}=5mV.

Let's start by computing the acquisition time. We know where the Vin is, the circuit has a loop and during sampling the switch is in close configuration. Let's see if the stage has a negative feedback. OA2 is a buffer, so the output increases, so we have a negative feedback, because we are forcing the error signal epsilon to decrease. If we have negative feedback, we can apply the VG concept, so V- of OA1 is at Vin.

 

$$V_{out} = (V_{in}/10k) \cdot (10k + 470k) = 1 + R_2/R_1 = 48.$$

This is the gain of the circuit. Let's now compute the acquisition time. The switch is open, so the voltage stored on the capacitor is buffered at the output of OA2. On the V- of OA1 we have an attenuation of


these 2V, and since the switch is open, OA1 output keeps saturating to PS high or PS low. When we close the switch the circuit has a feedback and we can compute the acquisition time.

We know the equation for t_{acq} , but τ is not $R_{on} \cdot C_H$ in this case, because the circuit has feedback.

$$t_{acq} = \tau \cdot \ln \frac{\Delta}{\epsilon} \quad \tau \neq R_{on} \cdot C_H$$


We need to compute the BW of the loop. Once we compute the BW, the τ to be used in the equation for the acquisition time is the inverse of the BW. So we need to plot the Bode diagram of the loop, hence extracting the pole. Then the BW will be $1/f_{pole}$.

 We can consider the first opamp to be the $A(s)$ and the remaining circuit is the beta, considering the buffer ideal eventually, so with a gain of 1.



Let's now plot the Bode diagram.

 To compute f^* , we prolong the $1/\beta$ trend, we compute the frequency and then we get f^* with the geometric average.



The circuit is not stable, the closure angle is bad, but f^* is not far away from the 160 kHz pole. Let's compute the phase margin.

$$PM = 180^\circ - 90^\circ - \arctan \frac{f^*}{160kHz} - 0 = 90^\circ - \arctan \frac{580k}{160k} = 15^\circ$$

So the circuit is not stable, but we don't want to compensate it, let's compute the pole of the circuit. The pole is at f^* , and since the closure angle is poor, we have two c.c. poles at f^* .

$$\tau \approx \frac{1}{2\pi f^*} = \frac{1}{2\pi \cdot 580k} = 275ns$$

$$t_{acq, min} \approx \tau \cdot \ln \frac{\Delta}{\epsilon} = 275ns \cdot \ln \frac{5V}{0.6mV} = 275ns \cdot 9 = 2.5\mu s$$

Once the τ is computed, we can compute also t_{acq} . Δ and ϵ must be considered where the capacitor is. ϵ is $FSR_{adc}/2^{12}$, so $5/2^{12} = 1.2mV$. This is the LSB at the entrance of the ADC, but I need it at the capacitor side. Since we have a buffer, the two are coincident. Then, $\epsilon = 1/2$ LSB. Now we have to consider Δ . We have two possibilities, the worst case amplitude is when at the output we reach 5V out of OA2. If so, Δ at the capacitor is also 5V. However, maybe the output voltage at the input of the ADC will never reach 5V if we have a certain maximum input signal.


If the $V_{in, max}$ is 100mV, the output maximum voltage is $100mV \cdot 48 = 4.8V$. So 5V was ok.

Let's now compute the static errors.

We have the I_{bias} of the opamp and the V_{os} of the opamp. Let's consider V_{os1} , at the + terminal of OA1; the gain of the stage is 48, so for sure the error in output is $V_{os1} \cdot 48 = 240\text{mV}$.

$LSB = 1.2\text{mV}$, so this error correspond to $240/1.2 = +200$ digits error.

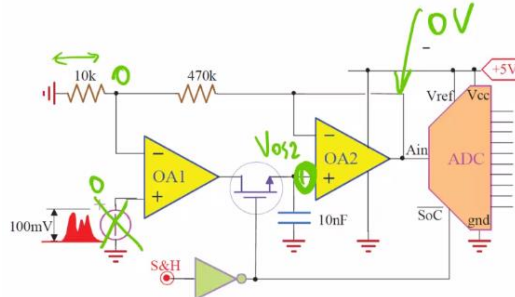
As for the offset due to the second opamp, we have negative feedback. If the circuit was ideal, no current in 470k and the output is 0V whatever is V_{os2} .



This because the ideal gain doesn't depend on $A(s)$ and so on its errors along the path. In the real case, if we have V_{os2} , it means that OA1 provided V_{os2} , and this can happen is epsilon at the input of OA1 is V_{os2}/A_0 , since V_{in} is off. Once we have this voltage, we can propagate this voltage back to the output. So the error at the output will be $V_{os2}/A_0 \cdot G$ that is almost 0.


Eventually, in this circuit we have two more errors, due to I_{bias} . I_{b+} of OA1 has no error because the input is shorted, while I_{b-} gives an error flowing through the 470k resistor.

I_{b-} of OA2 gives a negligible effect because it flows and comes from a voltage generator (the output one of OA2), while I_{b+} of OA2 is inside the loop. Ideally, this current doesn't have an effect, because the output is 0 no matter what. But to be precise, I_{b+} of OA2 flows through R_{on} of the MOSFET, so the voltage drop that develops on it is $I_{b+} \cdot R_{on}$. OA1 should provide this voltage, and this is done if at its input we have an epsilon = $I_{b+} \cdot R_{on} / A_0$. Then this epsilon experiences the gain $G = 48$, so also this contribution is negligible.

 

EXERCISES

Ex. 1

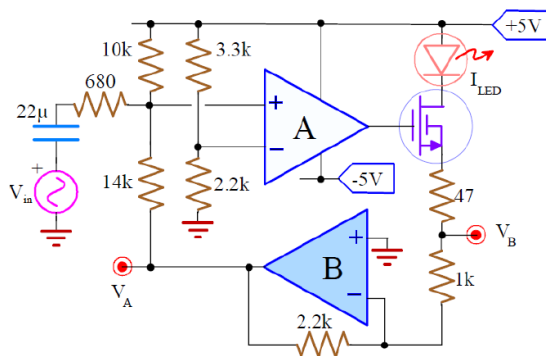


OpAmps with $A_0=50\text{V/mV}$, $V_{OS}=5\text{mV}$ and $I_B=200\text{pA}$. MOSFET with $k=10\text{mA/V}^2$ and $V_t=0.8\text{V}$.

- Compute the relationships of V_A , V_B and I_{LED} vs. V_{in} .
- Compute the input pole and plot $V_A(t)$ and $I_{LED}(t)$ waveforms when the input is a high frequency 200mV_{pp} sinusoid.
- Compute the maximum V_A static error due to V_{OS} and I_B of the OpAmps.

Resolution

We must investigate the operational regime of the schematic. The signal enters, reaches the node x and then we have OAA. The output will increase if we have the positive input, the transistor is in source follower configuration, so the source will follow and increase. If so, the second opamp has a local negative feedback and so the - terminal will behave as a virtual ground. So the current will increase and flow through the feedback resistance of OAB and so the output voltage decreases. If so also the input node will try to decrease due to the feedback \rightarrow overall negative feedback.

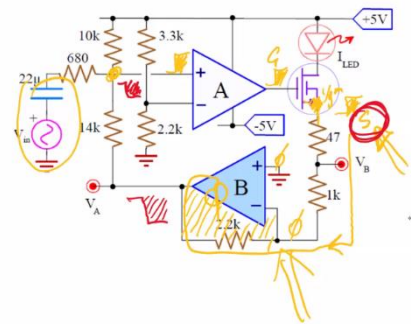

If we have a negative feedback, it means that we have the concept of VG that applies. Amplifier B is in inverting configuration with $G = -2.2\text{k}/(1\text{k} + 47)$. So the infinite gain will be provided by opamp A. So the virtual ground will be the epsilon = 0 at the input of OAA, so the + and - terminal are at the same voltage.

Due to the power supply we have 2V at - terminal of OAA, and also at the + terminal due to the negative feedback.

If there is no input signal, then the capacitor is open and the current that flows in the 10k resistor should be the same of the 14k resistor.


$$i = \frac{5-2}{10\text{k}} = 0,3\text{mA} = 300\mu\text{A}$$

This current flows in the 14k resistor so, in DC:

$$V_A = 5 - i(10\text{k} + 14\text{k}) = -2.2\text{V}$$

Then, in order to provide -2.2V at V_A and since B is in inverting configuration and its terminals are at 0V due to VG, there must be a current in feedback of 1mA, and this current will flow in the mosfet and in the led. Hence $I_{LED} = 1\text{mA}$ in DC, and the led is on.

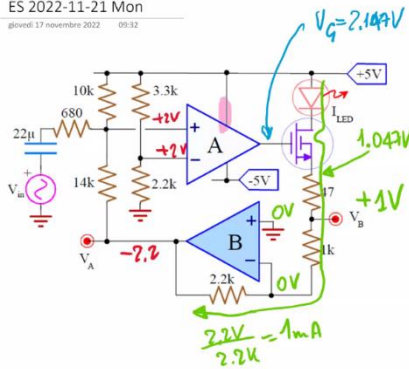We can also compute the voltage at the gate of the mosfet if we know the equation of a mosfet transistor. $V_{ov} = V_{gs} - V_t = \sqrt{I_d/k} \rightarrow V_{gs} = \sqrt{I_d/k} + V_t$, with $V_t = 0.8\text{V}$ and $k = 10\text{mA/V}^2$
In the end, $V_{gs} = 1.1\text{V}$.




This V_g value is coherent with the PS values.

Point a)

Let's now move to the signal analysis. For the signal we can consider the PS to be off and we let just the signal operate. If so, for the signal the input of OAA is 0V on the + and - terminals. So the current that enters is in 0 in DC, but now if the capacitor is shorted, is $V_{in}/680$. We can also compute the input pole of the network. Of course there also a zero at 0 frequency.

 Since the PS is off, there is no current in the 10k resistance, because it is between 0V, so the current will flow in the 14k resistance.



I know that the signal propagates clockwise, but I'm computing everything moving counterclockwise, till the position I want to reach.

To compute V_b , we know the voltage V_a and I know that $V_b \cdot (-2.2k/1k) = V_a$.

$$-N_B \cdot \frac{2.2k}{1k} = N_A \quad \frac{N_B}{N_{in}} = \frac{+14k \cdot 1k}{680 \cdot 2.2k} = 9.4$$

Now we can compute the I_{led} current, because we know the value of V_b . If V_a is positive, the current has a negative direction to be coherent. Hence we can compute the final gain $I_{led}/v_{in} = 9.4 \text{ mA/V}$.


$$i_{led} = -\frac{N_A}{2.2k} = + \frac{14k}{680} \cdot \frac{N_{in}}{2.2k}$$

Point b)

Since we are asked at high frequency, we are above the pole of the capacitor. So the input signal is a sinusoid at high frequency, 200mV pp, so between 100 and -100mV. Moreover, in DC $I_{led} = 1\text{mA}$ constant and $V_a = -2.2\text{V}$ constant.

Since the gain between V_{in} and V_a is 20.6, at 0V I'm at -2.2V, at -100mV I've reached a value -4.26V. the red one is the ideal V_a waveform. In fact, in principle the opamp could reach the value according to the PS. In this case -4.26V is ok because theoretically OAB has the PS that is +5V. But I should also consider the value of V_b and if also the ranges of OAA are compatible with this value of V_a .

 
The gain for I_{LED} is 9.4mA/V , so from 1mA I will reach 1.94mA . Also for the I_{LED} it's valid the reasoning on PS done for V_a . Moreover, I notice that the current I_{LED} is never becoming negative, and it is ok because the current cannot flow in the opposite direction in the MOSFET.



Let's see if V_a can be -4.26V . Of course we can because $V_b = V_a/(-2.2) = 1.9\text{V}$, that is also equal to the source voltage because the 470Ω resistance is very small. Let's now compute the V_{gs} of the mosfet, that is 1.6 , giving 3.6V in output of OAA. So the very negative voltage can be reached. We should also do the same for the -0.2V peak, but it is soon verified and reasonable.

Point c)

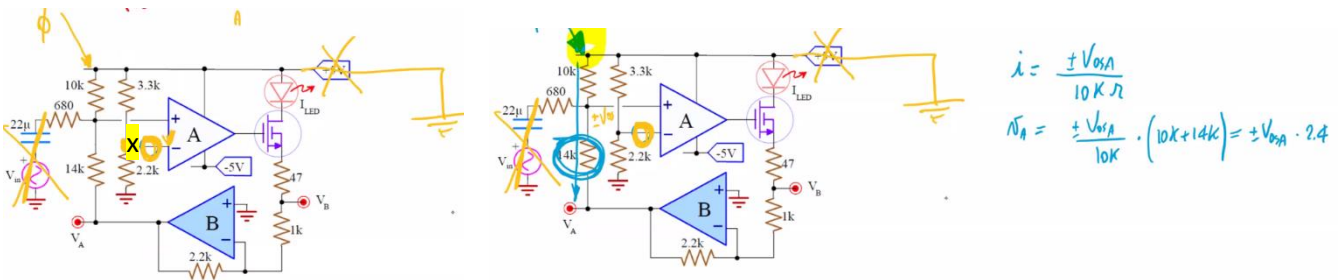We are considering the V_{os} on the $-$ terminal of OAA. If we have the offset there, we must turn off V_{in} and the PS. If so, x is at 0V , so $+$ terminal of OAA is at V_{os} .



Since the offset is a DC value, the current cannot flow in the capacitor because it is open. Since $V_{os} = \pm 5\text{mV}$, V_a varies between $\pm 12\text{mV}$.

I can now compute also I_{LED} .


$$i_{led} = \frac{V_A}{2.2k} = \pm \frac{V_{osA} \cdot 2.4}{2.2k} \approx \pm 5\mu A$$

This value is so small with respect to mA that is negligible.

Let's now move to V_{os} of OAB, that we place on the $+$ terminal. The $-$ terminal of OAA is at 0V , so also the $+$ terminal of OAA it is, so no current in 10k resistance and hence no current in the 14k resistance, so $V_a = 0\text{V}$. Hence we will have a current in the 2.2k resistance given by $\pm V_{os}/2.2\text{k}$. This is the I_{LED} current.

We see that the offset of OAB on I_{LED} is smaller with respect to the one of OAA.

Ex. 2

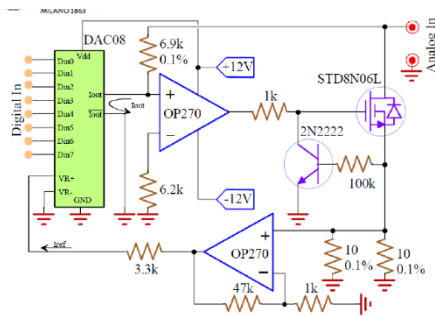


The DAC provides $I_{out} = I_{ref} \cdot D_{in} / 256$ (D_{in} is the Digital In value) and **virtual ground** at its V_{R-} input. OpAmps have $A_0 = 1500V/mV$ and $GBWP = 5MHz$. A voltage generator is applied at the Analog Input.

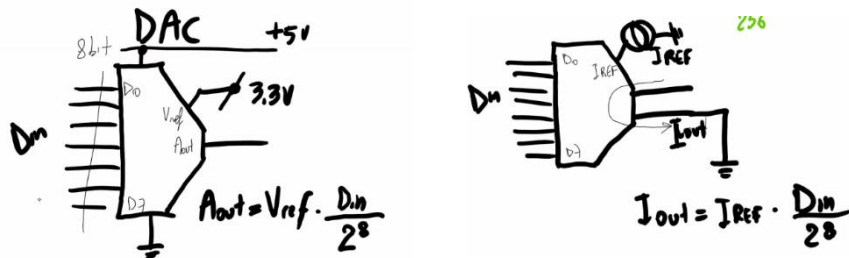- a) Obtain the analytical relationship V_{in} / I_{in} as a function of N.
- b) Reckon if the stage is stable or not when $D_{in} = 255$. Moreover, tell if stability improves by reducing D_{in} . (hint: assume $1/g_{mMOS} = 495\Omega$ and ignore the role of 2N2222 BJT).

Resolution

We have a DAC converter, which takes a digital input and gives an analog output.




In the exercise we are not using a voltage DAC (VDAC), but a current DAC. We can provide a reference current to the circuit, I_{ref} and the current I_{out} will be given by the same equation than in the case of the VDAC.

Point a)


We apply something in the Analog In port and in a Digital In port.

$$I_{out} = I_{ref} \cdot \frac{D_{in}}{2^8}$$

If I_{ref} increases, then also I_{out} increases. But if I_{out} increases, then the voltage at the - terminal of OAA (upper opamp, OAB bottom one) decreases, and so also the output. If so, let's forget the BJT, we have a source follower and then a non-inverting configuration, so also the output decreases, so we are causing a I_{ref} inside the opamp \rightarrow the loop acts trying to reduce the I_{ref} that we have at the beginning, so we have a negative feedback.

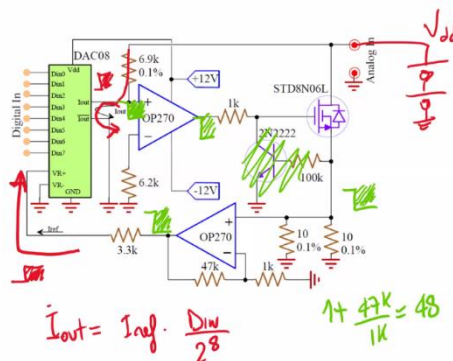


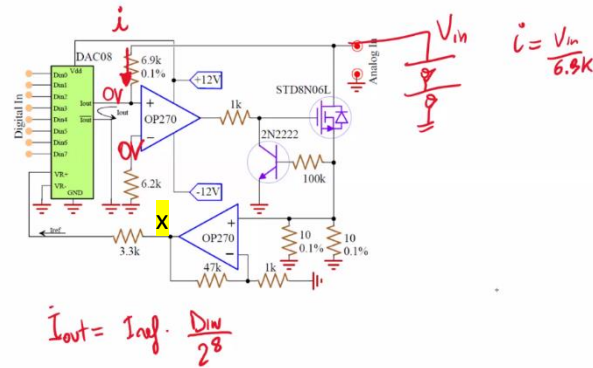The component that has a high gain is not OAB, which has a fixed gain, not the mosfet, which is a follower, so it is OAA. So both + and - terminals of OAA will be at 0V.



The current i must flow somewhere, but we cannot force a current into the DAC, so when we apply V_{in} the current causes the + terminal of OAA to increase and due to the feedback and the loop, I_{out} starts to flow and the full i will start to enter in the DAC, but not because we are forcing the current in the DAC, but because we have a loop that reacts to have the DAC drinking it.

Since we know the relationship between I_{out} and I_{ref} , I can compute I_{ref} and then V^* at node x.

 

Given V -hat we can compute the current i_d .

$$i_D = \frac{\bar{V}}{5R} = \frac{3.3k}{5 \cdot 48} \cdot \frac{2^8}{6.9k} \cdot \frac{V_{in}}{D_{1N}}$$

$$= V_{in} \cdot \frac{0.5}{D_{1N}} \text{ A/V}$$


But I need the value of I_{in} in the Analog In terminal, that is:

$$I_{IN} = i + i_D = \frac{V_{in}}{6.9k} + \frac{V_{in}}{2.8 \cdot D_{1N}}$$

The first contribution is negligible with respect to the second one. The final equation we get is the following.


$$\frac{V_{in}}{I_{in}} = 2.8 \cdot D_{1N}$$

 Hence this circuit is a programmable resistor. We apply our V_{in} , the current will enter and will flow in R , whose value will depend on the digital codification. Let's plot the relationship.



Of course, I cannot apply any V_{in} I want in input, because we could eventually get currents that must be compliant with the circuit. In fact, the value of current has to guarantee a valuable V_{gs} value on the MOSFET so that the opamp can provide it. So we should check that the circuit respects the biasing conditions and the power supply.

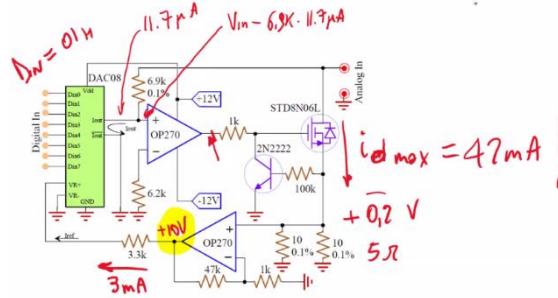To compute the maximum ratings in the circuit we have to consider the PS values in output of the opamp (even if we should have some headroom from the PS). Let's suppose the PS is +10V.




Since the voltage there is 0.2mV and the bottom resistor is 50ohm, the $i_{d,max}$ can be easily computed. 42mA is the input maximum current.

We cannot provide higher values of current because OAB saturates. To increase the 42mA value we can decrease the non inverting gain of OAB. If instead of 47k I use 1k, the $i_{d,max} = 400mA$.


Point b)

Let's compute the stability of the circuit, so we need to identify A(s) and beta(s). To choose A(s) better to select OAA, because it is a OL opamp without a local feedback.

I apply Vtest and measure Vloop.

 

 The transistor is a follower with a $1/g_m$, but in a first order approximation we can consider it negligible with respect to 50hm resistance.



$$\beta(s) = -\frac{5\Omega}{5\Omega + 1/g_m} \cdot \frac{48}{3,3k} \cdot \frac{D_m}{256} \cdot 6,9k$$


It's negative because I drink current from a resistor connected to ground, the 6.9k resistor.

$$\beta(s) = -\frac{5\Omega}{5\Omega + 1/g_m} \cdot \frac{48}{3,3k} \cdot \frac{D_m}{256} \cdot 6,9k = -0,392 \cdot \frac{D_m}{b_{D_m}}$$


$$1/\beta = \frac{2,55}{D_m}$$

Let's now draw the Bode diagram. $1/\beta$ depends on the value of D_m . In the exercise we are asked when it is $D_m = 255$.

In the worst case scenario, f^* is a decade after the second pole and we are very unstable. If we don't have a second pole, the circuit is always stable.

 

Ex. 3

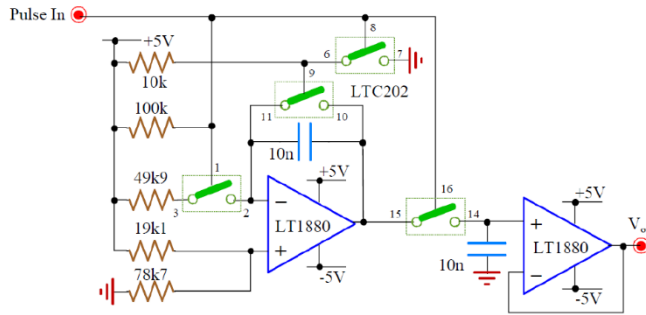


The LTC202 is a quad analog switch (closed when control pin is high). The input is a pulse, whose width T_{high} is in $1ms \pm 2ms$ range. The OpAmps have $I_b < 1.5nA$ in the $-40^\circ C \pm 85^\circ C$ range.

 - a) Compute V_{out} as a function of T_{high} .
- b) Reckon the min T_{low} that guarantees a precision of $1\mu s$.


Resolution

The switch is closed when the pin is high. The input is a pulse. If the pulse is low, e.g. 0V, we have the switch 8 open, so 9 is closed and first opamp is a buffer. Switches 1 and 16 are instead closed.




The capacitor 10u is charged to 0V and Vout is equal to the previous value stored on the 10nF capacitor.

 If Pulse In is high, 9 is open and all the other switches are closed.



We have a constant current that is 20uA. So the capacitor in feedback will be charged and the 10nF capacitor will start to discharge.

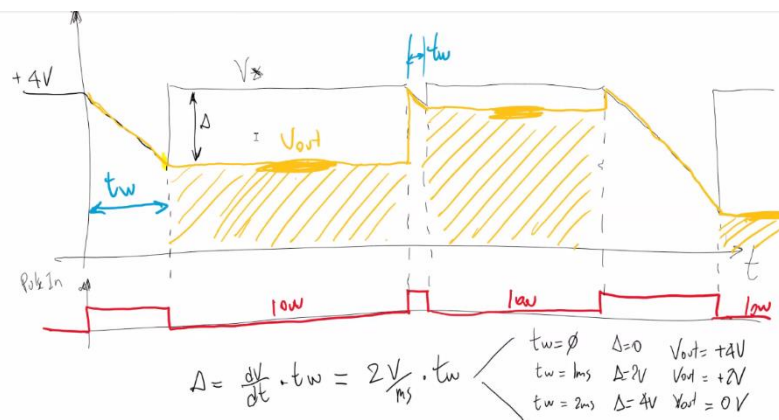Let's plot the time-dependent waveforms. When the pulse is high we start the integration and the output voltage decreases. Then, when the pulse resets to 0, the voltage in output to the first opamp resets to 4V.




The output voltage is equal to V^* when we have the switch closed, but then it remains to the previous voltage when the switch is open. Every time the pulse is low, the output is a constant voltage.

We can also compute the droop.

This circuit converts the duration of a pulse into a voltage.

 If the width is longer than 1ms, the current won't go in the second capacitor, but it is drunk by the first opamp, and the capacitor is forced to obey to V^* (output of first opamp). If the pulse lasts too long, V^* goes negative, and this can happen because we have also negative power supply. However, it cannot go lower than -5V.




$$t_{width_{max}} = \frac{9V}{\frac{dV}{dt}} = \frac{9V}{2V/\mu s} = 4.5ms$$

So better not to go longer than 4.5ms.


Point b)

I want to be capable of detecting a width of 1μs. This question is related to the tolerances due to I_{bias} . Due to the I_{bias} current, the second opamp I_{bias} causes a droop. The I_{b+} of OA1 causes an error, so V^+ won't be 4V but $4V - I_{bias} \cdot (19.1k \parallel 78.7k)$, while the I_{b-} of OA1 flows in the feedback capacitor.

Due to the I_{bias} of the opamps if the pulse is rectangular, we start from +4V and then it should go down and remain constant. But due to possible errors, we start not at 4V, but at a different value. Then due to the current in the feedback capacitor we cause a droop, so the decreasing slope can be higher or slower. Moreover, due to the I_{bias} of the second opamp, even if V_{out} should be constant it goes down due to the droop.

 

Ex. 4

 


The Offset Adjust pin is set in order to provide a +10mV output offset. $R_{off}=10\Omega$, $C_{off}=1nF$, $GBWP=10MHz$. The comparator has open-collector output.

- a) Draw the quoted waveforms at all nodes when a triangular input from 0V to 2V is applied at V_{in} , with 1ms period, and a reset pulse of 50% duty-cycle is applied every 1.5ms.
- b) Explain the circuit behavior and the role of the offset adjust.
- c) Compute the max input frequency that ensures an error lower than 1LSB for a 10bit ADC with $FSR=5V$.

Resolution

We don't know how the switch behaves, but we know that we have a S&H, and according to the indication on the circuit, when the pin is high, the switch is closed. Since we have an inverter, the input of the inverter must be low to have the output high, so either the output of the opamp is low or the reset pin is low.

The problem in this circuit is that we cannot connect a digital gain with an analog output, or we burn one of the two components because of short circuits. However, if we use gates that are open collector (also called open-drain) we can have the output connected. In them, we don't have the p-channel part. Then we use a pull up resistor that fixes the voltage. If then one gates wants to go low we are ok. So the output is high if no one is pushing it low, while it is low if one or more than the connected gates is 0.

 


So in reality the circuit is correctly wired.


The other opamp is a comparator that checks V_{in} and V_{out} . If V_{out} is higher than V_{in} , the output of it goes high. Hence I enter the sampling phase and the switch closes when either I apply a high voltage on the reset pin or when the comparator has the output low, that is when $V_{out} < V_{in}$.

If the switch is closed, $V_{out} = V_{in}$ and I store V_{in} on the capacitor C. Then when the switch will open, the capacitor will remain charged to V_{in} .

 Without the comparator, but just the reset pin:




However, if we consider the comparator:

 

First we have a reset pulse, and then is the comparator that is acting. During the reset pulse, $V_{out} = V_{in}$, but then when the reset pulse ends, if $V_{in} > V_{out}$, the switch is closed, otherwise it is open.

This circuit is a **peak stretcher**.

Ex. 5

 


A 5V zener is in series to a 1.5V LED. MOSFETs have $V_T=1V$ and $k=\frac{1}{2}\mu C_{ox} W/L=2.5mA/V^2$.


- Find the relationship I_{out}/V_{in} and the $V_{in,max}$ that ensures linear behavior for rail-to-rail OpAmps.
- Change the first stage in order to employ the same +5V power supply, but providing a $V_{in,max}=+5V$.
- Tell in which conditions the LED will light up and why the circuit is prone to burnings.

Resolution

 The first stage is a voltage to current converter, with a negative feedback.



 Then we have a 2.2k resistor and another stage that reads the voltage at the + terminal and has a p-type transistor, still with a negative feedback.




Given V^* , I can compute I_{load} .



The output current is independent on the PS, it depends on the V_{in} only. So this overall circuit is a perfect current generator, because the output impedance is infinite and it provides a current. In addition, we have a LED and a Zener diode.

 If the upper voltage of the series (24V) is higher than the bottom voltage of the series, the current should try to move top bottom, and the LED allows this, because forward bias, but the Zener not, only if we exceed V_z , which is 5V.




Hence the two will turn on if we try to increase higher than 6.5V. The LED will be brighter and the Zener will force 5V across it.


If the voltage across the pair cannot be more than 6.5V it means that there is a maximum out current.

So when V_{in} is low the current is low and the voltage drop is low and maybe the LED is not on. if we increase V_{in} , the current increases, voltage drop increases and maybe we have more than 6.5V on the series but if so, even if we increase it even further, the voltage drop cannot increase more and the output current will be fixed to a certain value.

 We can compute the value of $I_{load,max}$. We know the K value for the transistor, its V_t .



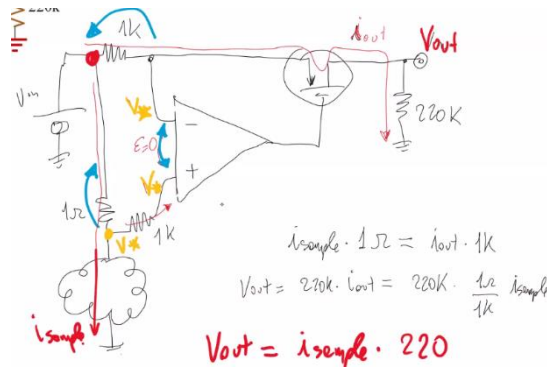
There is an overall negative feedback, so we can compute the ideal gain so that the epsilon error across the inputs of the opamp is 0. If so, no current flows in the 1k resistance on the + terminal, so the voltage V^* is copied on the - terminal. So the voltage drop across the 1 ohm resistance is the same over the upper 1k resistance if epsilon is 0.



The gain is in mV/mA. So this circuit is a current to voltage converter, it measures a current flowing into a sample and then converts it into a voltage with a sensitivity of 220 mV/mA.

Point b)


We have to design a circuit that provides a constant current of 10mA through the sample. We can use a p channel transistor and fix the voltage at its gate. Then knowing the V_t of the transistor and the K we can compute the V_{GS} we need to provide a 10mA current.

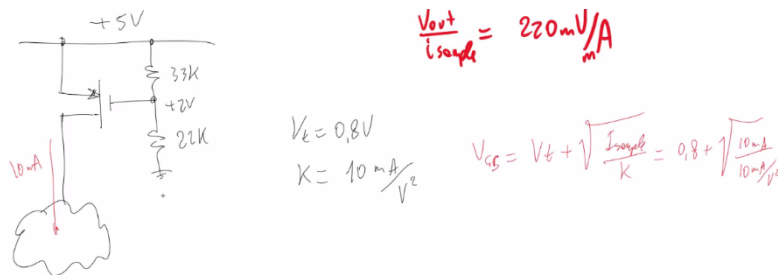


But 1.8V as V_{GS} is not true in the schematic drawn, so we need to add a resistor whose voltage drop will be equal to 1.2V for a current of 10mA, so $R = 1.2V/10mA = 120 \text{ ohm}$.

V_{drain} can move up and down but V_{ds} has to remain greater than 1 overdrive, so $V_d < 5 - 1.2 - 1 = 2.8V$.

 So the circuit is a current generator if the voltage across the sample is smaller than 2.8V.



 Hence node B, which experiences a falling edge when the light is off, thanks to the fact that node C goes low, immediately returns to a high value.




Hence voltage at node y stays high, so the voltage across the capacitor increases up until it becomes a high level. If so, node w becomes low level and node C, which was low, commutes to a high level (because node y is high and w is low).

If node C returns to a high value, node B decreases and, if there is still no light, we return to the previous situation. Hence the circuit continues to commute.




 If there is light, node C is permanently high because node B is permanently light. If there is no light, node C goes low and the led is on, and also B goes low. The oscillating condition keeps running until light is on.




So the LED is used to illuminate the environment if there is light, but it is also capable to detect if there is light in the environment and switch off.

Ex. 11

 


- $R=100\text{k}\Omega$, $C_F=10\mu\text{F}$. The digital counter provides +5V high levels and Q_0 is the least significant bit.
- Plot the V_{OUT} quoted waveform during the first 3 clock periods (10ms period).
 - Plot CK and V_{OUT} waveforms during the first 200ms.

 So we have a Schmitt trigger NAND gate (because we have an analog signal in input to it). When the output of the trigger is high, the capacitor charges and when the threshold is crossed the output of the trigger goes low \rightarrow we have an oscillator and voltage across the capacitor keeps going up and down between 2V and 3V.



 
We can compute t_{on} and t_{off} . If we look at the commutation between 3V and 2V, the delta is 3V, but then we have to wait for a time t_{acq} until the error is 2V. So we can use the equation $T_{\text{off}} = t_{\text{acq}} = \tau \cdot \ln(\Delta/\epsilon)$. Then T_{on} is almost T_{off} .



Hence we may say that $f_{\text{osc}} = 1/\tau = 100\text{Hz}$.


The clock is then provided to a counter. The Master Reset pin is connected to the Power on reset network at the beginning, which provides a reset at the power on. When we turn on the PS, node x is low, so the counter is reset. When the reset phase is finished, the node x is high and the reset is no longer active.

 The counter is a digital component with 4 output lines. At the beginning the output is 0000, then the circuit starts to oscillate, and every time we apply a rising edge, the clock increments its output.




Then the output bus of the counter is connected to an opamp. When Q3 is low and also the other wire, the NOR gate is off and the transistor is off, so we have an integrator.

 Let's draw the stage. We have an opamp with the + input grounded, the - input connected to a feedback capacitor and then we have a resistor R. If to R I apply a voltage, the circuit is an integrator and the output voltage will be 0 and then, when the switch is closed, the capacitor will integrate the current and the slope will be $-I/C$.



The problem is that here we don't have one resistor, but many of them, because we have different bits.

 
In a counter, we start from the LSB Q0 and at every clock pulse Q0 commutes, as for Q1, is commuting each rising edges of Q0.



So given f_{clock} , Q0 oscillates at $f_{clock}/2$ and so on. so the f_{clock} of the highest bit is $f_{clock}/2^{(i+1)}$. Every time a bit is high, it contributes to the current in the integrator. Of course, the higher the resistor in the output path, the lower the current. Total current in the integrator will be the following.


$$i_{in} = Q_0 \cdot \frac{5}{2R} + Q_1 \cdot \frac{5}{2R} + Q_2 \frac{5}{R}$$

This is like writing $i_{in} = 5/R * Dout$, where $Dout$ is the digital output of the counter. Once we reach the number 8, $Q3$ is high and the others are 0. If so, the NOR will have high in output and the n channel transistor behaves as a closed switch, so the capacitor is quickly discharged back to 0. Hence the output of the stage will be the following one. After the first clock, the circuit starts to integrate the current, and current that is integrated increments at each clock pulse.

 


Then at the 8th clock pulse the capacitor is discharged and V_{out} collapses back to 0. So the circuit provides an output voltage that is like a paraboloid curve.

Then for all the time $Q3$ is high the V_{out} is fixed to 0.

 


Ex. 13

 

- Employ 1.5V forward bias LEDs and a rail-to-rail OpAmp.
- Study circuit operation when the pot is turned to 100% and draw the quoted output waveform.
 - Compute the analytical dependence of the output main parameters on x pot position.


The opamp has two possible feedback path, so we have both a positive and negative feedback. Which one prevails? Of course, during fast transitions of the input, the capacitor is a slow component, so the upper path is very fast, while the green one is slow because we have the capacitor. So in fast transients we have a Schmitt trigger and the output saturates to PS. But then, after a transient the capacitor charges up and, at regime, the capacitor will open and the negative feedback becomes 1. So at regime there is negative feedback that prevails. So trigger during the transient and negative feedback at regime.

 This circuit is an oscillator. Once the output is at PS, it charges the capacitor and when the other threshold is reached, the output commutes to the other PS value.



However, in our circuit we have some differences, a LED that goes to a potentiometer and then to a capacitor and then a cursor biased by another LED.

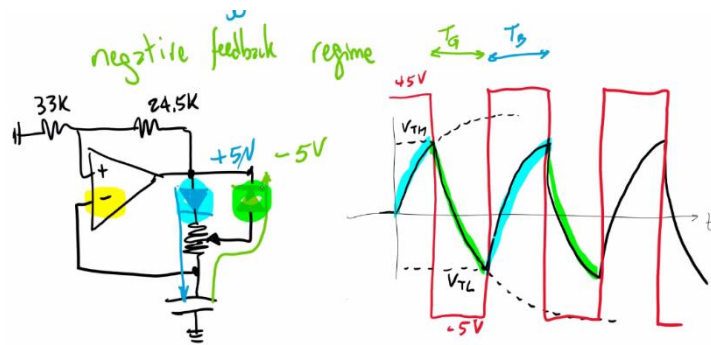
When the input is high, then the left LED is on, when low, the right LED is on. Again, we can compute the durations of the two phases and the thresholds.



$$V_{t_{H/L}} = \pm 5V \cdot \frac{33k}{33k + 24.5k} = \pm 2.9V$$

Once the capacitor has reached V_{th} , the asymptotic condition is not when we reach $-5V$, but $-5V + 1.5V$ of the green LED, so it is $-3.5V$. Hence the delta is the distance between where we start (V_{th}) and what we reach ($3.5V$) (the plot is wrong, the swing is not $+5V$).

 
In computing T_g we have to remember that the potentiometer changes its position, so we multiply its complete resistance $100k$ by x . Moreover, in this case the error is the difference between V_{tl} and the asymptotic value.




$$V_{t_{H/L}} = \pm 5V \cdot \frac{33k}{33k + 24.5k} = \pm 2.9V$$

$$T_g = 100k \cdot x \cdot 100n \cdot \ln \frac{2.9 + 3.5}{-2.9 + 3.5} = 10ms \cdot x \cdot 2.3 = x \cdot 23ms$$

We can now compute T_b .

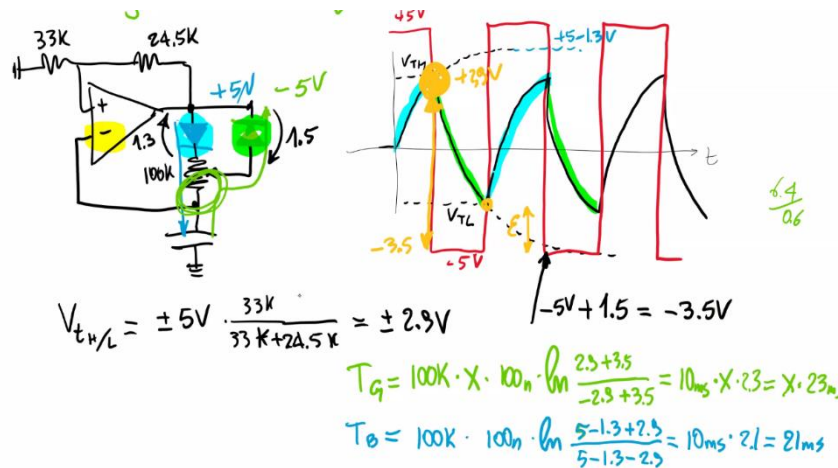


 So this circuit is an oscillator with the following output waveform.



We have a duration that is constant and set by the blue led, while the low duration is variable, it can be long or decreased down to zero. So in this circuit the period is variable and also the oscillation frequency.

Ex. 15

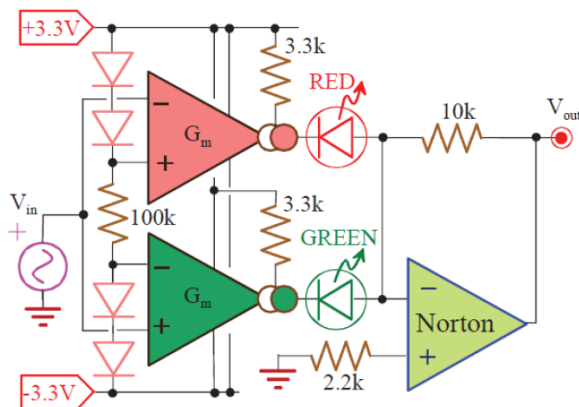

OTAs with control pin at 0V. Diodes with on-voltage of about 0.7V and LEDs with on-voltage of about 1.8V. Norton amplifier with $A_i=10$.

- a) Draw the light intensity of both LEDs vs. the V_{in} input voltage across the $-3V \div +3V$ range.
- b) Compute the V_{out} output voltage vs. V_{in} .

We have two OTAs and a Norton amplifier. We start from +3.3V and then we have the voltage drops of the two diodes, so at the + terminal of the upper OTA we have 1.9V, while at the - terminal of the bottom OTA we have -1.9V.

$G_m |_{OTA} = I_{control} / V_{th} = I_{control} / 25mV = 3.3V / 3.3k / 25mV = 40 \text{ mA/V}$


Then the second stage is a Norton amplifier, but let's start by considering it a normal VOA. The red and green led allow current only from right to left and not vice versa. The red OTA allows such current if - is higher than + terminal, so $V_{in} > +1.9V$.

In this case, $V_{out} = (V_{in} - 1.9V) * 40mA/V * 10k$

So every time V_{in} goes beyond +1.9V, then the voltage difference gets amplified by the factor above that is 400 V/V. So if $V_{in} > 1.9V$ the output is increasing with a slope of 400 V/V. For instance, if $V_{in} = 2V$, the output should be $V_{out} = 40V$, so probably the opamp saturates.

If $V_{in} < 1.9V$ then the output is 0V.

 As for the green OTA, current inward in the output is allowed if $V_{in} < -1.9V$. Still, in this case the V_{out} is positive. Again, if $V_{in} = -2V$, $V_{out} = 40V$.



So as soon as the OTA, either one or the other, activates, the LED is on and its light increases linearly.

However, the opamp is not a VOA but a Norton one. If we have a Norton amplifier, we should specify the voltage of the Z node.

For a Norton amplifier:


$$i_{out} = A_i \cdot (i_+ - i_-) = A_i (\phi - i_{out} + i) =$$

$$i_{out} = A_i \cdot \phi - A_i \cdot i_{out} + A_i \cdot i$$

$$i_{out} = \frac{A_i}{1 + A_i} \cdot \phi$$

i_+ is 0 and i_- is $i_{out} - i$, where i is the current either from the green or red LED. Since $V_{out} = i_{out} \cdot 10k$, we end up with a very similar characteristic we found in the VOA case.

Ex. 16

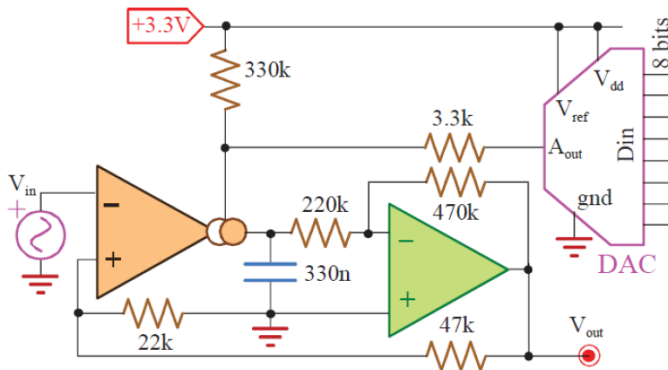


OTA with control pin at 0V and $\pm 5V$ power supply.

- a) Compute the OTA's transconductance as a function of D_{in} .
- b) Compute the real $v_{out}(f)/v_{in}(f)$ gain, bandwidth, and stability vs. the input digital code D_{in} .

Given the D_{in} of the DAC, the analog output A_{out} is the following, where D_{in} ranges from 0 to 255, so I need to divide by 2^8 .

$$A_{out} = V_{ref} \cdot \frac{D_{in}}{2^8} = \frac{3.3V}{256} \cdot D_{in} =$$


$$= 12.9mV \cdot D_{in}$$

 


Now we can compute the G_m of the OTA, and $I_{control}$ is the sum of the current from the PS and the current from the DAC. There is no current from the DAC that goes in the PS because the output of the OTA is at ground.

This spans with respect to D_{in} being the highest or the lowest value.

 Let's now simplify the circuit and analyze it.




 The second opamp is an inverting configuration with gain -2.1, and then we have another feedback in the OTA, but the feedback is negative.




Ideally, the gain is not depending on the G_m of the OTA. Now we want to compute the real gain and study the stability.

 As $A(s)$ let's consider the OTA, and all the rest is beta. In this case, $A(s)$ is not the A of an opamp, but it is the G_m , i_{out}/v_{diff} . beta is what remains, so $v_{diff}/i_{out} = v_{loop}/i_{test}$.



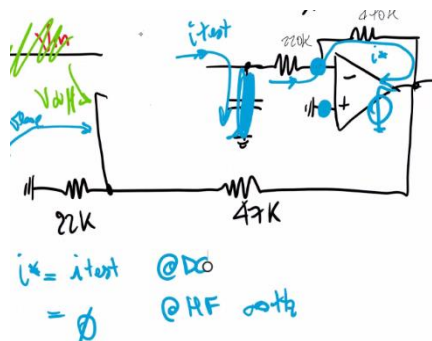Let's study the beta. + and - terminals of the opamp are at GND and VG. We can say the following.




Then we have a pole set by the capacitor. $F_p = 1/(2*\pi*R*C) = 2.2\text{Hz}$

So $\beta(\infty) = 0$ because of the pole. Instead, $\beta(0)$ is the i_{test} flowing in the 470k resistance and then in the input of the opamp.


$$\beta(0) = 470k \cdot \frac{22k}{22k + 47k} = 149900$$

 Let's plot now. Green is the G_m , blue the $1/\beta$. Unfortunately, the G_m varies because of the DAC, it can be 0.4 mA/V or 40 mA/V , but it is constant. Instead, $1/\beta$ has a zero at 2.2 Hz .




By varying the digital input code f^* changes, so we have a minimum bandwidth and a maximum one.

 The ideal gain is 3.1 , so the real gain is the ideal one and it drops down at the corresponding f^* .



We notice that by varying D_{in} we can change G_{loop} .

DAC

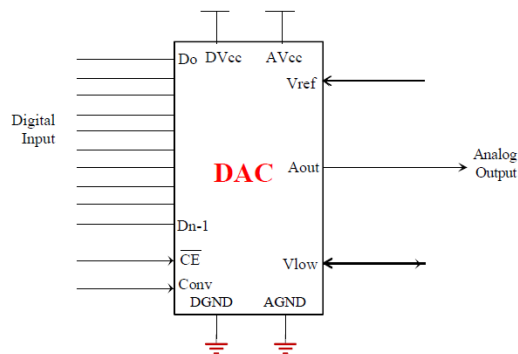


Number of bit:	n	8	16
Number of levels:	2^n	256	65536
F_{ull}S_{cale}R_{ange}:		5V	5V
Resolution:	$L_{east}S_{ignificant}B_{it} = FSR/2^n$ $1/2^n$	19.5mV 3.9‰	76μV 15ppm

Typically has both digital and analog components inside, therefore we have two different PS, so that one is not disturbing the other.


The need of two different PS is because typically the PS introduces disturbances due to the components attached to it. And if I drive with the same V_{dd} the analog and digital worlds, the disturbances are affecting both, and the quality of the output.

We have to keep the ground as much separated we can to avoid disturbances, so we connect all the digital parts of the circuit together and the analog ones together. Both V_{dd} and GND. To keep them separated, we try to reach the battery in just one position, as close as possible to it. Thus, any demand of current of the digital V_{dd} will experience voltage drops (parasitic resistances) but not at the battery level, so the analog world is preserved.

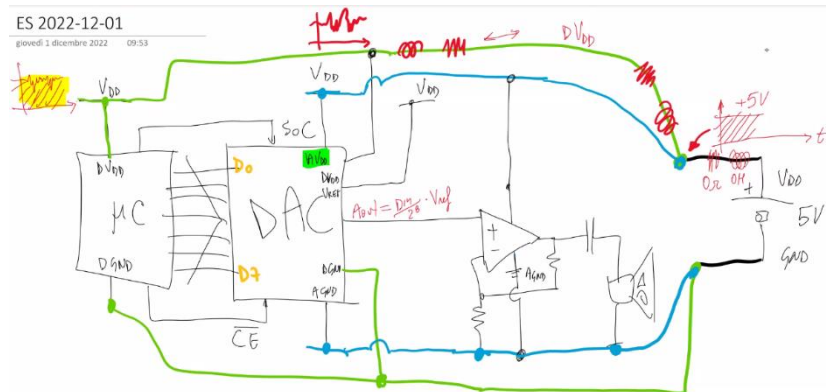


Also V_{ref} should be theoretically filtered as much as possible and not connected directly to the PS. So what we do is the following. In fact, we add capacitor to filter the possible noise due to parasitic resistances and eventually we could also include a very small value of the resistance (2.2 Ohm) to LP filter the disturbances.

If the PS is variable, we can include another precaution, that is a Zener diode, so that if PS increases to much, the voltage at the analog V_{dd} will be fixed but the Zener. Moreover, electrolytic capacitors with high value have a very high parasitic inductance, so usually in parallel to a high value capacitor we place a low value capacitor to reduce as much as possible the inductor contribution.

 

Moreover, we have also V_{ref} that is better not to connect directly to analog V_{dd} , but to further LP filter it. If we want V_{ref} to be very very stable we can also include a Zener diode.

 To avoid any possible disturbances, e.g. HF fluctuations from the PS, we also introduce a specific inductance with a low value so that the HF disturbances won't pass to the other side (yellow are parasitic inductances).




Every time we have a DAC we have the CE pin, that makes the chip work or not. This is for power consumptions reasons, so that it works only when needed.

Moreover, the digital input could change and we have the Conv pin (or SoC), that is a pin that allows for the conversion of the input only when needed and asked by the microcontroller, not always.

RESOLUTION, PRECISION AND ACCURACY

MILANO 1853

 


Resolution subdivision of output dynamics that the converter is able to resolve

Precision spread of output valuer, when the input is always the same

Accuracy maximum error between output analog value and theoretical expected one

In the case of DAC, the resolution is given by the number of bits. The precision is the maximum value minus the minimum one divided by 2. But there may be also another precision, not of different thermometers measuring the same quantity, but with the same thermometer on the same sample at different times.

ERRORS AND NON-LINEARITIES

 

Offset: output when input is 000

INL: real-ideal distance

Gain: output when input is 111

DNL: real-ideal step height


In the DAC we quote the input vs the output to see the errors. We have 8 bits and plot the value of the analog output, that is quantized. Since there are 8 steps and we want the first value to correspond to 0, the last point will be one LSB lower than FSR.

Due to errors in the DAC, if we apply 000 and the output is not 0, this error is the offset. Instead the gain error is measured when the input is 111 and the output is not FSR - LSB.


Even if we don't have these errors, we have some differences between the real and ideal behaviour. Given a specific digital input and the actual analog output, the distance between the ideal value and the real one is called INL. Instead, the distance from one point to the other should be 1 LSB ideally, but it is not always like this, so we have $LSB \pm DNL$. This is obtained by measuring the distance between one value and the other, so the step.

If DNL goes below one LSB it means that there is a missing code, and the same if $DNL > LSB$.

 Usually the manufacturer quotes the sigma of the DNL distribution, and the same applies for the INL. The INL increases to much if the conversion curve, instead of being an ideal 45° one, diverges.



VOLTAGE SCALING DAC

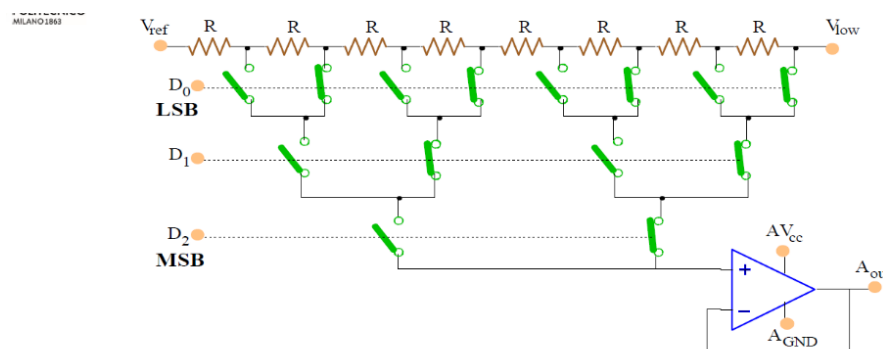

Components: 2^n resistors and 2^{n+1} pass-transistors (i.e. 2^{n+2} MOSFETs)
1 OpAmp

Advantages: easy scalability of resistors (all identical)
but OpAmp I_b current causes non-linearity issues


The idea is that we want to create all the possible combination of voltages, and in the case of n bits we need to introduce 2^n resistors. Then we have a decoder; the decoder could be an analog MUX where we provide in input the three digital lines, but it is very expensive. The smartest solution is to use switches, starting from 2^n , then $(2^n)/2$ and $(2^n)/4$ for each line.

The problem is that it requires 2^n resistors (big area) and also $2 \cdot 2^n$ switches.

The transistors must be all pass-transistors, so one issue is the high number of transistors. Another issue is the bias current of the opamp. If we have 000 we drink the I_{bias} current from ground, but each switch has a R_{on} that causes an offset error when multiplied to the I_{bias} current. Moreover, if we apply 111 we see an error $I \cdot R$, because $R \parallel 7 \cdot R$ is R . But if we apply 100, we are in the middle range and we see an impedance that is the number of total R divided by 4.

So the bias current causes an error that is not constant with the input.

 
Moreover, watch transistor has its R_{on} , that is in series with a variable resistance due to R. Hence the actual i/o curve will be something like the red one, with a very bad INL and bad INL.



Then the offset of the opamp shifts rigidly this curve up or down.

WEIGHTED-R DAC

POLITECNICO MILANO 1883

 

Components: n resistors (not quite...) and 2·n MOSFETs (p-MOS to V_{ref} , n-MOS to V_{low})
1 OpAmp


Problems: large silicon area tolerance of resistors OpAmp I_B

We are using resistances that are one the double of the other. There is a mistake in the image because the last resistance should be $2^{(n-1)} \cdot R$.

Then we use a deviator or just a switch. When we close the switch, we force a current to flow in the branch where we have the resistance. The highest current flows in the branch with the smallest resistance, so in the highest bit. Then the currents are fed to a current adder.

Another possible implementation of the upper circuit is the following one. If the uC is biased at 0-5V, the D_i are either at 0 or 5V, so we can design the DAC directly out from the uC, creating it with resistors.

 The resistance of the current adder in feedback should be half of the resistance of the LSB, so that the gain is half.




So the Weighted-R circuit seems good, because we have less switches, but the problem is that the resistors, to be multiple one of the other, should be a copy and paste several time of the smallest resistance, so we have a huge amount of resistances.

Conversely, switches are now very easy, because they should connect just +5V to the node, so it can be just a p-channel transistor. So we just need 8 p-transistors.

As for the offset voltage (at the + terminal), the gain of the circuit depends on the switches that are closed (and then we have the non inverting gain). So more or less if all switches are closed we see half R, so the gain is 2 → the bad thing is that the gain changes depending on the resistance and switches that are closed, so the offset depends on the resistance. This is the reason why we don't use just a p-channel transistor but a deviator, such that the resistor can be eventually connected to ground or power supply so that the offset sees always the same gain.


Moreover, each switch has its R_{on} , that is significant if the R is small, so the R_{on} causes an error proportional to V_{ref} .

CURRENT SCALING DAC

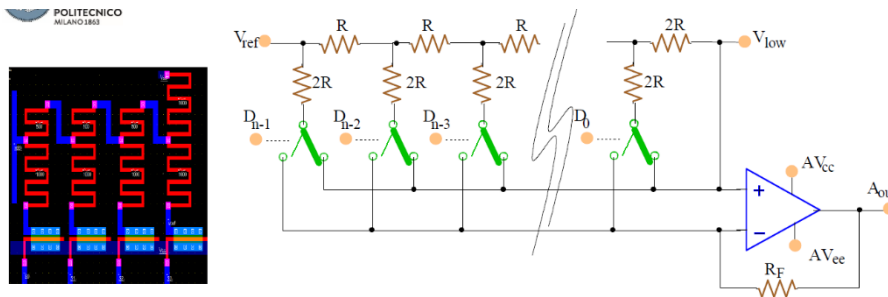

- Components:** 2·n resistors (3·n resistors) and 2·n MOSFETs (only n-MOS)
1 OpAmp
- Advantages:** easy scalability of resistors (just two different types)
easy driving of MOSFET switches

 We start from V_{ref} (e.g. 5V) and if we need half of it we take the middle node of a voltage divider with R and R. Then, to subsequently divide, we should do the following.




Then we take the current if we need (connect to - terminal, VG), or if we don't need it, we deviate to actual GND. R_f should be equal to...?

As for R_{on} , it doesn't play any effect because 2R is much larger, so we are just adding a constant error and we can add a resistance R_{on} in series to the horizontal R to compensate for this error. As for I_{bias+} and I_{bias-} and V_{os} will be asked at the exam.

The switches can also be n-channel mosfets on both sides.

SERIAL INPUT DAC

 

Components: only 2 capacitors and 5 MOSFETs (1 p-MOS, 2 n-MOS, 1 passtransistor)
1 OpAmp

Advantages: extremely compact and easy, but needs serial input (bit by bit)
MSB first? How many bits?


This is a very smart solution. We apply one bit at a time, not the full parallel bus. With 0 we apply 0V, with 1 I apply Vref to the capacitor, and we have two capacitors performing charge sharing. At start, Q1 and Q2 are open and Q3 and Q4 are closed, because we reset.

Now we open the reset, Q3 and we apply the first bit. If 0, Q2 is closed and C1 charged to 0. Then we open and we close Q3 so that charge is shared with C2. Then Q3 opens. If the second bit is 1, Q1 closed and Q2 open, so we store 5V on C1 (and C2 was at 0V). Then we open and close Q3, so we share 5V on C2 and they go to the average value between the two, that is 2.5V. Then Q3 opens and if the next bit is a 0 we close Q2, C1 is charged to zero. Then we open Q1 and Q2 and we close Q3. 2.5V were on C2, C1 was at 0V so we have 1.25V on both.


In the end, the Aout is the analog conversion of the digital input stream. Because of this, the first bit we should apply is the one that experiences more divisions, so the LSB, while the last one is the MSB.

This DAC has 4 bits (4 switches) and two capacitors.

MULTIPLYING ADC

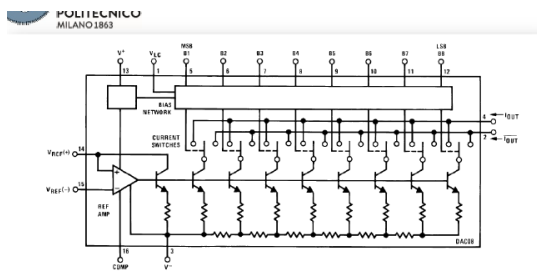

 Pin numbers represent the PDIP package. The SOIC package pin numbers differ from that of the PDIP package.



Pin numbers represent the PDIP package. The SOIC package pin numbers differ from that of the PDIP package.

Table 1. Basic Unipolar Negative Operation

	B1	B2	B3	B4	B5	B6	B7	B8	I _Q mA	I _{FS} mA	E _Q	E _{FS}
Full Scale	1	1	1	1	1	1	1	1	1.992	0.000	-9.960	0.000
Full Scale-LSB	1	1	1	1	1	1	0	1	1.984	0.008	-9.920	-0.040
Half Scale-LSB	1	0	0	0	0	0	1	1.008	0.984	-5.040	-4.920	
Half Scale	1	0	0	0	0	0	0	1.000	0.992	-5.000	-4.960	
Half Scale-LSB	0	1	1	1	1	1	1	0.992	1.000	-4.960	-5.000	
Zero Scale-LSB	0	0	0	0	0	0	1	0.008	1.984	-0.040	-9.920	
Zero Scale	0	0	0	0	0	0	0	0.000	1.992	0.000	-9.960	

ELECTRONIC SYSTEMS: 12 – DAC

www.ti.com SNAS330C – JUNE 1999 – REVISED FEBRUARY 2011

DAC0800/DAC0802 8-Bit Digital-to-Analog Converters

Check for Samples: DAC0800, DAC0802

FEATURES

- Fast Settling Output Current: 100 ns
- Full Scale Error: ± 1 LSB
- Nonlinearity Over Temperature: $\pm 0.1\%$
- Full Scale Current Drift: ± 10 ppm/ $^{\circ}\text{C}$
- High Output Compliance: -10V to $+18\text{V}$
- Complementary Current Outputs
- Interface Directly with TTL, CMOS, PMOS and Others
- 2 Quadrant Wide Range Multiplying Capability
- Wide Power Supply Range: $\pm 4.5\text{V}$ to $\pm 18\text{V}$
- Low Power Consumption: 33 mW at $\pm 5\text{V}$
- Low Cost

DESCRIPTION


The DAC0800 series are monolithic 8-bit high-speed current-output digital-to-analog converters (DAC) featuring typical settling times of 100 ns. When used as a multiplying DAC, monotonic performance over 40 to 1 reference current range is possible. The DAC0800 series also features high compliance complementary current outputs to allow differential output voltages of 20 Vp-p with simple resistor loads. The reference-to-full-scale current matching of better than ± 1 LSB eliminates the need for full-scale trims in most applications, while the nonlinearities of better than $\pm 0.1\%$ over temperature minimizes system error accumulations.

The noise immune inputs will accept a variety of logic levels. The performance and characteristics of the device are essentially unchanged over the $\pm 4.5\text{V}$ to $\pm 18\text{V}$ power supply range and power consumption a only 33 mW with $\pm 5\text{V}$ supplies is independent of logic input levels.

The DAC0800, DAC0802, DAC0800C and DAC0802C are a direct replacement for the DAC-08 DAC-08A, DAC-08C, and DAC-08H, respectively. For single supply operation, refer to AN-1525.

$$I_{out} = \frac{V_{ref}}{R_{ref}} \cdot \frac{D_{in}}{2^n}$$
 
$$I_{out} + \overline{I_{out}} = I_{FS} = \frac{V_{ref}}{R_{ref}} \cdot \frac{255}{256}$$




Pin numbers represent the PDIP package. The SOIC package pin numbers differ from that of the PDIP package.

Figure 1. ± 20 Vp-p Output Digital-to-Analog Converter

We have an opamp that drives BJT transistors. The feedback must be connected to the + terminal, otherwise we get a positive feedback. On the - terminal we can place the Vref, e.g. ground, and so +

 terminal is at ground. So we can set the current I_{ref} that will flow in the transistor. Now we can take the same transistor and the same resistor and have the same current. If I want a $I_{ref}/2$, we add a resistance. We have also to add deviators as switches. Then I_{out} will be the digital conversion of the currents.




The switches are current steerer. So we have a pin with the sum of the current, and also another, one is I_{out} , the other $I_{out-not}$.

If we buy this DAC, V_{ref-} is connected to V_{ref} , e.g. zero, and on the other pin we can connect whatever we wish to force I_{ref} , that is V_{in}/R_{ref} . Then I_{out} is given by equation x.

It's called multiplying DAC because V_{ref} can vary, and if V_{ref} varies, current varies and so all the currents vary. It performs the multiplication of an input signal analog voltage with an input digital bus.

DYNAMIC PERFORMANCES

 

Dynamic range: $D = 20 \cdot \log \frac{FSR}{LSB} = 20 \cdot \log 2^n = 6.02 \cdot n$


Quantization Noise: $\sigma^2 = \int_{-\frac{LSB}{2}}^{\frac{LSB}{2}} \epsilon_q^2 \cdot \frac{1}{LSB} \cdot d\epsilon_q = \frac{1}{LSB} \cdot \left[\frac{\epsilon_q^3}{3} \right]_{-\frac{LSB}{2}}^{\frac{LSB}{2}} = \frac{1}{LSB} \cdot \frac{2}{3} \cdot \frac{LSB^3}{8} = \frac{LSB^2}{12}$

Ideal Signal-to-Noise Ratio: $SNR|_{max} = \frac{\text{max signal power}}{\text{min noise, just quantization error}}|_{dB} = 10 \cdot \log \frac{(FSR/2\sqrt{2})^2}{(LSB^2/12)} = 6.02 \cdot n + 1.76$


Effective Number Of Bit: $n_{eff} = \frac{SNR - 1.76dB}{6.02dB}$

We want to know how much the converter distorts the input signal and the total errors on the input signal.

 Given a converter, e.g. a DAC, we have a digital stream in input and an analog output. The idea is that we know that the digital input is quantized, so also the analog output will be quantized. If we have more than 8 bits (right), we have to compute the ideal i/o characteristic, so it is difficult to understand the errors.




 So it is better to move to the digital domain instead than the frequency domain.
 So we have the signal and the ADC is divided in bits. So we have the problem of **quantization**. Selected the sampling time T_s , **the quantization error is a deterministic error**.



We can plot this error, that can be either positive or negative or 0. If the ADC is good, so the INL is not too big, so the distance between the ideal staircase and the actual one is sufficiently limited, so lower than 1 LSB, then we can say that the quantization error is in between $+1/2$ LSB and $-1/2$ LSB.

 We can also study the distribution of the deterministic quantization error. If V_{in} is constant it will accumulate in one position, but if V_{in} moves it changes, so we can assume the quantization error as randomly distributed between $1/2$ LSB and $-1/2$ LSB.



We know how to deal with noise, given the gaussian curve and the sigma. In fact, between $\pm 3 \cdot \sigma$ we have 99% of the total area.

The quantization error is different, but if V_{in} moves between different levels, I can consider this error as random and consider it as if it was a noise. So given the error that is at most $\pm 1/2$ LSB, at which noise level corresponds?

The peak to peak value of the error is 1LSB, and the peak to peak value of the sigma is $6 \cdot \sigma$. So the quantization noise is equivalent to a noise $\sigma = \text{LSB}/6$.

Let's compute now the power, not the peak to peak value, of the quantization error across the $\pm 1/2$ LSB range. Then we also divide by the range.


$$\frac{1}{\text{LSB}} \int_{-1/2 \text{ LSB}}^{+1/2 \text{ LSB}} E_q^2(x) dx$$

The result I get is the one in the slide, so $\text{LSB}^2 / 12$. But we know that the power of the noise is sigma squared, so I can say that:

$$\frac{\text{LSB}^2}{12} = \sigma^2$$

So if the introduced error is LSB, the equivalent noise is $LSB^2 / 12$. Basically we get an ideal signal plus a quantization error that gives me the real signal, but this can be also seen as an ideal signal plus the noise (right).

 Then noise has a gaussian distribution whose sigma is $\sigma = \sqrt{LSB^2 / 12}$. If the quantization error is $\pm 1/2$ LSB the two are the same.



Moreover, if a signal has a peak value that is V_p , the power of the signal is the following.

$$P_{\text{power signal}} = \left(\frac{V_p}{\sqrt{2}} \right)^2$$

I also know the power of the quantization error because I can describe it as equivalent noise.

$$P_{\text{power Bad stuff}} = P_{\text{power quantiz}} = P_{\text{power noise}} = \frac{LSB^2}{12}$$

Lastly, I can also define the SNR. The ideal one is the one with the maximum signal, when it reaches FSR, and the minimum noise. The minimum noise is instead when the noise is just due to quantization, so $LSB^2 / 12$. But $LSB = FSR / 2^n$.

$$\begin{aligned} SNR_{\text{ideal}} &= SNR_{\text{max}} = \frac{S_{\text{max}}}{N_{\text{min}}} = \frac{\left(\frac{FSR}{2\sqrt{2}} \right)^2}{\frac{FSR^2}{12 \cdot 2^{2n}}} = \frac{\left(\frac{FSR}{2\sqrt{2}} \right)^2}{\frac{FSR^2}{12 \cdot 2^{2n}}} = \frac{12 \cdot 2^{2n}}{4 \cdot 2} \\ &= \frac{3}{2} \cdot 2^{2n} \end{aligned}$$

Given my dynamics, so the FSR, we can have a theoretical maximum signal but we have also an ideal signal. So we have to introduce also the concept of theoretical SNR, that is the real signal over the minimum noise.




This is nothing else than the $SNR_{\text{ideal}} - \Delta S$, where ΔS is the ratio between the maximum signal and the real one ($S_{\text{max}}/S_{\text{real}}$).

$$SNR_{\text{theoretical}} = \frac{S_{\text{real}}}{N_{\text{min}}} = SNR_{\text{ideal}} - \Delta S$$

If $S_{\text{max}} = S_{\text{real}}$, $\Delta S = 0$ dB and the signal is the maximum one. If instead the signal maximum has a maximum value of 5V peak to peak and the S_{real} moves by just 50 mV, then I'm doing it wrong because I could have exploited the full dynamics of the DAC, and the quantization is worse because I'm using just a portion of the FSR, just 50 mV compared to 5V.

Hence $\Delta S = 5V/50mV = 1/100 = -20$ dB, so I'm loosing -20 dB.

 So we are applying the LSB to a much smaller sinusoid.



So the real quality is worsen with respect to the case in which we amplified the signal before to use the FSR.

Moreover, the electronics could be noisy, so on top of the real curve there may be also noise. Hence I also need to define a SNR real (N_{real} is the real noise, that is the noise due to quantization plus extra noise).

$$SNR_{real} = \frac{S_{real}}{N_{real}} = \frac{S_{ideal} \cdot \Delta S}{N_{quant} + \Delta N} = SNR_{ideal} - \Delta S - \Delta N$$

So on top of the signal there is an extra noise and if we use for instance an 8 bit DAC, the SNR_{ideal} is:

$$SNR_{ideal} = 6.02 \cdot n + 1.76 = 50dB$$

But then the real is just 50 mV peak to peak, so the SNR_{theoretical} is less. Since there is also some real noise, I'm even more unlucky.

$$SNR_{theor} = SNR_{ideal} - \Delta S = 50dB - 20dB = 30dB$$

$$SNR_{real} = SNR_{theor} - \Delta N = 30dB - 15dB = 15dB$$

This means that me could have entered the ADC or DAC with full dynamic, with an ideal quality that results in a SNR_{ideal} = 50 dB but instead no, because I'm using a smaller signal; the steps are equal but the quality is worse. Even worse, the actual real output has the extra noise.



So if I use a 8 bit ADC and then a low amplification we are not properly using it.

So the question is: how many bits should an ideal ADC or DAC have to have a good SNR? When the ideal SNR is equal to the real one?

The equivalent number of bits will be the following.

$$SNR_{ideal} = 6.02 \cdot ENOB + 1.76$$

$$ENOB = \frac{SNR_{real} - 1.76}{6.02} = 2.3$$


Moreover, usually the signal is in the time domain; the real signal will be quantized and maybe even noisy. How can we say how much the ideal signal is good with respect to the real one?



Instead of remaining in the time domain, let's move to the frequency domain. A sinusoid in the time domain is a delta in the frequency domain; if the frequency of the sinusoid is 7 kHz, we have two deltas at + and - 7 kHz.


If the peak voltage of the sinusoid is 2V, the power will be (2V/sqrt(2))^2. If we compute the spectrum of the sinusoid, the deltas have an height of power/2 (half at +7 kHz and half at -7 kHz).

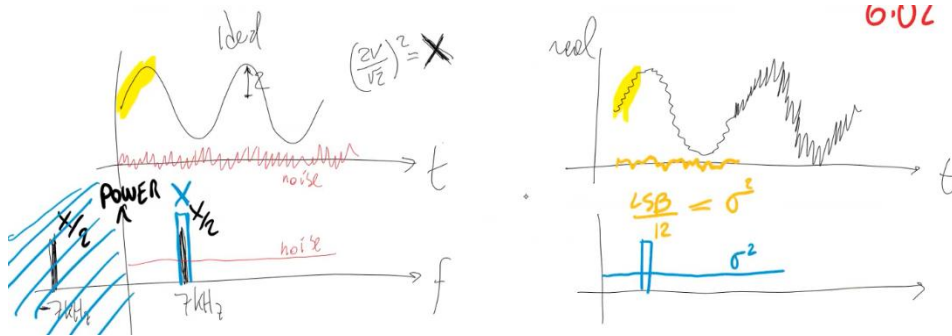We can consider just positive frequencies and saying the sinusoid has a power of x at +7 kHz. If I have noise on the sinusoid, the spectrum of the noise is a constant plateau over all the frequencies.



As for the real signal, I have quantization, and quantization error is deterministic (yellow one), but the quantization LSB can be considered as a noise whose sigma-squared is $LSB/12$. Hence the spectrum of the real signal will be the spectrum of the sinusoid and then the power of the quantization error will be equal to sigma-square.

 Moreover, if we have a time continuous signal, the spectrum goes to infinity. If instead we have a time discrete signal, the spectrum is periodic.



$T_{measure}$ is the time we take to measure the signal. If we have a long $T_{measure}$, the histogram is very well defined.


If the signal is real (not complex number), then the spectrum is symmetric around $fs/2$, so it is enough to study the spectrum between 0 and $fs/2$.

Furthermore, it is better to consider the vertical axis in the frequency domain not the power but the power per bin.


Finally, given a signal with its FSR, we measure for a time T_{meas} and the distance between samples is T_s . Then let's use a FFT algorithm and in the frequency domain we plot from 0 to $fs/2$. The number of samples inside will be $N_{sample}/2$ because I'm not using the full fs . The peak in the frequency domain will be equal to the power of the sinusoid in the time domain.

However, we have also the quantization error. The total noise due to quantization is $LSB^2/12$, and since we are plotting the power per bin, since the quantization error is a white noise and I want to compute the noise in each bin, and the bins are $N_{sample}/2$, the quantization noise will be $(LSB^2/12)/(N_{samples}/2)$.

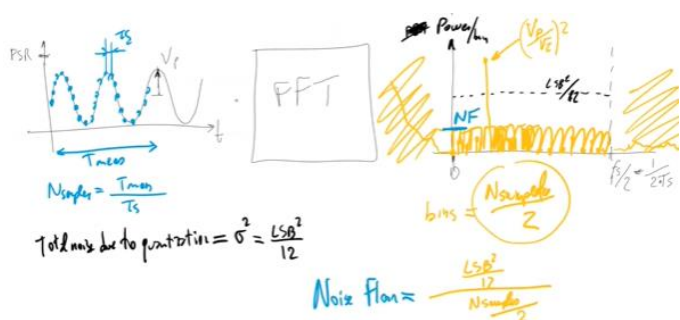So the noise is divided into many histograms and the height of each histogram is called **Noise Floor NF**.



SPECTRAL PERFORMANCES

 


Total noise (only quantization error): $\sigma_q^2 = \frac{LSB^2}{12}$

Bin-width: $bin\text{-width} = \frac{f_s}{N_{samples}}$

Noise in each bin: $\sigma_q^2 / N_{samples} = \frac{LSB^2}{12 \cdot N_{samples}}$

... hence $Noise\ Floor = - \left\{ 6.02 \cdot n + 1.76 + 10 \cdot \log \left(\frac{N_{samples}}{2} \right) \right\} = -SNR|_{theoretical} - 10 \cdot \log \left(\frac{N_{samples}}{2} \right)$

 
We have a signal that we don't want to study in the time domain but in the frequency domain. The real signal can be seen as the superposition of the ideal signal and the quantization error.



We know how to deal with noise so the idea is to consider the quantization error as if it was due to noise. Once we know the LSB we can quote the variance of the equivalent noise. Now we want to plot the power of the signal within each histogram, and the sinusoid is within a given bin width at the frequency of the sinusoid. Conversely, the total power of the noise is along all the frequencies. But since we want to describe the power due to all contributions, since the number of samples is given, the height of the sample is the noise floor, which is the full power divided by the number of samples.

If we change the FSR, the LSB changes and so maybe it is better to plot the power in terms not of V^2 , but in terms of maximum possible signal.

 We consider the maximum input signal we can apply within the FSR of the converter. The maximum peak value is half the FSR. If we want to compute the power of the maximum signal S_{max} , we have the following.



$$S_{max} = \frac{FSK}{2} = V_p$$

$$S_{max}^2 = \text{power of the max signal} = \left(\frac{V_p}{\sqrt{2}}\right)^2 = \left(\frac{FSK}{2\sqrt{2}}\right)^2$$

The idea is now to perform a sort of normalization, saying, from now on, that $S_{max}^2 = 0 \text{ dBc}$ (dBc = dB carrier).

If so, we can define the SNR_ideal that is S_{max}/N_{min} . In terms of power, it is $S_{max}^2/(LSB/12)$. If we substitute S_{max} :

$$SNR_{ideal} = \frac{S_{max}}{N_{min}} = \frac{S_{max}^2}{\frac{LSB^2}{12}} = 6.02 \cdot n + 1.76$$

This means that the noise minimum N_{min} is S_{max}^2/SNR_{ideal} .

$$N_{min}^2 = \frac{LSB^2}{12} = \frac{S_{max}^2}{SNR_{ideal}} = S_{max}^2 - (6.02 \cdot n + 1.76)$$

$$N_{min}^2 = \frac{LSB^2}{12} = - (SNR_{ideal} \text{ dB})$$

If signal is in dBc and noise is in dBc, SNR = S/N means:


$$SNR = 0 \text{ dBc} - (-50 \text{ dBc}) = 50 \text{ dB}$$

So the power is in dBc but the ratio is in pure dB.

Now we can draw our spectrum, which is symmetric around $f_s = 1/T_s$. If $N_{samples}$ is the number of samples acquired in the time domain, they are also in the frequency domain, but since we plot only from 0 to $f_s/2$, we will have just $N_{samples}/2$ in the range of interest.

The power of a signal should also be described in the negative frequencies domain, but we can forget about them, and double by two the height of the power in the positive frequencies to take into account both of them.

 From now on we will use the following codification to plot.




$$0 \text{ dBc} \equiv S_{max} \equiv \left(\frac{FSK}{2\sqrt{2}}\right)^2$$

If the real signal $S_{real} \neq S_{max}$, for instance $0.5V_p$, we can define the attenuation $\Delta_S = S_{max}/S_{real}$. Then I convert Δ_S in dB.

$$S_{\text{red}} \neq S_{\text{max}} = 2.5V_p$$

$$S_{\text{red}} = 0.5V_p = 500mV_p$$

 

$$\Delta S = \frac{S_{\text{max}}}{S_{\text{red}}} = \frac{2.5V_p}{0.5V_p} = 5 = 7dB$$

So my sinusoid won't have the maximum height, but a height that will reach $-7dBc$, so $7dBc$ lower than $0dBc$.

Now we have to plot also the power of the noise. $N_{\text{min}} = \text{LSB}^2/12 = -\text{SNR}_{\text{ideal}}$ because we defined $S_{\text{max}} = 0dBc$.

$$N_{\text{min}} = \frac{\text{LSB}^2}{12} = \dots = -\text{SNR}_{\text{ideal}}$$

$$\text{SNR}_{\text{ideal}} = 6.02 \cdot n + 1.76 = 50dB$$


Hence $N_{\text{min}} = -50dBc$.

Moreover, we are using a given number of samples to acquire the signal, e.g. 1024. So the total power is the sum of many histograms and the height of each histogram describing the noise is called **noise floor**.

$$NF = \text{Noise Floor} = \frac{N_{\text{min}}}{N_{\text{samples}}/2}$$

Translated in dB: $-\text{SNR}_{\text{ideal}} - 10 \log \frac{N_{\text{samples}}}{2}$

 Eventually, the noise floor sets to $-50dBc$ over 1024 samples, so $-50dBc - 27dBc = -77dBc$. This is the value at which the noise floor sets from the peak. The blue is the noise floor.



Now we can perform all the other possible computations. Given NF, we can compute the total noise reverting the computations.


$$N_{\text{red}} = NF \cdot \frac{N_{\text{samples}}}{2} = NF_{dBc} + 10 \log \frac{N_{\text{samples}}}{2}$$

Example 1

POLYTECHNICO MILANO 1863

The 12bit DAC has 5V FSR. The measured output spectrum has a 2kHz bin-width. There is a distortion tone at 5MHz.

 - Compute $\text{SNR}_{\text{ideal}}$, $\text{SNR}_{\text{theor}}$, SNR_{real} , and ENOB.
- Compute the THD and the SINAD.



Resolution

We know FSR = 5V, n = 12 bit, so we expect $SNR_{ideal} = 6.02 \cdot n + 1.76 = 74 \text{ dB}$.

But from the plot I see that $S_{real} = -20 \text{ dBc}$ (dBc and not dB because I'm considering power).

$$\begin{aligned} FSR &= 5V & n &= 12 \text{ bit} \\ SNR_{ideal} &= 6.02 \cdot n + 1.76 = 74 \text{ dB} \\ S_{real} &= -20 \text{ dBc} \\ SNR_{th} &= SNR_{ideal} - \Delta S \end{aligned}$$

$\Delta S = 20 \text{ dB}$.

Hence $SNR_{theoretical} = 74 \text{ dB} - 20 \text{ dB} = 54 \text{ dB}$.

Now I should check the N_{real} (ideal noise) in the ADC (or DAC). I need to check also the NF intensity and if it corresponds to the ideal one.

The ideal noise N_{ideal} (noise just due to quantization) is expected to be $-SNR_{ideal}$, so -74 dBc .

The number of bins in the spectrum is $N_{samples}/2$, and over the bins we spread the N_{ideal} . The width of each histogram is 2 kHz and the plot stops at 64 MHz, so $f_s/2 = 64 \text{ MHz}$, so $f_s = 128 \text{ Msps}$. In the range 128 Msps I find:

$$N_{sample} = \frac{f_s}{\text{bin-width}} = \frac{128 \text{ MHz}}{2 \text{ kHz}} = 64 \text{ k sample}$$

The total real noise is the noise floor real (in the plot) multiplied by the number of samples. From the plot, NF_{real} is more or less -110 dBc (in dB multiplication is the sum):

$$N_{real} = NF_{real} \cdot \frac{N_{sample}}{2} = -110 \text{ dBc} + 10 \log \frac{N_{sample}}{2} = -110 \text{ dBc} + 45 \text{ dB} = -65 \text{ dBc}$$


Now we can compute the real signal to noise ratio. The real signal is -20 dBc , the real noise is -65 dBc . Since we are in dBc, we are subtracting the two values, and the result is in dB (ratio between powers in dBc results in dB).

$$SNR_{real} = \frac{S_{real}}{N_{real}} = \frac{-20 \text{ dBc}}{-65 \text{ dBc}} = -20 \text{ dBc} - (-65 \text{ dBc}) = 45 \text{ dB}$$

The real SNR is not the ideal one because I loose ΔS and the extra noise, so I can also compute the extra noise.

$$\begin{aligned} SNR_{real} &= SNR_{ideal} - \Delta S - \Delta N \\ \Delta N &= 74 \text{ dB} - 20 \text{ dB} - 45 \text{ dB} = 9 \text{ dB} \end{aligned}$$

 So the DAC is not ideal because it has this extra noise. Theoretically we are in a situation like the following.




$$\begin{aligned} NF_{ideal} &= \frac{N_{ideal}}{\frac{N_{sample}}{2}} = -74 \text{ dBc} - 10 \log \frac{N_{sample}}{2} \\ &= -74 \text{ dBc} - 45 \text{ dB} = -119 \text{ dBc} \end{aligned}$$

Thus I can confirm that the increment in noise is 9 dB, as already done with the previous computation. In the time domain it means that we could have expected a signal with a certain quality, then due to quantization we have a 'staircase' signal. But in reality we enter with a much lower sinusoid whose peak is -20 dB with respect to the best one. When we shift from dB to normal amplitude we have to divide by 20, while when we work with power by 10. So $10^{(20/20)}$, that is a factor 0.1 less of the maximum peak.

Since I know the FSR of the circuit was 5V, the V_p (peak voltage) will be one tenth of the FSR. And since the LSB is constant ($FSR/2^n$), I can say that the quality is much poorer than before.


Because the real peak is only 250 mV and noise N_{min} is the same of before, because the quantization is the same, so the theoretical SNR is smaller, 54 dB. But instead no, because the NF_{real} is higher than the ideal one by a ΔN of 9 dB.

 This means that the real signal is not the small one with just the quantization error, but with more noise. The real situation is the black one. N_{real} will be the minimum noise plus the delta noise. This is the reason why SNR_{real} is less dB.




So we started with a 12 bit ADC and ended up with a quality that is bad, and that could eventually be reached with a smaller number of bits.

 Hence we can define the ENOB, that is 8 bit.



 
So we took the signal, we amplify it, then we go in the S&H circuit, then the ADC (e.g. 12 bit) and we reach the uC. If the amplification is not enough the SNR is poor and of 45 dB, so we don't reach the FSR. Moreover, at the end of the conversion we have a worsening due to the noise in the analog electronics and quantization error.




The concept of ENOB is to have an amplification higher to have a bigger signal reaching the FSR and the ADC could use just 8 bit instead of 12 because eventually what reaches the uC will have the same SNR.

Furthermore, looking given the plot, we know S_{real} and N_{real} and SNR_{real} and we have also minor peaks. In the text I've told there is a disturbance at 5 MHz, that is on top of the signal and always at a fixed frequency.

The other peaks are due to **harmonic distortion, they are due to ADC or DAC non linearities**. If the converter has a i/o characteristic that should be a straight line of 45°, if we enter with a precise sinusoid, we have a perfect output sinusoid. But since the converters have some non linearities (INL and DNL), we may experience compressions and decompressions. So the output is no longer an ideal sinusoid. It is still periodic for sure. But at the same time some tones are created.

 


 To differentiate between a disturbance and tones of the real sinusoid we have that if we change the frequency of the sinusoid, the disturbance stays fixed, while the harmonics change as below, coherently with the sinusoid.



Now we want to compute how big the harmonics are compared to the signal, so we have to compute the power of those signals.

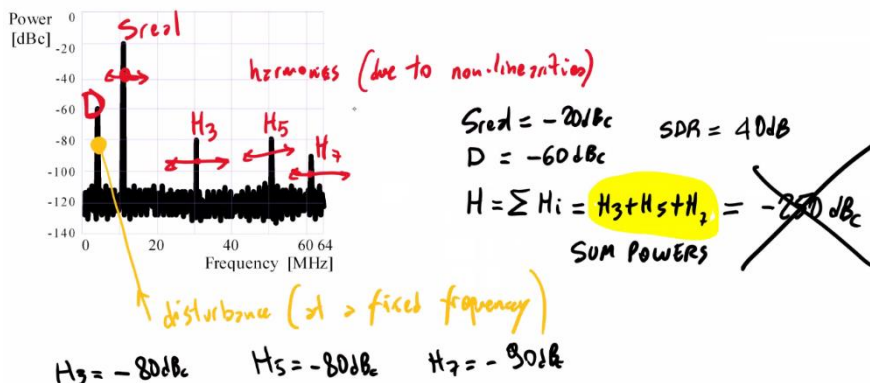$S_{real} = -20$ dBc, and from the plot the distortion is at -60 dBc. So the signal distortion ratio is 40 dB.



When we sum powers, we don't have to sum dB directly, but $10^{(-80\text{dBc}/10)}$ ecc...

$$\begin{aligned} & / \quad \frac{-20\text{dBc}}{10} \quad \frac{-80\text{dBc}}{10} \quad \frac{-90\text{dBc}}{10} \\ & = 10 + 10 + 10 = \\ & = 10^{-8} + 10^{-8} + 10^{-9} = 2.1 \cdot 10^{-8} \\ & = -77\text{dBc} \end{aligned}$$

Now we can compute the total harmonic distortion THD, which is the harmonic divided by the S_{real} .

$$\text{THD} = \frac{H}{S_{\text{real}}} = \frac{-77\text{dBc}}{-20\text{dBc}} = -77\text{dBc} + 20\text{dBc} = -57\text{dB}$$


This means that given our sinusoid, the distortion is as such that the sinusoid gets impaired by 57 dB less than the signal.

Finally, we can define the SiNAD, that is the signal over the noise plus distortion and harmonics. All of them are the real terms.

$$\begin{aligned} S_{\text{INAD}} &= \frac{S}{N+D+H} = \frac{S_{\text{real}}}{N_{\text{real}}+D+H} = \frac{-20\text{dBc}}{-65\text{dBc}-60\text{dBc}-77\text{dBc}} \\ &= -20\text{dBc} - 10\lg(10^{-65} + 10^{-6} + 10^{-77}) = \\ &= -20\text{dBc} + 59\text{dBc} = 39\text{dB} \end{aligned}$$

So coming back to understand what this means, we have the ideal case with a perfect sinusoid and quantization. But we didn't amplify the signal enough and we have a theoretical quality. To worsen the situation, we have also the noise, so we have SNR_{real} .


Then, even worse, there are also two other contributions: disturbance and harmonics.

 

 Example 2

A 16bit DAC with $\text{FSR}=5\text{V}$ receives a 2MSPs stream of a sinusoidal signal at $f_c=400\text{kHz}$ with $200\text{mV}_{\text{peak}}$ amplitude. A noise is superimposed to the signal, thus lowering the SNR by 20dB . The number of samples used for the FFT is $512,000$.

- Compute $\text{SNR}_{\text{ideal}}$, SNR_{real} , ENOB and real NoiseFloor.
- Draw the spectrum, properly quoted in [Hz] and [dBc], adding also a harmonic at $3 \cdot f_c$ due to a $\text{THD}=-70\text{dB}$.



Resolution

We have a 16 bits DAC. We don't care about S_{max}^2 because we set it at 0 dBc. Then I can compute the SNR_ideal and the noise due to quantization N_{quant} .

$$SNR_{ideal} = 6.02 \cdot n + 1.76 = 98 \text{ dB}$$

$$N_{quant} = \frac{LSB^2}{12} = \dots = N_{min} = -SNR_{ideal} = -98 \text{ dBc}$$

As for the ideal noise floor:

$$NF_{ideal} = \frac{N_{ideal}}{\frac{N_{samples}}{2}} = \frac{-98 \text{ dBc}}{\frac{512'000}{2}} = -98 \text{ dBc} - 10 \log \frac{512'000}{2} = -98 \text{ dBc} - 54 \text{ dB} = -152 \text{ dBc}$$

This is NF if the ADC was ideal. But if we have some extra noise, the $NF_{real} = NF_{ideal} + \Delta N$. Indeed, we have noise overimposed of 20 dB.

$$NF_{real} = NF_{ideal} + \Delta N = -152 \text{ dBc} + 20 \text{ dB} = -132 \text{ dBc}$$

So ideally the noise floor should be at -152 dB but in reality it's higher.


Let's now compute the SNR_theoretical, that is not the SNR_ideal because maybe we loose ΔS , and this is the case, because $FSR = 5V$ but we are entering with a 200 mV peak sinusoid. Hence the ΔS is the total signal I could apply (5V peak to peak) divided by the signal I apply (400 mV peak to peak); in dB it is 11 dB. So SNR_theoretical is 87 dB.

$$SNR_{th} = SNR_{ideal} - \Delta S = 98 \text{ dB} - 11 = 87 \text{ dB}$$

$$SNR_{real} = SNR_{th} - \Delta N = 87 \text{ dB} - 20 \text{ dB} = 67 \text{ dB}$$

Moreover, SNR_real is not SNR_theoretical because we loose also ΔN because we have an extra noise added. ΔN is 20 dB.

 Moreover, the input signal is at 400 kHz = f_{in} . Then I'm sampling at 2 Msps = f_s . So the plot will stop at $f_s/2 = 1 \text{ Msps}$. Let's plot the spectrum.



$$bin\ width = \frac{f_s}{N_{samples}} = \frac{f_s/2}{N_{samples}/2} = \frac{2 \text{ MHz}}{512 \text{ k}} = 3.9 \text{ Hz}$$

Furthermore, we know that the number of samples is 512'000, meaning that the bin width will be $f_s/512'000 = 3.9 \text{ Hz}$.


Let's now compute the ENOB = $(SNR_{real} + 1.76)/6.02$

$$ENOB = \frac{SNR_{real} + 1.76}{6.02} = \frac{67 + 1.76}{6.02} = 11.4 = 12 \text{ bits}$$

Hence we started from a 16 bit DAC but due to noise and extra noise the performances are the same of a 12 bit DAC.

The final request is to add a harmonic at 3 - f_c due to total harmonic distortion of 70 dB. The third harmonic will be at 3 times 400 kHz.

 The result would be at 1.2 MHz and in theory I should not see it if I plot up until 1 MHz, but the spectrum is symmetric, so I also see it at 800 kHz.



It's height will be 70 dB lower than the signal, since we have a distortion only due to this third harmonic. Since the signal is -11 dBc, the H3 will be at -81 dBc.


NOTES

$$\frac{N_{\text{um}}}{D_{\text{en}}} = \frac{\text{Power}}{\text{attenuation factor}} = \frac{70 \text{ dBc}}{20 \text{ dB}} = 70 \text{ dBc} - 20 \text{ dB} = 50 \text{ dBc}$$

$$H_1 + H_2 + D + N = -80 \text{ dBc} - 90 \text{ dBc} - 85 \text{ dBc} - 69 \text{ dBc} = 10 \log [10^{-8} + 10^{-9} + 10^{-8.5} + 10^{-6.9}] = -65 \text{ dBc}$$

ADC

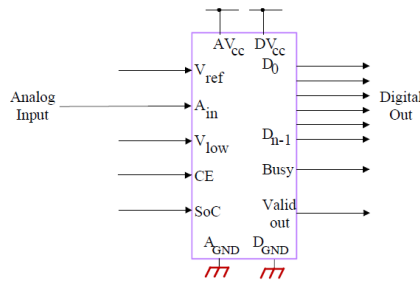The idea is to start from an input analog signal and convert it into a digital one.




Number of bit:	n	8	16
Number of levels:	2^n	256	65536
Full Scale Range	$V_{ref} - V_{low}$	5V	5V
Resolution:	$L_{least\ significant\ bit} = FSR/2^n$	19.5mV	76 μ V
		3.9 $^{0/00}$	15ppm


It requires some time to convert the signal, ranging from ns (SAR) to ms (dual-slope ADC).

As for the DAC, also in the ADC there are errors, that are the INL, DNL and missing codes. In the DAC the input was quantized and to the i/o characteristic was a set of dots; in the ADC the input is continuous, so the plot is a set of flat regions.

DNL and INL

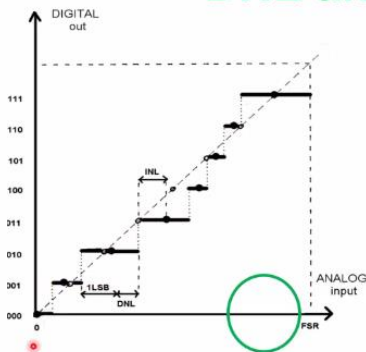


Missing codes

 

The difference between the actual step and 1LSB is the DNL. The first step has a width of 0.5LSB and the last one of 1.5LSB because the centroid starts from 0V.

As for missing codes, it may happen due to errors in the components inside the ADC.

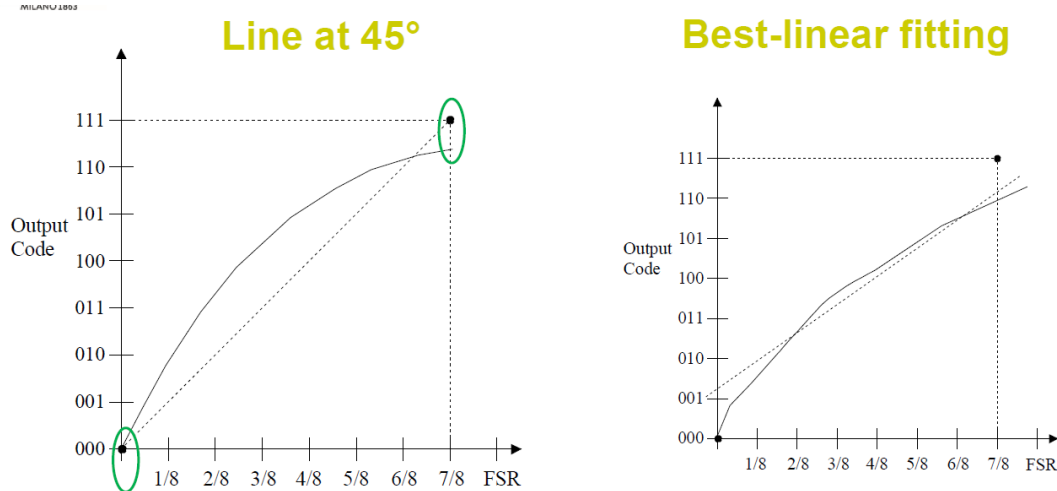Moreover, we may have also gain, offset errors and also non-linearity errors.




The INL is the distance between the real curve and the ideal one, but sometimes the INL is not important, the important thing is to have a i/o characteristic that is as much straight as possible.

SIGNAL CONDITIONING

Signal conditioning:

adjust amplitudes and impedances

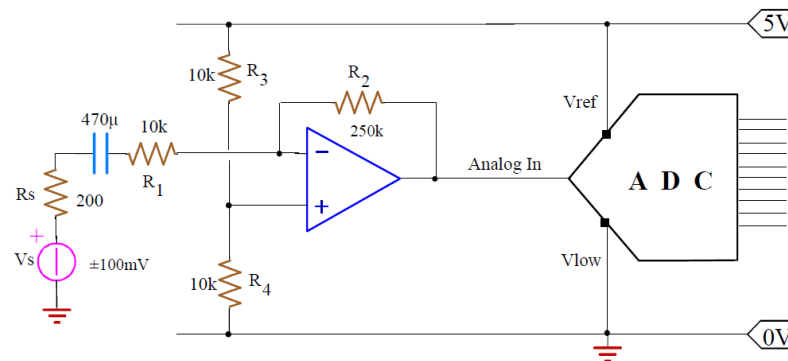

We cannot apply directly the signal to the ADC, because to exploit all the range we need some amplification. Moreover, in this example we cannot apply negative signal, so I want to shift 0V midrange and then shift all the input signals. R3 and R4 shift the range to 2.5V in input in DC, and above this we have the input signal coherently amplified.


Example of sizing

Product:	temperature meter		
Specs:	resolution	0.1°C	
	temperature	-100°C ÷ +140°C	
Components:	thermoresistance PT100	100 Ω at 0°C	+0.385Ω every 1°C
		(61.5Ω ÷ 215.5Ω)	
discretization	240°C / 0.1°C = 2400 ≈ 4096 = 2 ¹²		
bits	12		
LSB	38.5 mΩ		

The choice is to use a 12 bit ADC that discretizes the range in 4096 values. The LSB will be 38.5 mOhm. A first solution is the following.

12bit ADC and setting of V_{low} and V_{ref}

€0.5 + €3
but low precision

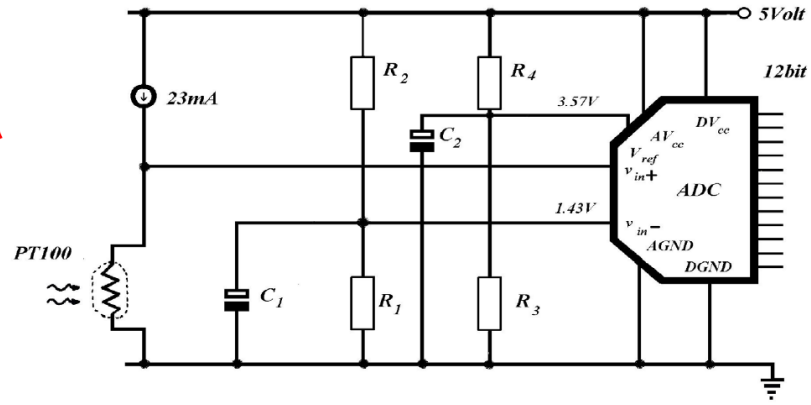


Limitation due to resistors' tolerances:
$$V_{in-} = +5V \frac{R_1(1 \pm \text{tol})}{R_1(1 \pm \text{tol}) + R_2(1 \mp \text{tol})} = +5V \frac{R_1(1 \pm \text{tol})}{R_1 + R_2} \approx +5V \frac{R_1}{R_1 + R_2} (1 \pm \text{tol})$$

We pump e.g. a current of 23 mA and we will have a given voltage that will vary. Since we use a 12 bit ADC and we want 0x000 at the output when the input is -100 °C and 0xFFFF when the input temperature is 140 °C, we could use Vref of 3.5V and a Vlow that is 1.4V. To extract those voltages we can use a voltage partition and use a capacitor to avoid a variation of the voltages due to ripple noise.

If for any reason R4 has its own tolerance (e.g. 10%), it may happen that the voltage in Vref or Vin- is not constant, but affected by the tolerance and change a lot.

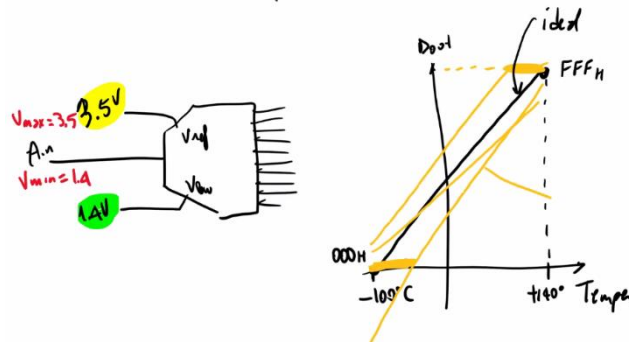
The ideal characteristic I want is the black one, which occurs if Vmin = 1.4 V and Vmax = 3.5V (with the PT100 characteristics of the previous image). but if for any reason the reference values 3.5V and 1.4V change, the i/o characteristic changes as the yellow one and we have saturations.



If I want to increase as much as possible the range, I can connect directly the Vref to PS and the other to ground the following.


14bit ADC

€4
need of calibration

 

Limitation due to self-heating

 V_{in} still moves from 1.4V to 3.5V, so I cannot use a 12 bit ADC because the FSR is 5V. In this approach I connected V_{low} to 0V and V_{ref} to 5V but the analog in varies between 1.4V and 3.5V. So I'm using just a little portion of the dynamics. To have a lot of levels to sample the signal I have to increase the number of bits to have the same LSB.




The issue is that we pump 23 mA in a resistor. But if so, there is the Joule effect and power dissipation. Since the value of the resistor is around 100 Ohm, there will be power dissipation $P = VI = RI^2 = 53 \text{ mW}$.

It is not low, because we want to measure a temperature and the resistor is heating up the sample due to power loss. To reduce power dissipation and self-heating we have to reduce the current.


Let's use 500 μA .

14bit ADC plus INA gain input stage

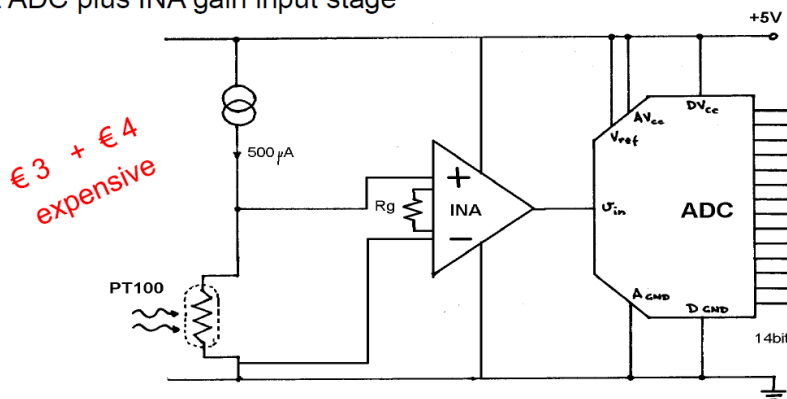

Expensive

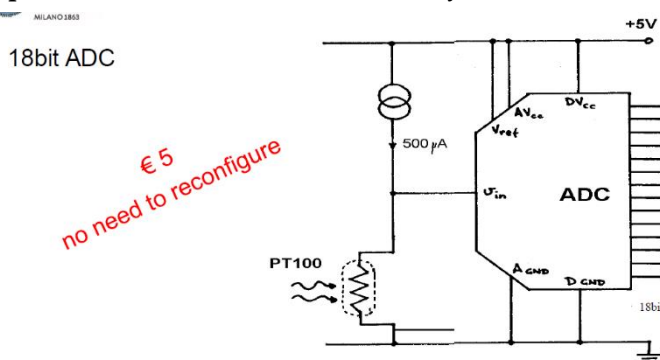Now power dissipation is very much reduced. But if we reduce the current, also the dynamics are reducing, so the 14 bit ADC is seeing a lower signal, so we need to put an INA in the middle to amplify the signal. The problem is that this solution is costly. So let's remove the INA and use another solution.



Cheap and no need for calibration or re-redign in case of different sensor, temperature range, resolution

We directly put the signal in the ADC, but the signal is much smaller (we reduced the current), so we increase the number of bits of the ADC.


$$5V: 2^n = \frac{(3.5-1.4)}{46} : 2400$$

$$n = 18 \text{ bit}$$

The advantage of this solution is that we pay just for a more expensive ADC and we spare the INA.

FLASH ADC

POLITECNICO
MILANO 1883

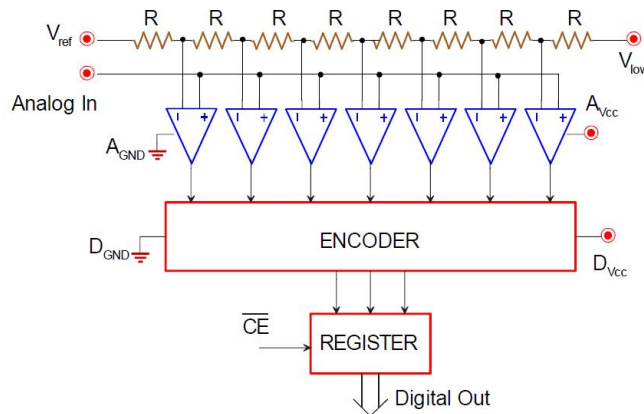

Components: 2^n resistors and 2^n comparators
1 "thermometric" encoder

Pros & Cons: very fast ($T_c < 50\text{ns}$) few bits though ($n < 10$) offset and IB of comparators

It is a fast ADC because it provides all the possible analog voltage and depending on the analog input it provides a digital output. We have an analog input, a V_{ref} and a V_{low} and we partition the FSR within these two levels. The number of resistors and comparators is 2^n . If the analog input is higher or lower than all the voltages, some comparators will be triggered and others not. Eventually we will have a digital code depending on the comparators that are active and we encode this digital code into a binary one with an encoder.

As we can see, we have a digital and analog V_{dd} and GND . It is a complex architecture in terms of number of components, even if it is very fast, we just need to wait for the comparator to trigger and the encoder to convert in a binary stream.

It is suitable for a low number of bits, otherwise we would need too many comparators.

Typical errors are due to tolerances of resistors, offset and bias currents I_b of the comparators. Since V_{os} is limited and much lower than the LSB when V_{ref} is high, this is not a problem, but if V_{ref} is too small, the offset remains constant and the quality of the ADC is worsening, and we may have some missing codes. Typically, the datasheet provides INL, DNL gain and offset if $V_{ref} = V_{dd}$, but if V_{ref} is smaller, the errors increase.


Moreover, the comparators don't have a positive feedback, they are OL opamp, so it may happen that one differential pair is fully imbalanced on the + or - depending on the analog signal, so the bias current of the comparator might be on one pin and not on the other. So the actual voltage on the reference node of the comparator will change depending on the analog input signal. Hence the characteristic will have some non-linearities, and INL increases in the middle of the conversion range.

STAIRCASE ADC

We simplify the ADC and we don't use 2^n resistors. We apply a V_{in} and compare it with a voltage that we keep updating with an internal DAC and internal counter. When we apply a low level to SoC, the latch is reset, and Q goes low and Q-not goes high, so the latch is permanently reset. So if we apply pulses to Clock line, we are applying pulses to the counter. If SoC is high, counter is at 0 and output of the DAC is 0. To start the conversion, SoC goes low.

Only when $V_{dac} > V_{in}$, the comparator triggers and Q goes high, so we have the EoC.

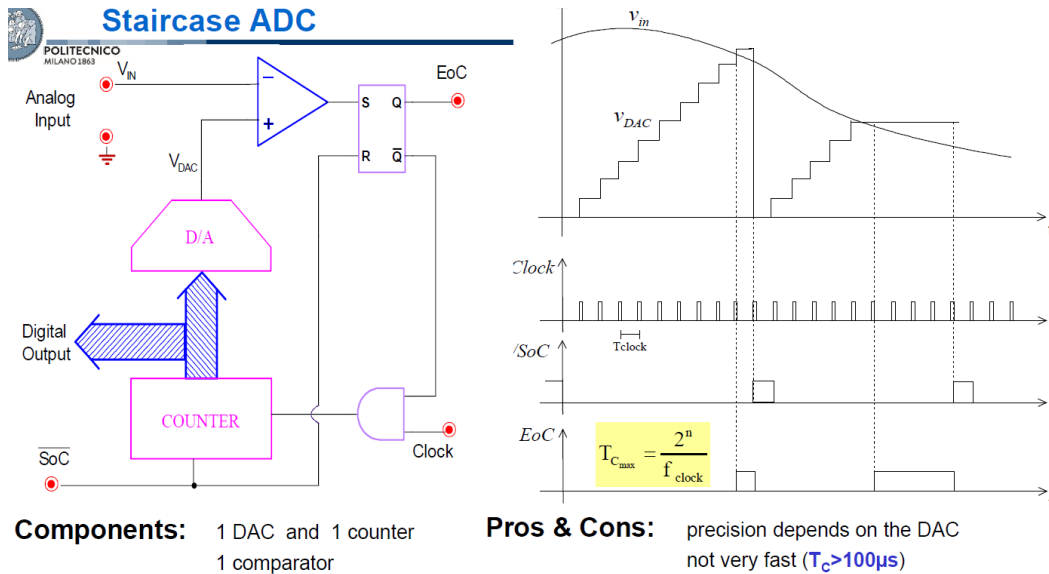Now we have only one comparator, one latch, an 8 bit counter (8 flip-flops) but also a DAC, which may be composed by resistors and opamp. So in terms of area it seems smaller than the Flash ADC but not always.




The precision depends on the DAC, if it is not precise, the EoC arrives with a wrong number of samples. Moreover, we still have the problem of offset and it is not so fast. In the worst case we have to wait 256 clock pulses if we are sampling the FSR.

Moreover, every time the conversion is over, there is another issue. The EoC goes high, the uC reads the data bus and re-applies a conversion to the SoC, and so on. But we cannot reapply SoC whenever we want, because we have to respect the Shannon theorem.

Furthermore, I give a certain SoC but I don't get the sample at the SoC time instant, but after some times, because I need to track the signal, and I run the risk that the values I convert are at different time durations because the delay between the SoC and the conversion depends on the variation of the signal.

 To avoid this problem, we can place a S&H before the ADC, even if sometimes is already integrated in the ADC.



TRACKING ADC

To improve the previous solution, we allow the staircase to go both up and down. Once we have the conversion, we don't restart then from 0, but from the last converted value. Again we have a comparator, and a counter that now can move up and down. If the comparator is high, so the analog input is lower than V_{dac} , I need to decrease the voltage, so the counter goes down. And eventually up again. Once we reached V_{in} , the counter will go up and down chasing V_{in} .


Of course, the clock should be fast enough to cope with the maximum slope of the input signal. So the tracking condition is the one aside, when the slope of the signal is smaller than the slope of the counter.

$$\frac{dV}{dt} \Big|_{max} = 2\pi f_{max} \cdot V_{pmax} \leq \frac{1LSB}{T_{ck}}$$


$$2\pi f_{max} \cdot \frac{FSR}{2} \leq \frac{FSR}{2^n} f_{ck}$$

$$f_{ck} \geq \pi \cdot 2^n \cdot f_{max}$$

 
In a kind of oversampling, it is better to use a higher clock frequency.



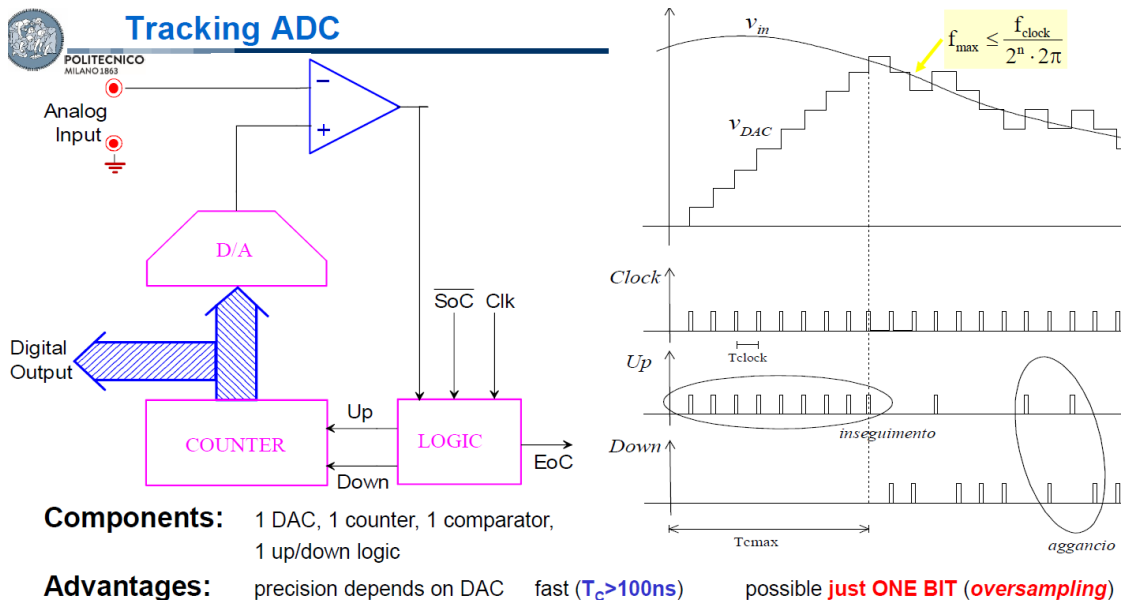The initial acquisition may be long but then, once we locked it, we can stay locked if f_{max} is the one computed before, and at every clock pulse we can have a conversion. We have a valid data at every clock pulse.



 
Moreover, we don't need to feed all the ADC output lines to the uC, because it's sufficient that the output signal up or down is given back to the uC in correspondence of the clock pulse it provides, so that it can update an internal register that the uC has.



This is also called delta modulator because it doesn't provide a digital bus to the output but simply the up or down pin.

Another possible solution is the following.


SINGLE SLOPE ADC

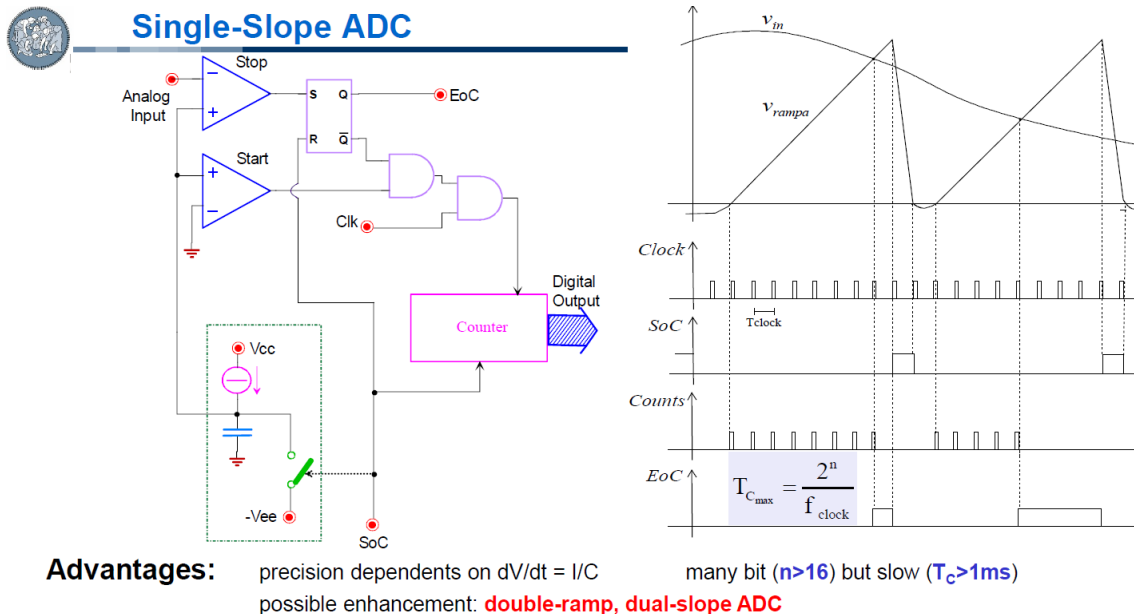

We have a constant current generator pumping current in the capacitor. When the voltage exceeds the analog input, then we stop the conversion. We start from a slightly negative value to compensate the V_{os} of the comparators. At the beginning we also reset the counter, which counts now the time. Once SoC goes low, the switch is open and the capacitor starts to charge up, with a constant ramp. The start comparator is used so that we start counting only when the cross the 0V threshold. Then the counter is enabled and it counts.

The problem is that in the worst case scenario T_{conv} is high if we need to reach FSR.

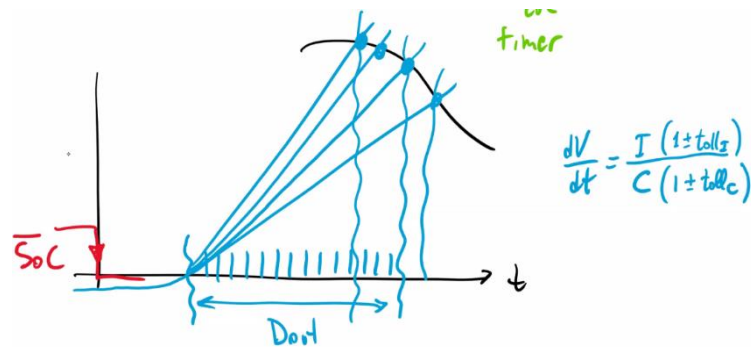The issues of this ADC are the offsets of the comparator but also the tolerances in the analog part with the current generator and the capacitor, so the slope can be different and so also the crossing with the analog signal → the digital output may vary.




In this case we have a poor reproducibility and INL and DNL are very bad.

DUAL SLOPE ADC

Since we know that we have tolerances in the components, we double them.

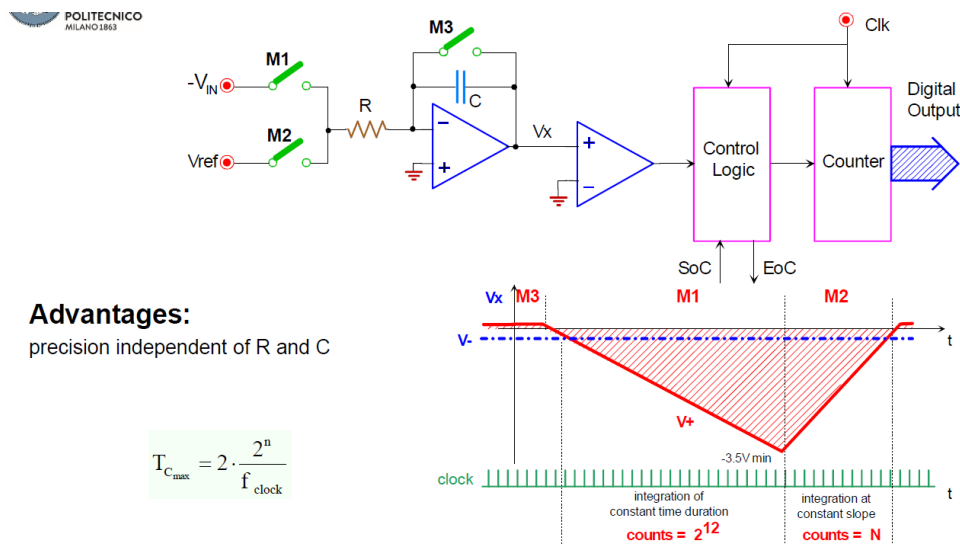We start by integrating a current in the capacitor, and there is no current generator. We start by connecting Vref and we have an integrator that is reset if M3 is close. When we start the conversion, M3 is open, Vin applied, a current Vin/R is applied to the capacitor and we decrease the voltage with a




Advantages:

precision independent of R and C


$$T_{c_{max}} = 2 \cdot \frac{2^n}{f_{clock}}$$

constant slope. Then I wait for enough time until I reach FF (2^n clock pulses) and the counter keeps counting up until then. Then M1 opens and M2 closes. The counter is reset (even if it is not needed because it is in overflow), now I integrate Vref (I must use a positive Vref and negative Vin or viceversa) on the capacitor. During this second phase we revert the direction of integration, the integration is faster because Vref = 5V and so it gets completed. The digital output is the number of pulses needed to bring the voltage Vx back to 0.

 The slope during the deintegration is V_{ref}/RC . So in the second phase the slope is steeper and the number of ck will be lower and it will be our digital output.



 We can perform the following calculations.



$$D_{out} = \frac{V_{in} \cdot 2^n}{V_{ref}}$$

$$\frac{V_{in}}{R \cdot C} \cdot 2^n \cdot T_{ck} = \frac{V_{ref}}{R \cdot C} \cdot D_{out} \cdot T_{ck}$$


So the output conversion doesn't depend on C or on the clock frequency. This because the mismatches compensate in the two phases.

We can compute the maximum conversion time, that occurs when $V_{in} = V_{ref}$, and the result is in the slide. Unfortunately, this type of ADC is slow, but at the same time I can use a large number of bits with a very fast clock.

Of course, the bias current of the opamp may impact the result, but since it has a finite and the same direction during both the integration and deintegration phases, its effect cancels out. But what about charge injection in the switches and V_{os} ? Should we add a dummy cell to compensate charge injection?


1st advantage of dual-slope ADC:

rejection of tolerances of R and C

 


2nd advantage of integration ADCs:

 
rejection of disturbance at given frequencies



The other major advantage of the dual slope ADC is that it is an integrating ADC, which means that during the first phase V_{in} is integrated, which means that the integral of V_{in} is V_{final} . But if V_{in} changes, the area (integral) changes. So if V_{in} is constant, during the first phase the slope will allow to reach a certain V_{final} , but if V_{in} varies, the final value will change and the result of the conversion will change.

 

 However, if on top of V_{in} we have a disturbance, the slope changes but the V_{final} is the same, because the areas of the disturbance cancel out. To reject the disturbance we need to obey the formula in the image.




All the frequencies following this relationship are rejected.

NMR is the **normal mode rejection factor** and it increases the higher the frequency of the disturbance.

The higher the frequency gets, the smaller is the residual area, and this is the reason why the higher the frequency gets, the higher is the rejection factor.


SAR ADC

POLITECNICO MILANO 1863

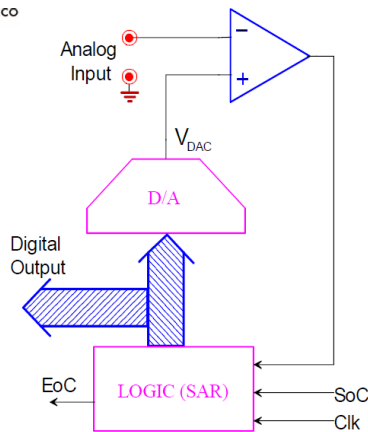

Components: 1 DAC and 1 sequential SAR logic

Advantages: precision depends on the DAC

 

We consider the 0000, then we set just the MSB to 1 to have half of the range (half of FSR). Then we compare V_{dac} with the analog in. If V_{in} is still higher, we were right in setting the MSB, otherwise we set it low. Then we set the second MSB bit to 1 and make the same comparison up until I get the correct codification.



So we need a DAC but not a counter, a logic component instead. It takes $n+1$ clock pulses to get the data (one last to fetch the data). So it is much faster than the staircase ADC.

The logic of the SAR is composed by flip-flops.

Frequencies of the SAR

If V_{in} is constant, the SAR works perfectly, and after T_{conv} the result will be perfect. But if V_{in} changes it's a mess, because we are always comparing with a new different value. So better not to vary V_{in} , but this condition is pretty tough to fulfill.

Maximum input signal frequency:

  

With NO S&H at the input:

$$f_{in,max} \leq \frac{f_{clock}}{2\pi \cdot 2^n \cdot (n+1)}$$

with S&H at the input:

$$f_{in,max} \leq \frac{f_{sampling}}{2} = \frac{f_{clock}}{2 \cdot (n+1)}$$

We want V_{in} to move less than 1 LSB; the maximum slope of V_{in} $2\pi \cdot f_{max} \cdot V_{peak}$. If I consider $8 \cdot T_{ck}$, we have to respect:

$$2\pi f_{max} \cdot \frac{FSR}{2} \leq \frac{FSR}{2^n \cdot 8} \cdot f_{clock}$$

$$f_{clock} \geq \pi \cdot 2^{n+3} \cdot f_{max}$$

Which in turns becomes:

If for instance I want to use 10 bits and $f_{max} = 20$ kHz:

$$f_{clock} \geq \pi \cdot 2^{10+3} \cdot 20kHz = 500MHz$$

It is a too high frequency for f_{clock} .

But $T_{conv} = (n+1) \cdot T_{clock}$, so the conversion time is $11 \cdot T_{clock}$. Moreover, $1/T_{conv} = 1/T_s = f_{sampl}$.

Since f_{max} should be lower than $f_{sampl}/2$, we have the following.

$$T_{conv} = (n+1) \cdot T_{ck} = 11 \cdot T_{clock}$$

$$\frac{1}{T_{conv}} = \frac{1}{T_s} = f_{sampl} = \frac{1}{11} \cdot f_{clock}$$

$$f_{max} \leq \frac{f_{sampl}}{2} = \frac{f_{clock}}{22}$$

$$T_{clock} \geq 22 \cdot f_{max}$$

So the condition from Shannon is $f_{\text{clock}} > 22 \cdot f_{\text{max}}$, and on f_{clock} I have also another condition from the SAR ADC.


So the condition for the SAR that outputs 500 MHz is the correct one. The other condition is valid if V_{in} is constant, so with a S&H in input. The limitation to be considered is the most stringent one, so if V_{in} changes the first one.

But V_{in} should not change during the conversion, so better to use a S&H in between the source of the signal and the SAR ADC to keep V_{in} constant during the conversion.

TIMINGS

Single-shot ADCs

single-shot ADCs:

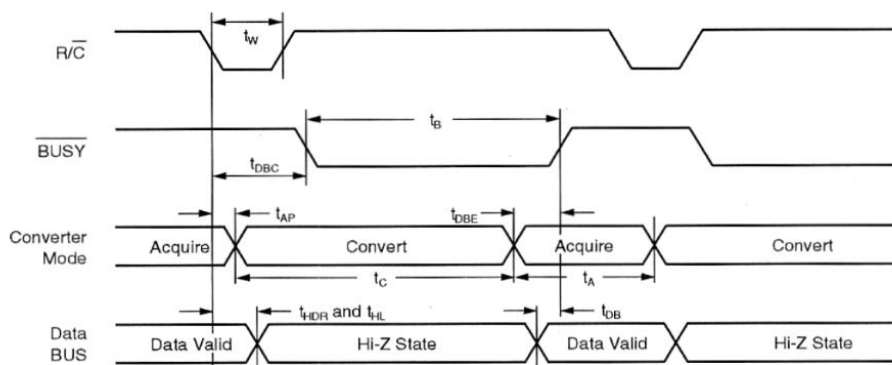

We can have single shot ADC or free running. A single shot ADC is in a condition, e.g. ready, that is $1e$ first line and it is high. If the ADC is not busy, the BUSY line is high. the data bus provides a valid data of the previous conversion. Then SoC (first line) goes low and we have the start of a conversion. Inside the ADC the S&H opens the switch and we enter the hold mode and the ADC starts converting. During conversion the output data bus is left in tri-state, which means that the output levels are in output impedance, so floating. Only at the end of the conversion, once the internal logic is done, then the logic says that the conversion is done and the digital output bus is provided to the external bus. Hence the during the conversion BUSY is low and once the data is outputted it returns to a high level.


So some ADC instead of having the EoC pin have the BUSY pin, that has the same functionality. In the single shot ADC the uC asks for the data and then it is given to it.

ADVANCED ADCs


The basic idea is to improve the previous architecture to increase the speed of the ADC or to reduce the complexity. To increase the speed we can improve a serial pipeline or a parallel architecture.

SUBRANGING ADC

In the Flash ADC we have to put in input all the possible voltages. It is not an efficient architecture because we also have a lot of comparators and we run the risk of having a lot of comparators keep consuming power and so silicon area. So the basic idea is to implement segmented quantization, a coarse quantization with less bits to locate the range where the signal is and then apply the fine conversion.

 


 In standard Flash ADCs, comparators near V_{in} are important just for the "fine" conversion, hence they are useless for the "coarse" one, thus the architecture wastes resources and is not efficient



This is the idea of the subranging ADC. The idea is that in a standard flash ADC we would need 2^n resistors and the same comparators. Now we group the resistors in 4 groups, so that we need 3 comparators that are used for the coarse definition. Once the two MSB bits are known, we close the respective set of switches depending on the thermometer code on the coarse flash encoders. Once the switches are closed, we move to the fine flash.

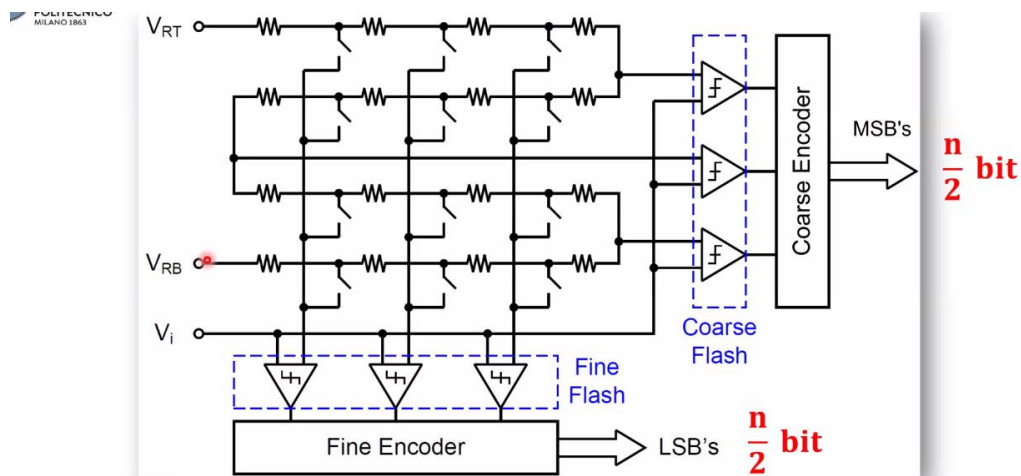
So we have developed a 4 bit ADC without needing 15 comparators, but just 6 comparators and digital electronics to drive the switches.



Coarse comparators are connected to the coarse reference ladder taps
After getting MSBs, the fine ladder taps are enabled and fine LSB are computed

This ADC consumes less power and area.

INTERPOLATION FLASH ADC

 

Example, for an 8 bit interpolation ADC:


- instead of 256 comparators, it needs just 64 ($\frac{3}{4}$ are removed)
- huge reduction of silicon area, power dissipation, input stray capacitance, layout
- improved dynamic performances (settling time, speed, ...)

Another improvement of the flash ADC. This improvement relies on the interpolation of the output voltage. In the classical ADC we have the thermometric output. The other possibility is to reduce the number of comparators, keeping only the first and last one. So just $\frac{1}{4}$ of all comparators. Now the output of each comparator should be digital.

The upper comparator won't have a digital output, so a very high gain and sharp transition, because we want to use comparators with lower gain.

In the classical flash ADC we used a comparator for each bit and the output should have been digital, so we need a high gain, to have a vertical sharp transition.

 
The concept of interpolation is that we remove some comparators and we add resistors. In this way we reduce the area occupation and we have not only the digital output of the comparator but also the intermediate values, that won't be digital of course. So the output will be like below (red and black are comparators 5 and 1).



If we vary V_{in} , the interpolating value will just be the average between the levels high and low of the comparators. The problem is that in this way we have the same output value with different analog in.

So the idea is to have not an infinite gain, but to reduce it in the comparators. Since the gain is lower, it requires a lower number of transistor so it occupies less area on the chip.

 
Now the averages follow the slope of the comparator, and with the value of analog in, the intermediate point can be above or below 0. With this information we can reconstruct the position of analog in (now the LSB is 4 times the LSB of the traditional flash ADC).





After the resistors we need to place some electronics so that we can see which analog output is above zero, and we can regain in this way the 4 bits that were lost removing the comparators. The drawback is that we have a larger area occupied by the resistors.

Higher order interpolation


Using a differential comparator. In its internal architecture, instead of using a current mirror and employing a single mode output, we remove the mirror and have a differential output. The advantage of this configuration is that when we apply a V_{diff} between the inputs of the opamp, instead of having just one commutation we have also the one on the other output. Thus, we can duplicate the network of resistors at the output of the comparator.

 

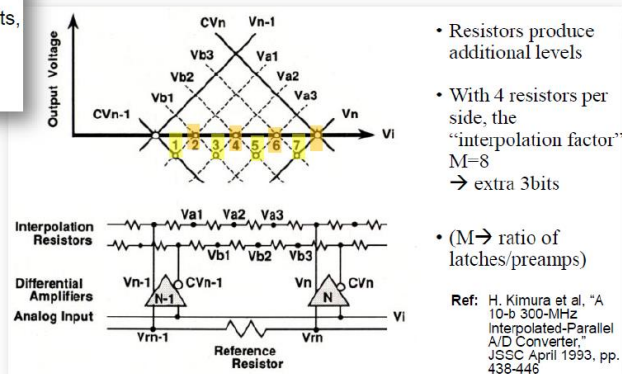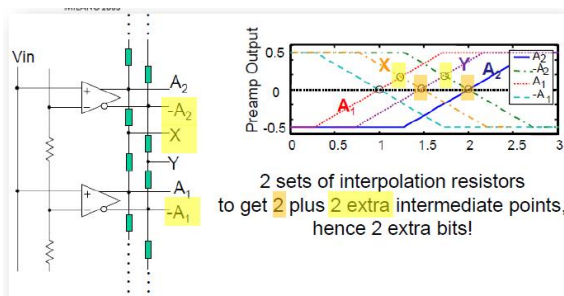We will have the intermediate values X and Y and, in this way, we have more input signal available to understand where we are.



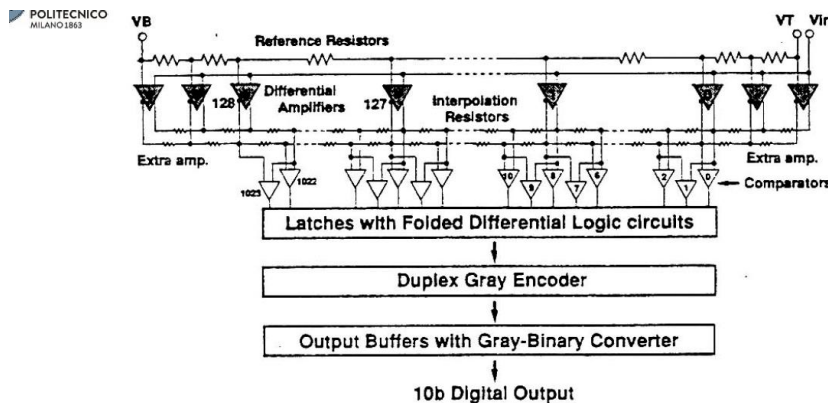
To find more commuting threshold we need to take adjacent points on the two lines of resistors.



Example of a 10bit ADC with 300MSPs:

- 128 differential OpAmps ($G=10$), each with 4+4 resistors and 8 comparators
- same total number of comparators ($128 \cdot 8=1024$), hence same area and dissipation
- but advantages for a reduced C_{in} ($128/1024$), better DNL ($V_{osOpAmp}/8$ e $V_{osComp}/Gain$)

FOLDING FLASH ADC

 


Analog pre-processing aimed at obtaining separately:

- the MSBs through a low-resolution flash ADC)
- the LSBs through a “folding” analog circuit followed by (amplification and) ADC

Let’s suppose we want to develop a 8 bit ADC and we have just two 4 bit ADC. Maybe we can use the two in parallel. Of course not, because the i/o characteristic is split in just 16 levels for both, and it is the same, not divided in 256 levels. So we cannot do this.

But we can use two comparators but on the path to one of them we need to introduce something more. A V_{in} is applied to one ADC, so we can get the 4 MSB of the conversion. Then we need to check in which range we are and the residual error on the range.

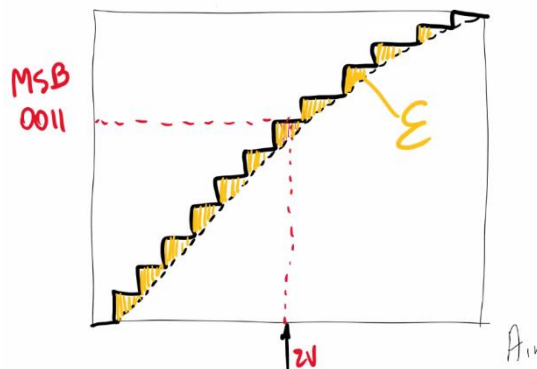So at first we convert the analog in in 16 levels, but we have also a very big error. So we need a circuit to compute the residual error that we have (yellow). If I’m able to predict the error with a certain circuit, from that I can retrieve the LSB.





The **folding circuit** tells the residual error of the 4 bit ADC. Then the error is fed to an identical ADC used for the MSB conversion and we retrieve the LSB. Thus we need less comparators but a folding circuit.

The folding circuit is not a comparator, but it tells us the error that a 4 bit ADC provides.

There can be different kind of folding ADC. Usually the following is the better transition, because having sharp transition over the folding one because in the sharp one we should be able to create very vertical transitions, and when we do this usually it implies very high gains and smoothing at the edges.

Then if for instance we need to regain two bits in the folding circuit, what we can do is taking the output of the folding circuit and compare the output and feed it to a two bits ADC (3 comparators). So the folding should be compared with 3 levels introduced by 3 comparators.

  
So if we enter with a certain analog input, the coarse ADC will give us the 3 most significant bits and the folding ADC will provide a residual analog voltage that will feed the fine ADC which will be composed by a given number of comparators. If the fine ADC has to be of 2 bits, then we would require $2^2 - 1$ comparators, so just 3.




There may be different ways of folding

So the fine ADC provides the least significant bits. So if e.g. we want to convert in 8 bits, we can have 5 bits for the coarse ADC and 5 bits of fine ADC. In the end we require less comparators.

An analog implementation of the folding circuit is the following (not asked at the exam).




Folding Flash ADC

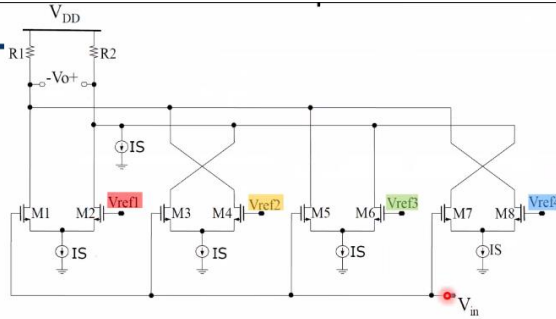

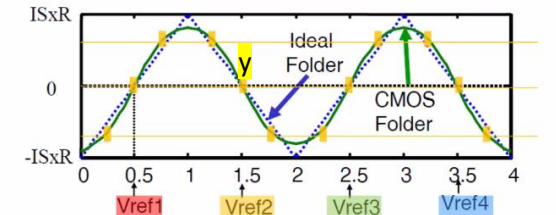Example of how to generate folds:

- via source-coupled pairs
- with $V_{ref1} < V_{ref2} < V_{ref3} < V_{ref4}$
- as V_{in} changes, only one of M1, M3, M5, M7 is on

- Actually, curves are rounded,
- Hence, accurate only at zero-crossings
- In fact, most folding ADCs do not use the folds, but only the zero-crossings!




It requires 4 different Vref and differential stages, so that we can provide an analog signal that varies as the green one. It is similar to the ideal blue one (triangular) but not actually it, due to the linear behaviour of the transistors.

Now the output of this folding circuit should feed the fine ADC. But if the fine ADC is just a 3 bit one, the green curve should be partitioned by 3 comparators. Depending on the V_{in} we apply we will see which threshold we are exceeding.


Even with a triangular i/o curve like x, or almost sinusoidal, we run the risk of having a linear transition in y, while at the top of the curve we might suffer a saturation. This is the reason why in many real implementation of the folding ADC architecture we don't use one folding circuit and one fine ADC, but two folding circuits delayed by a proper amount so that one folding circuit operates in the linear region and the other one not, so it will suffer from smoothing. Vice versa, when the V_{in} requires the first folding circuit to operate in the worst region, then the second will work in the linear region. This requires a duplication of the folding circuits and of the ADC. Hence the digital selector electronics is more complex.

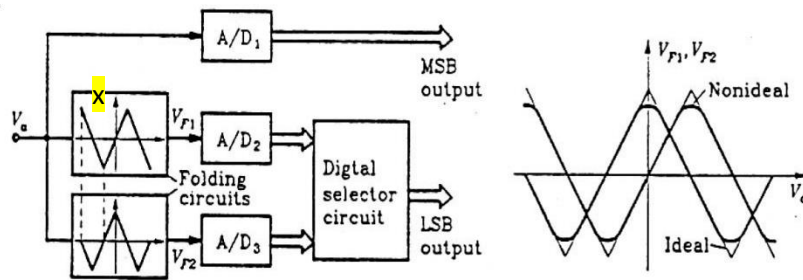However, the overall performance of this duplicated flash ADC is better.



 Example of a double folding circuit, in order to avoid non idealities of folded edges
 ... other folding shapes can be used...


There are also other architectures, like the one below (not asked at the exam). Instead of using one folding ADC and a fine ADC and a coarse ADC, we could use an architecture with 4 different folding ADCs and each folding ADC drives a comparator such that we can provide the required LSB.



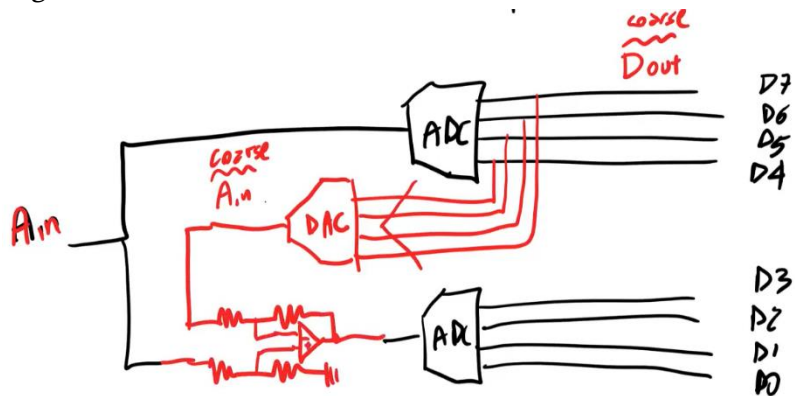Example of 4 folders with 4 folds each, so 16 zero-crossings, hence + 4 LSB bits
 ... anywayt upper limit... due to added complexity.


So the folding ADC requires a folding circuit that should be able to foresee which is the error that the coarse ADC causes. So it should provide the folded signal (triangular shaped). But how can we create this folding circuit? We need to check the digital output code of the coarse ADC, reconvert it in an analog signal, make the difference between the reconverted V_{in} and the original one to provide the residual error.

The one above is the coarse ADC, and the folding circuit could be done by taking its output code, putting a DAC to convert it into an analog signal and then we compute the difference between the signals with a standard analog stage.



This circuit works, but I would like to have a folding circuit with just analog components (without the DAC). So the correct name for this circuit is **half flash ADC**.

HALF FLASH ADC

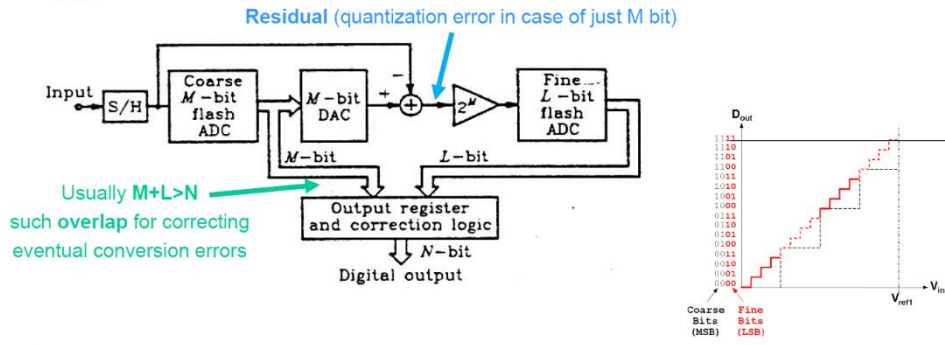

Conversion is a two-steps process through two cascaded stages
 Such "half-flash" (or "two-step flash") approach drastically reduces:
 components count power dissipation input capacitance


We apply an analog in, we use a coarse n bit ADC, we have a certain output composed by the most significant bits and then we convert these bits in analog with a n bit DAC, we do the difference to get the error and then we multiply the error by 2^n . Then we can use a L bit fine ADC.
 Hence e.g. in the case of a 8 bit ADC I would require two 4 bits ADC, so 30 comparators instead of 255.

So the coarse ADC divides the input range in a given number of levels (very large steps) and the fine LSB will describe the smaller steps.

In reality, if we do simulate the circuit, something bad happens every time we have commutation of the coarse ADC. When we are very close to the commutation of the coarse ADC (e.g. from 01 to 10), we run the risk that, due to errors introduced by the DAC, by the voltage difference stage and in the voltage gain stage, the MSB is still 01 but the fine LSB sees 10. For this reason, if we require 8 bit, we don't convert 4+4 but we add some overlapped bits. E.g. we convert 5 bits, we compute the error and then 4 bits in the fine ADC, and we use them to have 8 bits at the output and avoiding jumps in the commutating regions. This could have been avoided if all the components in our analog part would have been ideal.

The problem of this configuration is that the conversion time is prolonged because we have the input, S&H, and during hold we need t_{conv} for the coarse ADC; then we require another t_{conv} for the DAC, some analog settling time to have a proper error subtraction and then again t_{conv} for the fine ADC. Hence a 8 bit flash ADC requires 10 ns, while the half-flash 40 ns.

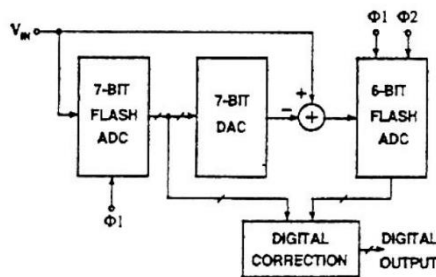It is called half-flash because we step the conversion in two steps. The one below is another implementation for a 12 bit ADC.





PERFORMANCE OF A/D CONVERTER	
Differential Linearity	12 b
Conversion Rate	5 MHz
Peak SNDR	65 dB
Input Range	5 V
Power	200 mW
Power Supply	5 V
Input Capacitance	15 pF
Active Area	1.2 mm × 3.0 mm
Technology	1-μm CMOS

 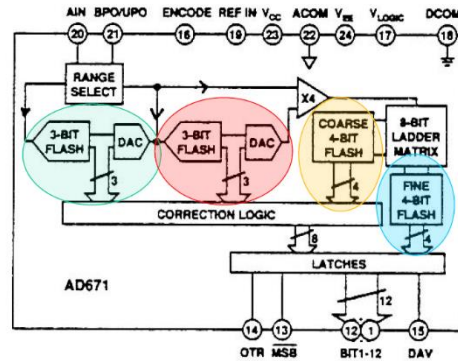Example 12bit ADC:
 a flash ADC should require 4096 comparators
 the half-flash ADC instead needs 27+26=192 comparators (1bit overlap)

MULTISTEP ADC

Instead of splitting the conversion in two steps, we use a multistep approach and we split the conversion in multiple steps.



Example of a 4-step ADC:

First 3bit and second 3bit flash ADCs, then first 4bit and second 4bit half-flash
Overall just 48 comparators !

In the example that we have in the image, we have a 3 bit flash ADC (blue), then we convert them with the DAC, we compute the error, we amplify the error and use another 3 bit ADC (red one), we get the 3 bits, we reconvert them, we compute the difference, amplification and then reconverted back with 4 + 4 bits (yellow and blue). The total 12 bit output is achieved with multiple steps.


Given the idea of the half flash ADC, we copy that idea and implement how many conversion we wish. Ideally, we can use how many conversions we want → **pipelined ADC**.

PIPELINED ADC

So we use an ADC and then a DAC and a subtraction node, many times iteratively. The problem with this configuration is the long conversion time.

It is a multistep ADC where we add a S&H circuits in the middle before each conversion stage. If we do so, we apply V_{in} , we close the first S&H and open it in the first hold phase. The first ADC will start the conversion. After t_{conv} we get the MSBs. Then the second S&H stores the error related not to the V_{in} , but to the previous sample. So the second ADC can convert the error. Hence every time we apply our analog input, it takes t_{conv} to get MSBs from the first ADC and also the other bits, because of the S&H circuits. So from when I apply analog in to when we get the digital output code we need, it takes $n \cdot t_{conv}$, where n is the stages I use. But once analog in has propagated, every time we apply a new clock pulse so we close and open the S&H circuits, the digital output of the pipelined ADC will be valid. So we have improved the conversion time of the ADC by a factor N , where N is the number of stages.

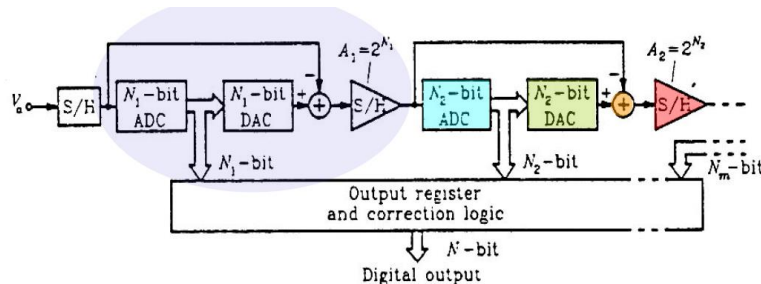The only complexity to add are the additional S&H circuits.




m -stages each one composed by:

ADC Flash (low resolution 1-4bit), DAC, analog adder and amplifying S&H

Compared to multistep ADC, now S&Hs allow parallel-pipelined processing (like bucket-brigade)

Latency

 

New output data every clock, but a latency of 8 clock cycles
Need for data alignment

Let's exaggerate the reasoning and let's suppose that we convert the analog in with many stages. If we want a 8 bit converter, instead of using 2 stages of 4 bits each or 3 stages of 3 + 3 + 2 bits, I could use 8 stages of 1 bit each. Each stage could be a 1-bit ADC that converts the signal and gives e.g. the MSB, then we have a 1 bit DAC, the output will be amplified and fed to the second stage and so on. After 8 stages I have converted the 8 bits. Of course the first bit is ready after one clock pulse, the second after two clock pulses, and so on. In the end, after 8 clock pulses I can reach all the digital output code.


An additional thing we can do, instead of reading the bits in parallel, is to read them in a serial way, when also the final bit will be ready. To do so I use a serial bus and a FIFO.

Thanks to the pipelined architecture, once we want to acquire analog in, we don't have to wait 8 clock pulses to get the full digital bus of the conversion, because thanks to the x latches and the analog sample and hold before each stage, every time we give a clock pulse it will be converted in 8 clock pulses but the following clock pulse will allow the MSB to be reconverted, while the second MSB will be converted taking into account the previous data and not the present MSB and so on. Hence the conversion time of a single shot acquisition is $8 \cdot t_{conv}$, but if we keep converting, it becomes t_{conv} , we have a valid data at every clock pulse.

Architecture

For 8 bits I need to use 8 stages, not just 2 as in the previous approach, but each stage is very simple because it deals with 1 bit.

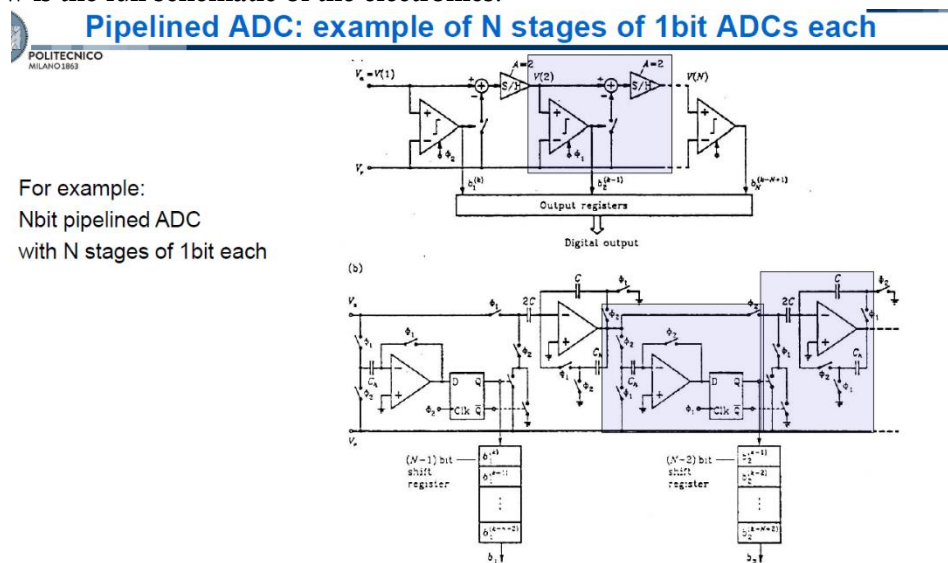
The one below is the full schematic of the electronics.



A 1 bit ADC is a comparator with a certain threshold voltage equal to $FSR/2$. Then we want a 1 bit DAC, that is a switch. Then we have a subtractor, that is basically analog electronics (e.g. 4 resistors and an opamp) and then we have the S&H. In the output register we need to introduce shift registers because the value in output from each bit is at every clock pulse.

The voltage subtractor can be even simpler than a classical subtractor. It can be made by switch capacitors, instead of resistances. This is good because in this case the opamp is capable of performing both the subtraction and the hold phase of the S&H.

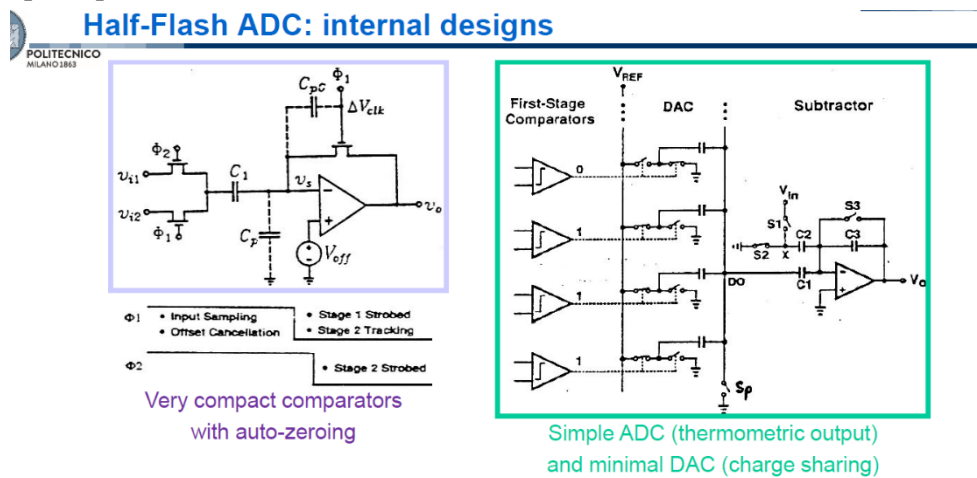When we introduced the half flash, we performed a first conversion and then a second one (coarse and fine). In output of each conversion we have a line for each bit. But if we buy the components separately, we would need 3 ICs, 2 ADCs and one DAC. The thing is, we don't need to design a full ADC and a full DAC. In principle we can have the circuit below (not asked at the exam).



Compared to flash ADCs, half-flash ADCs minimize area occupation and power dissipation, though with slower conversion time


We need comparators. The comparator is the one in the purple box, and I connect it to the analog in. The other pin of the comparator should be the V_{ref} .

But the comparator has its own offset, so we want to use the commutating auto-zeroing comparator. The same – terminal is used to connect either to analog in or to V_{ref} . The capacitor C_1 is used because firstly I store V_{ref} and V_{os} closing the feedback switch, so that we have a buffer. So I close the feedback switch and store V_{ref} on the capacitor. Then I close the switch of V_{ref} and C_1 charges up to $V_{ref} - V_{os}$. Now the V_{ref} switch is opened and the analog in is closed. The new voltage I apply is applied to C_1 , which was charged to $V_{ref} - V_{os}$. The output is high or low depending if analog in + $V_{ref} + V_{os}$ is higher or lower of V_{os} . V_{os} cancels out and hence the output is the comparison between analog in and V_{ref} , because the two are in series.


Then the comparator provides a thermometric code, so we need an encoder after the comparators to get the final 7 bits. But why should we provide a binary code to the DAC that then has to reconvert it in analog signal? We can directly use the thermometric code to feed the DAC. So the outputs of the comparators are used to drive the following DAC, that should not be a 'state-of-the-art' DAC. We use capacitors and n-channel and p-channel switches. The output after the capacitor is the analog output of the DAC. Then the next stage computes the subtraction.

TIME INTERLEAVED ADC

MILANO1863

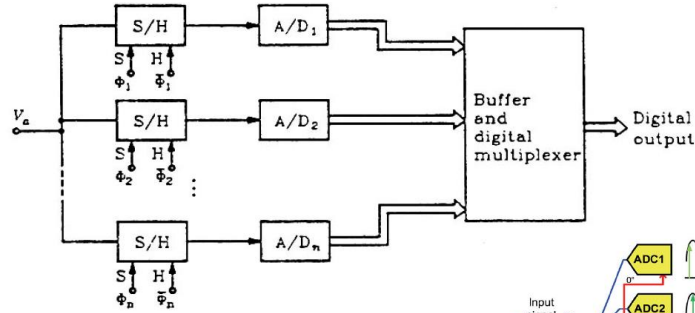

 - For high f_s more ADC can run in parallel on different samples:
- C channels with identical Nbit ADCs each, with individual S&H
 - Each channel samples the input signal at a rate $(C \cdot T_{\text{clock}})^{-1}$
 - The channel operate in sequence
 - Overall sampling rate is N-fold that of a single channel




Instead of using different ADCs one after the other in a series approach, this approach relies on the parallel acquisition from multiple ADCs in parallel.

We have the analog in, then we implement different channels, e.g. 3 in the example. Each channel has its S&H, ADC and the digital output feeds a digital electronics that multiplexes one of the outputs to the digital output bus.


Let's suppose that we have a HF signal in the range of MHz; to properly acquire it we should need an ADC that should run in the giga-sample per second regime, so one sample every ns, so an ADC with 1 ms t_{conv} . Even the fastest ADC doesn't provide such speed, so we could use 4 fast ADCs and drive one or the other by time shifting the opening and closing time of S&H such that each channel acquires a sample in a specific time instant. In this way the digital output electronics will contain the conversion of each channel delayed in time and so we can provide the digital output code every $1/4^{\text{th}}$ of ns (from the bottom image).

Mismatches

 

Offsets:


spurious tones at multiples of f_s/C

 

Gains:

spurious tones at frequencies :
 
$$f_s/C \pm f_{in} \quad 2 \cdot f_s/C \pm f_{in} \quad \dots \quad (C-1) \cdot f_s/C \pm f_{in}$$




Sampling time:

spurious tones of intensity increasing with f_{in}


Errors now must be treated in a more complex way than in the standard case. Let's suppose that each channel has its V_{os} . They are DC errors, so the output error that we can find is a DC value. So theoretically we can subtract a constant number from the digital output but it is not like this.

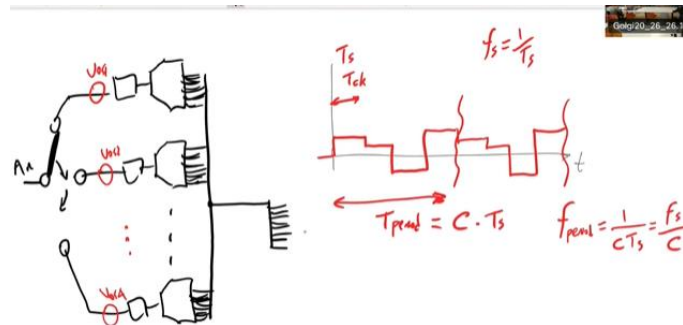We have different channels and in the time domain, even if the input is 0, the output will be the offset voltages of the different channels, repeating in time. The error repeats with a periodicity equal to the number of channels per the sampling time T_s .



This means that the digital output code won't have a constant error, but a periodic one. Because of this offset error, new harmonics appear in the spectrum, with a fundamental tone given by F_s divided by the number of channels.

 Instead, in case of gain error, we know that each S&H has its own gain. So if we have the signal and each channel has its own gain, the input might suffer from a magnification or a decrease, so we would convert the wrong value.




This is for sure not a constant error, because it depends on the V_{in} . So to model it, we see that every time a channel acquires the signal, the error we cause is an amplified version of the input signal. We are suffering from an **amplitude modulation**, that happens every 4 times T_{clock} . So on the top of f_s we modulate the amplitude, so we have f_{in} that appears on the left and right of each harmonic of f_s , f_s included.

Eventually, there is a third error that is the time jitter, which can also be modelled as an amplitude modulation of the input signal.

EXAMPLE OF WRITTEN TESTS

Ex. 1

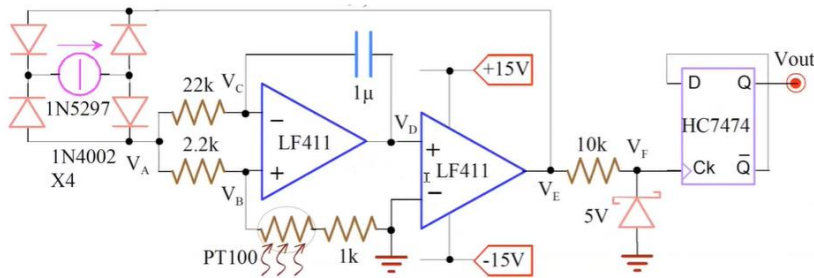


Il 1N5297 è un generatore di corrente integrato che genera 1mA.
 Il sensore termico è una PT100 che vale 100Ω a 0°C e varia di circa 0.4Ω/°C.
 Studiare il funzionamento del circuito a 0°C.

- Spiegare il funzionamento del circuito. (Si suggerisce di partire dall'istante in cui $V_E = +15V$, per poi ricavare le correnti nelle resistenze da 22kΩ e 2.2kΩ e le tensioni V_B e V_C .)
- Disegnare le forme d'onda quotate delle tensioni ai nodi e ricavare la frequenza di commutazione di V_{out} .
- Dire come si modificano le forme d'onda al variare della temperatura misurata dalla PT100.

Resolution

The first opamp has a capacitor in feedback that should be an integrator. Then the second opamp could be a comparator. But we have also an overall feedback, so maybe we have an overall negative feedback. Because of the integrator, I can suppose that the signal in the forward branch changes slowly. Hence it is not a negative feedback circuit, but maybe an oscillator because of this delay.

If I still suppose that the circuit is a comparator, the output of the comparator can be one of the two PS. Let's suppose that we have +15V in output when we connect the PS. Let's suppose the C is not charged (0V across it). If this is the case, V_b is free to move, while V_c not because it is VG, to it is the copy of V_b . The current should go from high voltages to low one, so in the upper left diode and bottom right one.

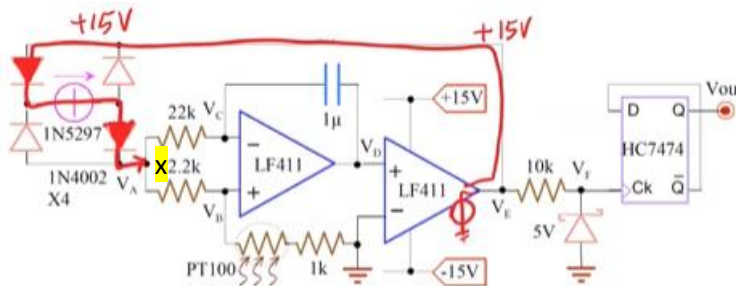

This current must be 1 mA because we have the current generator. At node x we have two paths. Thanks to virtual ground, node V_b and V_c are like connected together, so in parallel.

$$R_{PT100} = 100\Omega + 0.4 \frac{\Omega}{^\circ C} \cdot T$$

$$i = 1mA \cdot \frac{22K}{22K + 2.2K} = 1mA \cdot \frac{22}{24.2} = 0.91mA$$

$$i^* = 1mA - i = 0.09mA$$

$$V^* = i \cdot (2.2K + 1K + R_{PT100}) = 0.91mA \cdot 3.2K + 0.91mA (100 + 0.4 \cdot T)$$


$$= 3V + 364 \cdot 10^{-6} \cdot T$$

$$\bar{V} = i \cdot (R_{PT100} + 1K) = 0.91mA \cdot 1.1K + 0.364 \cdot 10^{-6} \cdot T = 1V + 0.364 \cdot 10^{-6} \cdot T$$


V_{bar} is the voltage at the + terminal of the opamp.
Then the i^* flows in the capacitor.

$$\frac{dV}{dt} = \frac{I}{C} = \frac{i^*}{C} = \frac{0.03 \text{ mA}}{1 \mu\text{F}} = 30 \frac{\text{V}}{\text{s}}$$

 If so, the voltage V_d is decreasing. It starts from 1V when the capacitor is discharged and then it decreases. We are interested in when the 0 is crossed to trigger the comparator. It is the delta in voltage divided by dV/dt .



 Once we crossed this voltage, V_d goes below 0 and the output commutes to -15V. If so, the other diodes are activated, and still we have 1 mA, but in the other direction into node x. Hence when we commute V_{bar} goes to -1V (and also V_d) and the capacitor will start charging in the opposite direction, up to the point where the comparator is triggered again.




V_{bar} varies with temperature, so the period eventually will be longer \rightarrow the oscillation frequency depends on the temperature.

$$f_{\text{osc}}(0^\circ\text{C}) = \frac{1}{2 \cdot 11.1 \text{ ms}} = 45 \text{ Hz}$$

$$f_{\text{osc}}(T) = \frac{1}{2 \cdot \frac{1\text{V} + 0.364 \text{ mV} \cdot T}{30 \text{ V/s}}} = \frac{45 \text{ V/s}}{1\text{V} + 0.364 \text{ mV} \cdot T}$$

$$T_{\text{osc}}(T) = \frac{1\text{V}}{45 \text{ V/s}} + \frac{0.364 \text{ mV}}{45 \text{ V/s}} \cdot T = 22.2 \text{ ms} + 8.1 \mu\text{s} \cdot T$$

 Then we have the Zener diode, a 5V one. When the voltage is positive, it sets to +5V. When negative it is off and so it will be more or less 0.7V.




The flip flop has the D connected to the Q_{not} , so it behaves like a toggle flip flop.

Ex. 2


Es. 1

 Il circuito impiega due OTA aventi transconduttanza $g_m=1\text{mA/V}$ e monitora la corrente in una $R_{\text{sense}}=1\Omega$.
 a) Quando l'interruttore è in posizione B, determinare la funzione del circuito ed il legame tra V_{out} e I_{sense} .
 b) Quando l'interruttore è in A, dire **quantitativamente** cosa cambia rispetto al caso precedente.



Resolution

 The switch has two different positions, let's start from position B and study the schematic. We have the PS and we need to check the negative feedback.




If the feedback is negative we can consider the circuit as ideal, with $G_{\text{loop}} = \text{inf}$ and then we check later if it is infinite or not. If G_{loop} is infinite, we should have 0V on the + terminal of the third opamp due to negative feedback.

This means that the two currents i^* must be equal if we have a negative feedback. Given this, we can compute V_{out} .

Es. 1

 Il circuito impiega due OTA aventi transconduttanza $g_m=1\text{mA/V}$ e monitora la corrente in una $R_{\text{sense}}=1\Omega$.
 a) Quando l'interruttore è in posizione B, determinare la funzione del circuito ed il legame tra V_{out} e I_{sense} .
 b) Quando l'interruttore è in A, dire **quantitativamente** cosa cambia rispetto al caso precedente.



$$i^* = V_{\text{diff}} \cdot g_m = I_{\text{sense}} \cdot R_{\text{sense}} \cdot g_m = I_{\text{sense}} \cdot 1 \cdot 1\text{mA/V}$$


$$i^* = V^* \cdot g_m$$

$$V^* = I_{\text{sense}} \cdot 1\Omega$$

$$V_{\text{out}} = \frac{V^*}{10\text{k}} (10\text{k} + 330\text{k})$$

$$V_{\text{out}} = I_{\text{sense}} \cdot 1\Omega \left(1 + \frac{330\text{k}}{10\text{k}}\right) = I_{\text{sense}} \cdot 1\Omega \cdot 34$$

 This is in the ideal case, but we need to check how big G_{loop} is. To compute G_{loop} we switch off the PS and we have the following.



$$G_{\text{loop}} = A(s) \cdot \frac{10\text{k}}{330\text{k} + 10\text{k}} \cdot g_m \cdot 22\text{k} = A(s) \cdot \frac{10}{340} \cdot 22\text{k} \cdot 1\frac{\text{mA}}{\text{V}} = A(s) \cdot 0.65$$

Since G_{loop} is very high we can consider it ideal.

Let's now study the case when the switch is connected in position A, so the third opamp is a buffer. The circuit has a negative feedback.

The relationship between out and Isense should remain the same, but if we compute Gloop, it is only 0.65.

$$G_{loop} = 1 \cdot \frac{10k}{330k+10k} \cdot 3m \cdot 22k = 0.65$$

This means that it is not strong enough, so the stage cannot be considered ideal and the relationship between Vout and Isense of the case B is not valid.

Given this, we should compute the real gain.


$$G_{real} = \frac{V_{out}}{I_{sense}}(f) = \frac{G_{ideal}}{1 - \frac{1}{G_{loop}}} = \frac{34 \frac{V}{A}}{1 + \frac{1}{0.65}} = \frac{34 \frac{V}{A}}{1 + 1.5} = 136 \frac{V}{A}$$

Ex. 3

Es. 3

Usando un OpAmp con $V_{supply,max} = \pm 14V$, per potere erogare in uscita delle tensioni tra $\pm 50V$, ossia oltre i **maximum absolute ratings**, si impiega il bootstrap.

 - Determinare la tensione di alimentazione $V_{dd}-V_{ee}$ dell'OpAmp e disegnare l'andamento di V_{out} , V_{dd} e V_{ee} quando $V_{in}=10V$ sinusoidali.
- Determinare il massimo guadagno dello stadio, oltre il quale si eccede il common mode input voltage range dell'OpAmp, sapendo che è un *rail-to-rail* sia come *input common range* che come *output voltage swing*.



Resolution

The PS to the opamp is given by two transistors, a npn on the top and pnp on the bottom. The network made by resistors and diodes senses the Vout and provides the voltage to the bases of the transistors. The maximum PS of the opamp is $\pm 14V$, but I'm applying $\pm 50V$.


Let's suppose the input signal is 0, and the circuit has an overall negative feedback, so VG applies. The voltage drop on the two diodes is of 0.6V, that is similar to the one we have on the base emitter junction. Voltage of the base will be $V_{dd} + 0.6V$. Voltage across the top 10k resistor will be $V = (50 - 0.6) \cdot (10 / (10 + 33))$.

Usando un OpAmp con $V_{supply,max} = \pm 14V$, per potere erogare in uscita delle tensioni tra $\pm 50V$, ossia oltre i **maximum absolute ratings**, si impiega il bootstrap.

- Determinare la tensione di alimentazione $V_{dd}-V_{ee}$ dell'OpAmp e disegnare l'andamento di V_{out} , V_{dd} e V_{ee} quando $V_{in}=10V$ sinusoidali.
- Determinare il massimo guadagno dello stadio, oltre il quale si eccede il common mode input voltage range dell'OpAmp, sapendo che è un *rail-to-rail* sia come *input common range* che come *output voltage swing*.

$$0.6V + (50V - 0.6V) \cdot \frac{10k}{10k + 33k} = V^*$$

 
$$V_{dd} = V^* - 0.6V = 49.4 \cdot \frac{10}{43} = 11.5V$$



The same can be computed for Vee, and it is -11.5V. Hence the resistive network we have is needed just to provide the correct PS to the opamp → the opamp works correctly.

But let's now see what happens if we apply Vin. The Gain is the one of a non inverting stage, so $1 + R2/R1 = 1 + 100k/100k = 2$.

 
We should recompute the voltage at the bases of the bjts.



$$Gain = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1} = 1 + \frac{100k}{100k} = 2$$

$$V^* = V + (V - V - 0.6) \cdot \frac{10k}{43k}$$

 Let's plot the i/o relationship, or even better the Vout and Vin. Vout should be Vin but amplified because of the gain.




The final result is that the net accommodates the PS so that it is in between the acceptable ranges for the PS of the opamp.

The next point is to compute the maximum gain of the stage beyond which the common mode input voltage range of the opamp is no more correct.

The thing is, every time we apply a certain Vin, the PS moves accordingly to the output that is 2*Vin. But we run the risk that if Vin is no longer between the two PS, then we are applying to the opamp an input voltage that is no more between VDD and VEE and we destroy it.

 This happens if the gain is large, and the situation is the one below.



We see that in some points Vin is below VDD and in some other points is above it, and this is not good because the opamp could be damaged.

By using one of the previous equations we can compute the maximal Vout value.

$$V_{DD} = (50 - G \cdot V_{in} - 0.6) \cdot \frac{10k}{43k} + G \cdot V_{in} \geq V_{in}$$


$$45.4 - G \cdot V_{in} \geq V_{in} (1 - G) \cdot 4.3$$

Ex. 4

Es. 2

Il circuito monitora l'assorbimento di un carico in alternata a 50Hz. L'alimentazione è flottante a batteria.

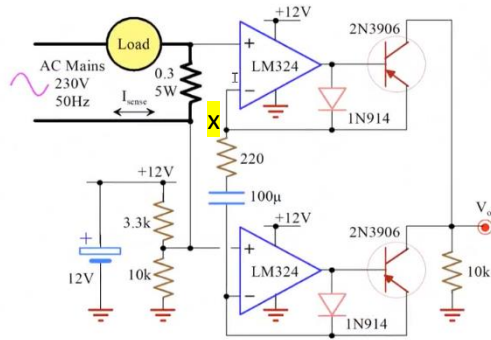- a) Disegnare la forma d'onda quotata di V_{out} nel caso sia collegato un carico resistivo di 50W e determinare il guadagno V_{out}/I_{sense} .
- b) Realizzare l'alimentazione continua del circuito (circa 12V) partendo dalla tensione di rete, senza usare alcun trasformatore.




Resolution

PS is floating thanks to a battery, and let's forget it for the moment. A current flows through the bold part of the circuit and it is connected to the mains of the sinusoidal PS. So it can be clockwise or counterclockwise in direction. Voltage V_{diff} across the 0.3 Ohm resistance is $V_{diff} = i \cdot 0.3$. Then shit voltage is applied to the two opamps and let's see if they have or not a negative feedback.

If something positive is applied to the + terminal of the upper opamp, the output goes positive and if so the current flows through the diode that is on, and the pnp transistor is off, because the base is at higher voltage than the emitter and it is n doped.

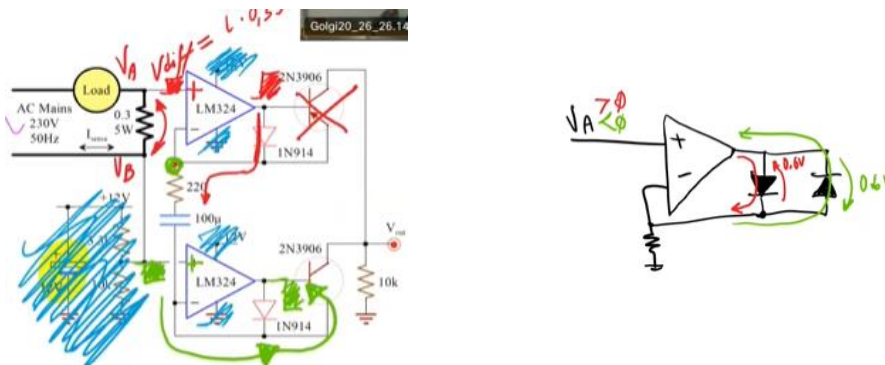
The same concept applies at the bottom opamp. the + terminal goes down, and the output goes negative. But the voltage at node x is positive, current would like to flow to bottom, so it must enter in the transistor and not in the diode.




It's like having a situation on the left. Hence we have a buffer.

When the current from the mains flows clockwise in the sensing resistor, then the voltage V_{diff} is connected as below.

 Current cannot flow in the diode of the bottom opamp, it should go in the bjt but it cannot if the transistor is connected like in the image.



 Almost the full current i^* flows in the output resistor. In reality, in a BJT, I_c is $\beta \cdot I_b$ and $I_e = I_c + I_b$.




$$V_{diff} = i_{sense} \cdot 0,3 \Omega$$

$$i^* = \frac{V_{diff}}{Z_{in}} \approx \frac{V_{diff}}{R} = i_{sense} \cdot \frac{0,3 \Omega}{220 \Omega} = \frac{i_{sense}}{733}$$

$$V_{out} = + \frac{i_{sense}}{733} \cdot 10k = + i_{sense} \cdot 13,6$$

 Even when the current in the load changes direction, the reasoning is the same but the direction in the output resistance is the same. We can plot what is happening in the circuit, that is the fact that the input signal is magnified and brought positive. The gain is a transimpedance gain.




To the opamp, we should apply the proper power supply.

Ex. 5

Es. 1


L'OpAmp ha $A_0=120\text{dB}$, $\text{GBWP}=10\text{MHz}$, $I_{OS}=100\text{pA}$, $V_{OS}=0,5\text{mV}$. L'uscita è lasciata aperta.

 - Determinare V_{out}/V_{in} in continua e ad alta frequenza ed il guadagno V_{out}/V_{ref} . Disegnare il trasferimento $V_{out}/V_{in}(f)$ e commentare il ruolo del circuito.
- Calcolare l'impedenza di uscita del circuito a 10Hz quando $V_{in}=+2\text{V}$.
- Calcolare l'errore in uscita dovuto all'offset di corrente (NON alle I_B) ed a quello di tensione.




Resolution

 For sure there is a local negative feedback, but in the outer loop we don't have any overall negative feedback loop because we have a voltage generator that is touching the feedback loop, and whenever this happens we kill the loop. We can rewrite the schematic as below.




If there was the red resistance it would have been true that we have an outer feedback loop, that however would have been positive and I would have had a Schmitt trigger. But since there is no resistor, we apply a V_{in} to the loop and we cannot move node x because it is an ideal voltage generator, so there is no feedback at all, just an open circuit.

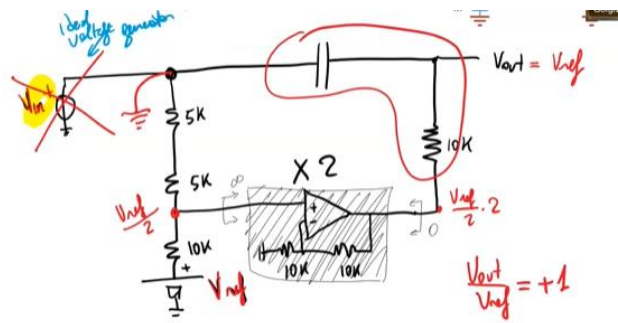
Let's kill V_{in} and compute V_{out} due to V_{ref} , so we ground V_{in} . V_{ref} is in DC so the capacitor is open and $V_{out} = V_{ref}$.



 Let's now consider V_{in} , so we switch off V_{ref} (grounded). Across the capacitor and the 10k resistor we have V_{in} and V_{in} , but V_{in} has a frequency dependence. At DC, the capacitor is open so the output is open. At HF, V_{out}/V_{in} is still V_{in} .



 
The thing is, in the circuit of the exercise there is another capacitor of 100u. At DC nothing changes for V_{out}/V_{in} , while at HF the relationship is still 1 because V_{in} feeds the output.



Let's study the i/o relationship for V_{in} . We saw that at DC the gain is 1 and also at HF. But is it always 1? We have to check the poles and who enters in shortcircuit.

The pole due to the 100u capacitor is $1/(2\pi \cdot 100\mu \cdot R)$, where R is $5k \parallel (5k + 10k)$. The pole is at 0.42 Hz. Maybe this capacitor also introduces a zero. Every time we enter and we have a capacitor in the path of the signal, the capacitor is not introducing a zero.

 As for the 20n capacitor, at HF, we have a HP filter whose pole is $1/(2\pi \cdot 20n \cdot 10k)$ (V_{in} must be grounded). The frequency of the pole is 796 Hz, and then we have a zero at 0Hz. So the circuit is like having a LP stage in parallel to a HP stage. When they are both working, we have the product of them.




We can see that the circuit has two coincident zeros at the intermediate frequency (geometric average).

Ex. 6

Il sensore di temperatura MAX6605 fornisce $V_T(T) = 744mV + T \cdot 11.9mV/^\circ C$.

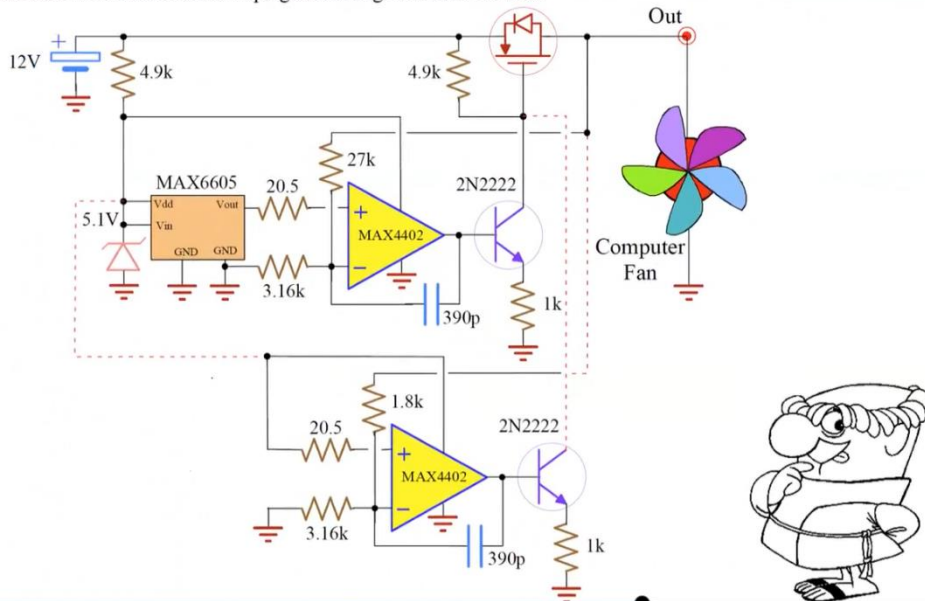
- a) Scollegando il circuito in basso, disegnare il grafico quotato di $V_{out}(T)$ nell'intervallo $0^\circ C \div 50^\circ C$.
- b) Determinare l'intervallo di temperature per cui il circuito è in zona lineare, sapendo che il MAX4402 è *rail-to-rail*.
- c) Includere ora il circuito in basso e spiegarne dettagliatamente il ruolo.



Resolution

We have a temperature sensor that is the MAX6605. At first let's not consider the bottom circuit and see how the circuit behaves.

We have a +12V battery and a Zener diode. So if the battery is higher than the voltage of the Zener diode, the Zener diode is clamping the voltage to 5.1V. This voltage is used to bias the temperature sensor and also the opamp. The 3.16k resistor is connected to ground, while V_T varies with temperature. $V+$ of the upper opamp is equal to V_T because no current can flow in the input terminal. If something positive is applied to the + terminal, the output goes positive; if so, then also the emitter goes positive and the current increases, and if so the voltage across the 4.9k resistor is increasing. Then the V_{gs} of the mosfet increases, so also the current in it increases. Then V_{out} increases to the load. If so, also the - terminal of the opamp increases \rightarrow negative feedback.

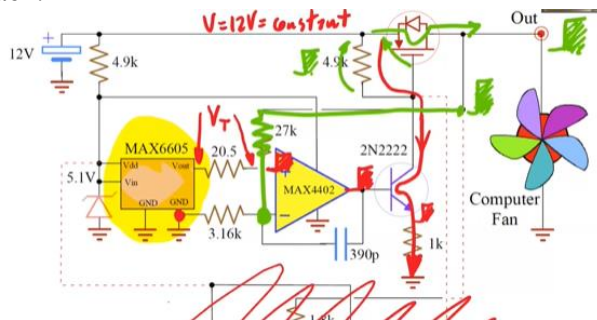

If Gloop is infinite, we can consider the ideal feedback and the concept of virtual ground, so on the two terminals I should have V_T . $V-$ is given thanks to a voltage partition with V_{out} as top voltage.

$$V_{out} \cdot \frac{3.16k}{3.16k + 27k} = V_T$$

$$V_{out} = (744mV + 11.9 \frac{mV}{^\circ C} \cdot T) \cdot 9.5 = 7.1V + 113 \frac{mV}{^\circ C} \cdot T$$

So V_{out} is proportional to the temperature plus a constant offset of 7.1V. Theoretically, if we apply the maximal temperature of $50^\circ C$, the voltage should reach 12.8V, but this is a problem for the bias. But V_{out} cannot reach 12V because the transistor requires something between source and drain.


We want to compute the range of temperatures withing which the circuit can operate in the linear zone. The maximal voltage in output of the opamp is 5.1V because the opamp is rail-to-rail. So we can compute the current in the bjt.

$$i = \frac{5.1V - 0.6V}{1K} = 4.5mA$$

Then for the mosfet, $V_{gs} = i \cdot 4.9k = 4.5mA \cdot 4.9k = 22V$. This means that the opamp will never saturate to the power supply because the current in the BJT would be so high that the V_{gs} of the MOSFET would have been too high and the collector would decrease too much.

The limiting factor of the BJT is when the collector is so low that we don't have anymore a reverse bias junction between base and collector.

 When V_o in output of the opamp is max, we have the maximum current in the BJT and the minimum V_c of the bjt. When V_c is almost $V_{o,max}$, the transistor enters the saturation regime, when V_{ce} is almost 0.2V and the base collector junction is forward biased with 0.5V.



The condition for not having saturation is the following.

$$12V - \left(\frac{V_{o,max} - 0.7}{1K} \right) \cdot 4.9k \geq V_{o,max} - 0.5$$

Performing the calculations:

$$12 - V_{o,max} \cdot 4.9 + 3.43 \geq V_{o,max} - 0.5$$

$$V_{o,max} \leq \frac{16}{5.9} = 2.7V$$

We know hence the maximal V_o in output of the opamp.

Let's now include also the circuit at the bottom of the schematic. Also this part senses the same voltage as the circuit above, and they drive the same nodes. The only difference is the resistor of 20.5 that is not connected to V_t but to PS. So if we perform the voltage partition with V_{out} as top voltage as before, we have:

$$V_{out} = \frac{3.16k}{3.16k + 1.8k} = 5.1V$$

The result is that $V_{out} = 8V$.

In the end the bottom circuit sets V_{out} to be 8V, the top one to $7V + 113mV/^\circ C \cdot T$.

If the bottom BJT is capable of providing the proper current the output will reach 8V, but if for any other reason there is another stage that pumps a different current to set a different voltage, one of the two transistors will not operate properly. If e.g. $T = 0^\circ C$, the top stage tries to force 7V, the bottom stage 8V. If the voltage on the collector of the bottom BJT is 7V, it means that the voltage on the - terminal of the bottom opamp will be lower than 5.1V on the + terminal. Hence the output of the opamp tends to increase, but if so, the current in the BJT increases, so the voltage drop on the V_{gs} of the mosfet increases and the current in the mosfet increases and so V_{out} increases. So V_{out} cannot stay at 7V because the bottom stage increases the current so that the output voltage is brought to 8V.


If the output is 8V, these are for top and bottom stages. The bottom stage is ok, but on the top opamp the voltage on the - terminal will be higher than the voltage on the + terminal and so the output of the opamp will go low decreasing the current in the BJT. So the V_{gs} of the mosfet decreases and so on.

At the most the upper stage can decrease its current, eventually even putting it to 0, but there is no problem because the current that sets the V_{gs} of the MOSFET is set by the bottom circuit.

So the second stage forces a constant 8V contribution to the output. Due to the second stage, the output will be 8V even for temperatures lower than a given amount.

If we change the values of the resistors of the bottom stage, e.g. by introducing a trimmer, we can change the $V_{out,min}$, and so the speed of the fan.


The i/o relationship we obtain will be the following.

 

Ex. 7

Es. 2

 I piedini di ShutDown *active-low* mandano in *three-state* la rispettiva uscita. Il segnale Control è a 1kHz.
 a) Determinare la funzione svolta dal circuito e il legame tra V_{out} e V_{in} . Si consiglia di studiare separatamente il caso Control=*low* e poi Control=*high*.
 b) Dire cosa accade quando Control=*low* per 1ms e si considerano tutte le $I_B=100\mu A$.




Resolution

We have two ICs with two opamps inside, that can be turned on or off through a control pin SD, that is active low.

When the opamps are not active, the output is in tristate, so it is fixed.

 
Let's start from the control pin set to low level. Opamps A1 and B2 are off.



As for when control is high.



 Hence during control = H we store V_{in} on the capacitor. When control = L, V_{in} is no more attached to the capacitor and the voltage is fed to the output. In the L phase $V_{out} = -V_{in}$.



V_h is the voltage on the 1n capacitor. This is a smart S&H because the hold phase lasts longer than in the normal S&H. Moreover, this stage also performs a voltage inversion.

